

Office hrs today: 9⁵⁰ AM - 11⁵⁰ AM

tomorrow: 2⁵⁰ PM - 3⁵⁰ PM

Wed: 9⁵⁰ AM - 11⁵⁰ AM

Th: 2⁵⁰ PM - 4³⁰ PM

* Opportunity 2 → Next Monday 11/23

* HW 4 due this Friday, 11/20!

Today: Current, Voltage, Resistance,
Resistivity (ρ)

resistance

↓

$$R = \rho \frac{L}{A}$$

material property

← length of wire

$$\rho - \rho_0 = \rho_0 \alpha (T - T_0)$$

initial resistivity

initial temperature

(K)

? K = 273 + Celsius.

or ~~ohm~~
Conductivity = ease at which charge moves through given material.


$$\sigma = \frac{1}{\rho} = \frac{1}{\text{resistivity}} = \text{conductivity}$$

$$\text{Current} = I = \frac{dq}{dt} \quad 1A = \frac{C}{s}$$

(Amps = A)

$$\text{Current density} = J = \frac{\text{Current}}{\text{Area}}$$
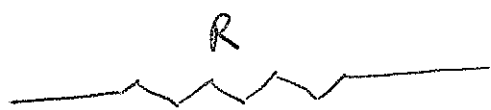
$$I_{\text{net}} = \int J \cdot dA \quad J = \text{may be non-uniform}$$



$$P = I^2 R = \frac{V^2}{R} = IV$$

Joule Heating \rightarrow rate at which energy is dissipated across a resistor.

$$\text{Ohm's Law: } V = IR \Rightarrow I = \frac{V}{R}$$

Example



26-11.)

$$J(r) = Br$$

$$B = 2 \times 10^5 \text{ A/m}^3$$

$$R = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$

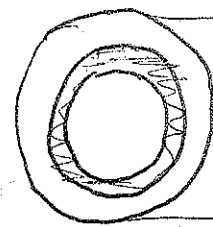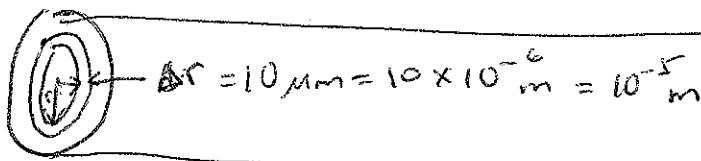How much current is contained within a the width of a thin ring concentric with the wire if ring has a radial width of $10 \mu\text{m}$ and is at a radial distance of 1.2 mm



$$r = 1.2 \text{ mm} = 1.2 \times 10^{-3} \text{ m}$$

$$R = 2 \times 10^{-3} \text{ m}$$


$$I = \int J dA \quad A = \pi r^2 \Rightarrow dA = 2\pi r dr$$

$$I = \int_{1.2 \times 10^{-3}}^{1.2 \times 10^{-3} + 10^{-5}} (Br) \cdot 2\pi r dr = 2\pi B \int_{1.2 \times 10^{-3}}^{1.2 \times 10^{-3} + 10^{-5}} r^2 dr$$

$$I = 2\pi B \left. \frac{r^3}{3} \right|_{1.2 \times 10^{-3}}^{1.2 \times 10^{-3} + 10^{-5}} = 18.1 \mu\text{A}$$

$J = J(r) \Rightarrow$ Current density non-uniform!

Series

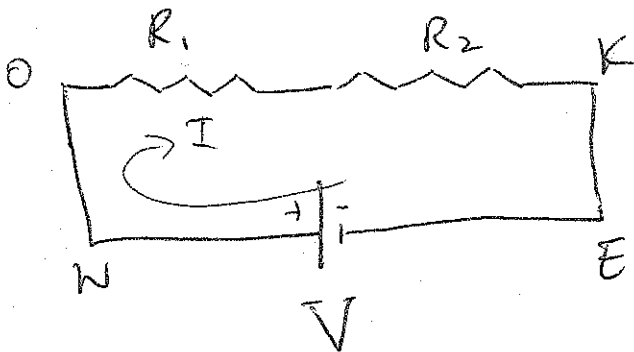


$$I_1 = I_2 = I_{\text{net}}$$

Loop EWOKE:

$$V - V_1 - V_2 = 0$$

$$V = V_1 + V_2$$

Parallel

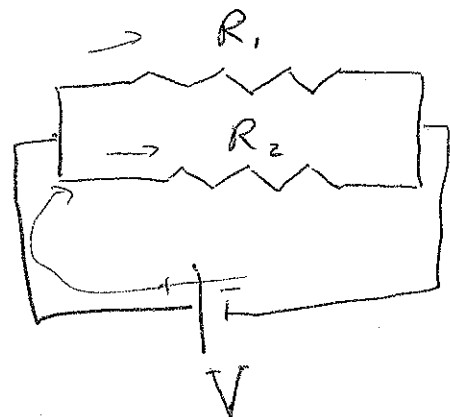

$$I_{\text{net}} = I_1 + I_2$$

$$V = V_1 = V_2$$


$$\frac{1}{R_{\text{net}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I = \frac{V}{R} \Rightarrow R = \frac{V}{I} \leftarrow$$

aside: $Q = VC \Rightarrow C = \frac{Q}{V} \leftarrow$

$$R_{\text{net}} = R_1 + R_2$$

Example:

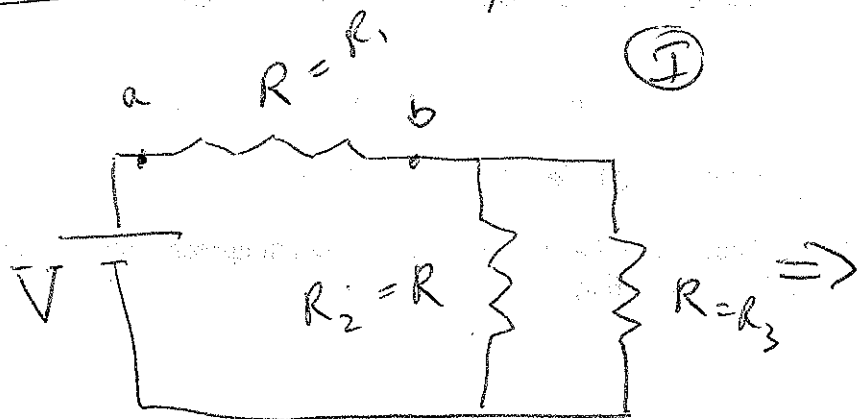

R_2, R_3 parallel \Rightarrow

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R} + \frac{1}{R} = \frac{2}{R}$$

$$R_{23} = \frac{R}{2}$$



$$R_{123} = R_1 + R_{23} = \frac{3R}{2} \checkmark$$

R_1, R_{23} Series



$$I_{\text{net}} = \frac{V}{R_{123}} = \frac{V}{\frac{3R}{2}} = \frac{2}{3} \frac{V}{R} \checkmark$$


For pic II: $I_1 = I_{23} = I_{123} = I_{\text{net}} = \frac{2}{3} \frac{V}{R}$

$$V_1 = I_1 R_1 = \frac{2}{3} \frac{V}{R} \cdot R = \frac{2}{3} V$$

$$V_{23} = I_{23} R_{23} = \frac{2}{3} \frac{V}{R} \cdot \frac{R}{2} = \frac{V}{3}$$

PIC I : R_2, R_3 parallel : $V_2 = V_3 = V_{23} = \frac{V}{3}$
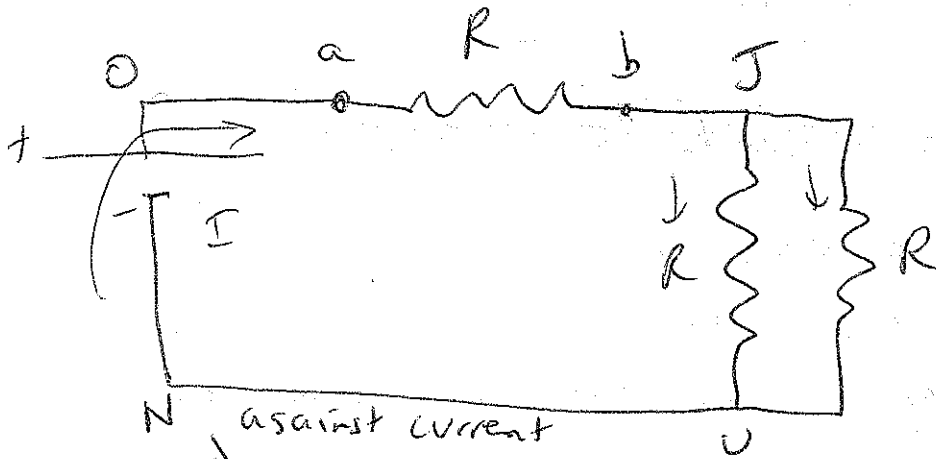
$$I_2 = \frac{V_2}{R_2} = \frac{V/3}{R} = \frac{1}{3} \frac{V}{R} \quad I_3 = \frac{1}{3} \frac{V}{R}$$



$$V_{ab} = +I_1 R_1 = \frac{2}{3} \frac{V}{R} \cdot R = \frac{2}{3} V$$

↑ ↑
end start

Loop bJUNOa : $-I_2 R_2 + V = V_{ab}$

$$-\frac{1}{3} \frac{V}{R} R + V = \frac{2}{3} V \quad \checkmark$$