

# WORCESTER POLYTECHNIC INSTITUTE MECHANICAL ENGINEERING DEPARTMENT

Engineering Experimentation  
ME-3901, D'2012

Lecture 07

02 April 2012



# General information

## Office hours

**Instructors: Cosme Furlong**

Office: HL-151

**Everyday:**

**9:00 to 9:50 am**

**Christopher Scarpino**

Office: HL-153


**During laboratory**

**sessions**

**Teaching Assistants: During laboratory sessions**




# Wheatstone bridge

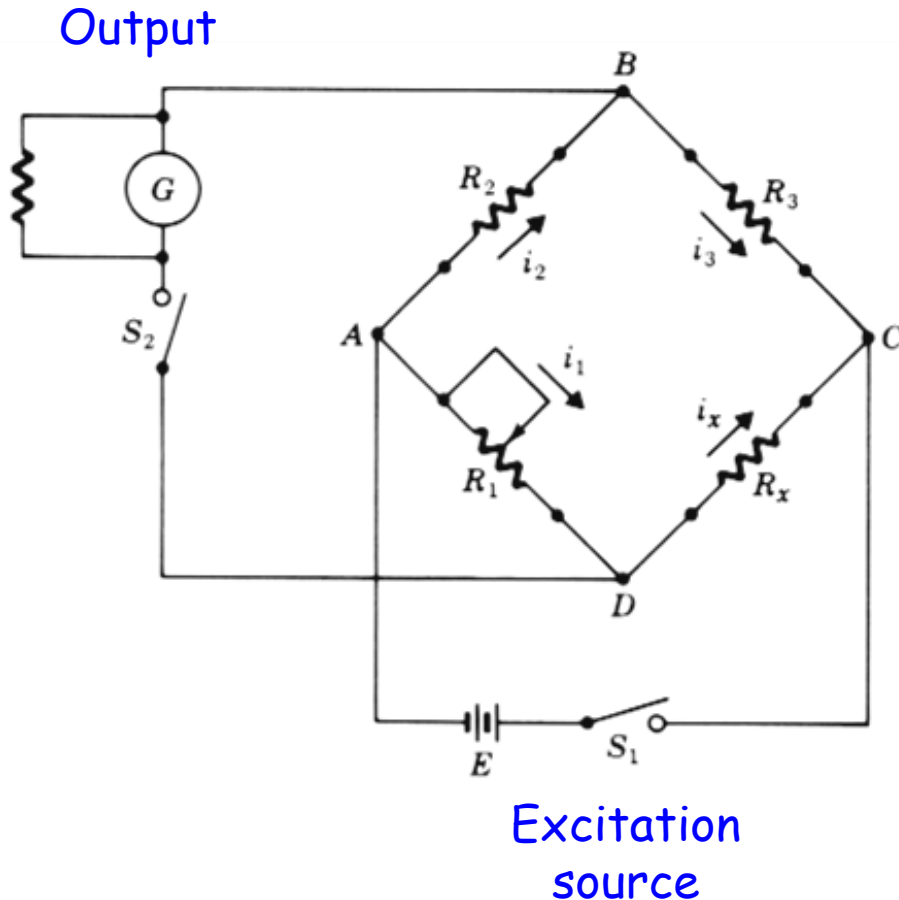

- Use for the comparison and measurement of resistances from  $1\ \Omega$  to  $1\ \text{M}\ \Omega$
- Resistances are arranged in a "diamond" shape
- $R_2$  and  $R_3$  are normally known resistors (of high-quality)
- $R_1$  is a variable resistor
- $R_x$  is the unknown resistor



# Wheatstone bridge

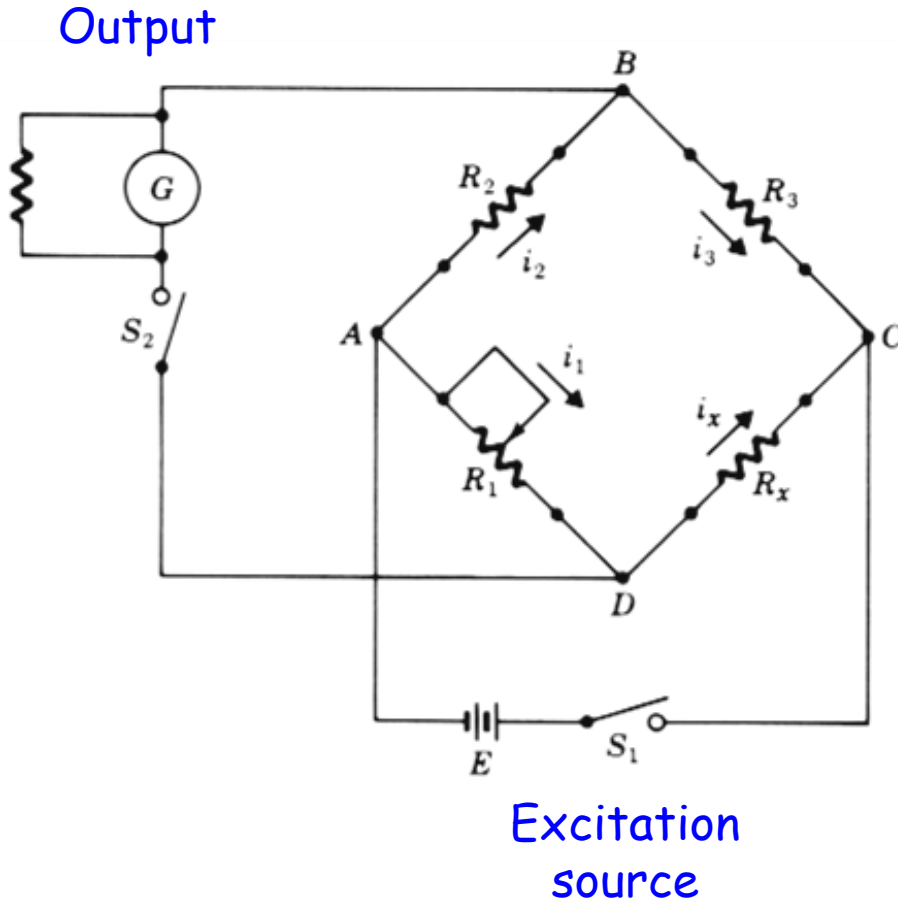


- Voltage  $E$  is applied to the bridge (by closing switch  $S_1$ )
- A "balanced" bridge is one with potential difference between  $B$  and  $D$  is equal to zero
- Balance is sensed by closing switch  $S_2$  and measuring output current and voltage - to be near zero
- Bridge can be balanced by adjusting resistance  $R_1$



# Wheatstone bridge

Output

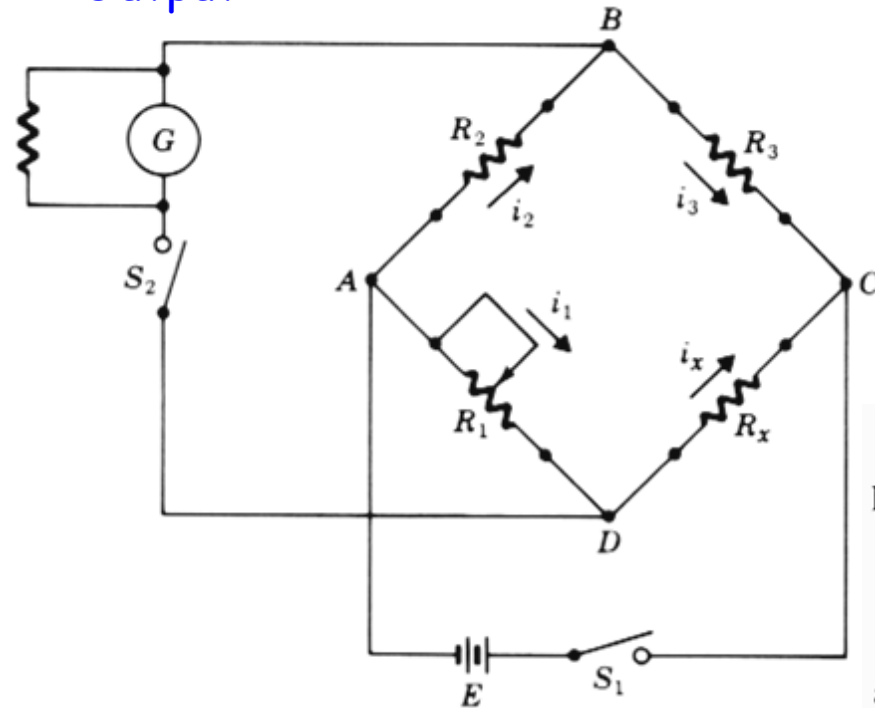

Excitation  
source

- When bridge is balanced: voltage drop across  $R_2$  is equal to voltage drop across  $R_1$ , since voltage difference between  $B$  and  $D$  is equal to zero. Therefore,

$$i_2 R_2 = i_1 R_1$$

Further,

$$i_2 = i_3 = \frac{E}{R_2 + R_3} \quad \text{if balanced}$$

and

$$i_1 = i_x = \frac{E}{R_1 + R_x} \quad \text{if balanced}$$

If the currents are eliminated from these relations, the result is

$$\frac{R_2}{R_3} = \frac{R_1}{R_x}$$

or

$$R_x = \frac{R_1 R_3}{R_2}$$



# Wheatstone bridge: balanced bridge

## Example: uncertainty analysis

- For a balanced Wheatstone bridge, determine uncertainty in the measured resistance  $R_x$ , as a result of an uncertainty of 1% in the known resistances

$$R_x = \frac{R_1 R_3}{R_2} \Rightarrow R_x = R_x(R_1, R_2, R_3)$$

Uncertainty: 
$$\delta R_x = \left[ \left( \frac{\partial R_x}{\partial R_1} \delta R_1 \right)^2 + \left( \frac{\partial R_x}{\partial R_2} \delta R_2 \right)^2 + \left( \frac{\partial R_x}{\partial R_3} \delta R_3 \right)^2 \right]^{1/2}$$

$$\frac{\partial R_x}{\partial R_1} = \frac{R_3}{R_2}; \quad \frac{\partial R_x}{\partial R_2} = -\frac{R_1 R_3}{R_2^2}; \quad \frac{\partial R_x}{\partial R_3} = \frac{R_1}{R_2};$$




# Wheatstone bridge: balanced bridge
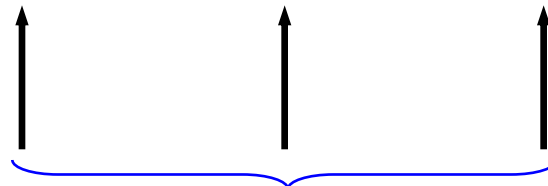
## Example: uncertainty analysis

Determine percentage:

$$\frac{\delta R_x}{R_x} = \left[ \left( \frac{1}{R_1} \delta R_1 \right)^2 + \left( -\frac{1}{R_2} \delta R_2 \right)^2 + \left( \frac{1}{R_3} \delta R_3 \right)^2 \right]^{1/2}$$



Percentages

(Same % contributions)


Recall:  $R_x = \frac{R_1 R_3}{R_2}$

Determine percentage (numerical value):

$$\frac{\delta R_x}{R_x} = \left[ (0.01)^2 + (-0.01)^2 + (0.01)^2 \right]^{1/2} = 0.01732 \Rightarrow 1.732\%$$



# Wheatstone bridge: unbalanced bridge

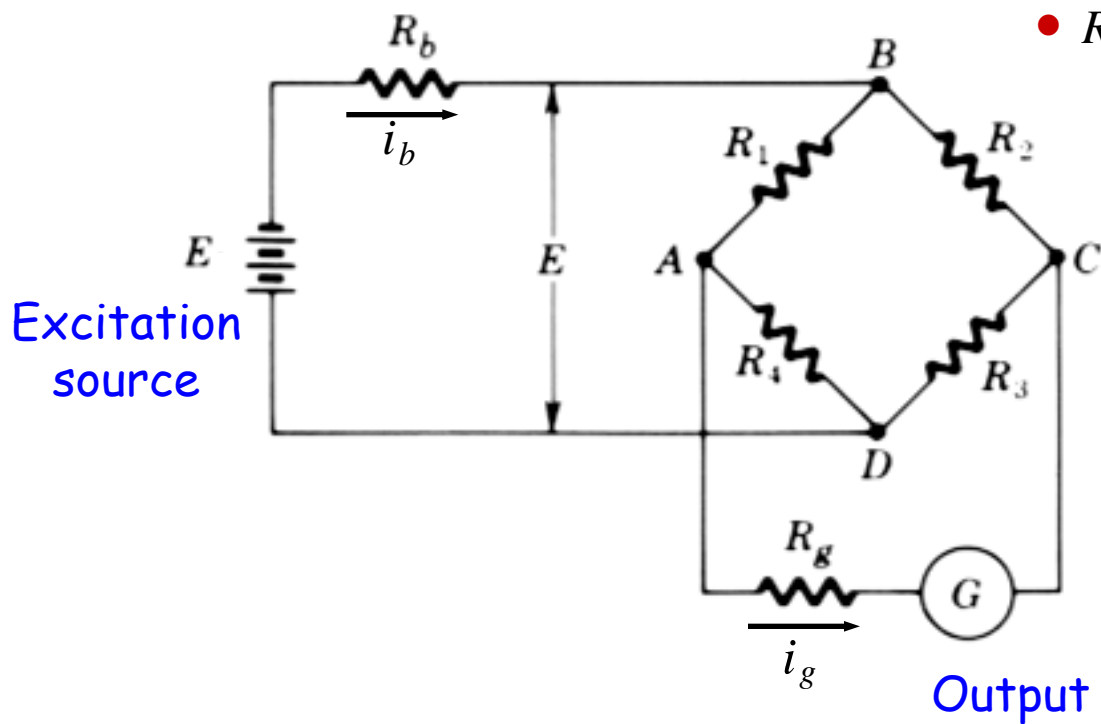


- $R_1, R_2, R_3, R_4$  are different






# Wheatstone bridge: unbalanced bridge

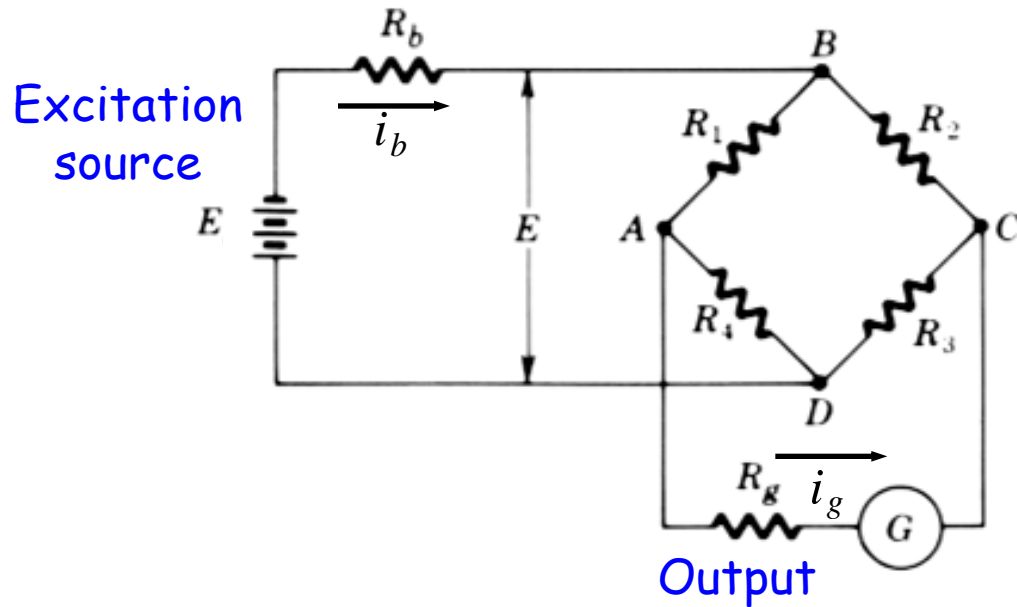

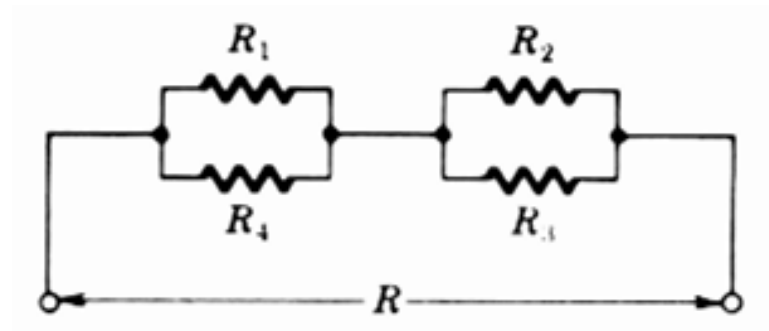Equivalent circuit of bridge at the output:




# Wheatstone bridge: unbalanced bridge

Equivalent resistance: 
$$R = \frac{R_1 R_4}{R_1 + R_4} + \frac{R_2 R_3}{R_2 + R_3}$$

Current at the output is: 
$$i_g = \frac{E_g}{R + R_g}$$

Recall a voltage divider:

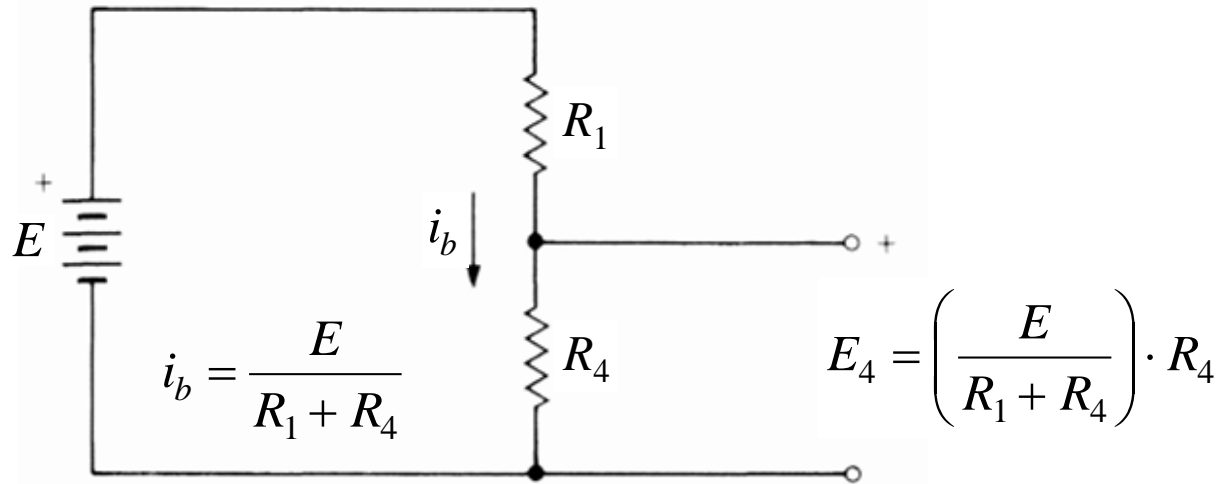

# Wheatstone bridge: unbalanced bridge

Considering voltage divider  
on a bridge:

$$\begin{aligned} E_g &= \left( \frac{E}{R_1 + R_4} \right) R_1 - \left( \frac{E}{R_2 + R_3} \right) R_2 \\ &= E \left( \frac{R_1}{R_1 + R_4} - \frac{R_2}{R_2 + R_3} \right) \end{aligned}$$

and

$$\begin{aligned} E_g &= \left( \frac{E}{R_1 + R_4} \right) R_4 - \left( \frac{E}{R_2 + R_3} \right) R_3 \\ &= E \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) \end{aligned}$$



# Wheatstone bridge: unbalanced bridge

What about if one resistance changes by a small amount?

Use:  $\Delta R_4 \Rightarrow \Delta E_g$

Therefore, 
$$E_g + \Delta E_g = E \left( \frac{(R_4 + \Delta R_4) R_2 - R_3 R_1}{(R_1 + R_4 + \Delta R_4)(R_2 + R_3)} \right)$$

Divide numerator and denominator by:  $R_2 R_4$

$$E_g + \Delta E_g = E \left( \frac{1 + \Delta R_4 / R_4 - R_3 R_1 / R_4 R_2}{(1 + R_1 / R_4 + \Delta R_4 / R_4)(1 + R_3 / R_2)} \right)$$



# Wheatstone bridge: unbalanced bridge

What about if one resistance changes by a small amount?

If all resistors are initially the same:  
( $E_g = 0$ ;  $R_i = R$ )


$$\frac{\Delta E_g}{E} = \frac{\Delta R_4 / R}{4 + 2(\Delta R_4 / R)}$$

But because changes in resistance are small, i.e.,  $\Delta R_4 \ll 1$

$$\frac{\Delta E_g}{E} \approx \frac{\Delta R_4}{4R}$$


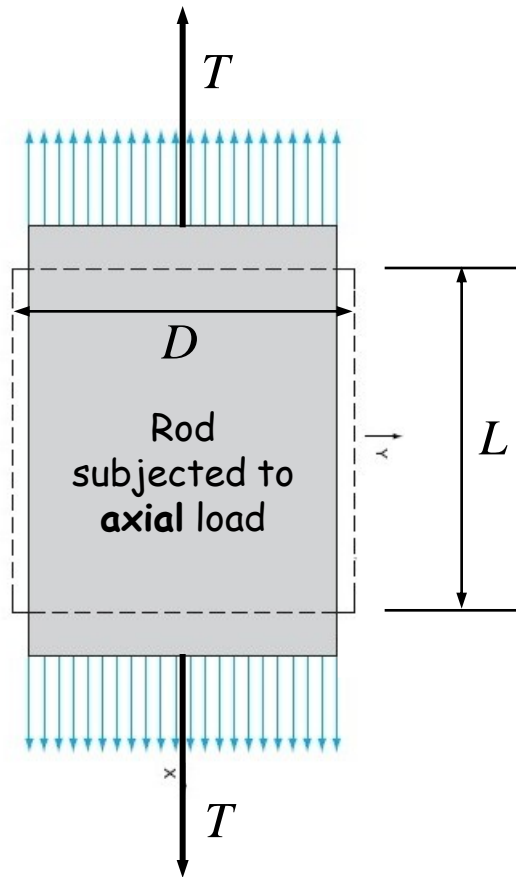
# Stress and strain (pay attention to nomenclature)



Axial strain: 
$$\varepsilon = \frac{T/A}{E} = \frac{\sigma_a}{E} = \frac{dL}{L} = \varepsilon_a$$

Poisson's ratio: 
$$\mu = -\frac{\varepsilon_t}{\varepsilon_a} = -\frac{dD/D}{dL/L}$$

( $\mu \approx 0.3$  for most metals)

Volume of rod is: 
$$V = L \cdot A = L \cdot \frac{\pi}{4} D^2$$

Volume is constant, therefore

$$dV = 0 = L dA + A dL$$

$$\Rightarrow \frac{dA}{A} = -\frac{dL}{L} \Rightarrow 2 \frac{dD}{D} = -\frac{dL}{L}$$

$$dV = 0 = D dL + 2L dD$$

(i.e.,  $\mu = 0.5$ , in this condition)



# Strain gages

Electrical resistance:  $R = \rho \frac{L}{A}$

← length  
← cross-sectional area  
↑ resistivity

Differentiate resistance:  $dR = \frac{L}{A} d\rho + \frac{\rho}{A} dL - \frac{\rho L}{A^2} dA$

$$\Rightarrow \frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \frac{dA}{A}$$

$$\Rightarrow \frac{dR}{R} = \frac{d\rho}{\rho} + \varepsilon_a - 2 \frac{dD}{D} = \frac{d\rho}{\rho} + \varepsilon_a - 2 \left( -\mu \frac{dL}{L} \right)$$

$$\Rightarrow \frac{dR}{R} = \frac{d\rho}{\rho} + \varepsilon_a - 2 \left( -\mu \frac{dL}{L} \right) = \frac{d\rho}{\rho} + \varepsilon_a (1 + 2\mu)$$




# Strain gages

Definition of gage factor:  $F = \frac{dR/R}{\varepsilon_a}$

(From previous page)  $\Rightarrow F = 1 + 2\mu + \frac{1}{\varepsilon_a} \frac{d\rho}{\rho}$

If resistivity does not change  $\Rightarrow F = 1 + 2\mu$

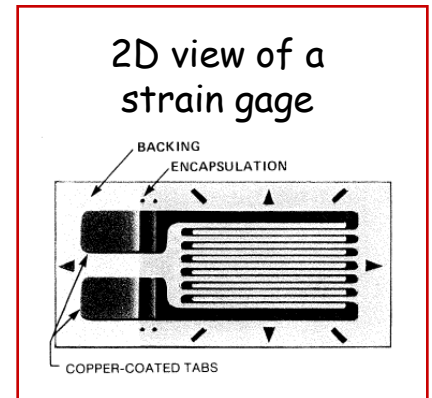And strain with change of resistance is:  $\Rightarrow \varepsilon_a = \frac{1}{F} \frac{\Delta R}{R}$



A typical strain gage has a gage factor  $\approx 2.095 \pm 0.5\%$ .  
Why? How is this possible? Open for discussions

