

Name SOLUTIONS

ECE Box # \_\_\_\_\_

A	90-100
B	76-89
C	60-75

M 79.9

$\sigma$  14.5

MED 82

Problem	Average Score	Points
1	<u>9.7</u>	10
2	<u>27.0</u>	30
3	<u>24.2</u>	30
4	<u>19.0</u>	30

ECE3204 D2009

Microelectronics II

Exam 1

- This is a **closed book, closed notes test!** Use of calculators is allowed. No pre-stored formulas or outside resource access!
- Show **all** your work. Partial credit may be given. If you think you need something that you can't remember, write down what you need and what you'd do if you remembered it.
- Look for the simple, straightforward way to solve the problem for the level of accuracy required. **Don't get entangled in unnecessary algebra.**
- As in real life, some problems may give you more information than you need. Don't assume that all information must be used! It's your job to decide what's relevant to the solution.
- Unless otherwise indicated or implied, you may assume all op-amps to be ideal.
- You will have 50 minutes to complete this exam. There are four problems on a total of 9 pages.



1) State the Microelectronics II Mantra:



[10]

IF AN OP-AMP IS CONNECTED WITH NEGATIVE FEEDBACK  
AND THE OPEN LOOP GAIN  $A$  IS SUFFICIENTLY HIGH  
THEN THE OP-AMP INPUTS  $V_- \approx V_+$  ARE  
APPROXIMATELY EQUAL

- 2) For each of the op-amp circuits in this problem, you may assume the op-amps to be ideal. For each circuit:
- First, circle one choice to indicate whether the circuit is configured for positive or negative feedback. Then,
  - ONLY FOR THE CIRCUITS THAT HAVE NEGATIVE FEEDBACK,** determine the indicated voltages/currents.

[30]

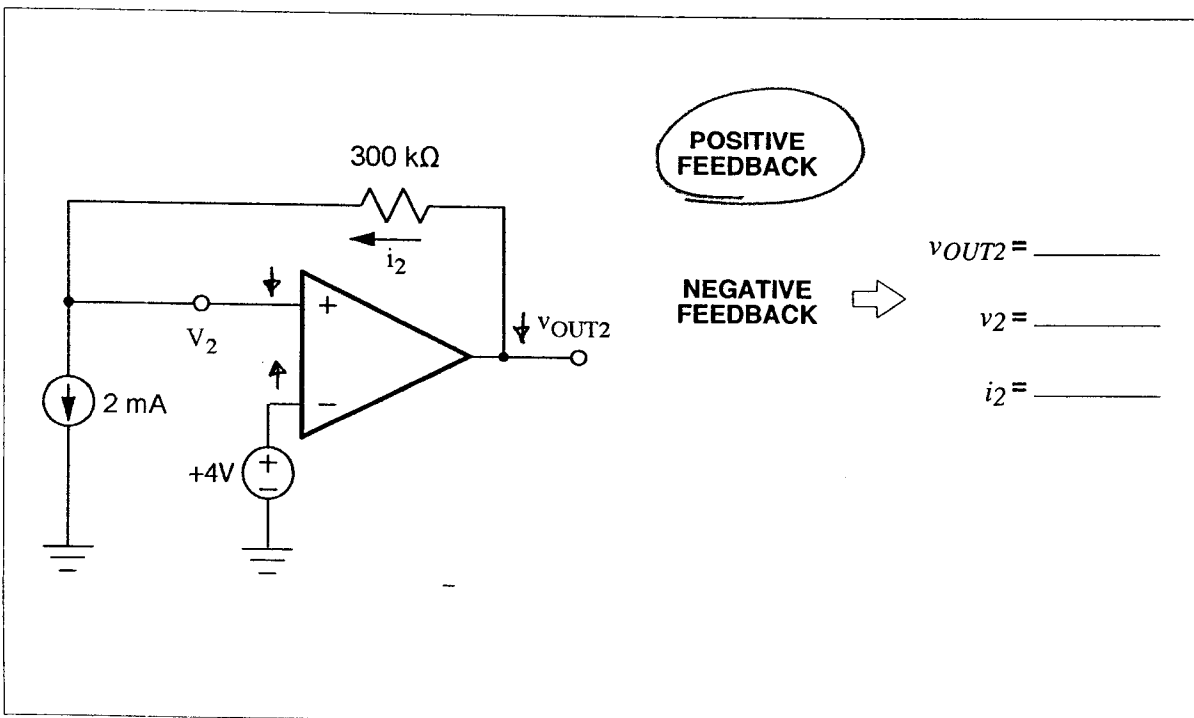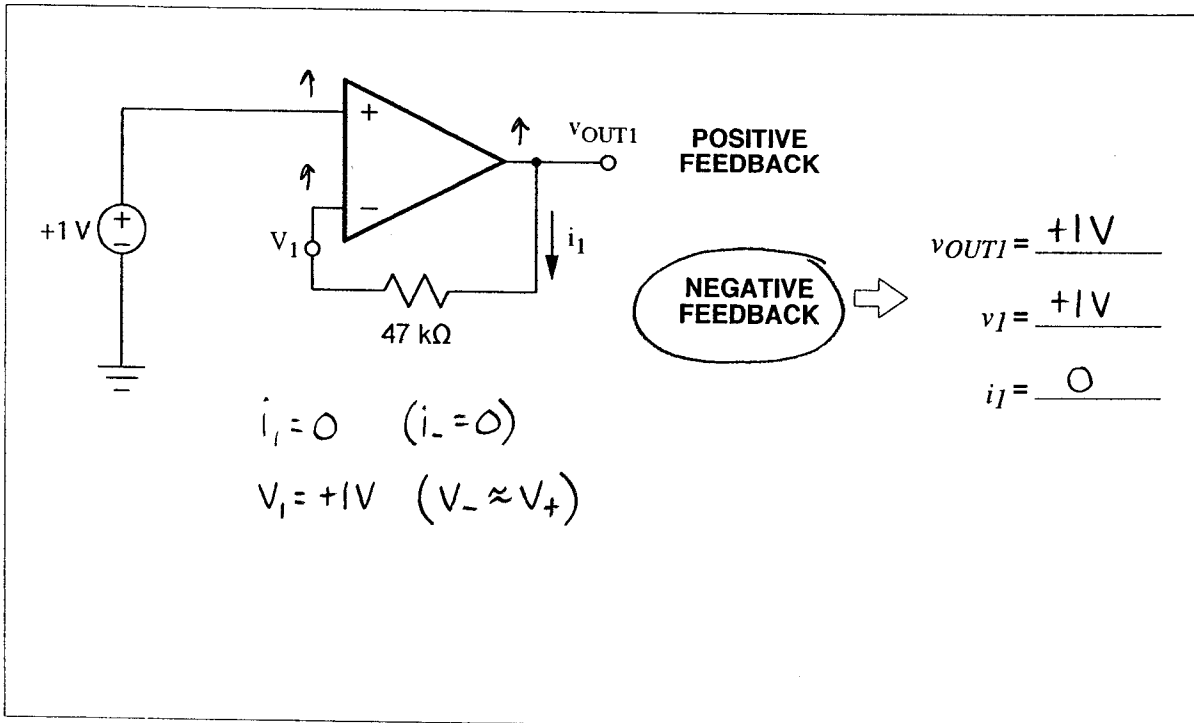

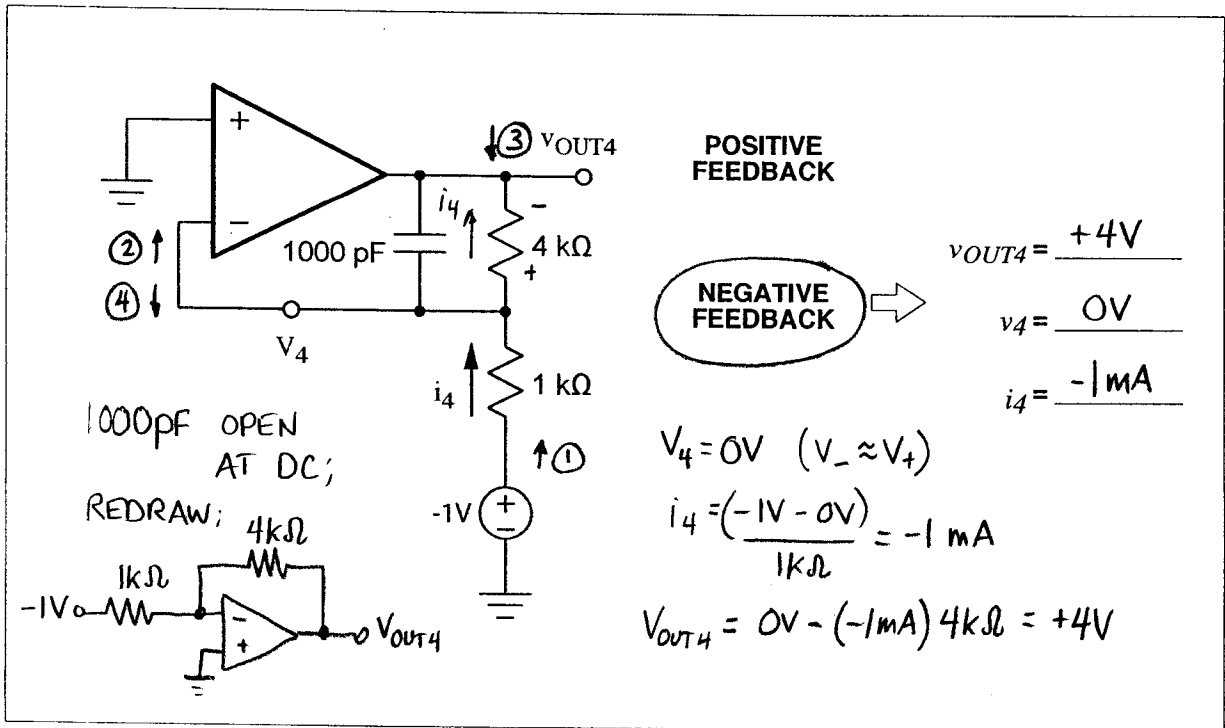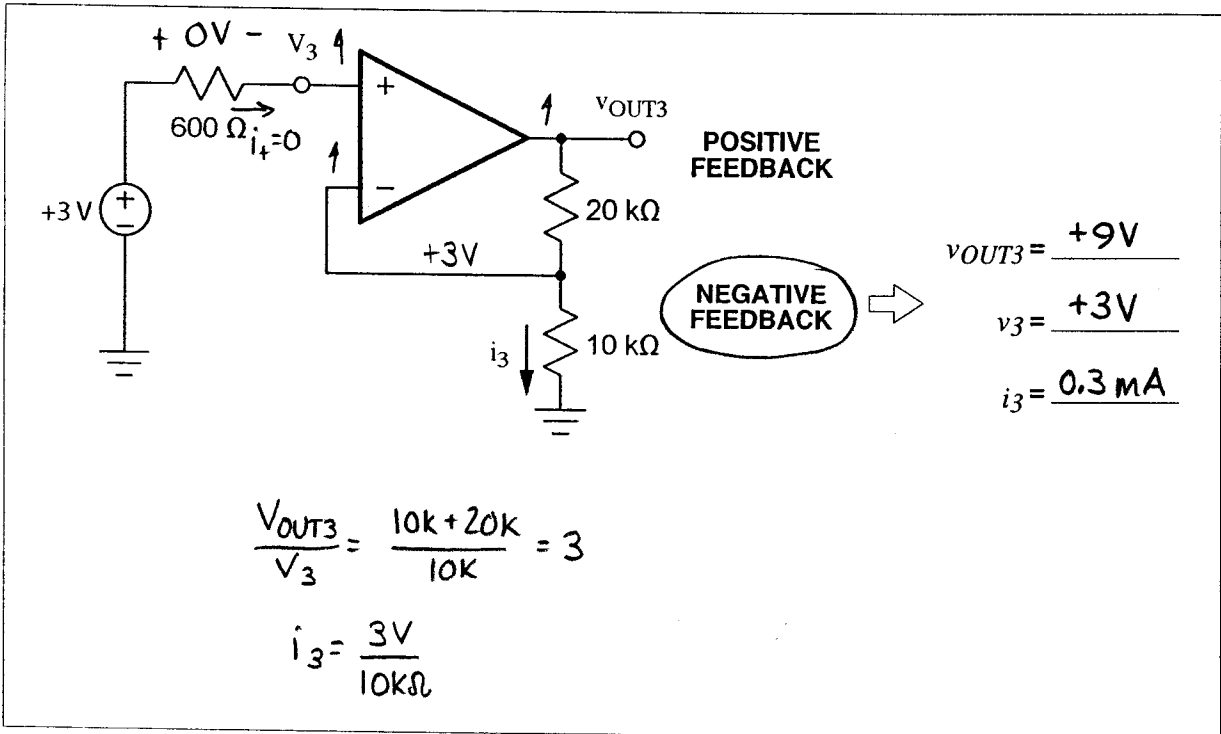

- 3) For the circuit shown on the opposite page, you may assume the op-amp to be ideal except for finite open-loop gain  $A$ . The open-loop DC gain is  $A_0 = 50,000$  and the unity gain frequency is  $f_T = 10$  MHz.
- a) Using the space on the opposite page, carefully plot  $|A|$  as a magnitude Bode plot over a frequency range from 1 Hz to 100 MHz. Be sure to label any interesting asymptotic values, intersection points, and/or slopes in your plot. [6]

- b) It is desired that the closed loop DC gain of the amplifier be +50. Find the required value of  $R_F$ . Nonstandard value is OK.

NONINVERTING GAIN CONFIGURATION [6]

$$R_F = \underline{490 \text{ k}\Omega} \quad \frac{R_F + 10 \text{ k}\Omega}{10 \text{ k}\Omega} = 50 \rightarrow R_F = 490 \text{ k}\Omega$$

- c) Given the choice of  $R_F$  in (b), what will the 3-dB bandwidth  $f_{3\text{-dB}}$  of the closed loop transfer function  $v_{\text{out}}/v_{\text{in}}$ ?

GAIN - BANDWIDTH RELATIONSHIP [6]

$$f_{3\text{-dB}} = \underline{200 \text{ kHz}} \quad 50 \times f_{3\text{-dB}} = f_T = 10 \text{ MHz}$$

$$f_{3\text{-dB}} = \frac{10 \text{ MHz}}{50} = 200 \text{ kHz}$$

- d) Using the same space on the opposite page, carefully superimpose a magnitude plot of the closed loop transfer function  $|v_{\text{out}}/v_{\text{in}}|$  over a frequency range from 1 Hz to 100 MHz. Be sure to label any interesting asymptotic values, intersection points, and/or slopes in your plot

$$\text{CLOSED LOOP DC GAIN: } 20 \log(50) = 34 \text{ dB} \quad [6]$$


- e) If a sine wave input of 1 MHz is applied to the closed loop amplifier, what will be the magnitude of the closed loop gain  $|v_{\text{out}}/v_{\text{in}}|$ ? (Accuracy  $\pm 10\%$ ; either a number or in dB is OK, just specify which)

[6]

$$\left| \frac{v_{\text{out}}}{v_{\text{in}}} \right|_{f=1 \text{ MHz}} = \underline{+20 \text{ dB}} \quad \text{GRAPHICALLY}$$


OR FROM TRANSFER FUNCTION
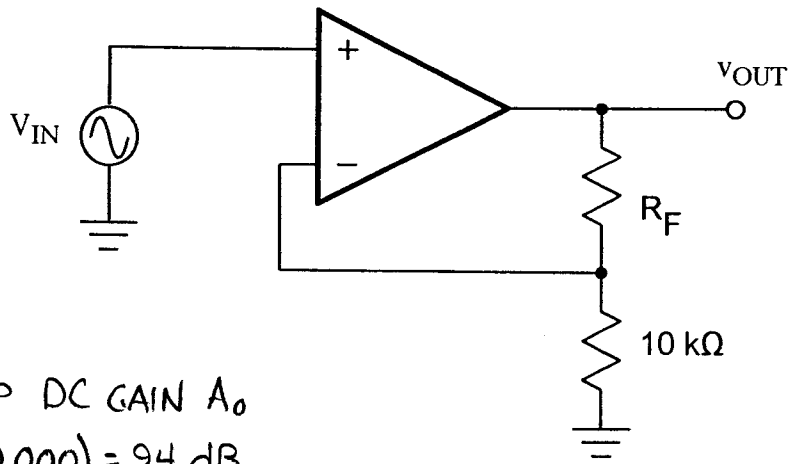
$$\frac{50}{\sqrt{1 + \left( \frac{1E+6}{200E+3} \right)^2}} = 9.8$$




OPEN LOOP DC GAIN  $A_o$   
 $20 \log(50000) = 94 \text{ dB}$

Axes for (a,d):

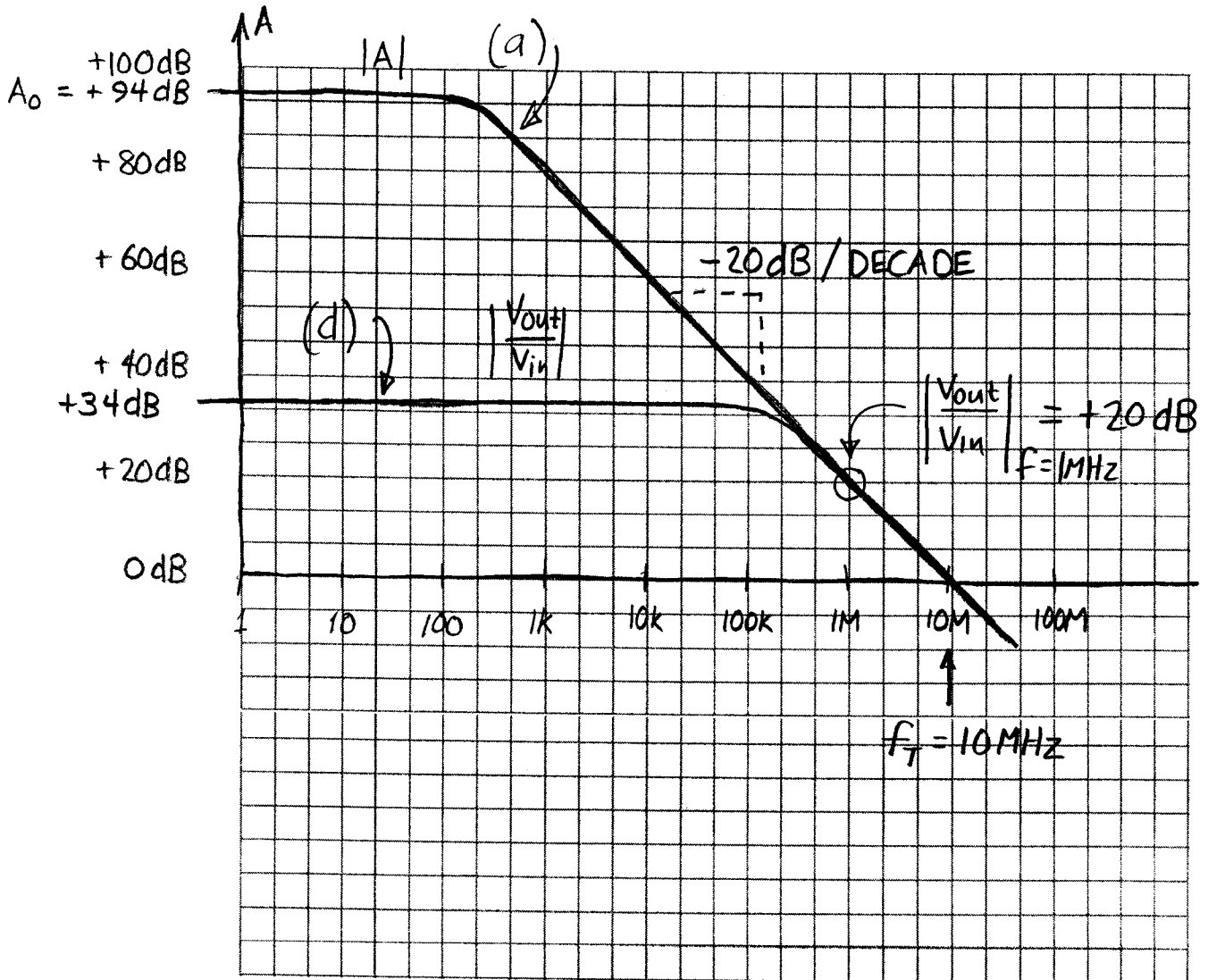




$(20\text{mV})\sin(2\pi ft)$

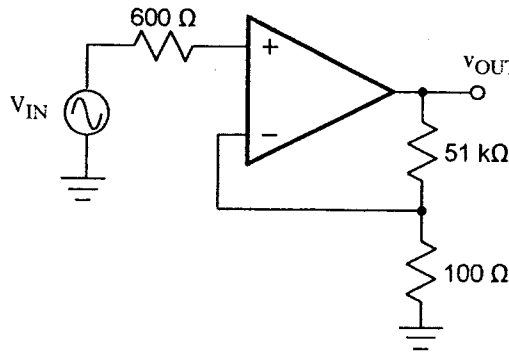



$$V_{OUT} = \left( \frac{51\text{k} + 100\Omega}{100\Omega} \right) V_{in} = 511 V_{in}$$

$$= (10.22 \text{ V}) \sin(2\pi ft)$$

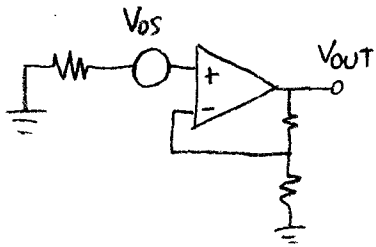V<sub>OS</sub> MODEL (SUPPRESS V<sub>IN</sub>)



Axes for (a):

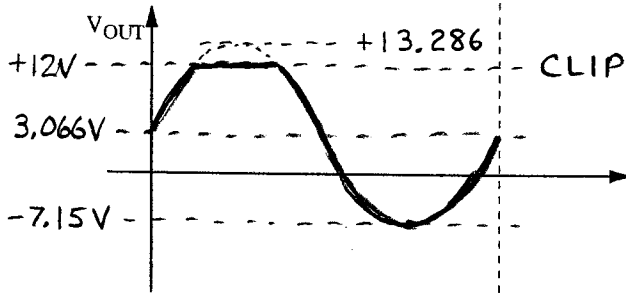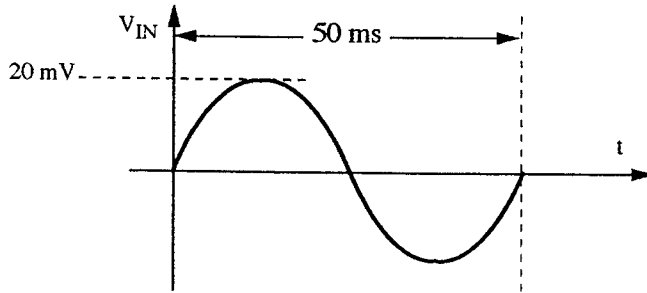

CHECK MAX  $\frac{dV}{dt}$

$$\left. \frac{dV_{OUT}}{dt} \right|_{MAX} = (10.22\text{V}) 2\pi f$$



$$= (10.22\text{V}) 2\pi (20\text{Hz})$$

$$= 1.28 \text{E}+3 \text{ V/sec}$$

$$\ll 0.5 \text{ V}/\mu\text{sec}$$

NO SLEW RATE LIMITING

Axes for (b):

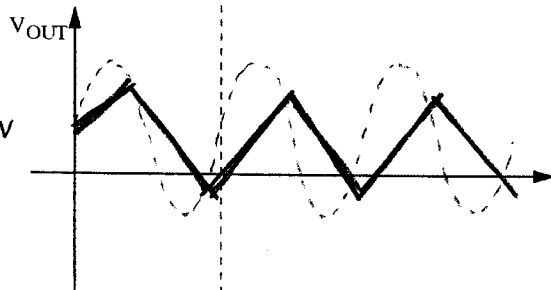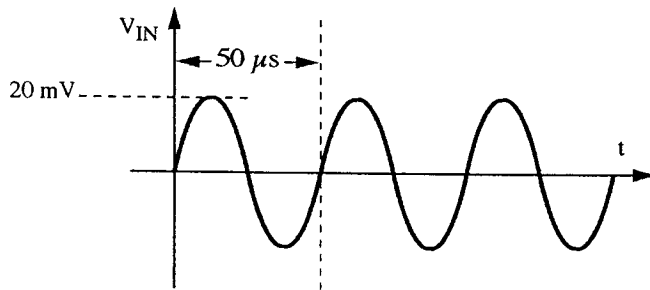

CHECK MAX  $\frac{dV}{dt}$

$$(10.22\text{V}) 2\pi (20\text{kHz})$$

$$= 1.28 \text{E}+6 \text{ V/sec}$$

$$= 1.28 \text{ V}/\mu\text{sec}$$

$$> 0.5 \text{ V}/\mu\text{sec}$$

OUTPUT WILL BE SLEW RATE LIMITED

$V_{OUT} = 511 V_{OS} = 3.066\text{V}$

741 WORST CASE: 6mV

ADD BY SUPERPOSITION:

$(10.22\text{V}) \sin(2\pi ft) + 3.066$

SAME DC OFFSET ERROR AS (a)