

**ECE3204 D2015**  
**HW Set 2**

Due in class Friday March 27.

To make life easier on the graders:

- Be sure your NAME and ECE MAILBOX NUMBER are prominently displayed on the upper right of what you hand in.
- When appropriate, indicate answers with a box or underline
- Work as neatly as possible

All problems from 6th edition

- 1) Text 1.66 (p. 49) [STC lowpass refresher]
- 2) Text F.10 (p. F-7 on DVD) [Transfer function, Bode plot practice]
- 3) Text D2.13 (p. 110) [Inverting op-amp design]
- 4) Text D2.44 (p. 113) [Noninverting op-amp design]
- 5) Text 2.53 (p. 115) [Unity gain buffer]
- 6) Text 2.107 (p. 122) [Op-amp open loop gain transfer function]
- 7) Text 2.108 (p. 122) [Op-amp open loop gain transfer function]
- 8) Text 2.113 (p. 122) [Gain-bandwidth product relationship]
- 9) Text 2.114 (p. 122) [Gain-bandwidth tradeoff]
- 10) Text D2.86 (p. 120) [Active single-pole lowpass filter]

This kind of configuration is often used prior to an analog-to-digital converter to combine the amplification and anti-aliasing lowpass filter functions in one circuit.

MORE ON THE FOLLOWING PAGES!!!


11) [Step response of active single-pole lowpass filter]

After completing the design of the previous problem, you have an inverting gain circuit with a DC gain magnitude of 20dB and a 3-dB frequency of 10kHz. Given that a negative-going input step waveform (transition from 0 to -1V) is applied at time  $t=0$ ,

- Sketch input  $V_i$  and output  $V_o$  waveforms
- Find the 10%-to-90% risetime at  $V_o$
- Find the time at which the output  $V_o$  has settled to within 1mV of its final value.

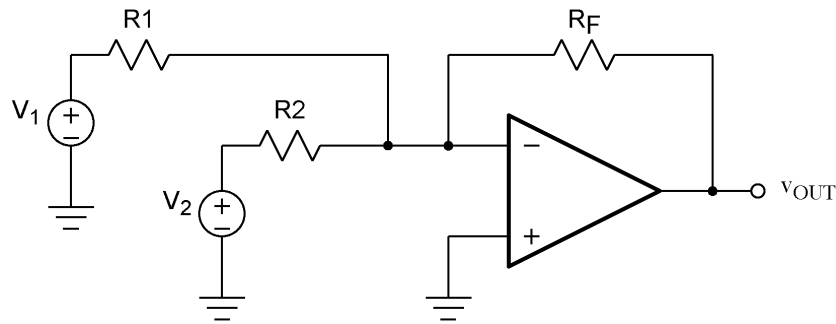12) [Ideal op-amp analysis refresher]

To find  $v_{OUT}$  for the ideal op-amp circuit below, perform the analysis in three different ways:



- Thevenin: Replace  $v_1/v_2/R_1/R_2$  with the Thevenin equivalent; then use the inverting gain equation.
- Superposition: Suppress  $v_1$  and find the output due to  $v_2$ ; then suppress  $v_2$  and find the output due to  $v_1$ ; then add for the total output.
- Virtual Ground: Use the virtual ground to calculate the currents in  $R_1$  and  $R_2$ ; then use KCL to determine the current in  $R_F$ ; then find  $v_{OUT}$ .

Show that since all three methods give the same answer, you can use whichever technique you are most comfortable with when analyzing an op-amp circuit.

13)

[Practice verifying negative feedback]

For each of the op-amp circuits shown below, determine if the op-amp is configured for negative or positive feedback.

