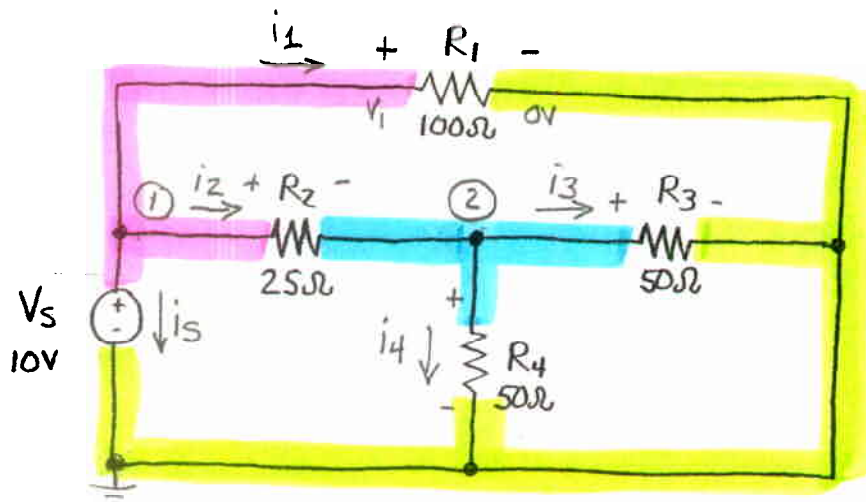


## Nodal Analysis Procedure

- 1 Select reference node (usually one end of a voltage source) mark with ground 0V symbol
- 2 Label node voltages (implied with respect to 0V reference)
- 3 Label element currents
- 4 Write KCL equation at each node
- 5 Write element V-I constraints (may eliminate some “unknowns”)
- 6 Solve system of equations

If circuit is properly defined, procedure will always work



- 1 REF NODE: BOTTOM OF  $V_s$
- 2 LABEL NODE VOLTAGES (ONLY 3 NODES: REF, ①, ②)
- 3 ELEMENT CURRENTS (PASSIVE REF CONFIG)
- 4 KCL AT EACH NODE

①  $i_s + i_2 + i_1 = 0$

②  $i_2 = i_3 + i_4$  OR  $i_2 - i_3 - i_4 = 0$

- 5 ELEMENT V-I CONSTRAINTS

$R_1 - R_4$ : OHM'S LAW  $V = iR \Rightarrow i = \frac{V}{R}$  VOLTAGE DROP ACROSS R

$$i_1 = \frac{V_1 - 0}{R_1} = \left(\frac{1}{R_1}\right)V_1$$

$$i_2 = \frac{V_1 - V_2}{R_2} = \left(\frac{1}{R_2}\right)V_1 - \left(\frac{1}{R_2}\right)V_2$$

$$i_3 = \left(\frac{1}{R_3}\right)V_2$$

$$i_4 = \left(\frac{1}{R_4}\right)V_2$$

$i_s = ?$  VOLTAGE CONSTRAINT:  $V_1 = V_s$   $V_1$  KNOWN

UNKNOWN ARE  $i_s, V_2$

- 6 SOLVE

6 SOLVE!

SUB INTO ①

$$i_s + \underbrace{\left(\frac{1}{R_2}\right) \overset{V_s}{V_1}}_{i_2} - \left(\frac{1}{R_2}\right) V_2 + \underbrace{\left(\frac{1}{R_1}\right) \overset{V_s}{V_1}}_{i_1} = 0 \Rightarrow -i_s + \left(\frac{1}{R_2}\right) V_2 = \left(\frac{1}{R_2} + \frac{1}{R_1}\right) V_s$$

SUB INTO ②

$$\left(\frac{1}{R_2}\right) \overset{V_s}{V_1} - \left(\frac{1}{R_2}\right) V_2 - \left(\frac{1}{R_3}\right) V_2 - \left(\frac{1}{R_4}\right) V_2 = 0 \Rightarrow \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) V_2 = \left(\frac{1}{R_2}\right) V_s$$


NUMERICALLY, IN MATRIX FORM

$$\begin{bmatrix} -1 & 0.04 \\ 0 & 0.08 \end{bmatrix} \begin{bmatrix} i_s \\ V_2 \end{bmatrix} = \begin{bmatrix} 1.4 \\ 0.4 \end{bmatrix}$$

SOLVING

$$\Rightarrow V_2 = +5V$$


$$i_s = 0.3A$$

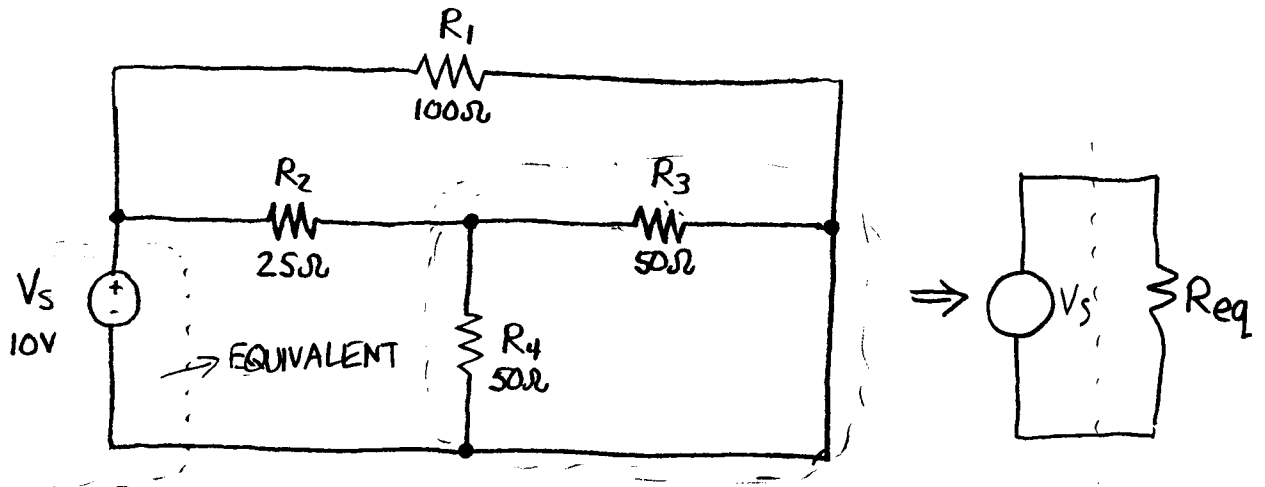


WHAT IF WE JUST NEEDED  $i_s$ ?  
USE SERIES, PARALLEL

$$R_3 \parallel R_4 = \frac{1}{\frac{1}{R_3} + \frac{1}{R_4}} = \frac{1}{\frac{1}{50\Omega} + \frac{1}{50\Omega}} = 25\Omega$$

"PARALLEL"

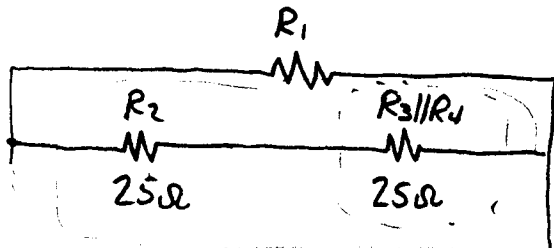


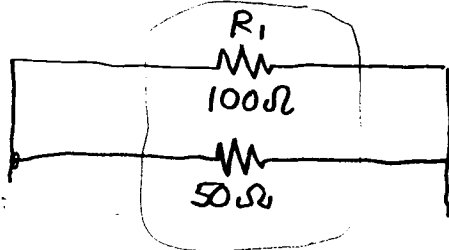SERIES:  $25\Omega + 25\Omega = 50\Omega$



$$\frac{1}{\frac{1}{100\Omega} + \frac{1}{50\Omega}} = 33.3\Omega$$

PARALLEL

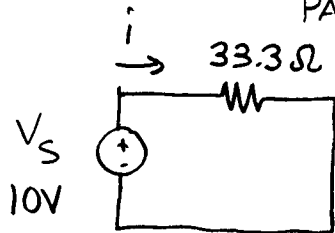

OHM'S LAW:  $i = \frac{10V}{33.3\Omega} = 0.3A \checkmark$