



OPEN LOOP GAIN A	OPEN LOOP		CLOSED LOOP, NEGATIVE FEEDBACK	
	GAIN v_{OUT}/v_{IN}	$ v_{OUT} $ for 10mV v_{IN}	GAIN v_{OUT}/v_{IN}	$ v_{OUT} $ for 10mV v_{IN}