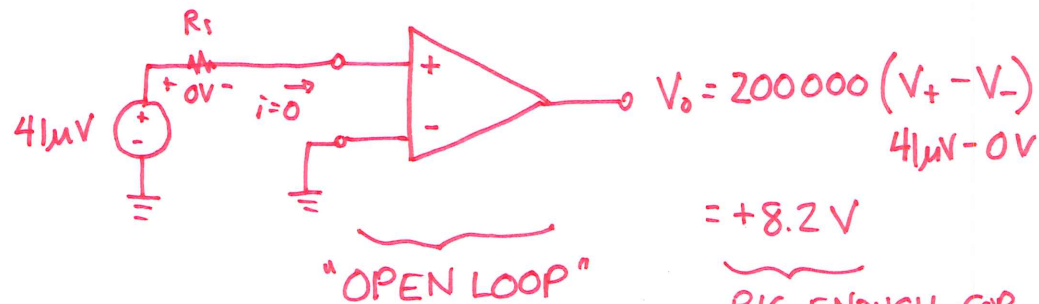


ECE3204 Lecture 3

THERMOCOUPLE → OPEN LOOP OP-AMP

Ideal Op-Amp (2.1)
Noninverting Gain (2.2)



Handout:
Open-Loop vs. Closed-Loop



ALMOST NEVER USED THIS WAY!


BIG ENOUGH FOR DVM! ✓

MICROPHONE

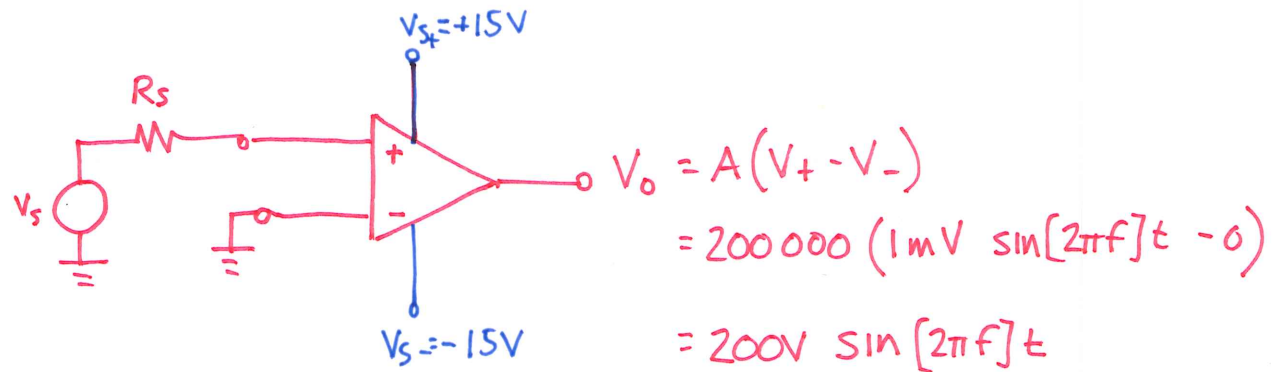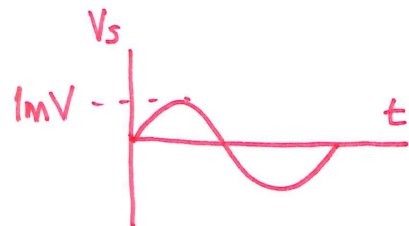

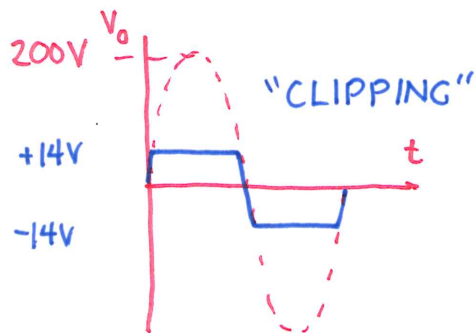PROBLEM: V_o NOT SCALED VERSION OF V_s INPUT!
⇒ DISTORTION

IF INPUT EXCEEDS INPUT LINEAR RANGE: CLIPPING
NEED TO STAY INSIDE $\pm 70\mu V$ LINEAR RANGE




KCL?

$i_- = 0 \quad i_+ = 0 \quad i_o \neq 0?$



POWER SUPPLIES
NEED V_{S+}, V_{S-}

LIMITS OUTPUT
VOLTAGE SWING

HOW FAR CAN
VOLTAGE MOVE
AT OUTPUT

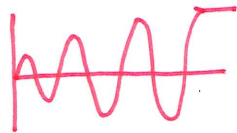

ECE3204 IDEAL OP-AMP SUMMARY

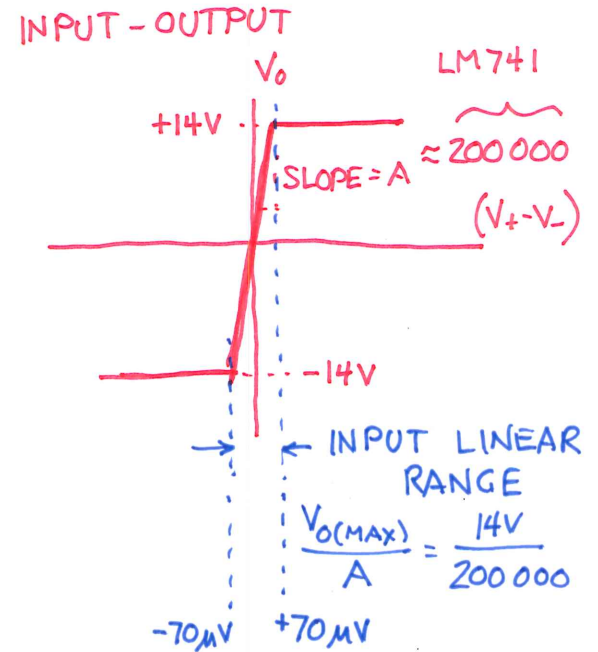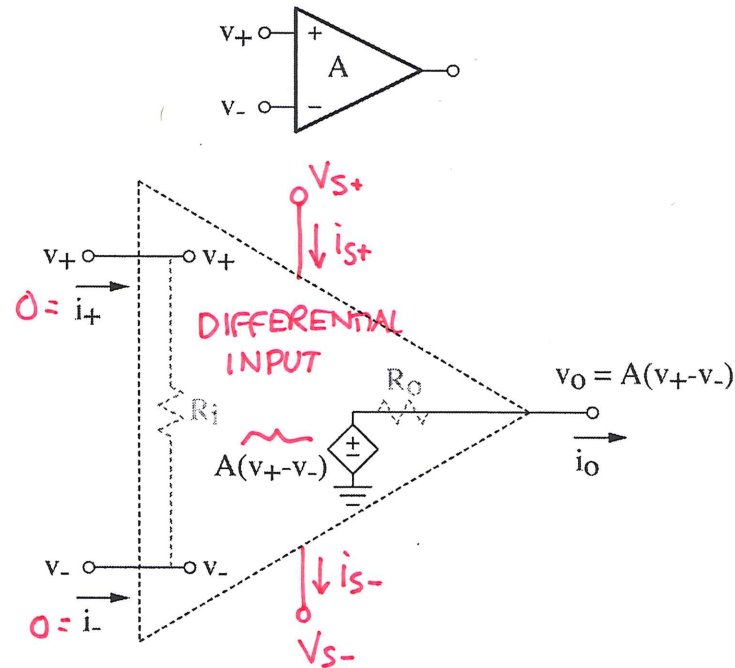

PROPERTY	INPUT RESISTANCE	OPEN LOOP GAIN	BANDWIDTH	OUTPUT RESISTANCE
IDEALIZATION	$R_i = \infty$	$A \Rightarrow \infty$	$BW = \infty$	$R_o = 0$
MEANING	Input currents = 0	Any v_o can be "supported" by infinitesimally small differential input ($v_+ - v_-$)	Signal of any frequency is OK	Output "looks like" ideal voltage source. Can drive any current required by load resistance
CONSEQUENCE	KCL at -, + terminals simplified. Always known that $i_- = 0$ and $i_+ = 0$	When negative feedback is present, $v_- = v_+$		Output current i_o determined by load

RANGE

LM741


Electrical Characteristics (Note 5) (Continued)

Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Large Signal Voltage Gain	$T_A = 25^\circ\text{C}$, $R_L \geq 2\text{ k}\Omega$ $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$ $V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$	50			50	200		20	200		V/mV V/mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$, $R_L \geq 2\text{ k}\Omega$, $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$	32			25			15			V/mV
	$V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$ $V_S = \pm 5\text{V}$, $V_O = \pm 2\text{V}$	10									V/mV V/mV
Output Voltage Swing	$V_S = \pm 20\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$	± 16 ± 15									V V
	$V_S = \pm 15\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$				± 12 ± 10	± 14 ± 13		± 12 ± 10	± 14 ± 13		V V
Output Short Circuit Current	$T_A = 25^\circ\text{C}$	10	25	35		25			25		mA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$	10		40							mA
Common-Mode Rejection Ratio	$T_{AMIN} \leq T_A \leq T_{AMAX}$ $R_S \leq 10\text{ k}\Omega$, $V_{CM} = \pm 12\text{V}$				70	90		70	90		dB
	$R_S \leq 50\Omega$, $V_{CM} = \pm 12\text{V}$	80	95								dB
Supply Voltage Rejection Ratio	$T_{AMIN} \leq T_A \leq T_{AMAX}$, $V_S = \pm 20\text{V}$ to $V_S = \pm 5\text{V}$										dB
	$R_S \leq 50\Omega$ $R_S \leq 10\text{ k}\Omega$	86	96		77	96		77	96		dB dB
Transient Response Rise Time	$T_A = 25^\circ\text{C}$, Unity Gain		0.25	0.8		0.3			0.3		μs
			6.0	20		5			5		%
Bandwidth (Note 6)	$T_A = 25^\circ\text{C}$	0.437	1.5								MHz
Slew Rate	$T_A = 25^\circ\text{C}$, Unity Gain	0.3	0.7			0.5			0.5		V/ μs
Supply Current	$T_A = 25^\circ\text{C}$					1.7	2.8		1.7	2.8	mA
Power Consumption	$T_A = 25^\circ\text{C}$ $V_S = \pm 20\text{V}$ $V_S = \pm 15\text{V}$		80	150							mW mW
	LM741A $V_S = \pm 20\text{V}$ $T_A = T_{AMIN}$ $T_A = T_{AMAX}$										mW mW
LM741	$V_S = \pm 15\text{V}$ $T_A = T_{AMIN}$ $T_A = T_{AMAX}$					60	100				mW mW
						45	75				mW


} OPEN LOOP GAIN A

200,000

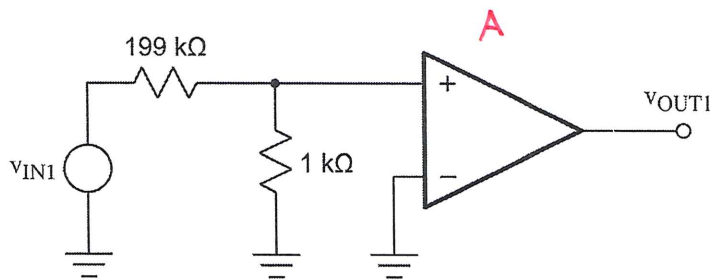Note 2: "Absolute Maximum Ratings" indicate limits beyond which damage to the device may occur. Operating Ratings indicate conditions for which the device is functional, but do not guarantee specific performance limits.



$$\left(\frac{1}{200}\right) A$$

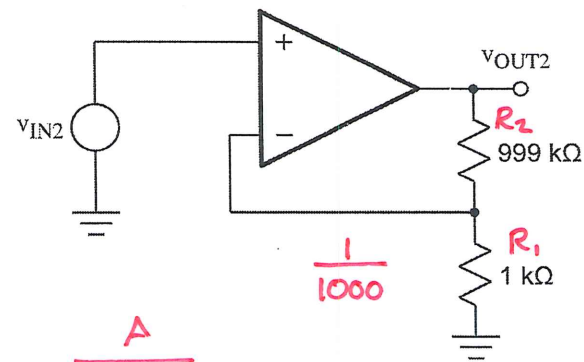

$$\frac{A}{1 + \frac{A}{1000}}$$

OPEN LOOP GAIN
A

OPEN LOOP

CLOSED LOOP,
NEGATIVE FEEDBACK

GAIN v_{OUT}/v_{IN}

$|v_{OUT}|$ for 10mV v_{IN}

GAIN v_{OUT}/v_{IN}

$|v_{OUT}|$ for 10mV v_{IN}

20 000

100

1V small?

952

9.52 V ✓

TYP → 200 000

1000

10V ✓

995

9.95 V ✓

2 000 000

10 000

~~100V~~ CLIP!

999.5



9.995V ✓

TOO SENSITIVE
TO VARIATIONS
IN OPEN LOOP
GAIN A!


MUCH LESS SENSITIVE
TO VARIATIONS IN A!

$(V_+ - V_-)$ WAS TOO BIG: MAKE SMALLER TO STAY INSIDE $\pm 70\mu\text{V}$ LINEAR RANGE

VOLTAGE DIVIDER

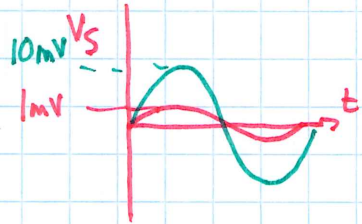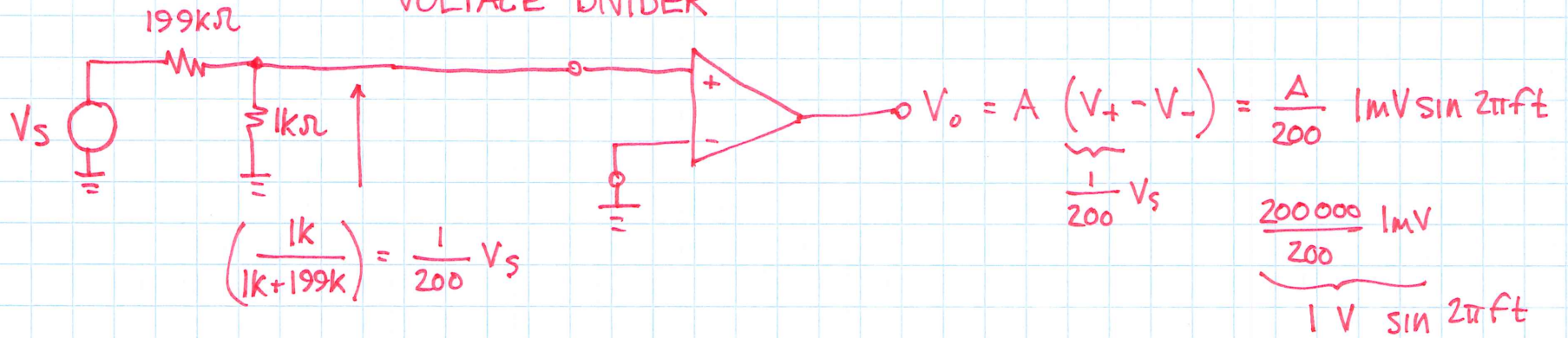


① TOO SENSITIVE TO A!

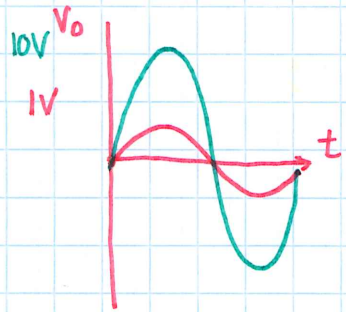

~~DON'T DO THIS!~~

② NEGATIVE FEEDBACK

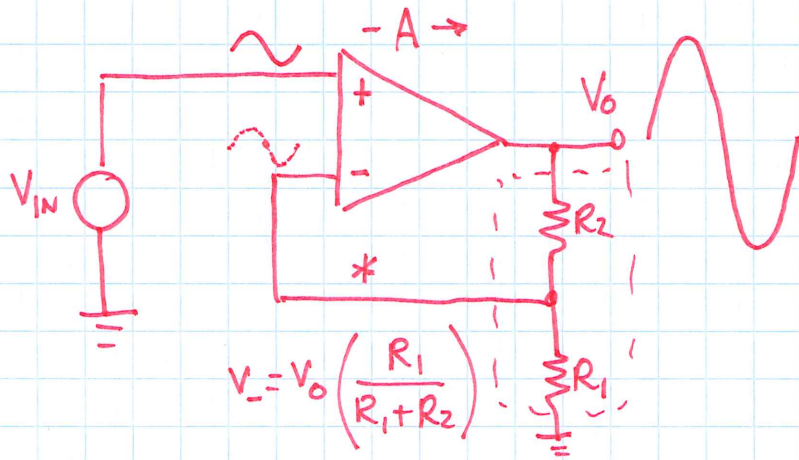

$$V_O = A(V_+ - V_-) = A V_{IN} - A V_O \left(\frac{R_1}{R_1 + R_2} \right)$$

SOLVE FOR V_O AS A FUNCTION OF V_{IN}

$$V_O \left[1 + A \left(\frac{R_1}{R_1 + R_2} \right) \right] = A V_{IN}$$

$$\text{GAIN } \frac{V_O}{V_{IN}} = \frac{A}{1 + A \left(\frac{R_1}{R_1 + R_2} \right)}$$

$$\frac{A}{1 + A \left(\frac{R_1}{R_1 + R_2} \right)}$$

$$A \rightarrow \infty \quad \frac{V_O}{V_{IN}} \approx \frac{R_1 + R_2}{R_1}$$

DEPENDS ONLY ON
FEEDBACK ELEMENTS!

THOUGHT PROCESS

PROBLEM: $(V_+ - V_-)$ TOO BIG
[OUTSIDE LINEAR RANGE]

APPLY ALL OF V_{IN} TO V_+

IF EVERYTHING'S WORKING:
AMPLIFIED VERSION OF
 V_{IN} AT OUTPUT V_O

MAKE $(V_+ - V_-)$ SMALL BY
SUBTRACTING A V_- THAT
IS ALMOST SAME AS V_+

SMALL DIFFERENCE;
 $(V_+ - V_-)$ INSIDE LINEAR RANGE

* ATTENUATE V_O TO MAKE
 V_- THAT IS $\approx V_+$