


ECE3204 Lecture 4

Negative Feedback
Noninverting Gain (2.3)
Inverting Gain (2.2)
Bandwidth Limit (2.7)

Hand in: HW 1

HW 2 online

Noninverting gain op-amp circuit

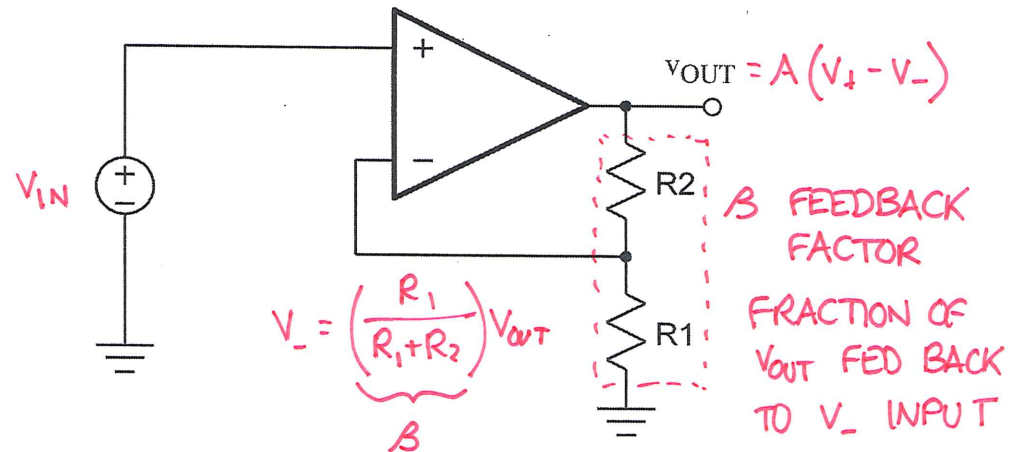

MATH
 \Rightarrow

$$V_{OUT} = A(V_{IN} - B V_{OUT})$$


$$V_{OUT}(1 + AB) = A V_{IN}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + AB} \Rightarrow \frac{1}{B}$$

$AB \gg 1$

DETERMINED
BY FEEDBACK,
NOT A \checkmark


"Guess my rule"

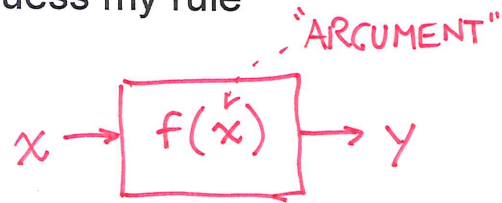

x	y
32	1022
0	-2
100	9998
5	23
1	-1

$$f(x) = x^2 - 2$$

Op-amp's "rule"

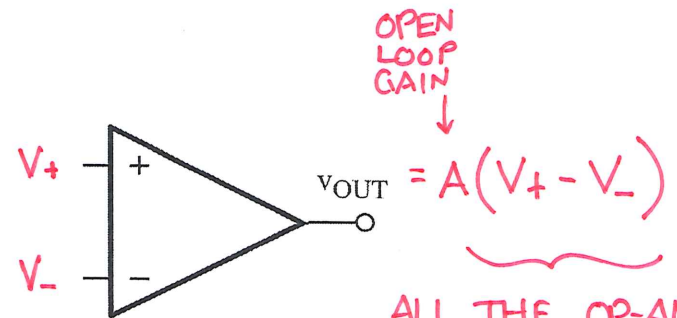

ALL THE OP-AMP
"KNOWS" ABOUT THE
EXTERNAL WORLD

HOW DOES V_{OUT} CHANGE?


$$V_{+} > V_{-} \Rightarrow V_{OUT} \uparrow$$

$$V_{-} > V_{+} \Rightarrow V_{OUT} \downarrow$$

⇒ WHICHEVER INPUT (+ OR -)
IS HIGHER (MORE POSITIVE) IN VOLTAGE
TELLS \uparrow OR \downarrow OF OUTPUT

Analog Stick of Knowledge

Height - Voltage analogy

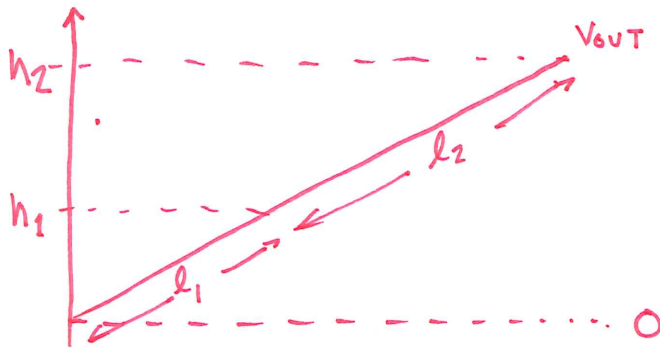


SIMILAR TRIANGLES

$$\frac{h_1}{l_1} = \frac{h_2}{l_1+l_2}$$

$$h_1 = h_2 \left(\frac{l_1}{l_1+l_2} \right)$$

Noninverting gain op-amp circuit

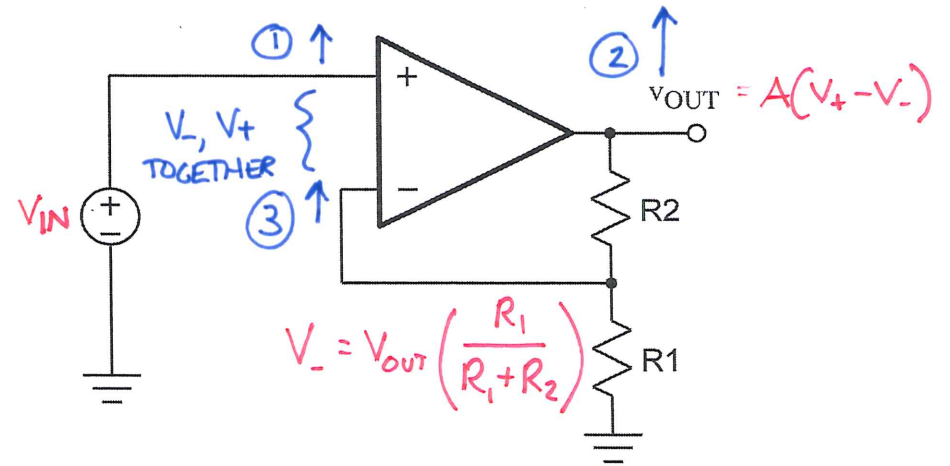

① $V_{IN} \uparrow$

② RULE: $V_{OUT} \uparrow$

③ VOLTAGE DIVIDER: $V_- \uparrow$ BY SOME FRACTION $\frac{R_1}{R_1+R_2}$

$$V_{OUT} = A(V_+ - V_-)$$

$$V_+ - V_- = \frac{V_o}{A} \quad \text{IF IN LINEAR REGION}$$

Op-Amp Analysis

FIRST: CHECK NEGATIVE FEEDBACK

1. Change v_{IN}
2. Follow change around loop
3. Does v_{OUT} change to keep v_- , v_+ together?
If yes: negative feedback


THEN $v_- \approx v_+$

(How \approx ? Depends on A large)

$$A = 200\,000$$

$$V_{OUT} = \frac{\pm 14V}{200\,000} \pm 70\mu V$$

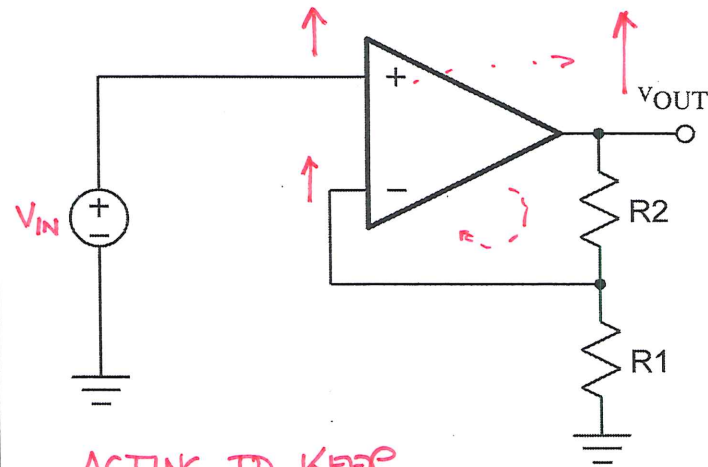Simpler analysis of noninverting gain op-amp circuit



ACTING TO KEEP

V_- , V_+ TOGETHER:


NEGATIVE FEEDBACK

$$V_- = V_+ \quad A \rightarrow \infty$$

$$\left(\frac{R_1}{R_1 + R_2}\right) V_{OUT} = V_{IN}$$

$$V_{OUT} = \left(\frac{R_1 + R_2}{R_1}\right) V_{IN}$$


Examples

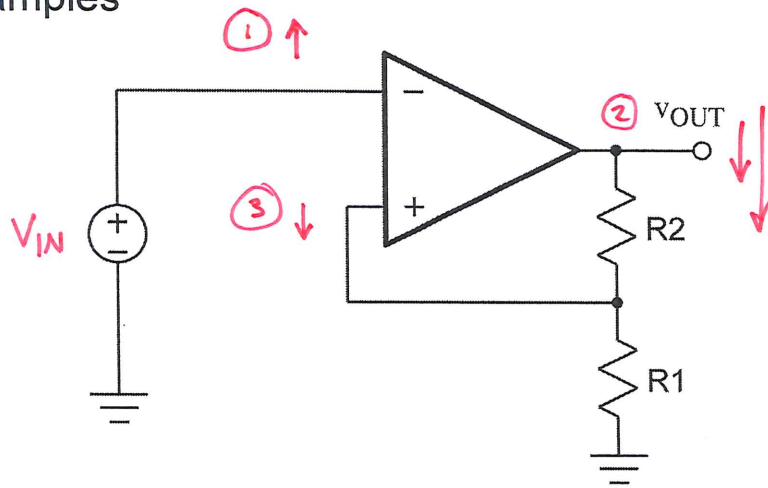

NEGATIVE FEEDBACK? NO!

V_-, V_+ APART!

$V_- \neq V_+$

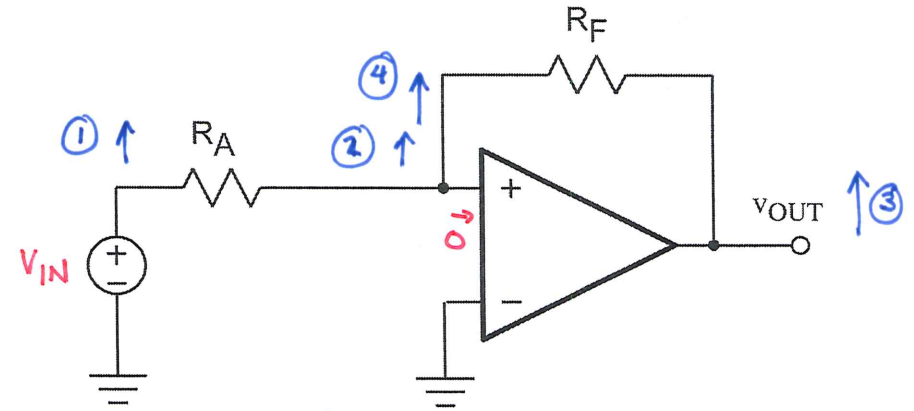


$$V_+ = \left(\frac{R_F}{R_A + R_F} \right) V_{IN} + \left(\frac{R_A}{R_A + R_F} \right) V_{OUT}$$

PULLS V_+ AWAY FROM V_-

NOT NEGATIVE FB!

Inverting Gain Op-Amp Circuit

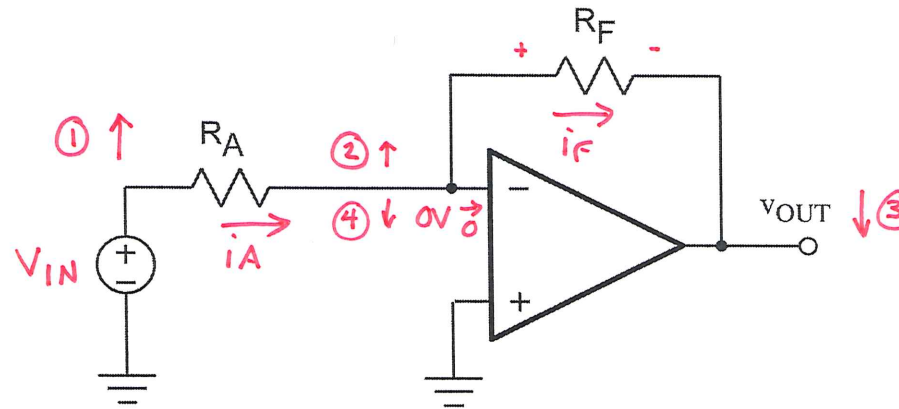

LOOP TRIES TO KEEP $V_- = V_+$: NEGATIVE FEEDBACK ✓

$$\Rightarrow \underbrace{V_- = V_+}_{\text{w}} = 0V$$

"VIRTUAL GROUND"

KCL AT V_- INPUT: $I_A = I_F$

OHM'S LAW

$$\frac{V_{IN}}{R_A} = \frac{-V_{OUT}}{R_F}$$

$$\Rightarrow V_{OUT} = \left(\frac{-R_F}{R_A} \right) V_{IN}$$

WHAT ABOUT XFMR?

