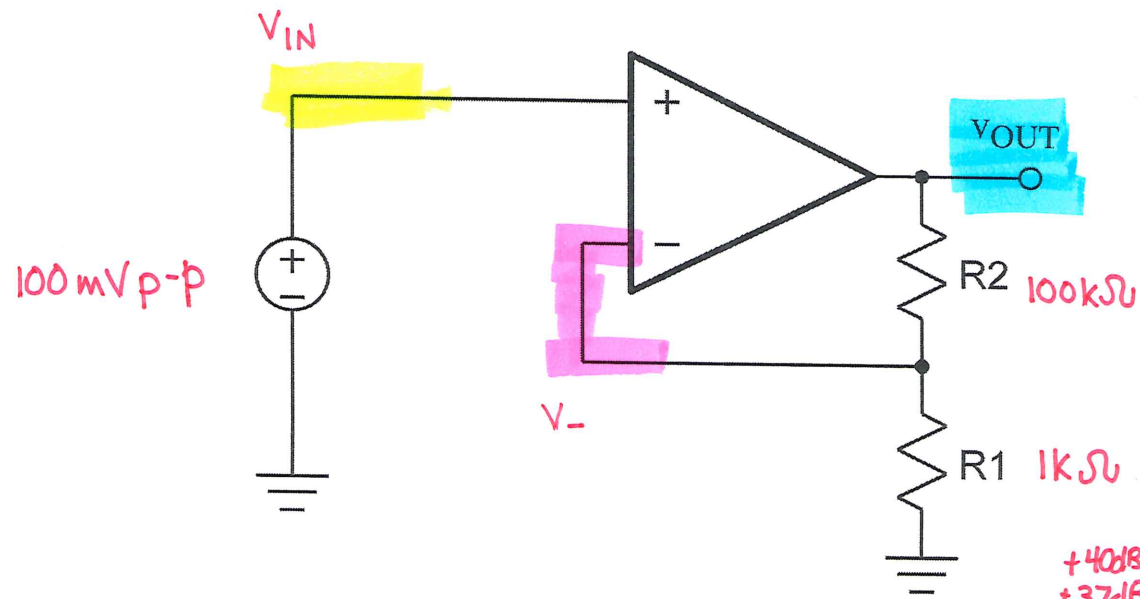



Noninverting gain op-amp circuit Scope Photos



10V p-p

	V_{IN}	V_{OUT}
100Hz	100 mV	10V p-p
10kHz	100 mV	7.5V pp

	$ V_{OUT}/V_{IN} $	
100Hz	100	+40dB
10kHz	75	+37dB

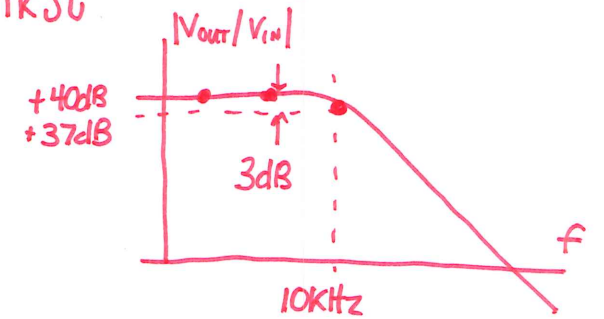

DELAYED: OP-AMP CAN'T "CATCH UP"

V_- , V_+ NOT REALLY EQUAL

WHAT TO DO? □ CHANGE MAJOR

✓ FIND A WAY TO TALK ABOUT IT