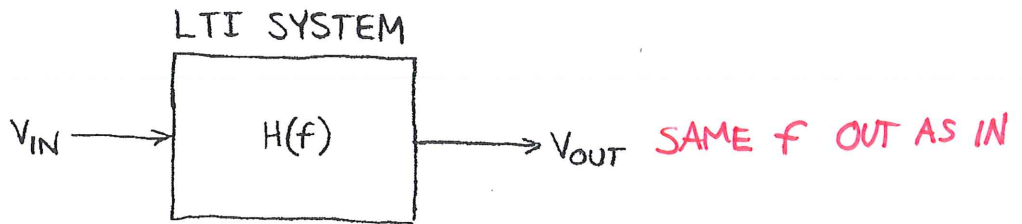



TRANSFER FUNCTION  $H(f)$  ( $H(s)$ ,  $H(\omega)$ ,  $H(j\omega)$ ,  $H(j2\pi f)$ )



MAGNITUDE : SCALE  
PHASE : SHIFT

$$\underbrace{V_{OUT}(f)}_{\text{OUTPUT SPECTRUM}} = \underbrace{V_{IN}(f)}_{\text{INPUT SPECTRUM}} \underbrace{H(f)}_{\text{TRANSFER FUNCTION}}$$

EXAMPLE

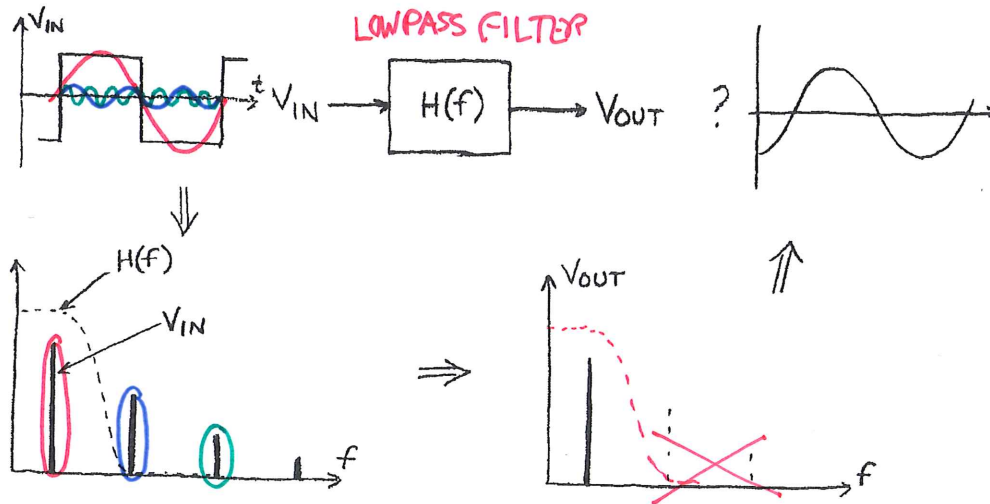

(DO THIS IN LAB 5!)

FOURIER TRANSFORM; REPRESENT  $V$  AS SUM OF COMPLEX EXPONENTIALS

$$V = V_0 e^{j\omega t}$$

$$V = V_0 e^{st}$$

WHY? I-V FOR CAPACITOR

$$I = C \frac{dV}{dt}$$

CAN THIS BE AS EASY AS  $\Omega$ S LAW:  $I = \frac{V}{R}$ ?

$$I = C \frac{d}{dt} V_0 e^{j\omega t}$$

$$I = j\omega C \underbrace{V_0 e^{j\omega t}}_V$$

$$I = (j\omega C)V$$

$$\frac{V}{I} = \frac{1}{j\omega C}$$

$\frac{V}{I}$  RATION

"IMPEDANCE": LIKE RESISTANCE, BUT COMPLEX

FREQUENCY DEPENDENT

$j$ : "ENCODES"  $90^\circ$  PHASE SHIFT

$e^{st}$

$$Z_R = R$$

$$Z_R = R$$


$$Z_C = \frac{1}{j\omega C}$$

$$Z_C = \frac{1}{sC}$$

$$Z_L = j\omega L$$

$$Z_L = sL$$

## ANALYSIS EXAMPLE: LOWPASS FILTER

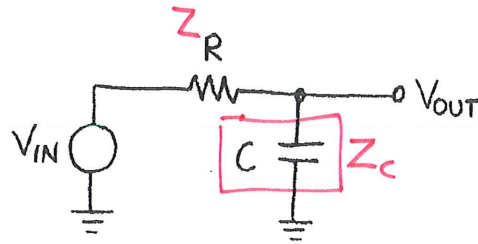

## IMPEDANCE DIVIDER

$$V_{OUT} = \left( \frac{Z_C}{Z_R + Z_C} \right) V_{IN}$$

$$V_{OUT} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{IN}$$

$$\frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

$$V_{OUT} = \underbrace{\frac{1}{1 + j\omega RC}}_{H(j\omega)} V_{IN}$$

TRANSFER FUNCTION: GENERALIZED GAIN  $V_{OUT}/V_{IN}$ 

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{1 + j\omega RC}$$

$$\frac{1}{1 + sRC}$$


"FREQUENCY RESPONSE": FIND MAGNITUDE, PHASE ( $s = j\omega$ )

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \left| \frac{1}{1 + j\omega RC} \right|$$

$$\angle \frac{V_{OUT}}{V_{IN}} = \angle \frac{1}{1 + j\omega RC}$$
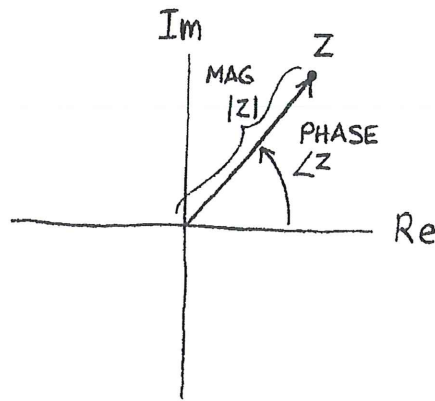
## COMPLEX NUMBER REFRESHER

$$z = \frac{a+jb}{x+jy} \quad \frac{\cancel{x-jy}}{\cancel{x-jy}}$$



## MAGNITUDE

$$|z| = \frac{\sqrt{a^2 + b^2}}{\sqrt{x^2 + y^2}}$$

$$|z| = \frac{|\text{NUM}|}{|\text{DEN}|}$$

## PHASE

$$\angle z = \tan^{-1}(b/a) - \tan^{-1}(y/x)$$

$$\angle z = \angle \text{NUM} - \angle \text{DEN}$$

TRANSFER FUNCTIONS (USUALLY) WILL BE RATIOS OF POLYNOMIALS IN COMPLEX VARIABLE  $s$

WE WILL LET  $s = j\omega$  TO GET FREQUENCY RESPONSE


MAGNITUDE, PHASE OF STC LOWPASS

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{\sqrt{1^2 + 0^2}}{\sqrt{1^2 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (2\pi f RC)^2}}$$

$$\angle H(j\omega) = \tan^{-1}(0/1) - \tan^{-1}(\omega RC/1) = -\tan^{-1}(\omega RC) = -\tan^{-1}(2\pi f RC)$$

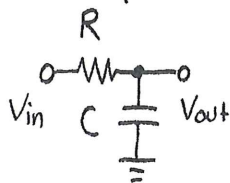EXAMPLE:  $R = 7.5 \text{ k}\Omega$   
 $C = 1000 \text{ pF}$




$$RC = 7.5 \mu\text{sec}$$


| f       | MAGNITUDE<br>$ H(f) $ | PHASE<br>$\angle H(f)^\circ$ | $20 \log(H(f))$<br>dB |
|---------|-----------------------|------------------------------|-----------------------|
| 1 Hz    | 1                     | -0.003°                      | 0 dB UNITY GAIN       |
| 10 Hz   | 1                     | -0.03°                       | 0                     |
| 100     | 0.9999                | -0.27°                       | 0                     |
| 1 kHz   | 0.9989                | -2.7°                        | -0.01 dB              |
| 10 kHz  | 0.9046                | -25.2°                       | -0.87 dB              |
| 21 kHz  | 0.707                 | -45.0°                       | -3.0 dB               |
| 100 kHz | 0.2076                | -78.0°                       | -13.7 dB              |
| 1 MHz   | 0.0212                | -88.8°                       | -33.5 dB              |
| 10 MHz  | 0.0021                | -89.9°                       | -53.5 dB              |

10X ↙  
BANDWIDTH  
f-3d  
"3dB FREQ"  
↖ 3dB down from max value  
-20dB ↘ } -20 dB PER DECADE f  
"ROLL OFF"

PLOT (LINEAR SCALE)

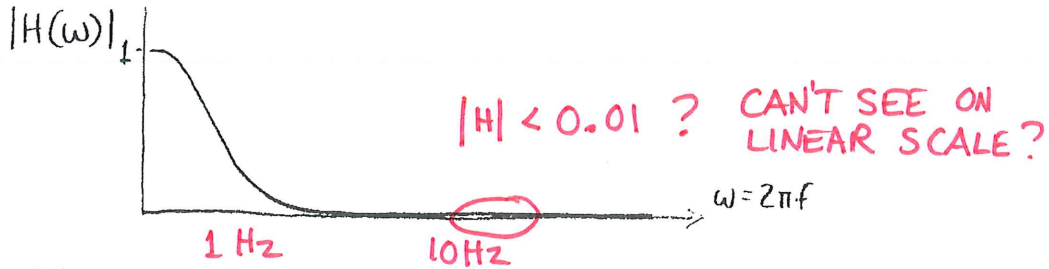

LOG/LOG SCALE

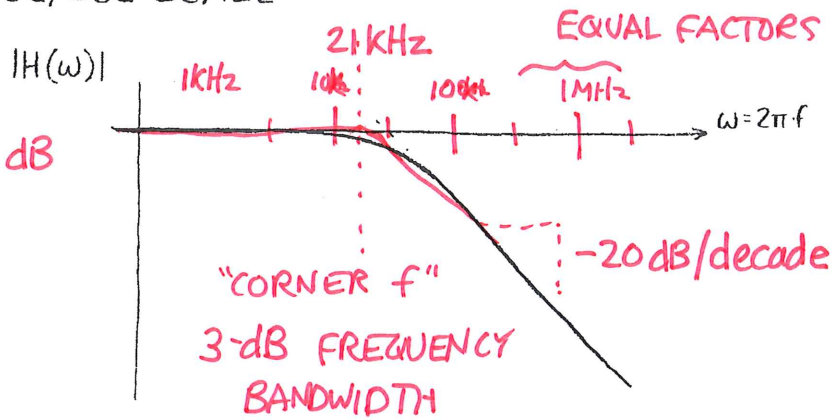

10 MHz  
INSTITUTE  
PARK

"BODE PLOT": USE dB

$$\left(\frac{V_2}{V_1}\right) \text{ dB} = 20 \log\left(\frac{V_2}{V_1}\right)$$

VOLTAGE RATIO

EXAMPLE:  $A = 50,000$

$$20 \log(A) = 20 \times 4.7 = +94 \text{ dB}$$

"3dB FREQUENCY"

$$20 \log\left(\frac{1}{\sqrt{2}}\right) = -3 \text{ dB}$$

$$\frac{1}{\sqrt{2}} = 0.707$$

$|H(\omega)|$  HAS DROPPED TO  $0.707 \times$  MAXIMUM VALUE

MAXIMUM VALUE = 1

$$|H(\omega_{3dB})| = \frac{1}{\sqrt{2}}$$

SOLVE

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (\omega_{3dB} RC)^2}}$$

$$2 = 1 + (\omega_{3dB} RC)^2$$

$$1 = (\omega_{3dB} RC)^2$$

$$1 = \omega_{3dB} RC$$

$$\boxed{\omega_{3dB} = \frac{1}{RC}}$$

GENERAL RESULT  $\omega_{3dB} = \frac{1}{\tau}$  } TIME CONSTANT

SINCE  $\omega = 2\pi f$

$$2\pi f_{3dB} = \frac{1}{RC}$$

$$\boxed{f_{3dB} = \frac{1}{2\pi RC}}$$

$$\frac{1}{2\pi \tau}$$

FOR THIS EXAMPLE:  $\frac{1}{2\pi (7.5 \text{ k}\Omega)(1000 \text{ pF})} = 21.2 \text{ KHZ}$