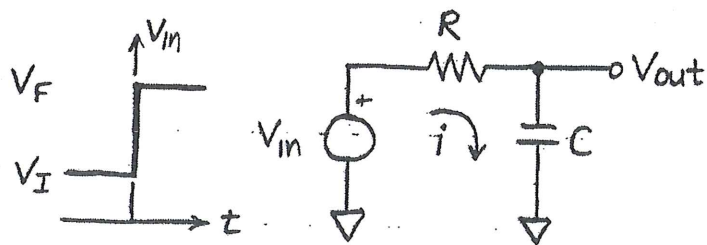


STEP RESPONSE OF FIRST ORDER SYSTEM



First order differential equation for V_{out}

$$\underbrace{V_{out} = V_{in} - iR}_{\text{KVL}} \Rightarrow \underbrace{i = C \frac{d}{dt} V_{out}}_{\text{CAPACITOR}} \Rightarrow \frac{d}{dt} V_{out} = \left(\frac{-1}{RC}\right) V_{out} + \left(\frac{1}{RC}\right) V_{in}$$

Solve differential equation; homogeneous solution: $V_{in} = 0$
 try solution of form $Ae^{-t/\tau}$; substitute

$$\frac{d}{dt} [Ae^{-t/\tau}] = \left(\frac{-1}{RC}\right) [Ae^{-t/\tau}]$$

$$\frac{-1}{\tau} Ae^{-t/\tau} = \frac{-1}{RC} Ae^{-t/\tau} \Rightarrow \tau = RC \quad \left. \vphantom{\tau = RC} \right\} \text{"TIME CONSTANT"}$$

Particular solution: when output is constant,
 $t \rightarrow \infty, dV_{out}/dt \rightarrow 0$; try constant solution $V_{out} = B$
 As $t \rightarrow \infty, V_{in} = V_F$


$$\left(\frac{-1}{RC}\right) B + \left(\frac{1}{RC}\right) V_F = 0 \Rightarrow B = V_F$$

Boundary condition: at $t=0, V_{out} = V_I$ (voltage across C cannot change instantaneously)

$$Ae^{-0/\tau} + V_F = V_I \Rightarrow A = V_I - V_F$$


General solution:
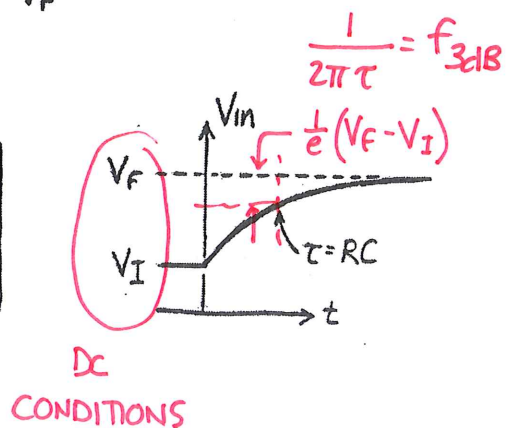
$$V_{out}(t) = V_F - (V_F - V_I) e^{-t/RC}$$



BANDWIDTH AND RISE TIME

Consider the single pole network

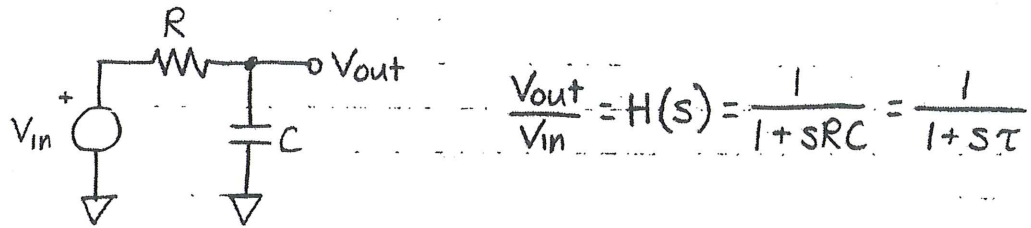


Letting $s=j\omega$, we have

$$H(j\omega) = \frac{1}{1+j\omega\tau} = \frac{1}{1+j\left(\frac{\omega}{\omega_0}\right)}$$

where $\omega_0 = 1/\tau$ is the 3dB bandwidth, in radians/sec

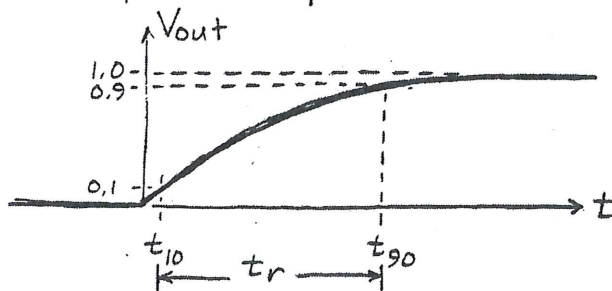The "rise time" t_r is defined as the time required for the output to rise from 10% to 90% of the output step:



$$BW = 8.5 \text{ kHz}$$

$$t_r = \frac{0.35}{8.5 \text{ kHz}} = 4 \mu\text{sec} \checkmark$$

From general step response

$$\left. \begin{aligned} 0.1 &= 1.0 - e^{-t_{10}/\tau} \Rightarrow t_{10} = -\tau \ln(0.9) \\ 0.9 &= 1.0 - e^{-t_{90}/\tau} \Rightarrow t_{90} = -\tau \ln(0.1) \end{aligned} \right\} t_r = t_{90} - t_{10} = \tau \ln(9)$$

$$\text{Or, } \boxed{t_r = 2.2\tau}$$

Since $\tau = 1/\omega_0$, and $f_0 = \omega_0/2\pi = BW$ (3dB bandwidth in Hz)

$$t_r = 2.2 \frac{1}{\omega_0} = \frac{1}{BW} \frac{2.2}{2\pi} \Rightarrow \boxed{BW \cdot t_r = 0.35}$$

Approximately valid for any linear system with poles near real axis (little overshoot in step response)