

ECE3204 Lecture 7

Gain-bandwidth product relationship

Op-Amp as a classical feedback system

Op-Amp Design Example



Handouts:

Design Example

Op-Amp Error Matrix


What's the difference between
OPEN LOOP GAIN CLOSED LOOP GAIN

?

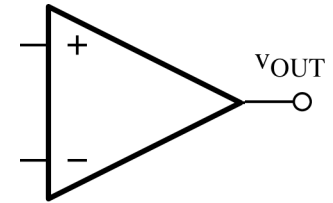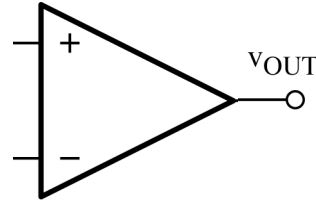

Op-Amp Design Example


- Design an inverting amplifier with an input resistance of $1\text{k}\Omega$ and a gain of -100
- If an LM741 ($f_T = 1\text{MHz}$) is used, determine the closed loop transfer function, and express in the form showing the DC gain and closed loop 3-dB frequency (bandwidth) $f_{3\text{dB}}$
- Determine $v_{\text{OUT}}(t)$ for an input step of 0 to 100mV . At what time will the output $v_{\text{OUT}}(t)$ reach within 100mV of its final value?
- Determine $v_{\text{OUT}}(t)$ for an input sine wave of $(100\text{mV})\sin(2\pi[100\text{Hz}]t)$
- Determine $v_{\text{OUT}}(t)$ for an input sine wave at the upper edge of the audio frequency range $(100\text{mV})\sin(2\pi[20\text{kHz}]t)$
- If we want a closed loop 3-dB frequency (bandwidth) $f_{3\text{dB}} = 20\text{kHz}$ for an audio application, determine the op-amp unity gain frequency f_T required


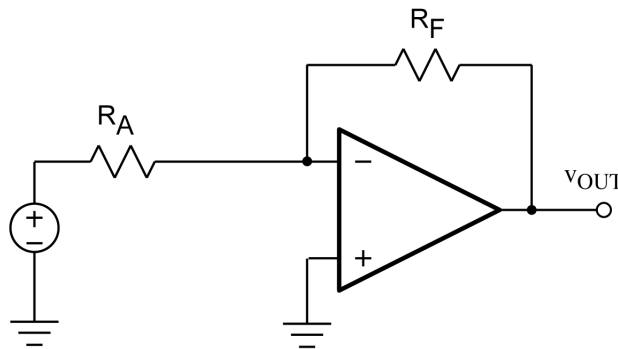


b) If an LM741 ($f_T = 1\text{MHz}$) is used, determine the closed loop transfer function, and express in the form showing the DC gain and closed loop 3-dB frequency (bandwidth) $f_{3\text{dB}}$


Gain-bandwidth product procedure:

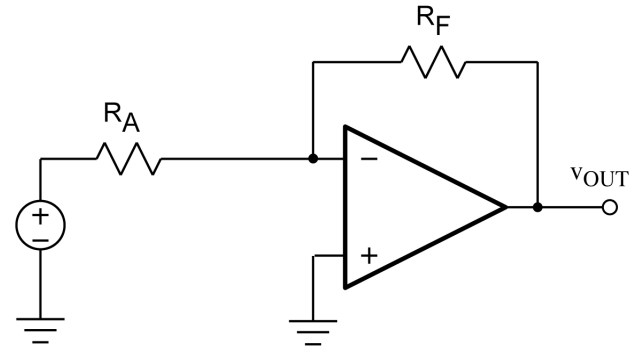1. Redraw circuit with all inputs suppressed (set = 0)
2. Find feedback factor β (fraction of output fed back to inverting input)
3. Closed loop bandwidth $f_{3\text{-dB}}$ will be unity gain frequency f_t multiplied by β




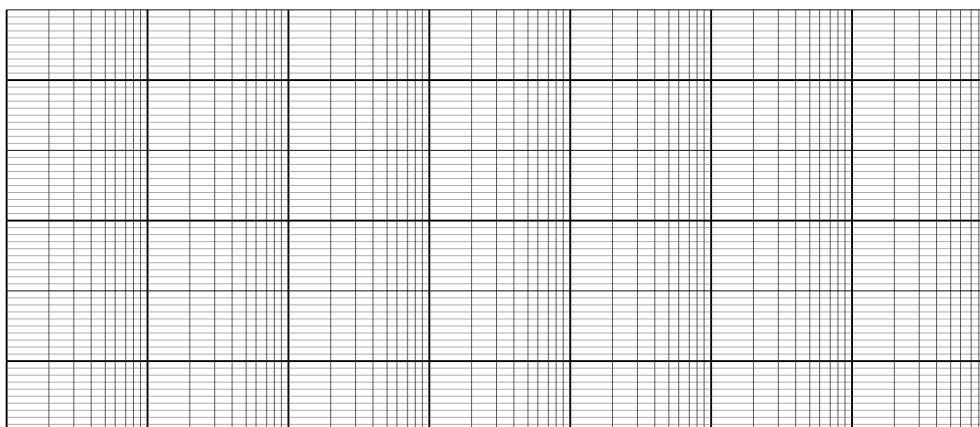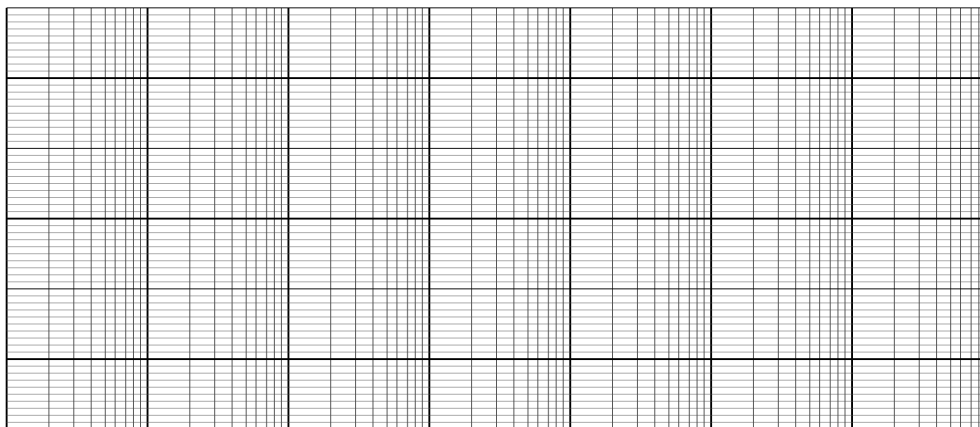

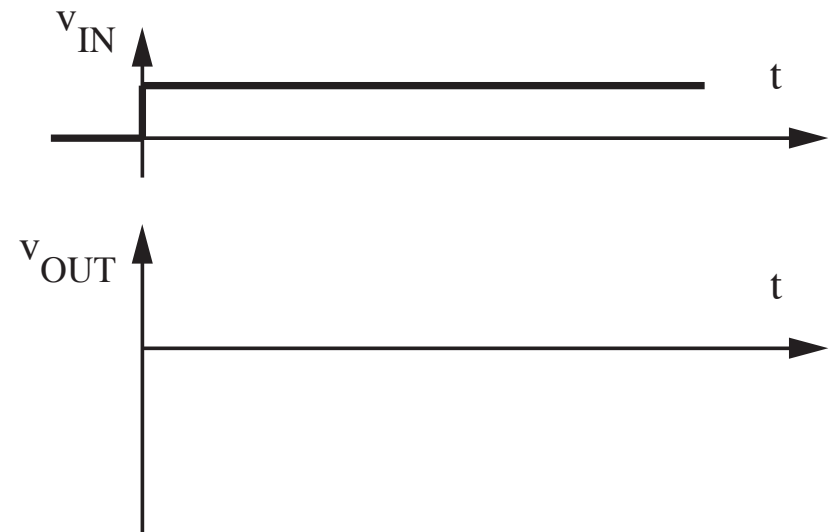
- c) Determine $v_{OUT}(t)$ for an input step of 0 to 100mV.
What is the 10%-to-90% rise time?
At what time will the output $v_{OUT}(t)$ reach within 100mV of its final value?



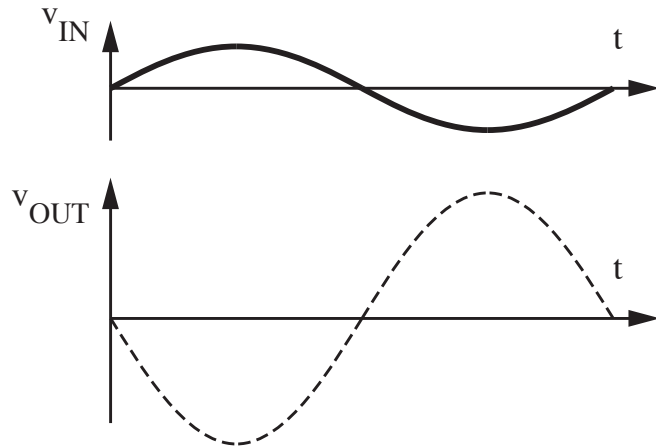d) Determine $v_{OUT}(t)$ for an input sine wave of $(100\text{mV})\sin(2\pi[100\text{Hz}]t)$



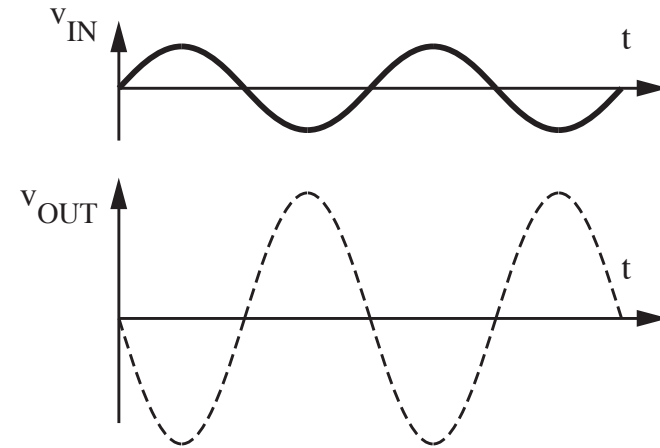e) Determine $v_{OUT}(t)$ for an input sine wave at the upper edge of the audio frequency range $(100\text{mV})\sin(2\pi[20\text{kHz}]t)$



- f) If we want a closed loop 3-dB frequency (bandwidth) $f_{3\text{dB}} = 20\text{kHz}$ for an audio application, determine the op-amp unity gain frequency f_T required

What about f_T (unity gain bandwidth) variability?

Electrical Characteristics (Note 5) (Continued)											
Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Bandwidth (Note 6)	$T_A = 25^\circ\text{C}$	0.437	1.5								MHz

LM741

If you need to depend on closed loop f_{3dB} , get it from (better controlled) passive element values