
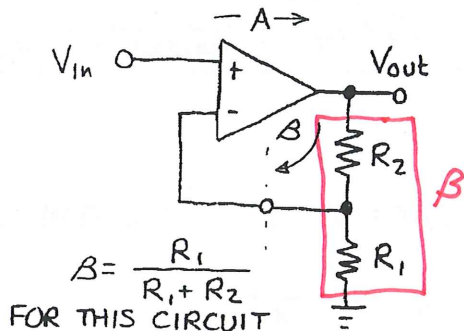


OP-AMP AS A CLASSICAL FEEDBACK SYSTEM

OP-AMP CIRCUIT:

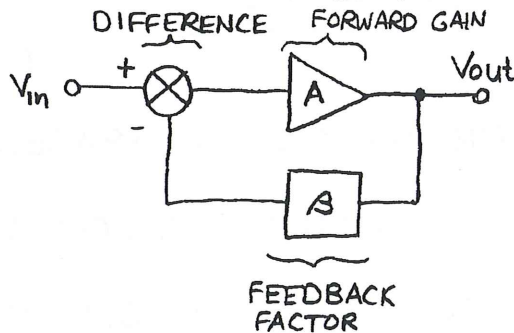

CLASSICAL FEEDBACK:




β : "FEEDBACK FACTOR" FRACTION OF V_{out} FED BACK TO V_-

FIND CLOSED LOOP GAIN $G = \frac{V_{out}}{V_{in}}$

$$V_{out} = A(V_{in} - \beta V_{out}) \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta} = G} \quad \begin{matrix} \checkmark \text{ AS EXPECTED} \\ G \rightarrow \frac{1}{\beta} \\ \text{AS } A \rightarrow \infty \end{matrix}$$

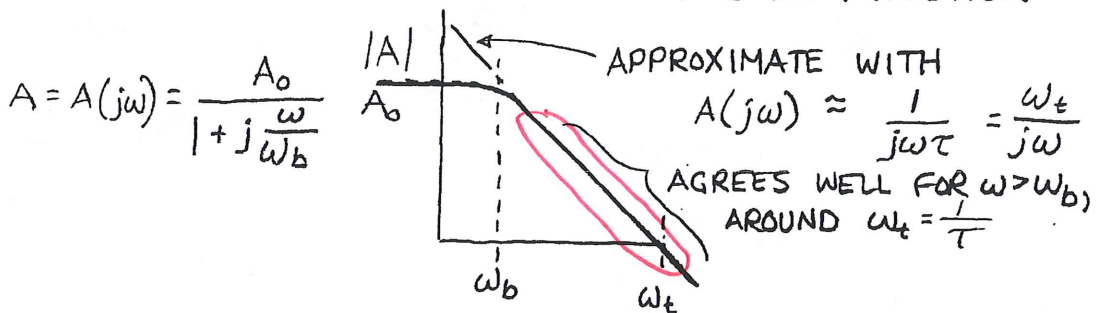WHAT IS CLOSED LOOP GAIN G WHEN A IS FINITE?
REAL OP-AMP HAS SINGLE POLE TRANSFER FUNCTION



SUBSTITUTE IN G EXPRESSION

$$G = \frac{A}{1 + A\beta} = \frac{\frac{\omega_t}{j\omega}}{1 + \beta \frac{\omega_t}{j\omega}} \quad \left. \begin{matrix} \text{MULTIPLY NUM, DEN} \\ \text{BY } \frac{j\omega}{\beta\omega_t} \end{matrix} \right\}$$

MESSAGE INTO GENERAL FIRST ORDER FORM

$$G = \frac{[\text{DC GAIN}]}{1 + j \frac{\omega}{\omega_{3dB}}}$$

$$G = \frac{\frac{\omega_t}{j\omega}}{\left(1 + \beta \frac{\omega_t}{j\omega}\right)} \frac{j\omega}{\beta \omega_t} \Rightarrow \frac{\boxed{\frac{1}{\beta}}}{1 + j \frac{\omega}{\boxed{\beta \omega_t}}}$$

} DC GAIN

} CLOSED LOOP BANDWIDTH ω_{3dB}

GAIN-BANDWIDTH TRADEOFF!:

WHEN WE CHOOSE A FEEDBACK FACTOR β (FRACTION < 1)

TO GET A CLOSED LOOP DC GAIN OF $\frac{1}{\beta}$

CLOSED LOOP BANDWIDTH ω_{3dB} IS $\beta \omega_t$

UNITY GAIN FREQUENCY ω_t REDUCED BY β FACTOR

INVERSE RELATIONSHIP: PRODUCT IS CONSTANT

$$\left[\text{CLOSED LOOP GAIN} \right] \times \left[\text{CLOSED LOOP BANDWIDTH} \right] = \left[\text{GAIN-BANDWIDTH PRODUCT} \right]$$

NON INVERTING CONFIGURATION $\frac{1}{\beta}$

$\beta \omega_t$
 ω_{3dB}

ω_t
UNITY GAIN FREQUENCY

FOR LM741, $f_t = 1 \text{ MHz}$

FOR LF356, $f_t = 4 \text{ MHz}$

GRAPHICALLY

