

Op-Amp Errors (Sedra & Smith, 6th edition)

		Static (DC)	Dynamic (AC)
Linear <i>TRANSFER FUNCTION</i> <i>SUPERPOSITION</i>	Error Source	<i>Offset Voltage</i> <i>DC Bias Current</i>	<i>Finite Bandwidth</i>
	Text	Sec. 2.6.1, 2.6.2	Sec. 2.7
	Analysis Strategy	<ol style="list-style-type: none"> Add DC sources to ideal op-amp to model errors Analyze with superposition to find contribution of each error source to output voltage Add in "worst case" fashion <ul style="list-style-type: none"> Offset voltage can be either polarity Bias current polarity known from type of op-amp input stage 	<p>Model closed loop behavior with first-order transfer function:</p> <ul style="list-style-type: none"> DC gain from ideal op-amp assumptions Closed loop bandwidth (3-dB frequency) f_{3-dB} from gain-bandwidth product relationship <p>Gain-bandwidth product procedure:</p> <ol style="list-style-type: none"> Redraw circuit with all inputs suppressed (set = 0) Find feedback factor β (fraction of output fed back to inverting input) Closed loop bandwidth f_{3-dB} will be unity gain frequency f_t multiplied by β
Non-Linear	Error Source	<i>Output voltage swing limit</i> <i>Output current limit</i>	<i>Slew rate limit</i>
	Text	Sec. 2.8.1, 2.8.2	Sec. 2.8.3
	Analysis Strategy	<ol style="list-style-type: none"> Determine maximum total v_{OUT}, i_{OUT}, excursion at op-amp output from linear system model Compare maximum, minimum to op-amp limits 	<ol style="list-style-type: none"> Determine $v_{OUT}(t)$ from linear system behavior (transfer function for sine wave, general exponential response for step) Calculate time derivative $dv_{OUT}(t)/dt$ Compare maximum positive and negative $dv_{OUT}(t)/dt$ to op-amp slew rate limit

Textbook: Sedra and Smith, Microelectronic Circuits, 6th ed.