



$$V_- = \left(\frac{R_F}{R_A + R_F} \right) V_{in} + \left(\frac{R_A}{R_A + R_F} \right) V_{out}$$

V_{out} MOVES TO
 "COUNTERACT" V_{in}
 CLIP $\Rightarrow V_- \neq 0$