

# ECE3204 Lecture 10

## Lab 2 Circuits

- Integrator
- Follower
- Push-pull

## Other Op-Amp Circuits

- Summation
- Subtraction

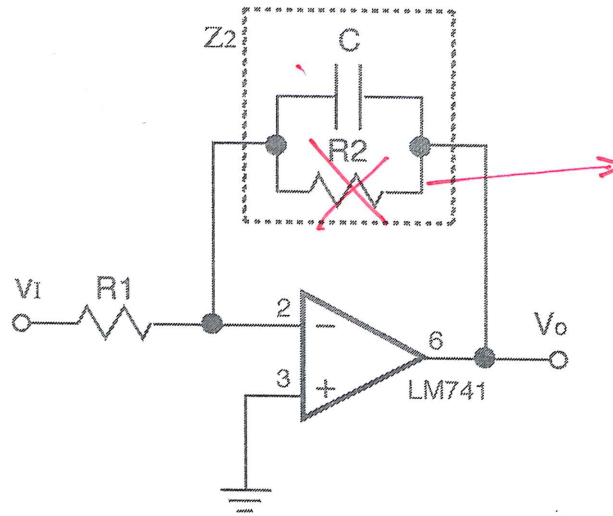


Figure 2.5



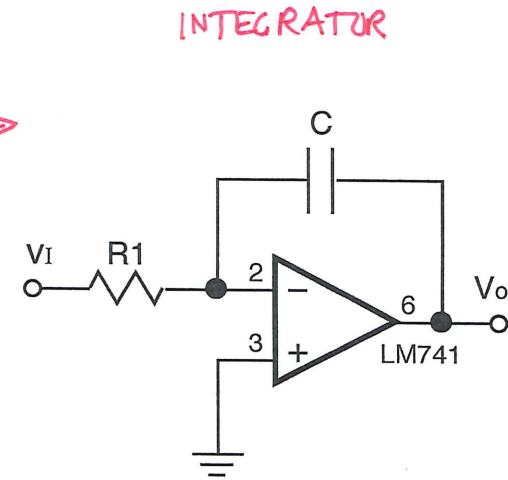
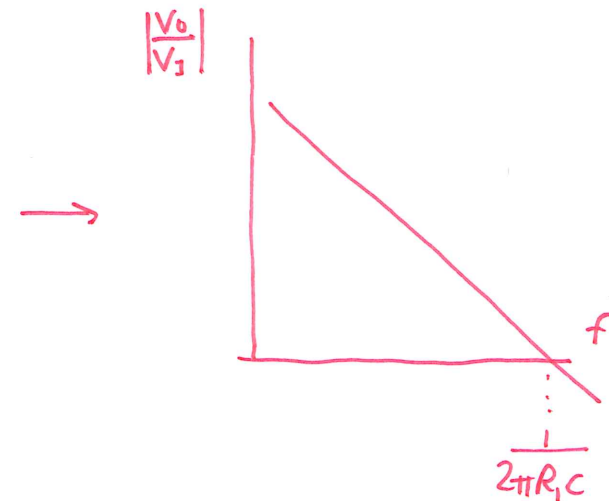


Figure 2.6

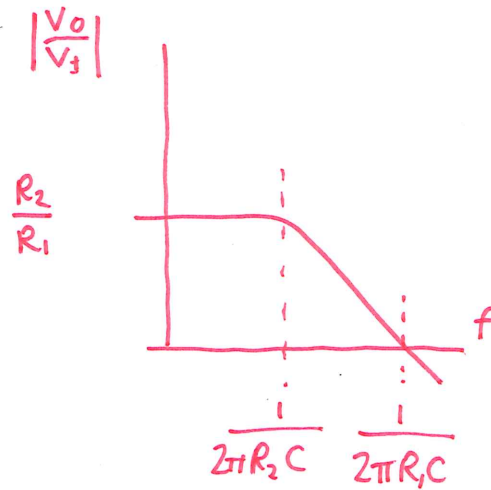
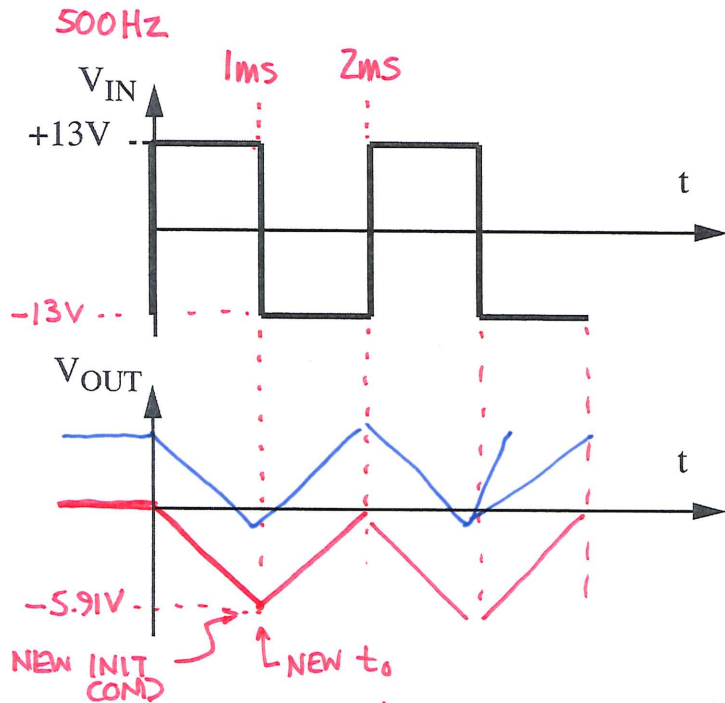
# Integrator Application: Square Wave - Triangle Wave



TIME DOMAIN: "PIECEWISE TIME" APPROACH

FROM  $0 < t < 1\text{msec}$ :  $V_I$  CONSTANT

$$V_o(t) = \frac{-1}{R_1 C} \int_{t_0}^t V_{IN}(t) dt + \underbrace{V_o(t_0)}_{\text{INIT COND}}$$


$$V_o(t) = \frac{-1}{2.2\text{ms}} \int_0^t (+13\text{V}) dt + 0$$

$$V_o(t) = \left( \frac{-13\text{V}}{2.2\text{ms}} \right) t$$

AT END  $t = 1\text{msec}$

$$V_o(1\text{ms}) = \frac{(-13\text{V})(1\text{msec})}{2.2\text{msec}} = -5.91\text{V}$$

INITIAL CONDITION

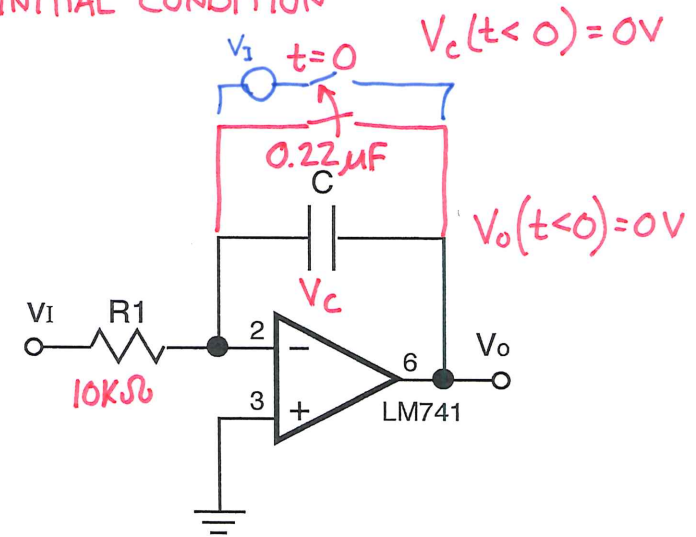

$$R_1 C = (10\text{k}\Omega)(0.22\mu\text{F}) = 2.2\text{msec}$$

$$\tau = R_1 C \text{ SIGNIFICANCE?}$$

FROM  $1\text{msec} < t < 2\text{msec}$ :  $V_I = -13\text{V}$  CONSTANT

$$V_o(t) = \frac{-1}{R_1 C} \int_{1\text{msec}}^t (-13\text{V}) dt + (-5.91\text{V})$$

$$V_o(t) = \frac{+13\text{V}}{2.2\text{msec}} (t - 1\text{msec}) + (-5.91\text{V})$$

AT END  $t = 2\text{msec}$

$$\frac{+13\text{V}}{2.2\text{msec}} (2\text{msec} - 1\text{msec}) - 5.91\text{V} = +5.91\text{V}$$

# INTEGRATOR





$$V_o = \frac{-1}{\tau} \int V_I(t) + V(t_0)$$

TAKE  $d/dt$  OF BOTH SIDES


$$\frac{dV_o}{dt} = \frac{-1}{\tau} V_I = \frac{-V_I}{\tau}$$

RATE OF CHANGE OF OUTPUT FOR A GIVEN INPUT  $V_I$

$$\tau = 1 \text{ msec}$$

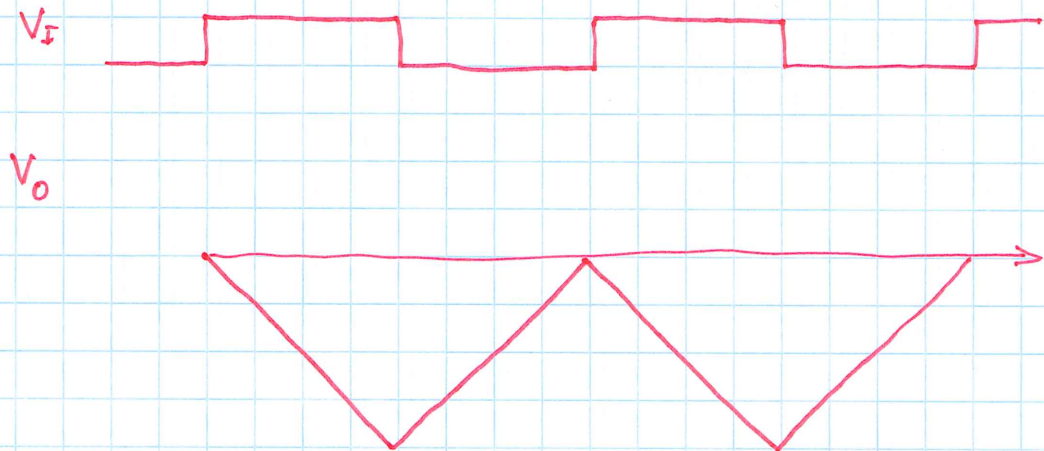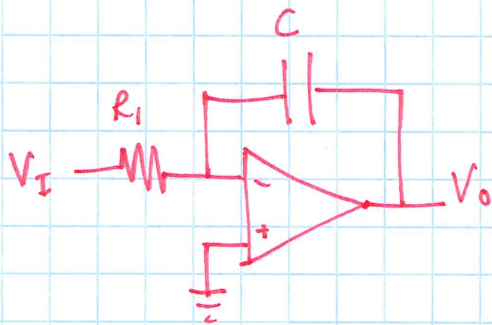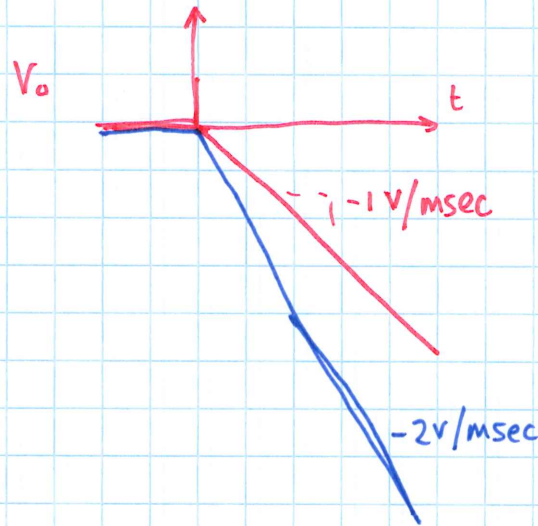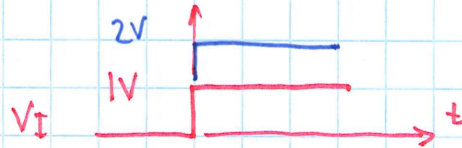
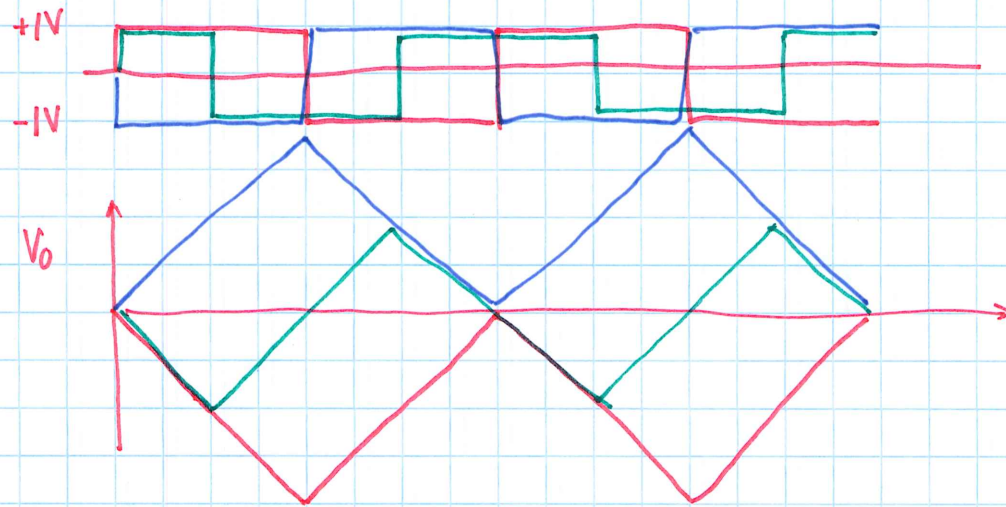
$$\frac{dV_o}{dt} = -\frac{V_{in}}{1\text{msec}}$$



# Voltage Follower

$V_o$  FOLLOWS  $V_s$


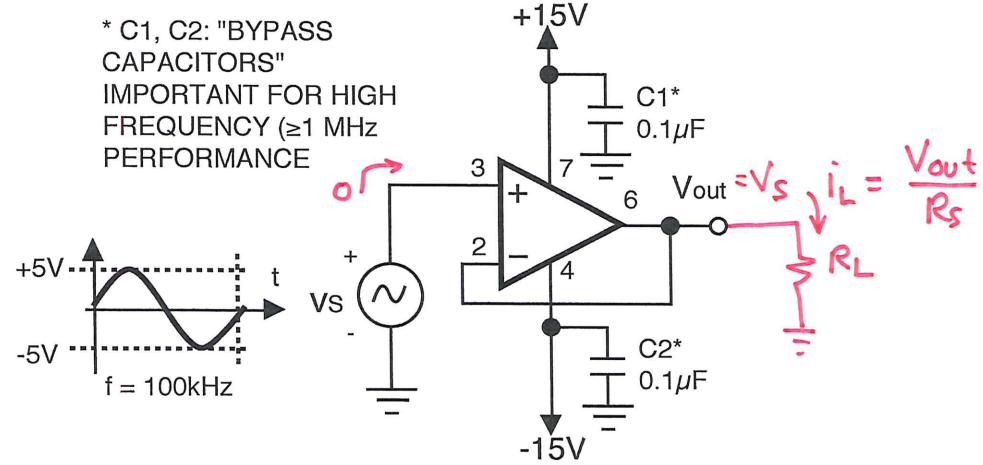
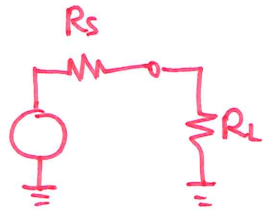


Figure 2.3

# Current Limiting

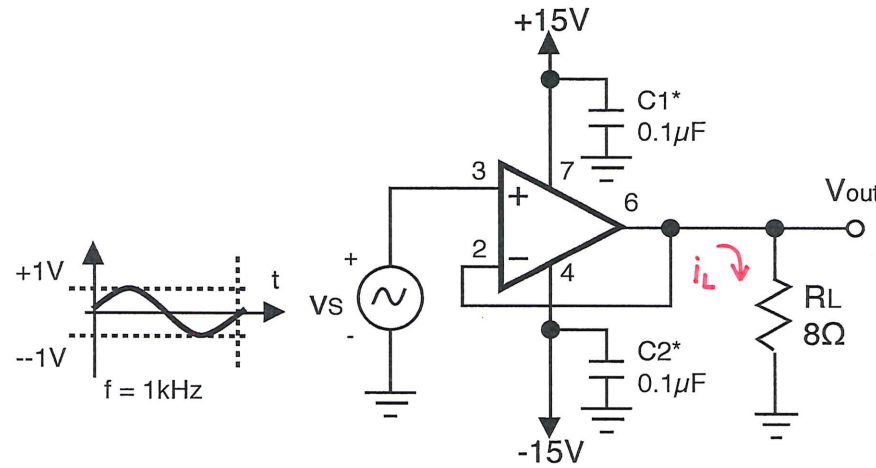

$$i_L = \frac{V_o}{R_L} = \frac{1V}{8\Omega} = 125mA$$


$$i_{L(MAX)} \approx 25mA$$

Fig. 2.4

# Push-Pull Amplifier

MICRO I: BJT

NPN

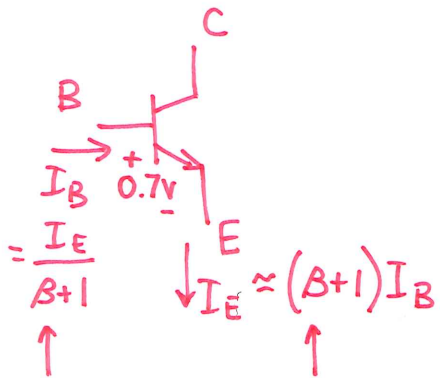

BJT CURRENT GAIN ~~X~~  
 100-200 FOR 3904, 3906

PNP



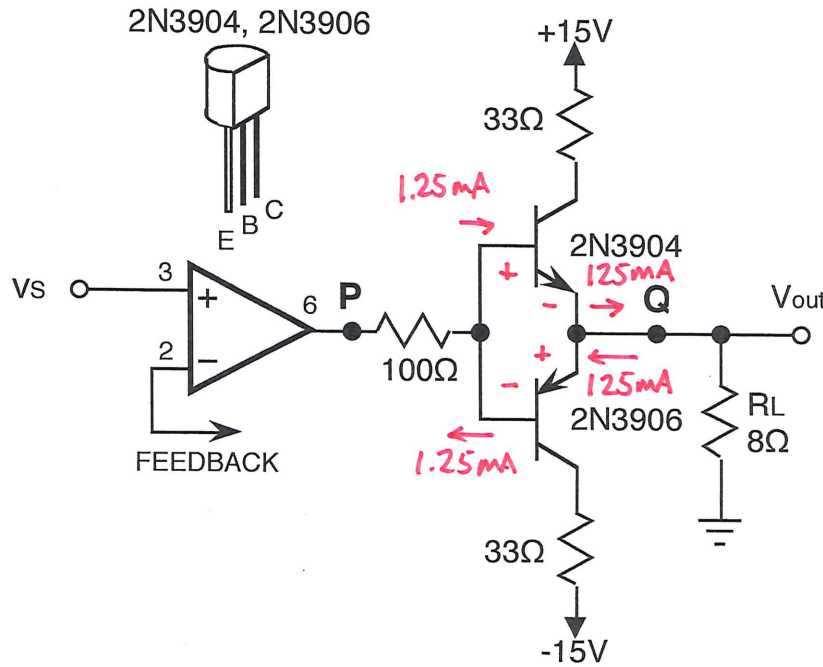
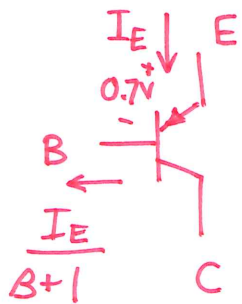
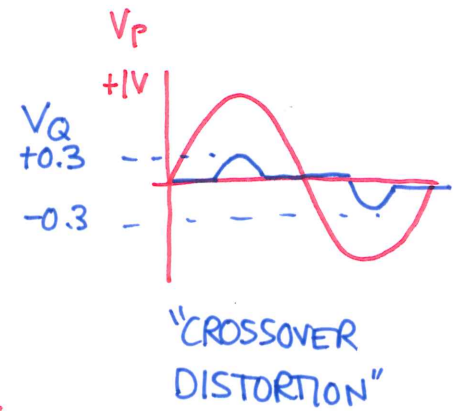


Figure 2.7

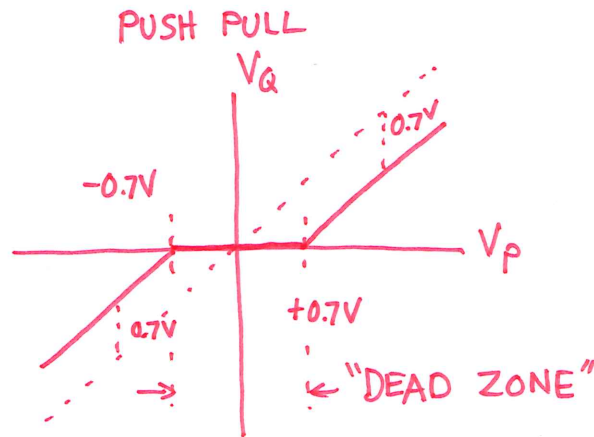

# Summation

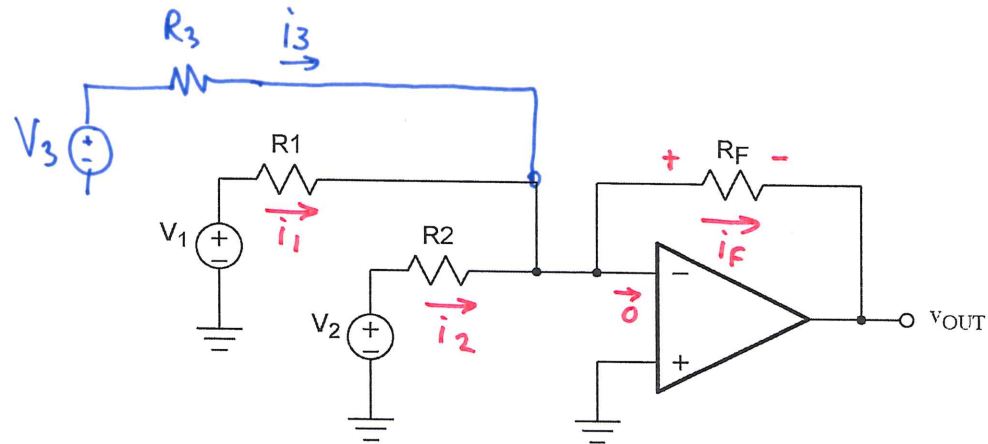

NEGATIVE FB  $\checkmark \Rightarrow V_- = 0V$

OHM'S LAW

$$i_1 = \frac{V_1}{R_1} \quad i_2 = \frac{V_2}{R_2}$$

OUTPUT

$$V_o = -i_F R_F$$

KCL AT -INPUT:

$$i_1 + i_2 = i_F \quad \left. \begin{array}{l} \\ \end{array} \right\} \begin{array}{l} \text{KCL IS} \\ \text{DOING} \\ \text{THE} \\ \text{SUMMATION} \end{array}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_o}{R_F}$$

REARRANGE

$$V_o = - \left[ \left( \frac{R_F}{R_1} \right) V_1 + \left( \frac{R_F}{R_2} \right) V_2 + \left( \frac{R_F}{R_3} \right) V_3 \right]$$

# Subtraction

