

ECE3204 Lecture 11

Lab 2 Circuits Review

- Integrator (2.5)
- Push-pull
- Bypass capacitors

Finish

- Summation (2.4)
- Subtraction

Comparator (17.4)

Handout:
LM311 data sheet



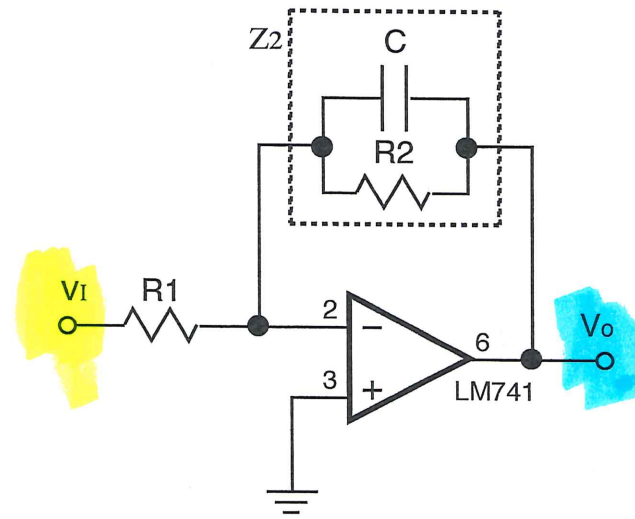


Figure 2.5

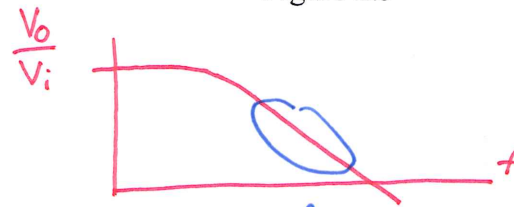

LOW FREQ
SQUARE
WAVE

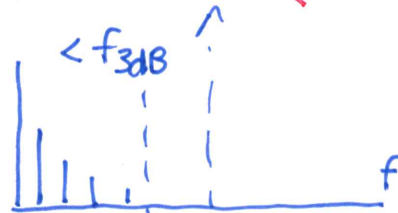

HIGH FREQ
SQUARE
WAVE


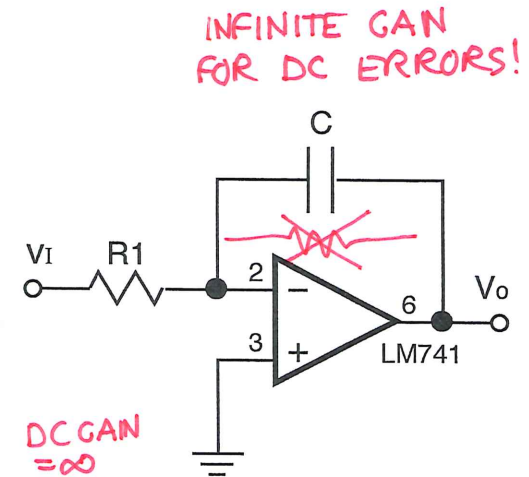
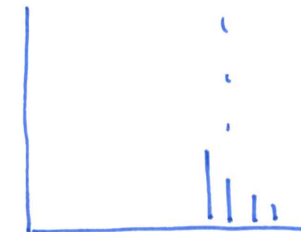


Figure 2.6

DC GAIN
 $= \infty$

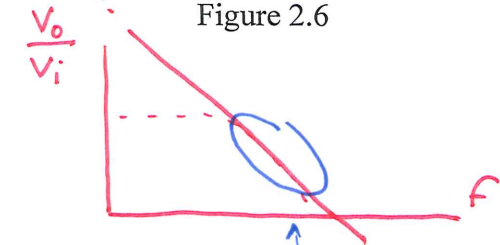

Push-Pull Amplifier

CROSSOVER DISTORTION


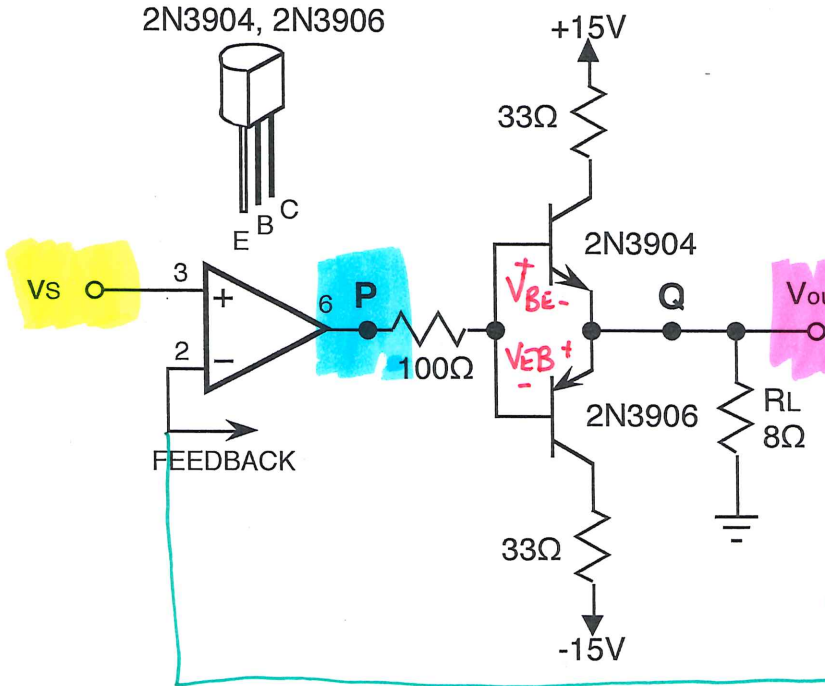
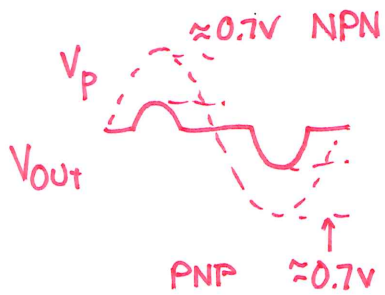



Figure 2.7

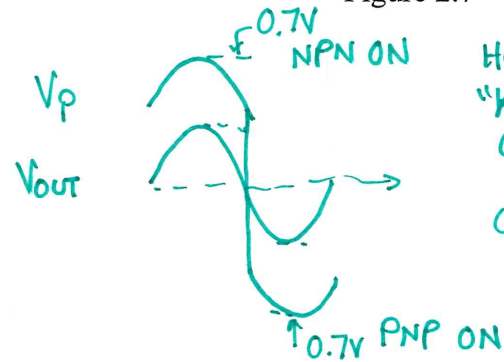TAKE FEEDBACK FROM POINT YOU WANT EQUAL TO INPUT



HOW DOES OP-AMP "KNOW" TO 0.7 HIGHER? 0.7 LOWER?

FIX (SMALLER) DISTORTION

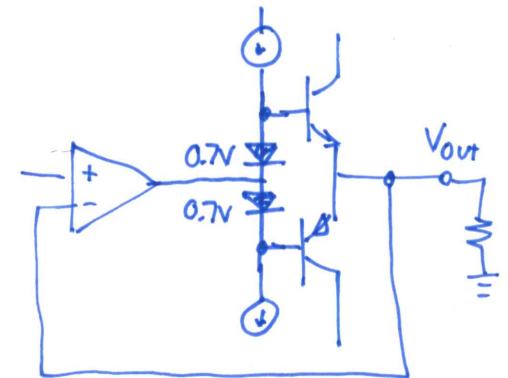

Bypass capacitors


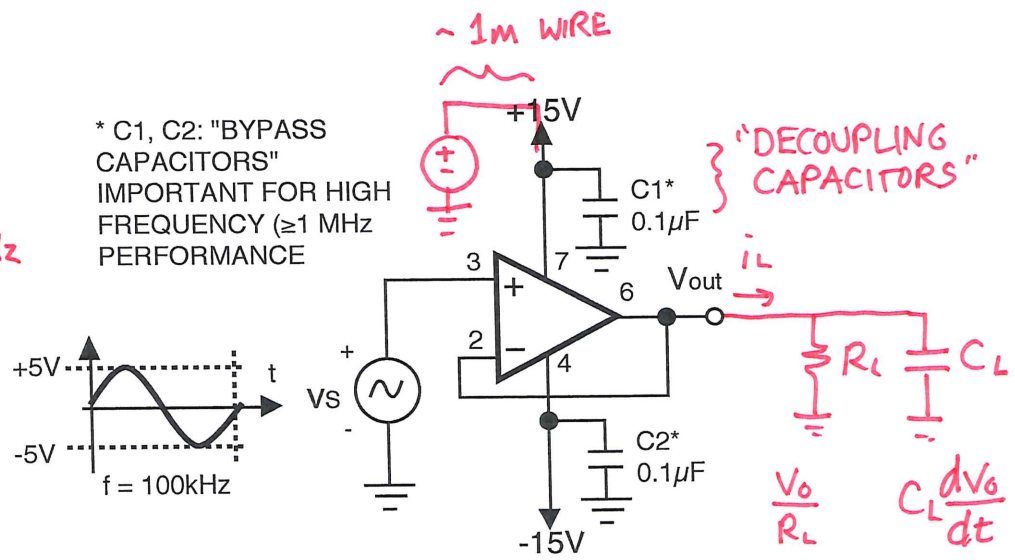
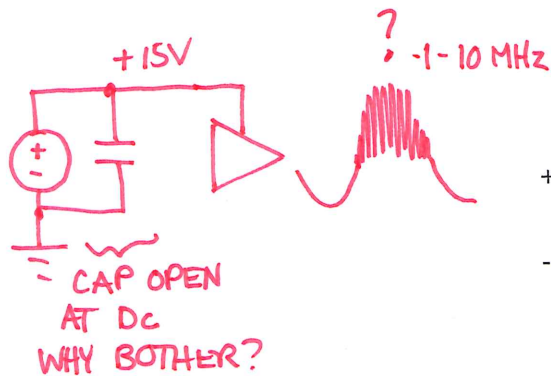



Figure 2.3

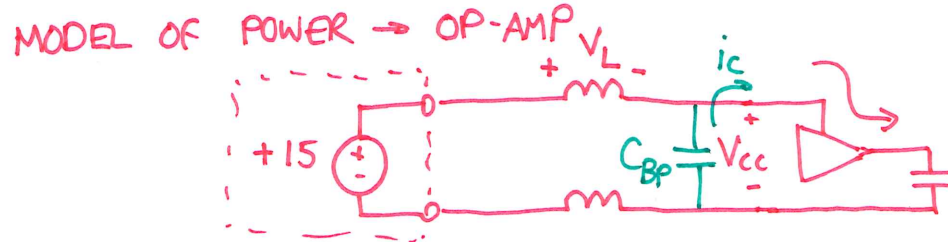


WIRE INDUCTANCE

$$V_L = L \frac{di_L}{dt}$$

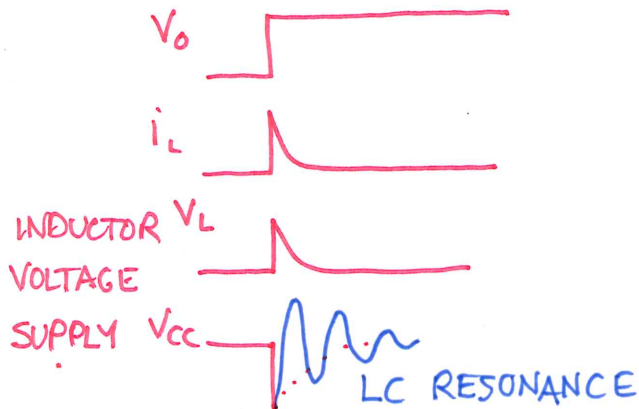C_{bp} LOCAL "RESERVOIR" OF CHARGE CAN PROVIDE QUICK CURRENT



Summation

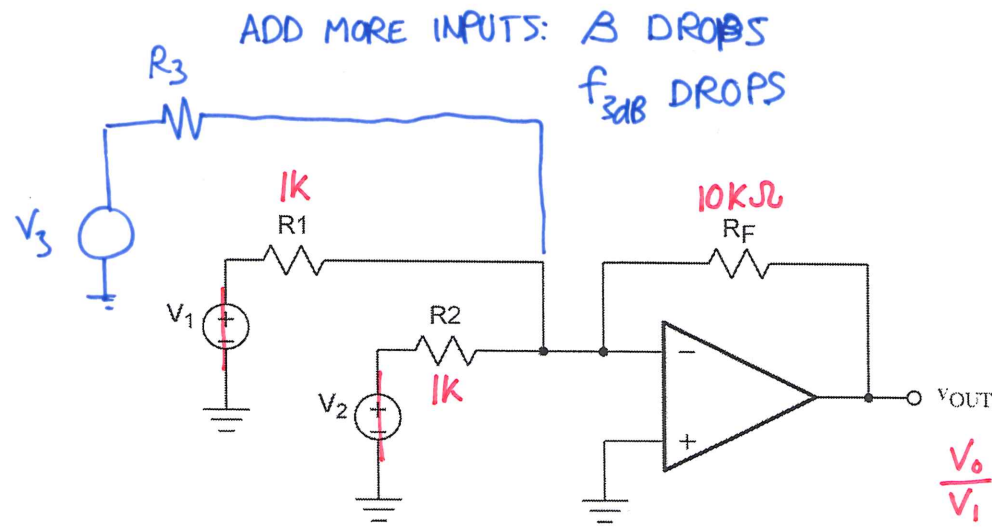

~~$f_{3dB} = 100kHz?$~~

$\frac{V_o}{V_1} = -10$ $\frac{V_o}{V_2} = -10$

GAIN - BANDWIDTH ?

V_1, V_2 OFF

REDRAW


$$B = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_F} = \frac{500 \Omega}{500 + 10K} = \frac{1}{21}$$

$$B = \frac{R_1 \parallel R_2 \parallel R_3}{R_1 \parallel R_2 \parallel R_3 + R_F}$$

CLOSED LOOP f_{3dB}


$$\frac{1}{21} 1MHz \approx 48 kHz$$

LM741

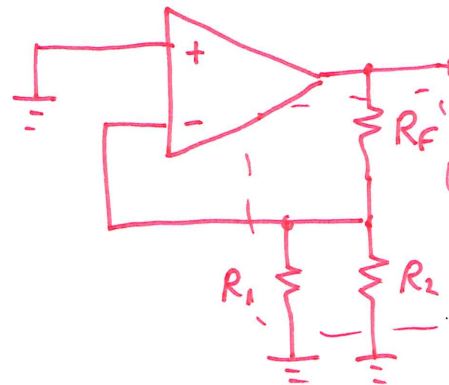

(INSTRUMENTATION AMPLIFIER)

Subtraction

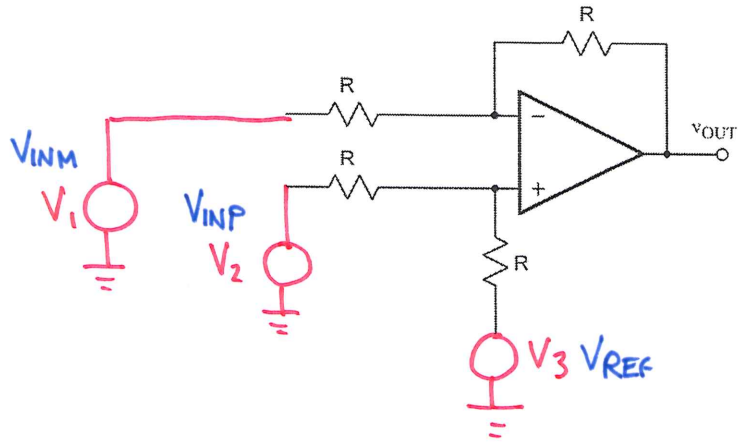





NEG FB: $V_- = V_+$

$$V_{OUT} = V_2 + V_3 - V_1$$

$$V_{OUT} = (V_{INP} - V_{INM}) + V_{REF}$$

CAUTION: RESISTOR RATIOS!





SUPERPOSITION

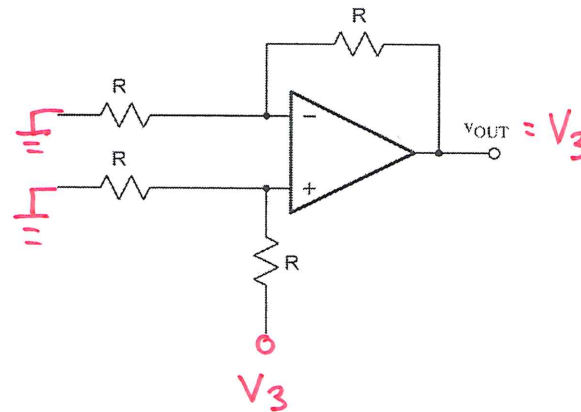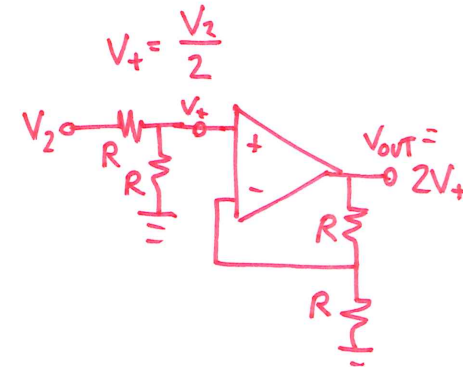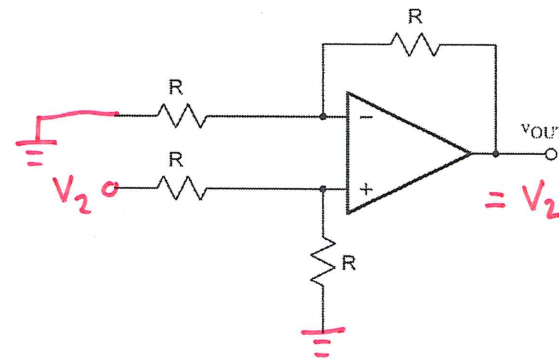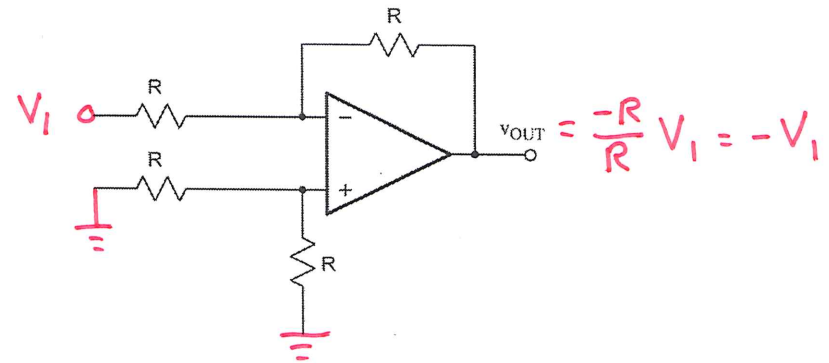


ON/OFF

Application: Temperature Sensor for Heating Control


OP-AMP "RULE"

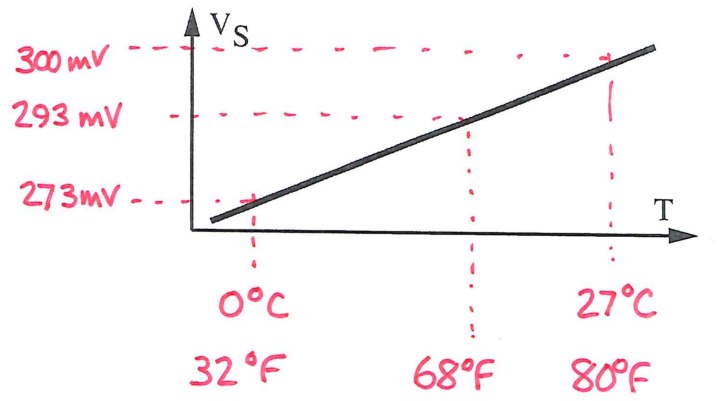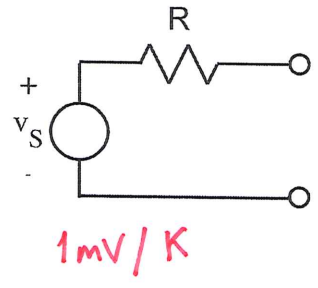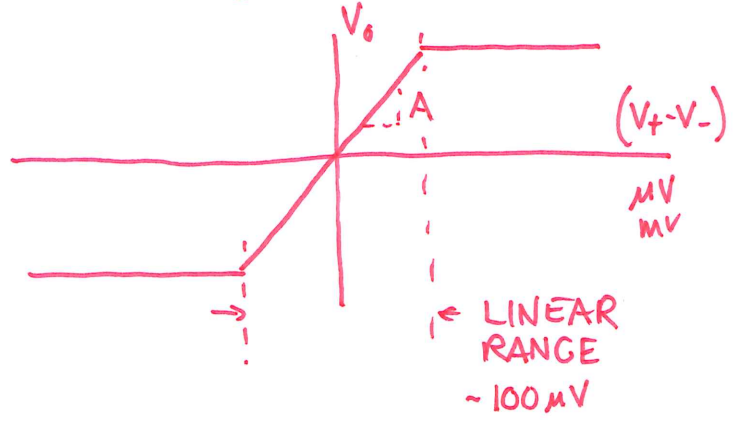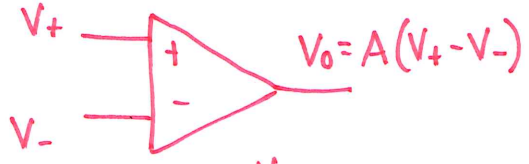

FURNACE CONTROL	1	ON
	0	OFF

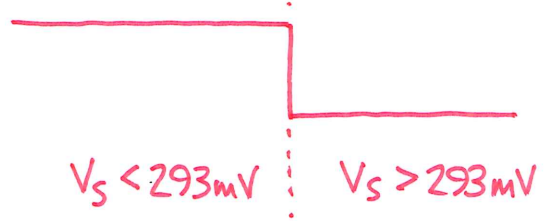

EXPAND HORIZONTAL AXIS

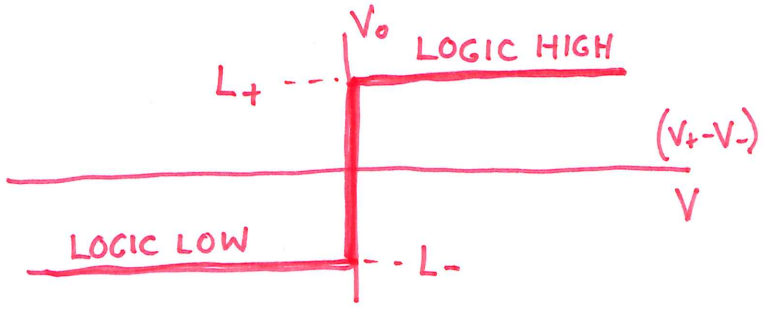

$V_- > V_+$

$V_+ > V_-$

USE OP-AMP OPEN LOOP TO COMPARE V_- , V_+
COMPARATOR

TRUTH TABLE

$V_+ > V_- ?$	V_0
YES	L_+
NO	L_-