
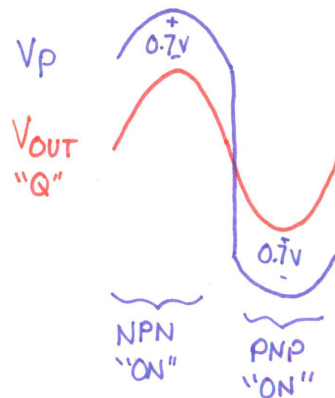


Figure 2.7

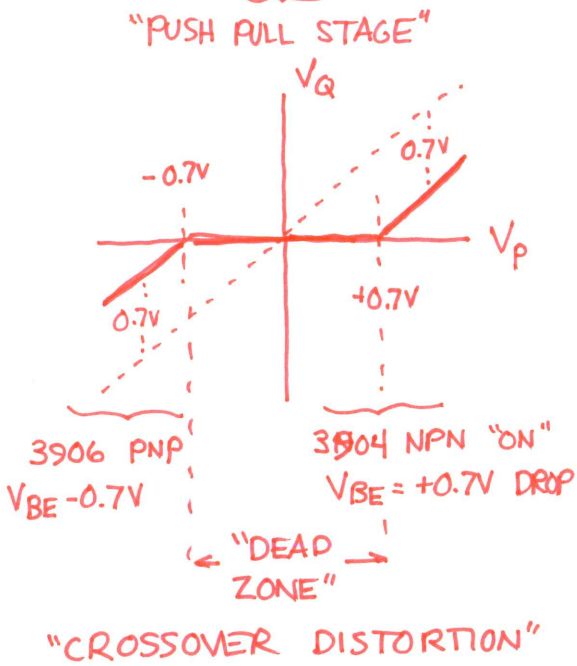LOOK AT THE POINT WE WANT TO BE EQUAL TO V_s
 NEGATIVE FB FORCES V_+ , V_- EQUAL



"CROSSOVER DISTORTION"

ANY SIGNAL IN "DEAD ZONE" LOST

