

ECE3204 Lecture 14

Schmitt Trigger (17.4) Key ideas

Review Lab 3





Clock Generation (17.5) Square Wave Oscillator LM555 Timer

Schmitt Trigger Key Ideas

Positive feedback forces v_- , v_+ apart \Rightarrow Output always at $\pm V_{SAT}$ rails (logic levels L_- or L_+)

Condition for input trip points V_{TL} , V_{TH} \Rightarrow When $v_- = v_+$ (this is an unstable equilibrium!)

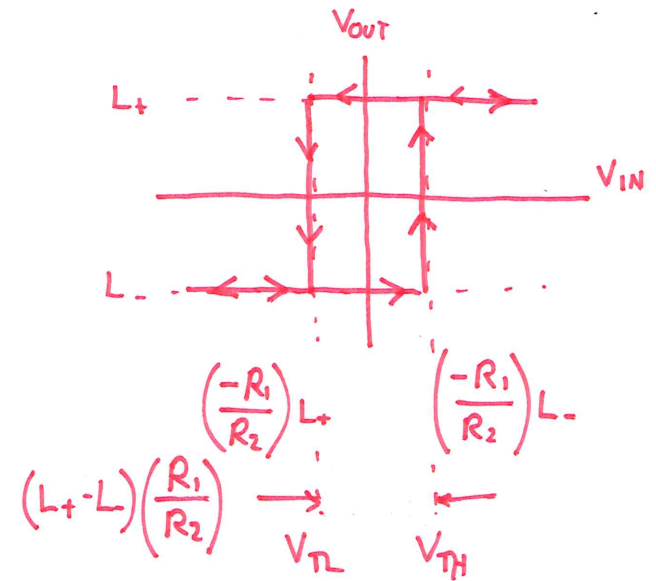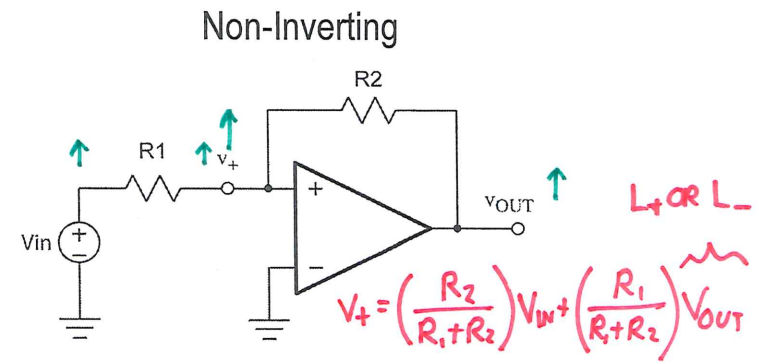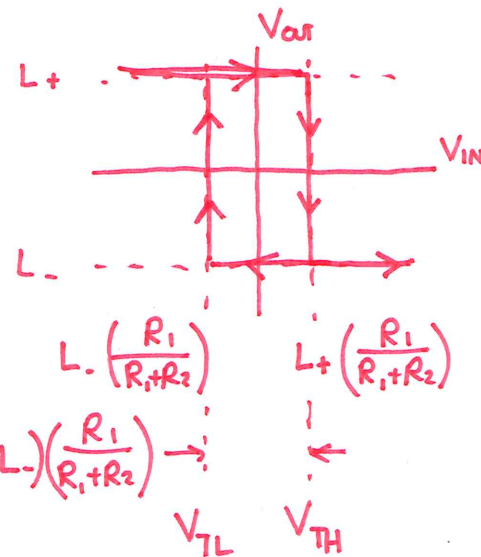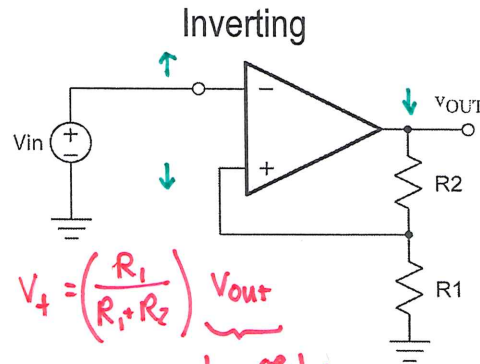
Hysteresis loop in $v_{IN} \rightarrow v_{OUT}$ plot \Rightarrow Need to know past history when v_{IN} between V_{TL} , V_{TH}




Schmitt Trigger: Asymmetric Trip Points

$L_- = 0$
 $L_+ = \text{SOME + VALUE}$

Inverting

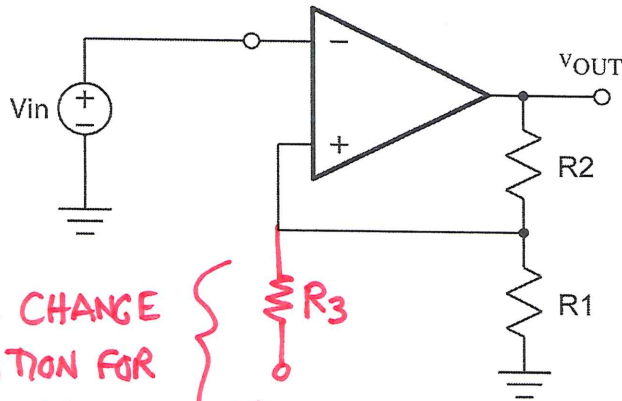


WILL CHANGE
 CONDITION FOR
 $V_- = V_+$

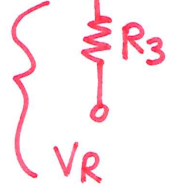

AT V_{TL}, V_{TH}

ADDING V_R, R_3
 GIVES EXTRA DEGREE
 OF FREEDOM IN DESIGN

Non-Inverting

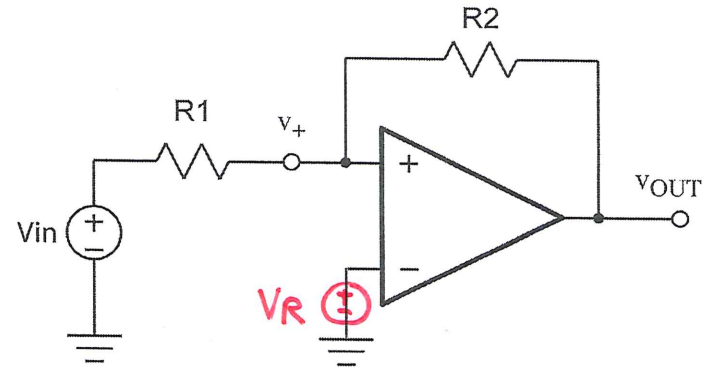

TRIP POINT CONDITION: $V_+ = V_-$


$$\left(\frac{R_2}{R_1+R_2}\right)V_T + \left(\frac{R_1}{R_1+R_2}\right)L_- = V_R$$

$\underbrace{\hspace{10em}}_{\text{WAS ZERO}}$



FIND V_T :

$$R_2 V_T + \frac{R_1 L_-}{R_2} = V_R \frac{(R_1+R_2)}{R_2}$$

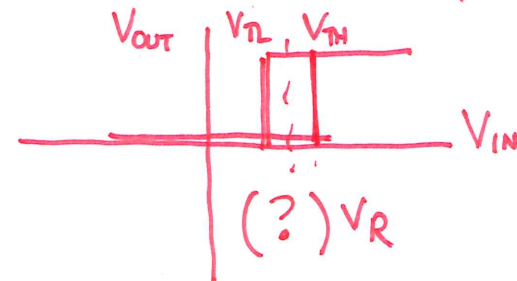
$$V_T = \left(\frac{R_1+R_2}{R_2}\right)V_R - \left(\frac{R_1}{R_2}\right)L_-$$




P4. Integrator

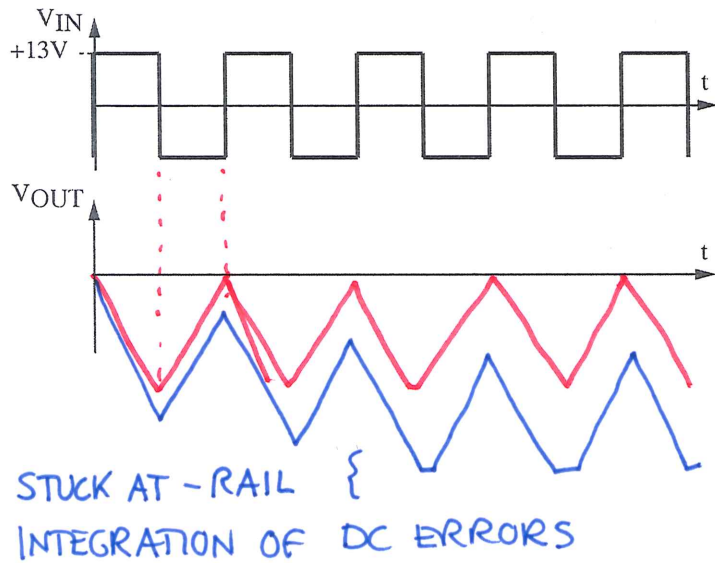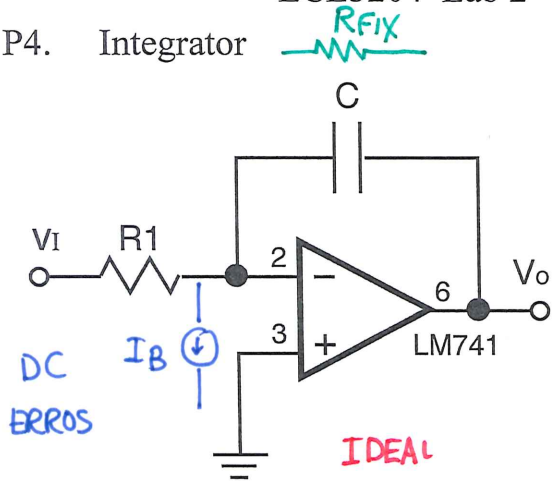

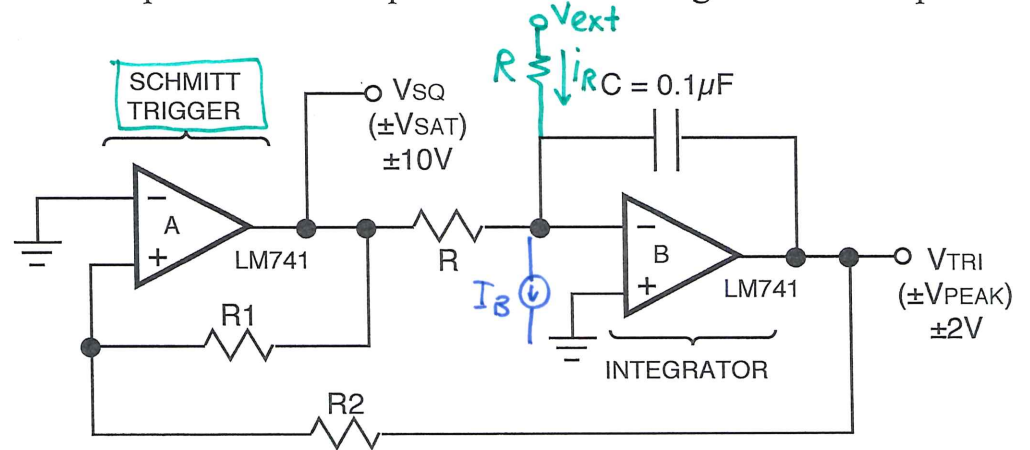P1. Function generator: Figure 3.1 shows a function generator circuit that produces both square wave and triangular wave outputs.




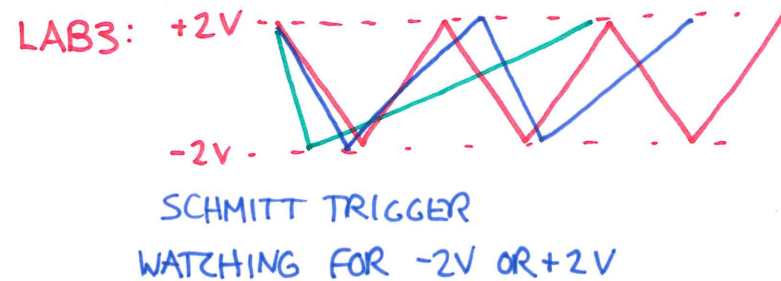WHY DID WE NOT SEE DC ERROR PROBLEM IN LAB 3?




Square Wave Oscillator (17.5)

Figure 17.24



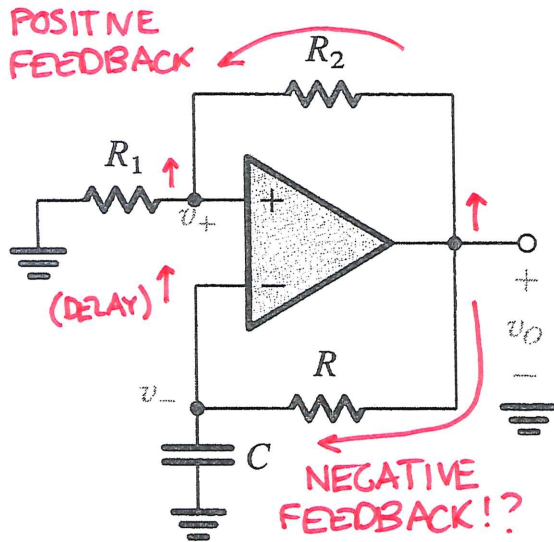


REDRAW

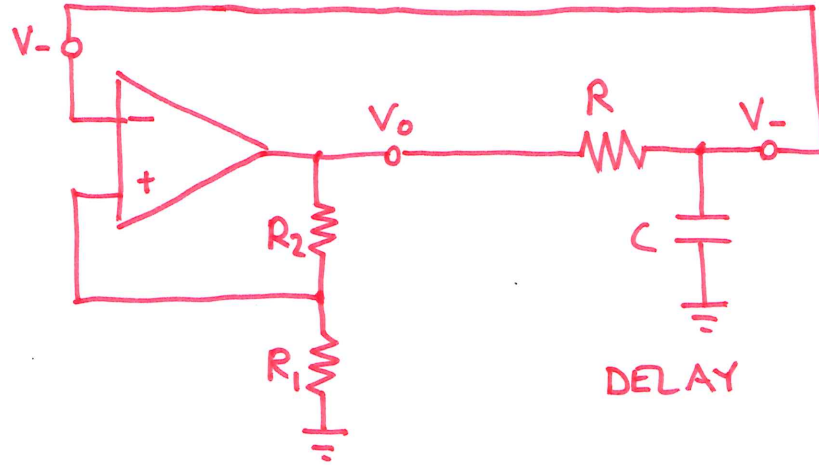

SCHMITT TRIGGER
(NONLINEAR)



RC LOWPASS

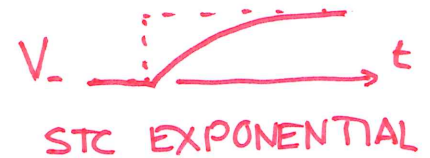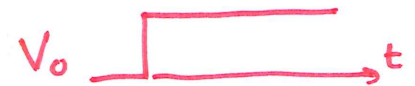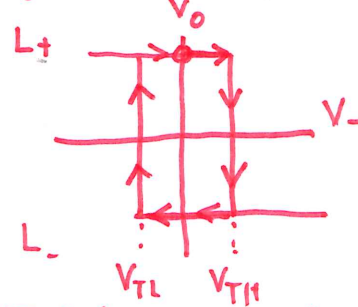


BOTH +, - FEEDBACK:
WHICH ONE WINS?

FAST SHORT TERM: LONGER TERM:
SCHMITT TRIGGER WINS $V_- \rightarrow V_+$

TIMING DIAGRAM

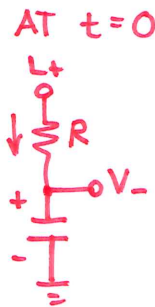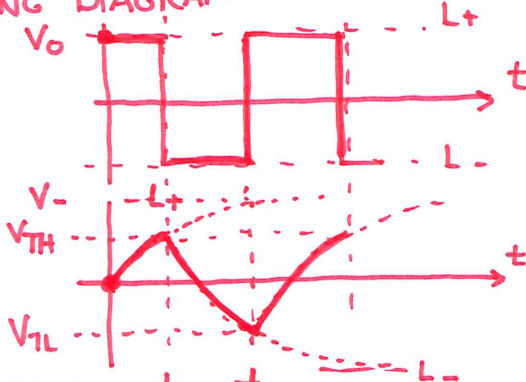

AT $t=t_1$

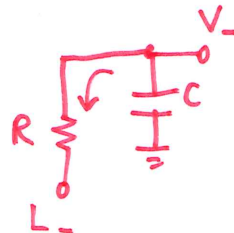

"BIG IDEA" FOR SQUARE WAVE OSCILLATOR

2 STABLE STATES

LINEAR TIME DELAY THAT CONTROLS SWITCHING

$$V(t) = V_F - (V_F - V_I) e^{-t/RC}$$