


Lab 4 Circuits

CMOS Inverter

MOSFET Switch (13.1)

Sample-and-Hold

Analog Multiplexer

 

MOSFET MODEL:




STATE  
CONTROLLED  
BY  $V_{GS}$  RELATIVE  
TO THRESHOLD  
VOLTAGE  $V_{TH}$

$R_{on}$  "ON  
RESISTANCE"


$|V_{GS}| \uparrow \Rightarrow R_{on} \downarrow$

# MOSFET Review

CIRCUIT SYMBOL

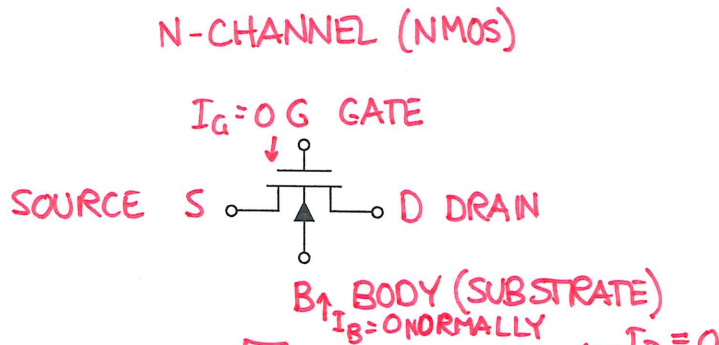


P-CHANNEL (PMOS)

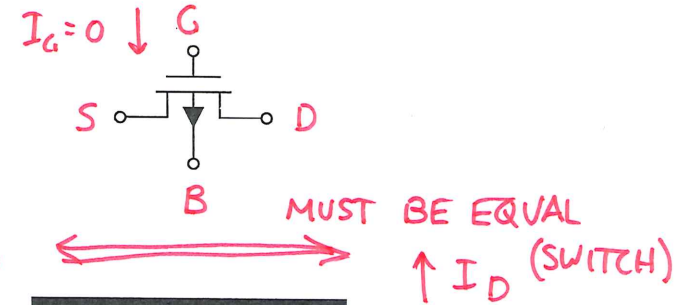


$V_{GS} = 0$   
OFF

BACK-TO-BACK  
DIODES IN  
D-S PATH!

NMOS  
 $V_{GS} > V_{TH}$   
ON

 

P  
B


 





E FIELD ATTRACTS  $e^-$   
CONTINUOUS n-TYPE  $S \rightarrow D$





$I_B = 0$   
KEEP S-B, D-B  
JUNCTIONS  
REVERSE BIASED

  B TO MOST - VOLTAGE ← → B TO MOST + VOLTAGE



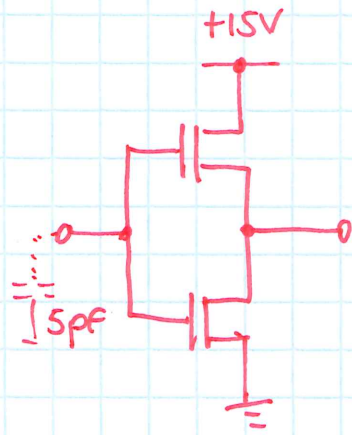 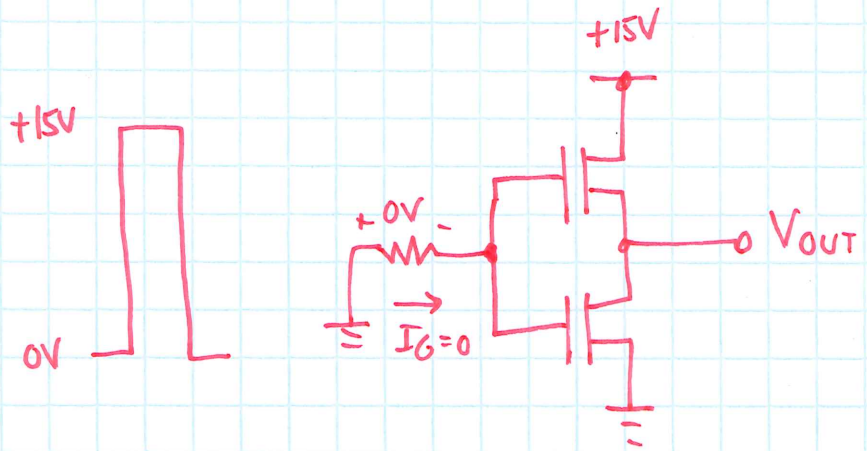

# CMOS Inverter

 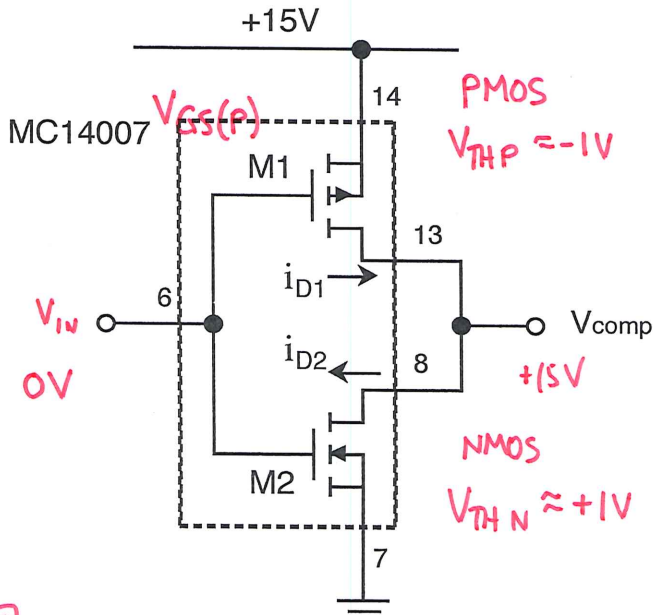


$V_{in}$	$V_{comp}$
0V	+15V
+15V	0V

MODEL


$$V_{GS(P)} = 0 - (+15) \approx -15V \ll -1V$$

$$V_{GS(N)} = 0 - 0 = 0V < V_{TH(N)}$$

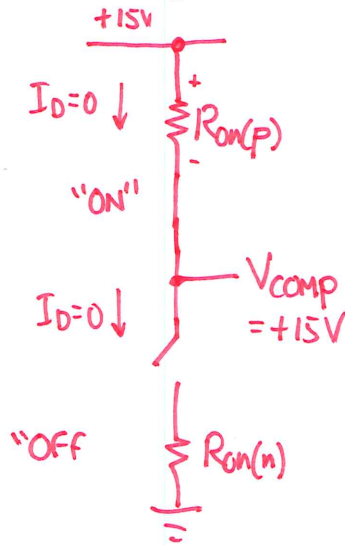


$$V_{GS(P)} = 0 \text{ OFF}$$
 
$$V_{GS(N)} = +15V - 0 = +15V > V_{TH(N)}$$




P3. Sample-and-hold

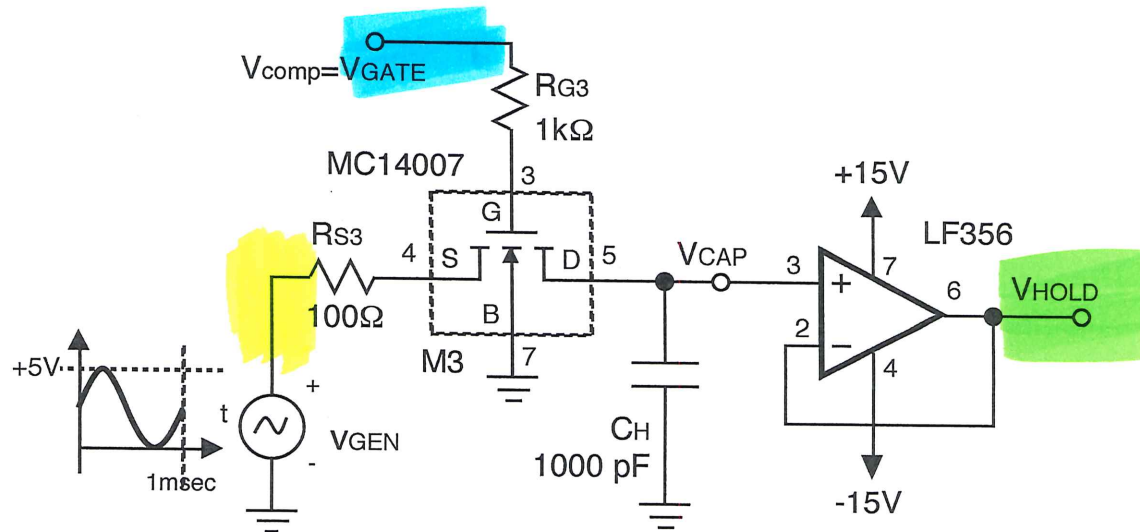The sample and hold circuit of Figure 4.3 uses one of the MC14007 N-channel MOSFETs as analog switch M3. Note that  $V_{GEN}$  is a 1kHz, 5V peak-to-peak sine wave with a +2.5V DC offset: the voltage swings from 0V to +5V. Resistors  $R_{G3}$  and  $R_{S3}$  are for protection of the analog switch.




# Sample-and-Hold Development

$V_G = +15V$  "SAMPLE" MODE

 



$V_{GS(MIN)} = +10V$   $V_{GS(MAX)} = +15V$   
 ALWAYS  $> V_{TH(N)}$  : NMOS "ON"

## EQUIVALENT CIRCUIT

 


LOWPASS FILTER

  CHOOSE  $C_H, R_{on}$  :  $f_{3dB} = \frac{1}{2\pi R_{TOTAL} C_H}$   
 $\gg f_{MAX}$  OF INPUT




"HOLD" MODE

 

$V_{GS} = 0V$   $V_{GS} = -5V$   
 ALWAYS  $< V_{TH(N)}$  : NMOS OFF

## EQUIVALENT CIRCUIT

 

KCL FOR CAP:

$$i_{sw} + i_t + i_c = 0 \Rightarrow i_c = 0$$

$i_c = C \frac{dv_c}{dt}$  CHANGE IN  $C_H$  VOLTAGE IS ZERO

$C_H$  WILL HOLD WHATEVER VOLTAGE IT HAD WHEN NMOS TURNED OFF