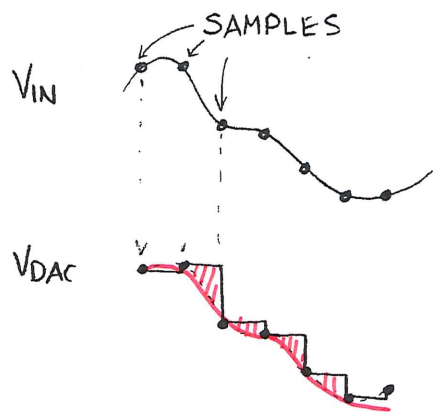



ECE3204 Lecture 18: FILTER DESIGN IN THE s-PLANE

Why filter? Look at reconstruction of signal with D/A converter:




TIME DOMAIN INTERPRETATION

NEED TO "SMOOTH OUT" STEPS FROM DAC

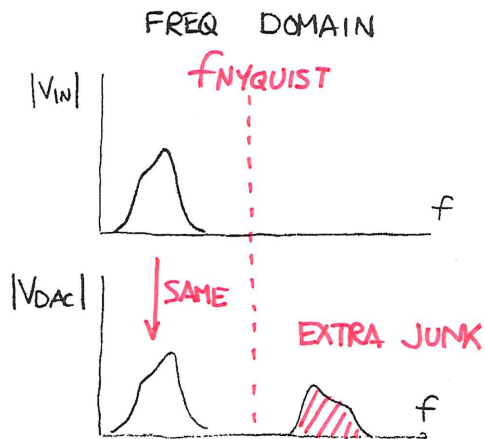

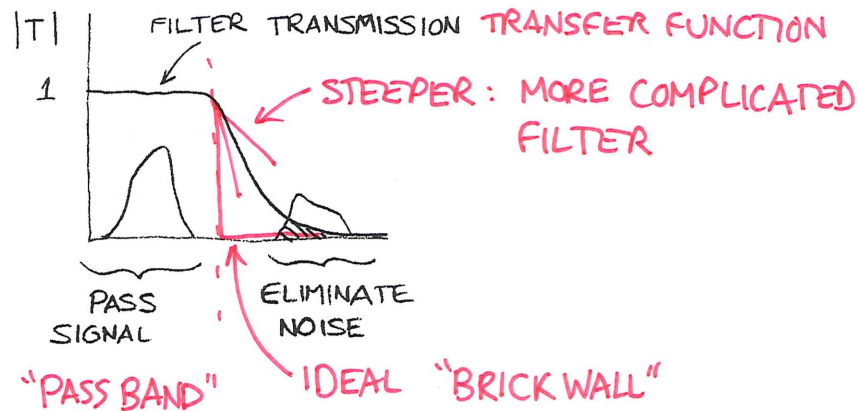
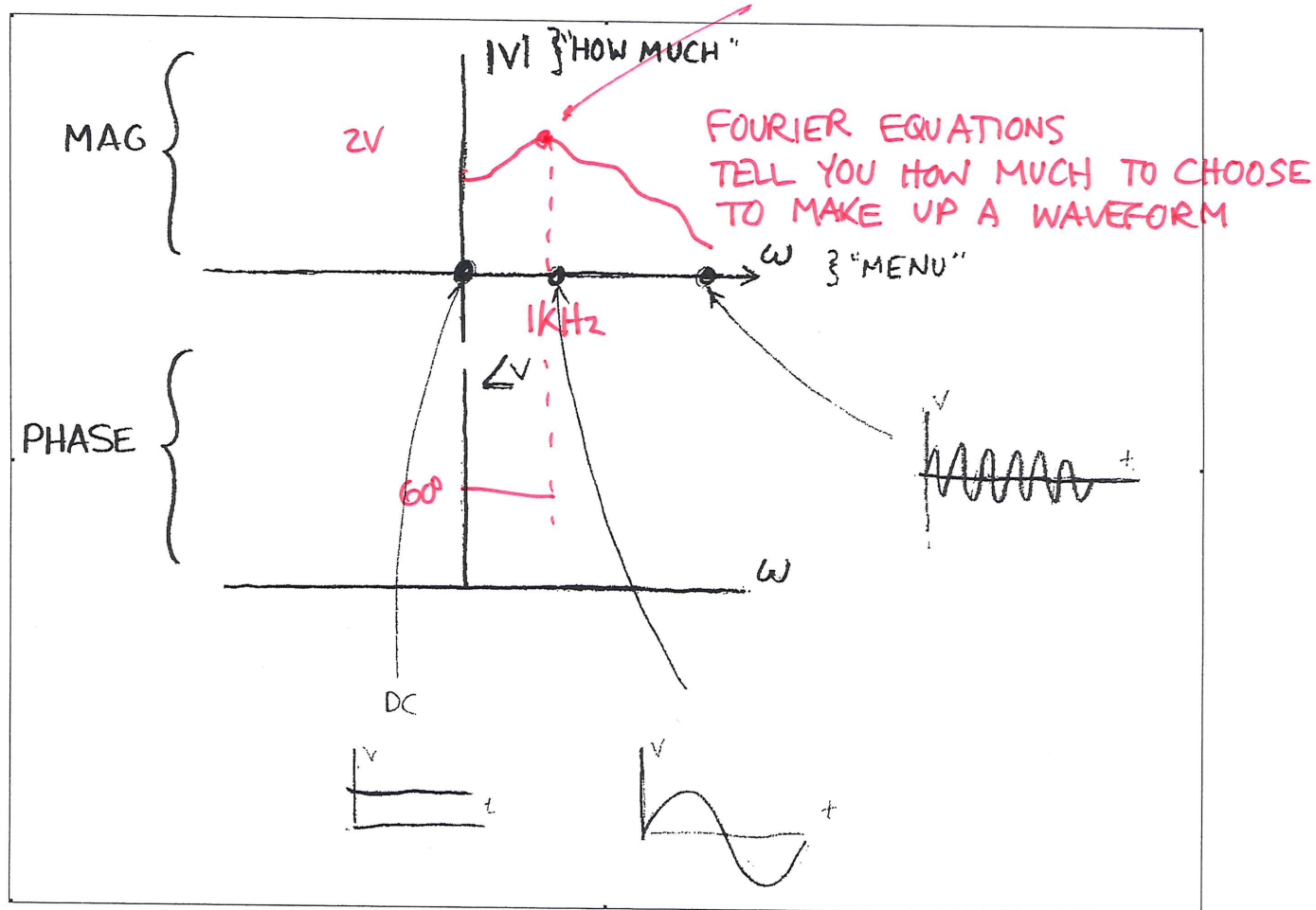
NOISE FROM DAC STEPS

FREQ DOMAIN INTERPRETATION



Fourier transform: Plot V as a function of frequency ω

$2V$  $2V (\sin(2\pi 1\text{kHz})t + 60^\circ)$




Assumes linearity: Adding sinusoids of different frequencies

Any waveform can be expressed as sum of sinusoids: Why bother with s for Laplace?

Why s? Look at STC exponential response

STC EXPONENTIAL RESPONSE

$$V = V_0 e^{-t/\tau}$$

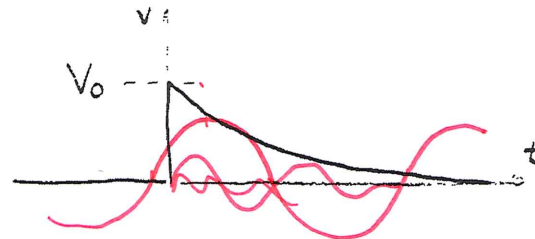

VERY EASY: JUST ONE NUMBER τ
IF I ALLOW e^{\pm} WAVEFORMS

NEED LOTS OF SINES TO MAKE THIS WAVEFORM!

EXPAND "MENU"

$$e^{j\omega t} \rightarrow e^{st}$$

$$s = \sigma + j\omega$$

COMPLEX FREQUENCY s

ALLOWS BOTH REAL, IMAGINARY PARTS
IN FREQUENCY

Transforms:

FOURIER: ω ($2\pi f$)

Fourier vs. Laplace

LAPLACE s ($\sigma + j\omega$)

WAVEFORM: SUM OF COMPLEX EXPONENTIALS

$$V = V_0 e^{j\omega t}$$

$$V = V_0 e^{st}$$

WHY? I-V FOR CAPACITOR EXAMPLE

$$I = C \frac{dV}{dt}$$

CAN WE MAKE THIS AS EASY AS OHM'S LAW $R = \frac{V}{I}$?

$$I = C \frac{d}{dt} [V_0 e^{j\omega t}]$$

$$I = C \frac{d}{dt} [V_0 e^{st}]$$

$$I = C j\omega \underbrace{V_0 e^{j\omega t}}_V$$

$$I = C s \underbrace{V_0 e^{st}}_V$$

$$I = j\omega C V$$

$$I = sC V$$

$$\frac{V}{I} = \frac{1}{j\omega C}$$

$$\frac{V}{I} = \frac{1}{sC}$$

Fourier is "subset" of Laplace: Let $s = j\omega$

Impedances:

$$Z_C = \frac{1}{j\omega C}$$

$$Z_C = \frac{1}{sC}$$

} C

$$Z_L = j\omega L$$

$$Z_L = sL$$

} L

$$Z_R = R$$

s-Plane as "map" of waveforms.

Plot real, imaginary parts of s

Waveform examples: DC


$s = 0$ TIME
DOMAIN

$e^{st} = e^{0t} = 1$

TIME




S-PLANE

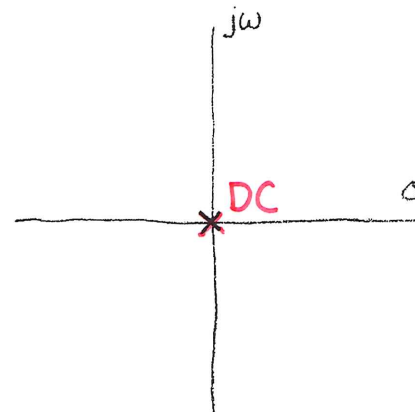


$$s = \frac{-1}{\tau}$$

$$e^{st} = e^{\left(\frac{-1}{\tau}\right)t} = e^{-t/\tau}$$

TIME

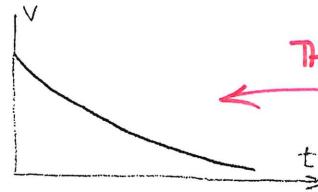


S-PLANE

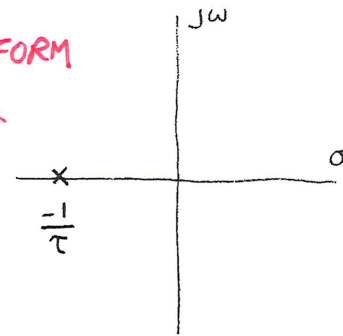

THIS ← WAVEFORM



REAL AXIS: EXPONENTIALS

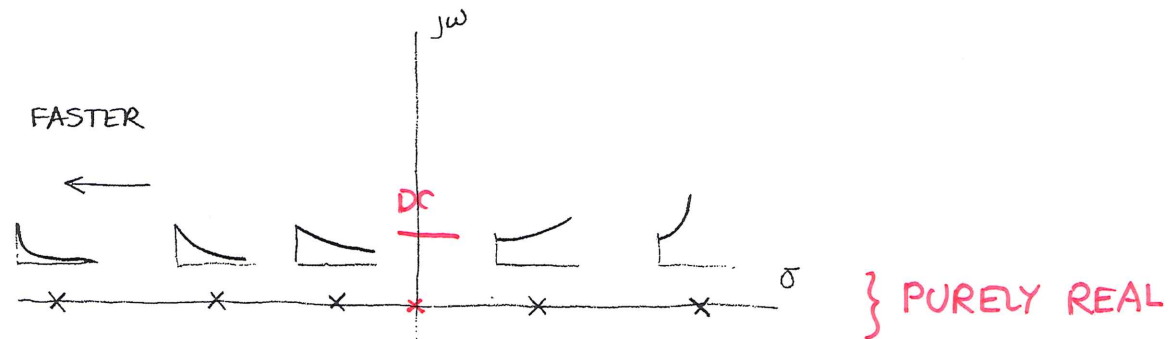

LHP: LEFT HALF PLANE
NEGATIVE REAL PART
DECAYING EXPONENTIAL

STABLE

RHP: RIGHT HALF PLANE
POSITIVE REAL PART
GROWING EXPONENTIAL

UNSTABLE

Pure sinusoids (complex conjugate pair)

$$s_1 = j(+\omega) \quad s_2 = j(-\omega)$$

$$e^{s_1 t} = e^{j\omega t} \quad e^{s_2 t} = e^{-j\omega t}$$

EULER RELATIONSHIP (COMPLEX NUMBERS)

$$e^{j\theta} = \cos\theta + j\sin\theta$$


$$e^{j\omega t} = \cos\omega t + j\sin\omega t \quad e^{-j\omega t} = \cos\omega t - j\sin\omega t$$

ADD BY SUPERPOSITION

$$e^{s_1 t} + e^{s_2 t} = \cos\omega t + \cancel{j\sin\omega t} + \cos\omega t - \cancel{j\sin\omega t}$$
$$= 2\cos\omega t$$

NEED CONJUGATE TO MAKE
IMAGINARY PART GO AWAY

IMAGINARY AXIS: SINUSOIDS

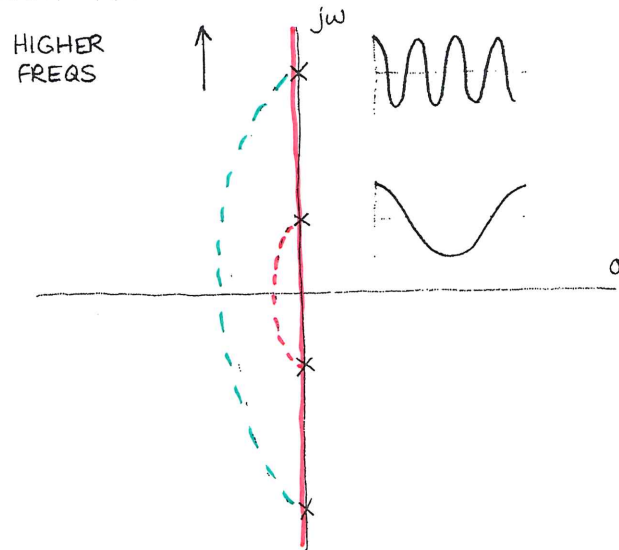

Both Real and Imaginary parts

$$s_1 = \sigma + j\omega$$

$$s_2 = \sigma - j\omega$$


$$e^{s_1 t} = e^{(\sigma + j\omega)t}$$
$$= e^{\sigma t} e^{j\omega t}$$

$$= e^{\sigma t} e^{-j\omega t}$$

ADD

FROM $\text{Re}\{s\}$

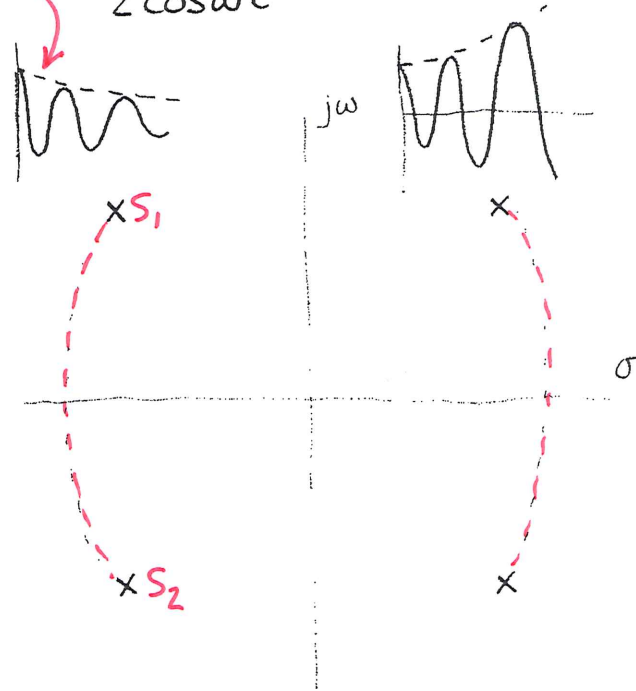
$$e^{\sigma t} (e^{j\omega t} + e^{-j\omega t})$$
$$2 \cos \omega t$$



STABLE

UNSTABLE

s-Plane summary

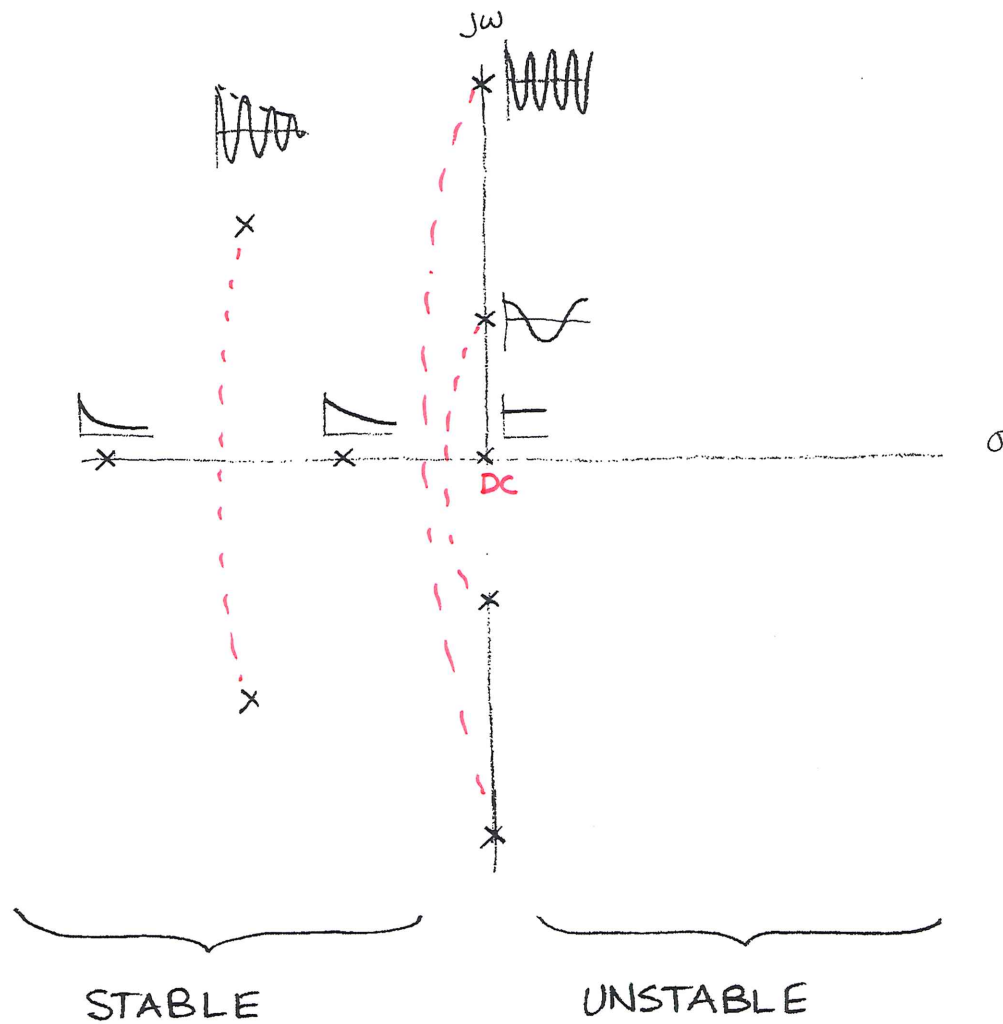

Forms of transfer function

$$\frac{V_{out}}{V_{in}} T(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_0}{s^n + b_{n-1} s^{n-1} + \dots + b_0}$$

$T(s)$ FILTER TRANSMISSION

$H(s)$ GENERAL TRANSFER FUNCTION

POLYNOMIALS IN s
 a_i, b_i REAL NUMBERS

n ORDER OF THE NETWORK

$m \leq n$ FOR REAL SYSTEM


BETTER FORM FOR TRANSFER FUNCTION!
 SHOW ROOTS EXPLICITLY

$$T(s) = K \frac{\left(1 - \frac{s}{z_1}\right) \left(1 - \frac{s}{z_2}\right) \dots \left(1 - \frac{s}{z_m}\right)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \dots \left(1 - \frac{s}{p_n}\right)}$$

$\underbrace{\hspace{10em}}_{\substack{\text{DC} \\ \text{GAIN} \\ (s=0)}}$

p_1, p_2, \dots, p_n POLES: VALUES OF s FOR WHICH
 DENOMINATOR $\rightarrow 0$
 $\Rightarrow |T| \rightarrow \infty$
 OUTPUT FOR $\rightarrow 0$ INPUT
 "NATURAL MODE OF A SYSTEM"

z_1, z_2, \dots, z_m ZEROS: VALUES OF s FOR WHICH
 NUMERATOR $\rightarrow 0 \Rightarrow |T| = 0$
 NO OUTPUT FOR ANY INPUT

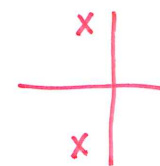


LOAD SYSTEM WITH INITIAL ENERGY


Poles, zeros: Plot these special values of s in the s -plane
Another way to specify transfer function

LOWPASS FILTER: DC GAIN OF 10
 f_{3dB} OF 20 KHz
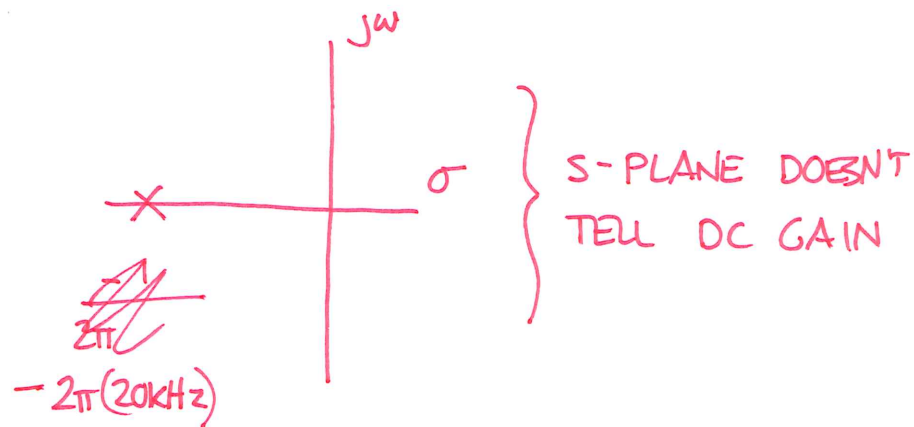
$$\frac{10}{1 + \frac{s}{2\pi \cdot 20\text{kHz}}}$$



Example:

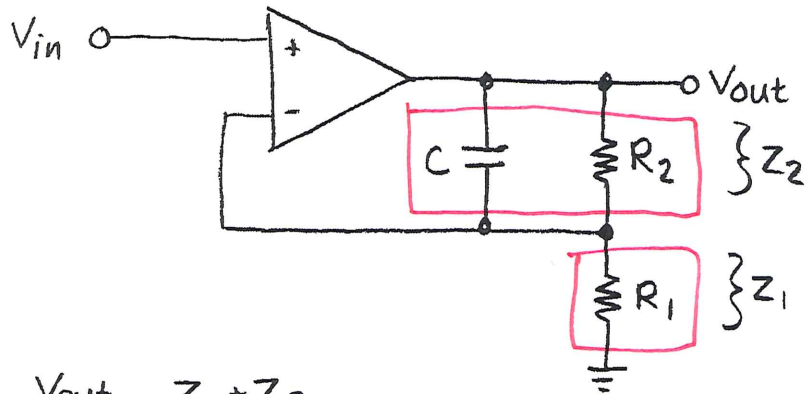

$$T(s) = \frac{V_{out}}{V_{in}} = \frac{Z_1 + Z_2}{Z_1}$$

$$= \frac{R_1 + \frac{R_2}{1 + sR_2C}}{R_1}$$

MESSAGE INTO STANDARD FORM

$$= \frac{R_1 + R_2 + sR_1R_2C}{R_1(1 + sR_2C)}$$



KNOW DC GAIN

$$T(s) = \underbrace{\left(\frac{R_1 + R_2}{R_1}\right)}_{\text{DC GAIN}} \frac{1 + s \overbrace{\left(\frac{R_1R_2}{R_1 + R_2}\right)}^{R_1 \parallel R_2} C}{1 + sR_2C}$$

1ST ORDER SYSTEM

$$\text{ZERO: } z_1 = \frac{-1}{(R_1 \parallel R_2)C}$$

$$\text{POLE: } p_1 = \frac{-1}{R_2C}$$

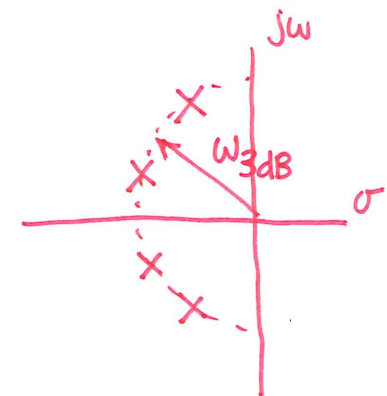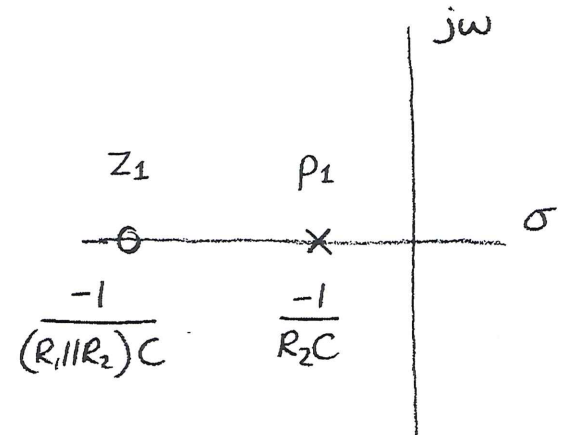

BUTTERWORTH
(4TH ORDER)

Bode plot

