
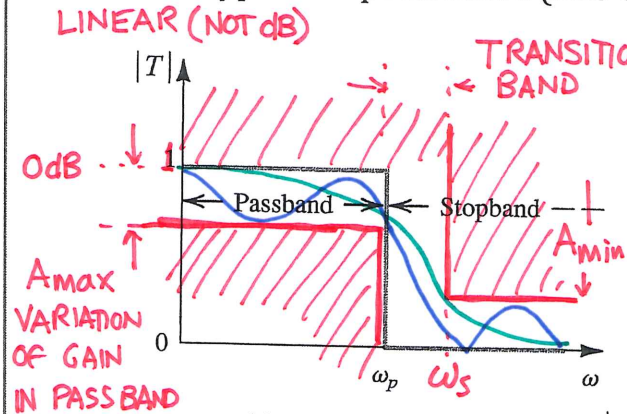


Filter Type and Specification (S&S Ch. 16 [6th edition])


IDEAL "BRICK WALL"

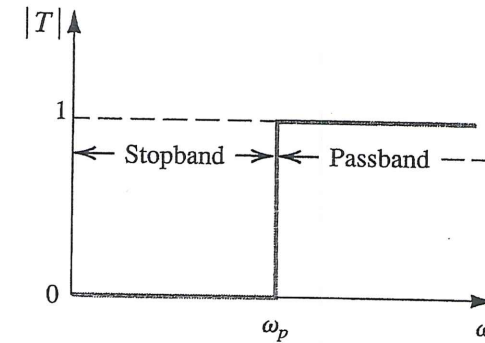


(a) Low-pass (LP)



(b) High-pass (HP)

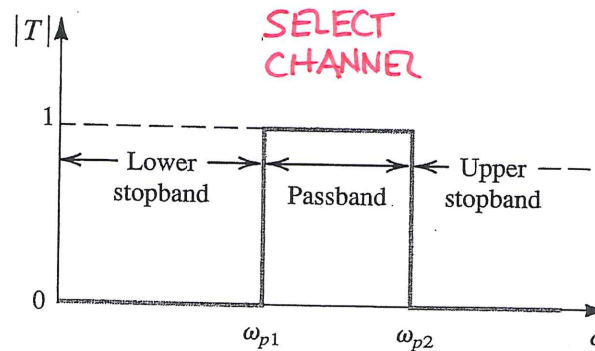

(c) Bandpass (BP)

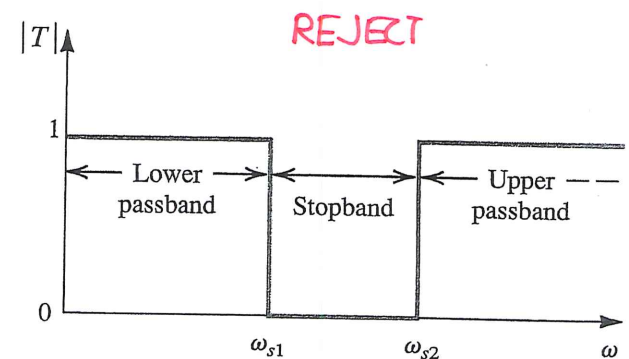

(d) Bandstop (BS)

Figure 16.2 Ideal transmission characteristics of the four major filter types: (a) low-pass (LP), (b) high-pass (HP), (c) bandpass (BP), and (d) bandstop (BS).


FILTER SYNTHESIS: 1) SPECIFY $\{ A_{max}, A_{min}, \omega_p, \omega_s, \dots \}$
 SHAPE: LP, HP, ...
 FAMILY BUTTERWORTH CHEBYSHEV

2) TRANSFER FUNCTION $T(s)$ IN S-PLANE

3) CIRCUIT WITH $\frac{V_{out}}{V_{in}} = T(s)$


Comparison of Filter Family Transfer Functions:

"MAXIMALLY FLAT"
IN PASSBAND

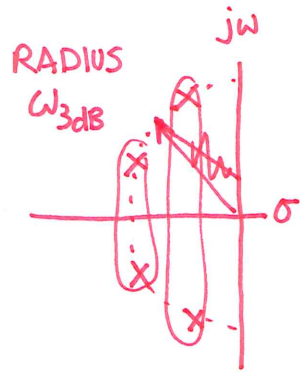


ALL POLE
FILTER

Butterworth

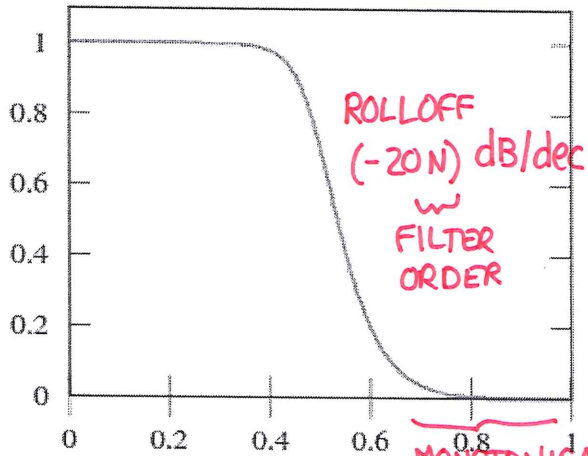


Chebyshev type 2


MONOTONICALLY
DECREASING
IN STOP BAND

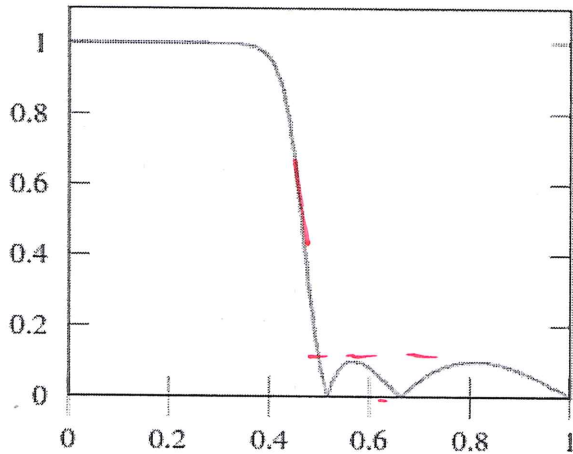

Chebyshev type 1

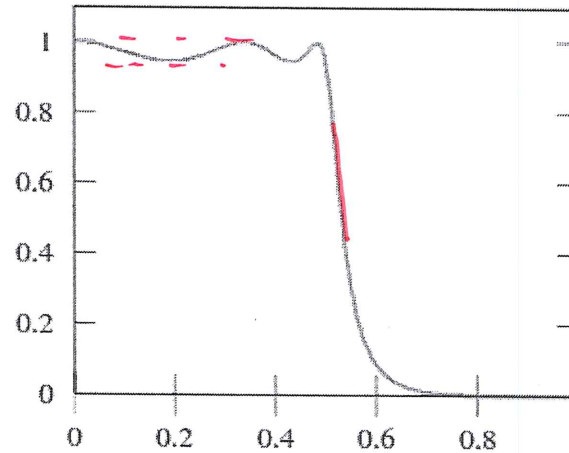


Elliptic

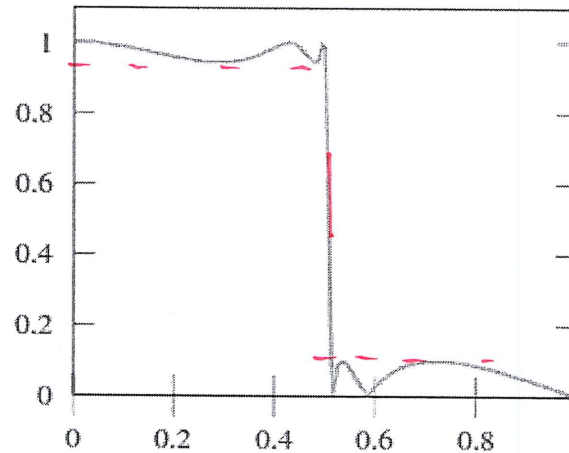


OTHER FAMILIES
STEEPER TRANSITION

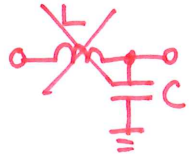http://en.wikipedia.org/wiki/Elliptic_filter (accessed April 16, 2013)



"SALLEN AND KEY" CIRCUIT

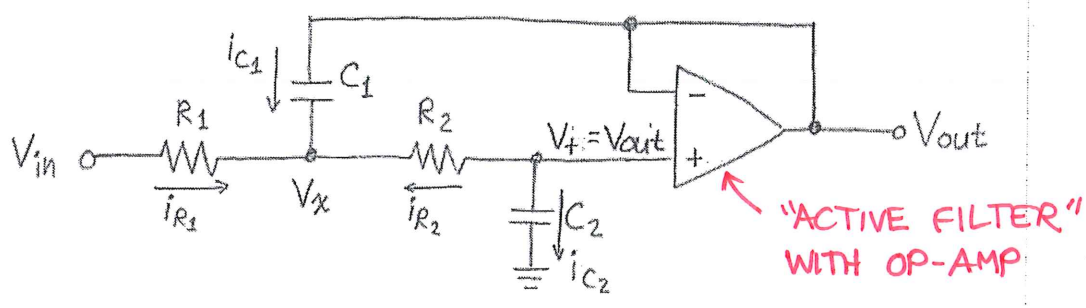For realizing a complex pole pair in the s-plane



Analysis: KCL using node voltages to describe currents.

At V_x (using $V_+ = V_{out}$, by ideal op-amp)

$$\underbrace{\frac{(V_{in} - V_x)}{R_1}}_{i_{R_1}} + \underbrace{(V_{out} - V_x) s C_1}_{i_{C_1}} + \underbrace{\frac{(V_{out} - V_x)}{R_2}}_{i_{C_2}} = 0 \quad [1]$$

Collecting terms and multiplying through by R_1 gives

$$V_{in} + V_{out} \left(s R_1 C_1 + \frac{R_1}{R_2} \right) = V_x \left(s R_1 C_1 + \frac{R_1}{R_2} + 1 \right) \quad [2]$$

KCL at V_+ gives


$$\underbrace{\frac{V_{out} - V_x}{R_2}}_{i_{R_2}} + \underbrace{V_{out} s C_2}_{i_{C_2}} = 0 \quad [3]$$

Collect and multiply by R_2 , giving

$$V_x = V_{out} (s R_2 C_2 + 1) \quad [4]$$

Substituting [4] into [2] to eliminate V_x and solving for V_{out}/V_{in} gives
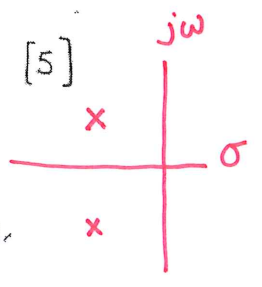
$$\boxed{\frac{V_{out}}{V_{in}} = \frac{1}{s^2 (R_1 R_2 C_1 C_2) + s (R_1 + R_2) C_2 + 1}} \quad \left. \begin{array}{l} \text{NO ZEROS} \\ \text{2nd ORDER} \end{array} \right\} \quad [5]$$



Which is a second order, all pole transfer function.

Design: How do we choose R_1, R_2, C_1, C_2 to place the complex pole pair where we want? We have 4 values to choose, yet the complex pole pair is completely determined by 2 numbers: the real and imaginary parts. So we have 2 free parameters among R_1, R_2, C_1, C_2 .

It turns out design is simplified by letting

$$R_1 = R_2 = R \quad [6]$$

Now S becomes

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2(R^2 C_1 C_2) + s(2RC_2) + 1}$$

The poles (roots of the denominator) are given by

$$p_1, p_2 = \frac{-2RC_2 \pm \sqrt{4R^2 C_2^2 - 4R^2 C_1 C_2}}{2R^2 C_1 C_2}$$


which reduces to

$$p_1, p_2 = \frac{-1}{RC_1} \left(1 \pm j \sqrt{\frac{C_1}{C_2} - 1} \right)$$

This can also be expressed in radial form. Some trigonometry gives

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$$

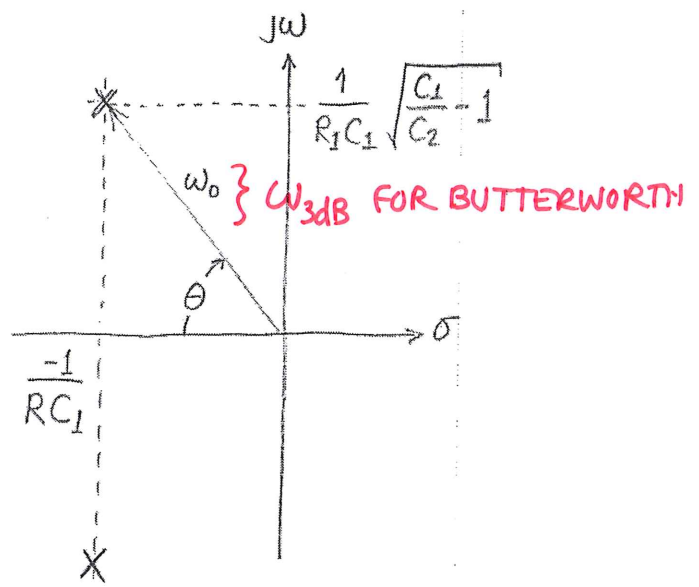
$$\tan \theta = \sqrt{\frac{C_1}{C_2} - 1}$$



We still have R and C_1 or C_2 as free parameters, with the constraint that $C_1 > C_2$.


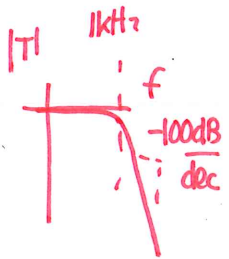
Example: DESIGN OF A 5th ORDER BUTTERWORTH LOWPASS FILTER USING SALLEN AND KEY CIRCUITS

Nth order Butterworth has N poles in the left half plane, on a semicircle of radius ω_0 , equally spaced $180^\circ/N$ apart. For $N=5$: $\times 20\text{dB/dec} = -100\text{dB/dec}$



Pole p_1 can be realized with a simple RC circuit. Pole pairs p_2/p_3 and p_4/p_5 can each be realized with Sallen and Key circuits

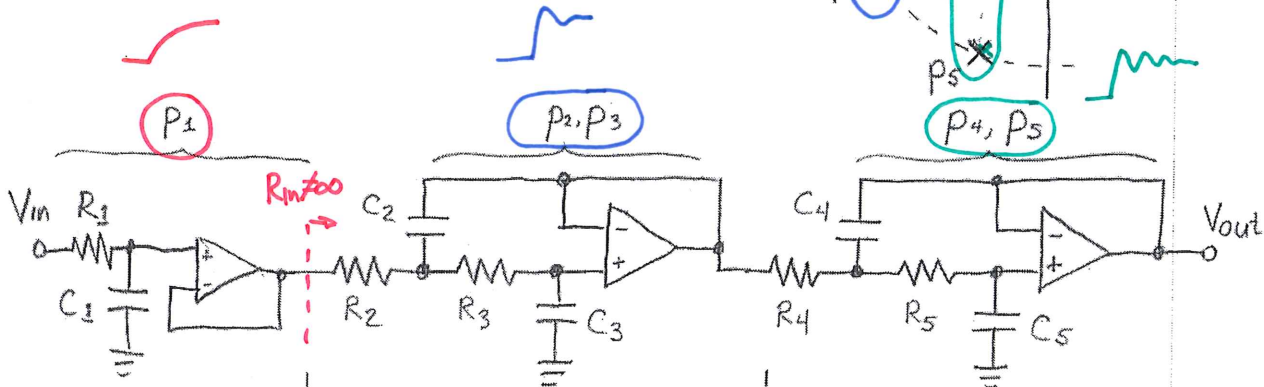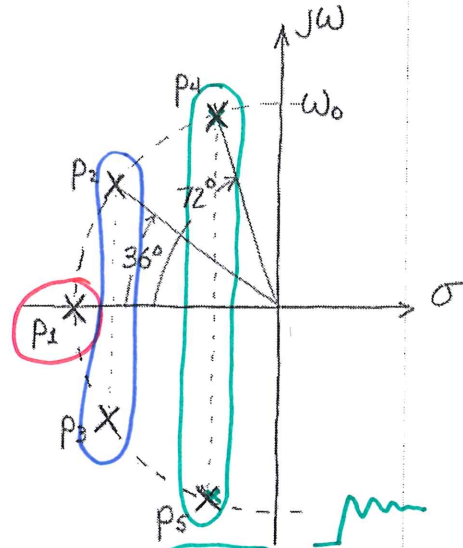Filter topology, for $f_{3\text{dB}} = 1\text{kHz}$
 $\omega_0 = 2\pi(1\text{kHz})$



$$\frac{1}{2\pi R_1 C_1} = 1\text{kHz}$$

$$R_1 = 16\text{ k}\Omega$$

$$C_1 = 0.01\ \mu\text{F}$$

$$\omega_0 = 995\text{ Hz}$$

$$\tan(36^\circ) = \sqrt{\frac{C_2}{C_3} - 1} = 0.7265$$

$$\frac{C_2}{C_3} = 1.528$$

$$\left. \begin{array}{l} C_2 = 0.015\ \mu\text{F} \\ C_3 = 0.01\ \mu\text{F} \end{array} \right\} \theta = 35.3^\circ$$

$$2\pi(1\text{kHz}) = \frac{1}{R\sqrt{(0.015\ \mu\text{F})(0.01\ \mu\text{F})}}$$

$$R = 12.99\text{ k}\Omega \approx 13\text{ k}\Omega$$

$$R_2 = R_3 = 13.0\text{ k}\Omega$$

$$\omega_0 = 999\text{ Hz}$$

$$\tan(72^\circ) = \sqrt{\frac{C_4}{C_5} - 1} = 3.078$$

$$\frac{C_4}{C_5} = 10.47$$

$$\left. \begin{array}{l} C_4 = 0.1\ \mu\text{F} \\ C_5 = 0.01\ \mu\text{F} \end{array} \right\} \theta = 71.6^\circ$$

$$2\pi(1\text{kHz}) = \frac{1}{R\sqrt{(0.1\ \mu\text{F})(0.01\ \mu\text{F})}}$$


$$R = 5.033\text{ k}\Omega \approx 5.1\text{ k}\Omega$$

$$R_4 = R_5 = 5.1\text{ k}\Omega$$


$$\omega_0 = 987\text{ Hz}$$

IDENTIFY FEEDBACK!

Review 1

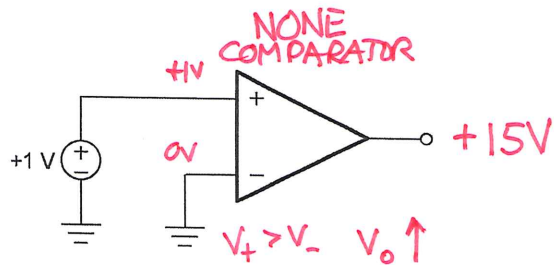

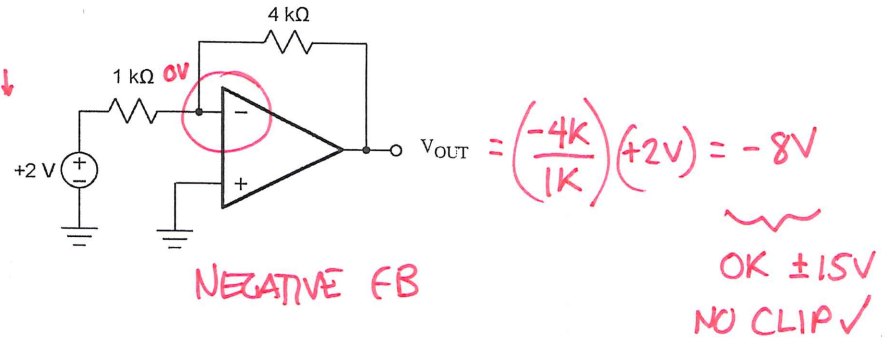
NEG $\rightarrow V_-, V_+ =$
 NONE COMPARTOR SIGN $V_+ - V_-$
 POS SIGN $V_+ - V_-$
 OUTPUT DRIVEN $\uparrow \downarrow$






VALUES OF V_+

$$V_+ = \left(\frac{15}{18}\right) 12V + \left(\frac{3}{18}\right) V_{OUT}$$

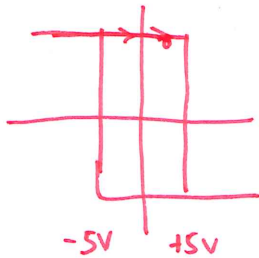
$$\frac{5}{6} (12V) + \frac{1}{6} (-15V) \quad V_+ > 0$$




INVERTING S.T.

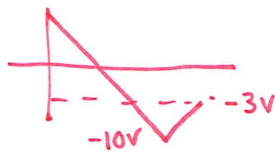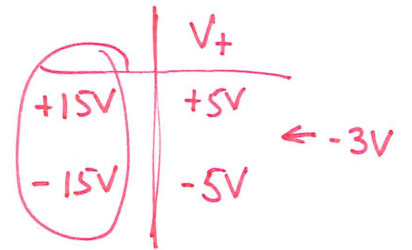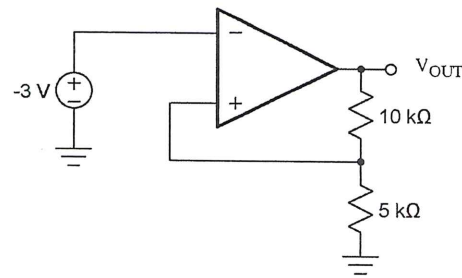

DON'T KNOW IF $V_+ > V_-$?! NEED PAST

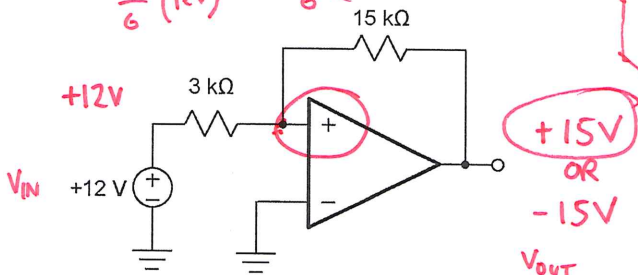


POSITIVE FB
 SCHMITT TRIGGER

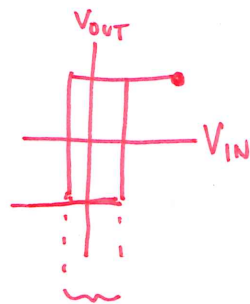

$V_{TL}, V_{TH} \quad \frac{3k\Omega}{15k\Omega} \pm 15V = \pm 3V$

INSIDE HYSTERESIS BOX?

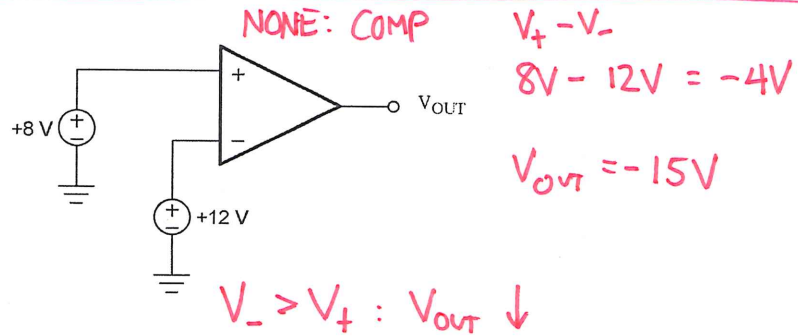

$V_- > V_+ : V_{OUT} \downarrow$

Review 2

