

ECE3204 Lecture 20

Differentiator

Stability analysis (Ch. 10)



Handouts:

Ch. 10 Reading Guide

Differentiator

P1. Differentiator

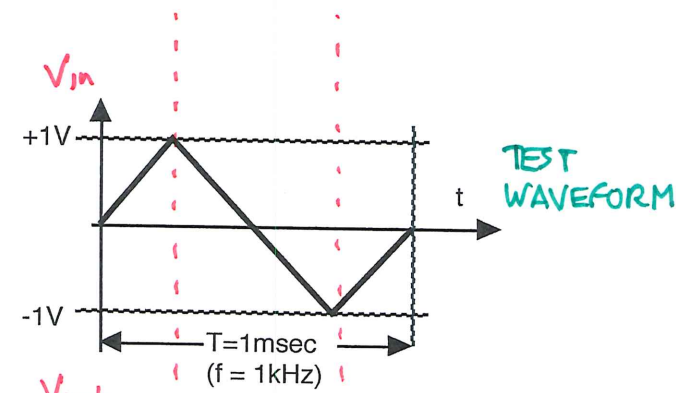
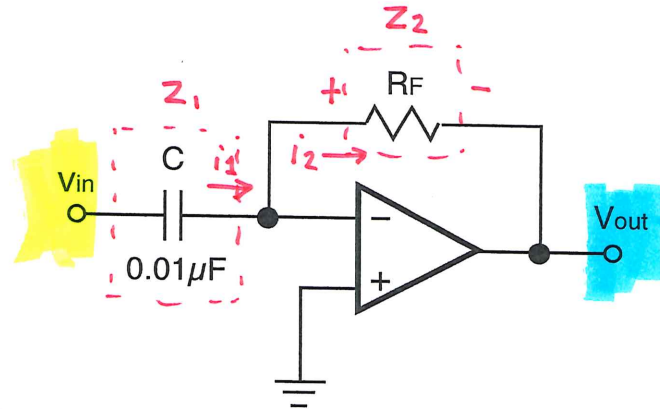
The basic differentiator topology is shown in Figure 6.1. This topology is rarely (if ever) used in practice - you will see why when you build this circuit in the lab.



FREQ DOMAIN:

$$\frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1} = \frac{-R_F}{1/sC} = -sR_F C$$

180° PHASE (MINUS SIGN)
ZERO AT ORIGIN

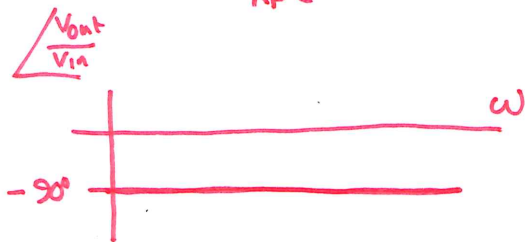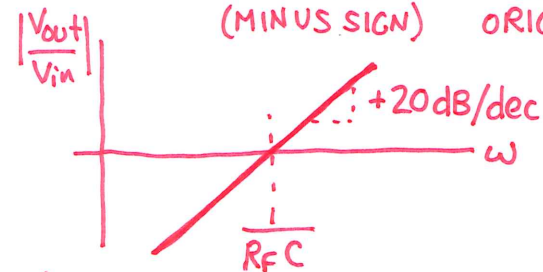

TIME DOMAIN:

KCL AT - INPUT:

$$i_1 = i_2$$

VIRTUAL GROUND:

$$V_{out} = -i_2 R_F$$

CAPACITOR

$$i_1 = C \frac{dV_{in}}{dt}$$

SUBSTITUTE

$$V_{out} = -R_F C \frac{dV_{in}}{dt}$$

sec V/sec

EXPECTED


OUTPUT

ACTUAL!?

WHY?

POLES OF THIS SYSTEM

HOW TO MAKE POLES MORE STABLE?

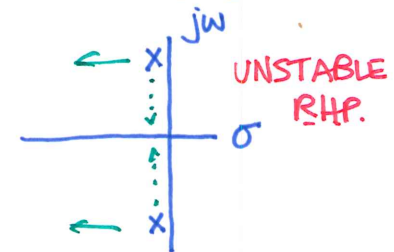


ASSUMED $V_- = V_+$ WITH A LARGE

A IS REALLY $A(\omega)$
NOT LARGE FOR ALL ω (GBWP)
 $|A(\omega)| \neq 0$ FOR ALL ω !

WHY CARE ABOUT DERIVATIVE ANYWAY?


TIME PLOT OF WAVEFORM

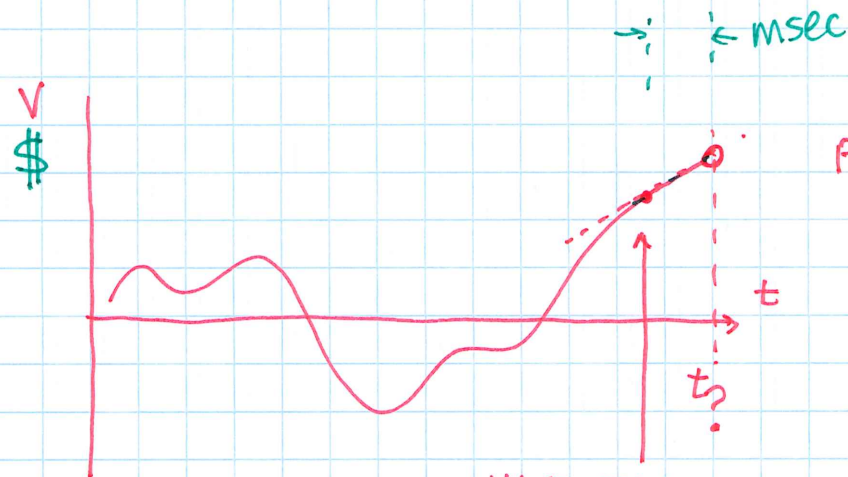

PREDICT; NEED $\frac{dv}{dt}$

HAVE THIS VALUE... WHERE WILL IT BE AT t_2 IN THE FUTURE?

Feedback Changes Pole Locations

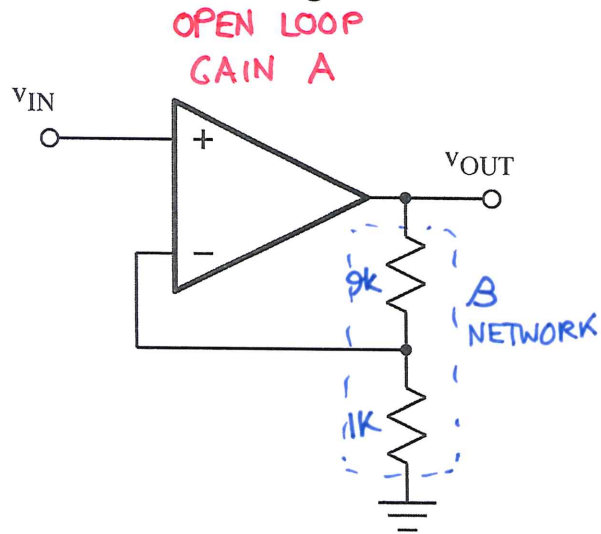

OPEN LOOP
GAIN A

$$V_{out} = A(V_{in} - B V_{out})$$

$$V_{out} (1 + AB) = A V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB} \quad \left. \begin{array}{l} \text{CLOSED LOOP} \\ \text{TRANSFER FUNCTION} \end{array} \right\}$$

SIMPLIFY IF $AB \gg 1$

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + AB} = \frac{1}{B}$$


$$B = 0.1$$

EXAMPLE


CHOOSE $R_2 = 9K$

$R_1 = 1K$

WANTED CLOSED LOOP GAIN = 10

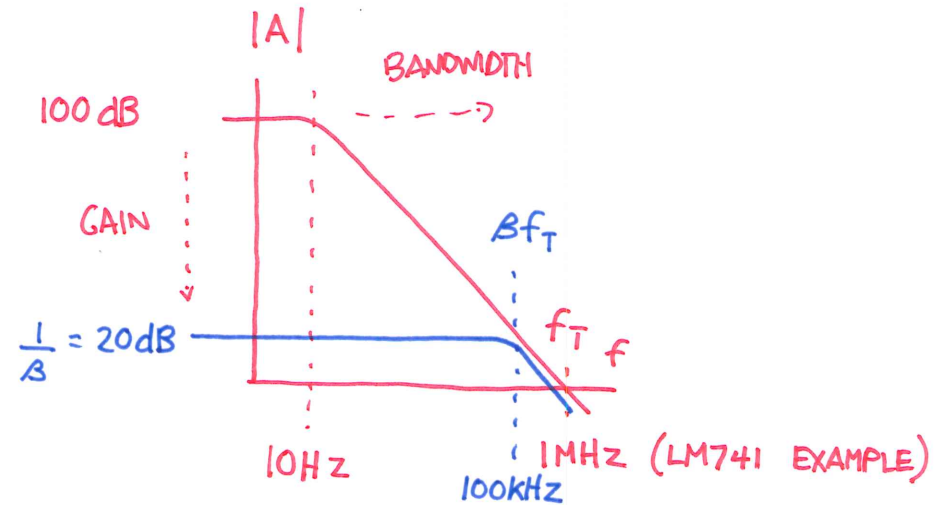

S-PLANE PLOT FOR $A(f)$

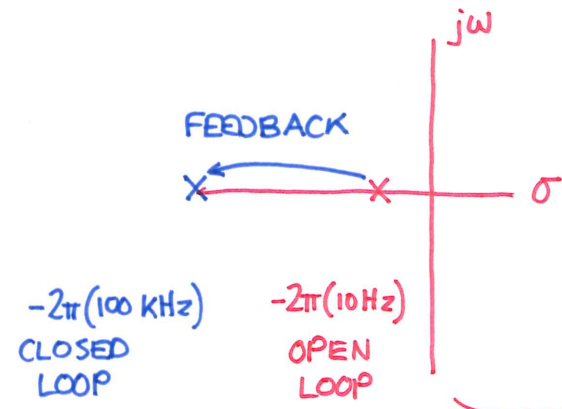

WHAT IF OUR FEEDBACK
MOVES POLES INTO RHP!?

BAD!

SYSTEM IS UNSTABLE

Closed Loop Transfer Function

$$\frac{V_{out}}{V_{in}} = \frac{A}{1+AB} \Rightarrow \frac{A(s)}{1 + \underbrace{A(s)B(s)}}_{\text{REALLY}}$$

CLOSED
LOOP
TRANSFER

BOTH A, B ARE
TRANSFER FUNCTIONS

FUNCTION: WHERE ARE THE POLES?

ROOTS OF DENOMINATOR POLYNOMIAL

$$1 + A(s)B(s) = 0$$

TO DO THIS


MULTIPLY OUT POLYNOMIAL

FIND ALL ROOTS s_{p1}, s_{p2}, \dots

PLOT IN s -PLANE

TOO MUCH
INFORMATION

MODE OF
NATURAL
RESPONSE

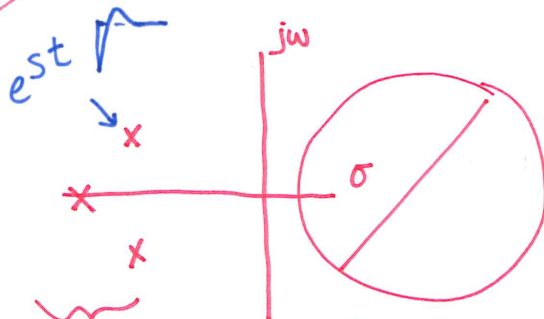


ONLY CARE THAT
WE ARE IN L.H.P.

NO POLES HERE!

EXACT LOCATION NOT CRITICAL

Do I HAVE TO find all exact pole locations? **NO!**

JUST LOOK ON BOUNDARY ON $j\omega$ AXIS

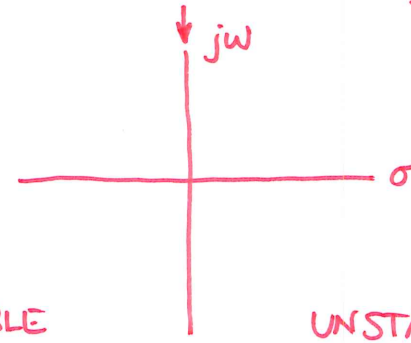

ANY POLES ON THE BOUNDARY?

$$1 + A(j\omega)B(j\omega) = 0$$

$s = j\omega$ LOOK ON $j\omega$ AXIS?

IS THIS REALLY EASIER?

RESTATE AS $A(j\omega)B(j\omega) = -1$

BODE PLOT!

$$|A(\omega)||B(\omega)| = 1$$

$$\angle A(\omega) + \angle B(\omega) = -180^\circ$$

CAN WORK WITH BODE
PLOTS OF A, B