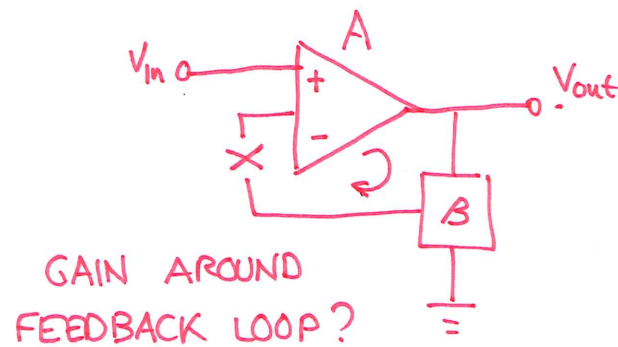


Loop Gain: AB QUANTITY



AB "LOOP GAIN" ← CAN GET STABILITY PROPERTIES JUST FROM AB


A "OPEN LOOP GAIN" (NO FEEDBACK)

$\frac{A}{1+AB}$ "CLOSED LOOP GAIN" (WITH FEEDBACK WORKING)

Finding Loop Gain; Differentiator




1
Set all independent sources equal to zero

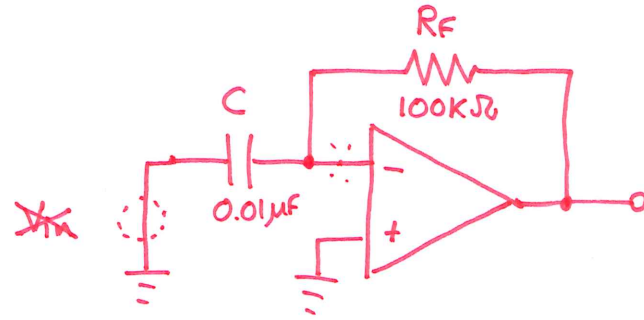STABILITY IS A PROPERTY OF THE SYSTEM (NOT V_{in} , V_{out})



2
Break feedback loop (don't change loading)

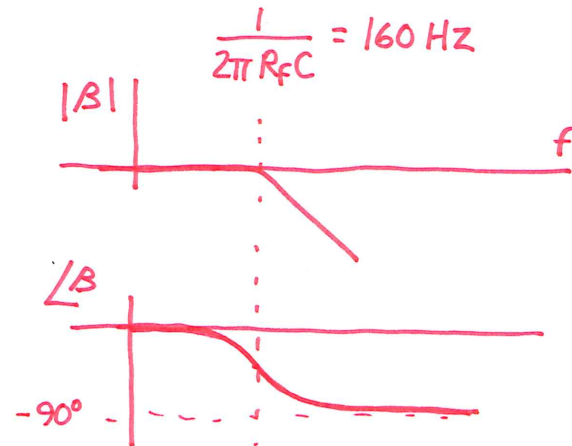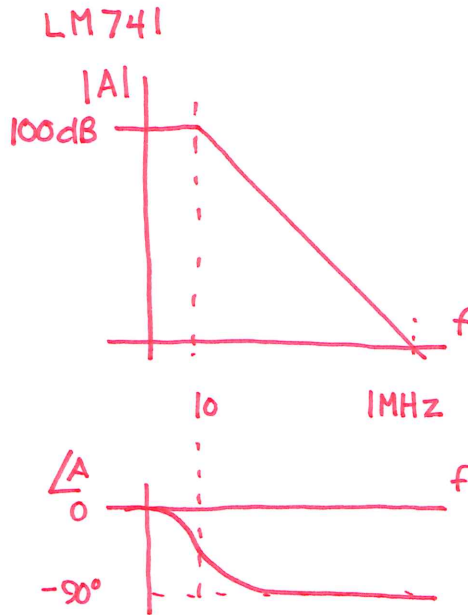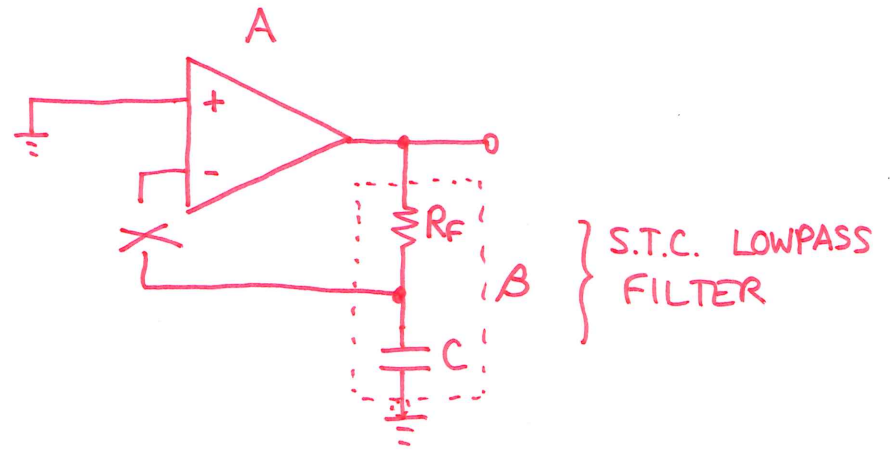2A
Redraw in A, β format for clarity (optional)



3
Find $|A|, |\beta| \angle A, \angle \beta$

Stability Analysis Procedure

1
Plot Loop Gain
 $|A\beta| \angle A\beta$

2
Find f_1
Frequency at
which $|A\beta|=1$

3
Check $\angle A\beta$ at f_1
compared to -180°

$$|AB| = |A| |B|$$


ADD dB

$$\angle AB = \angle A + \angle B$$

ADD PHASE

$|A|$ $|B|$ $|AB|$

$\angle A$ $\angle B$

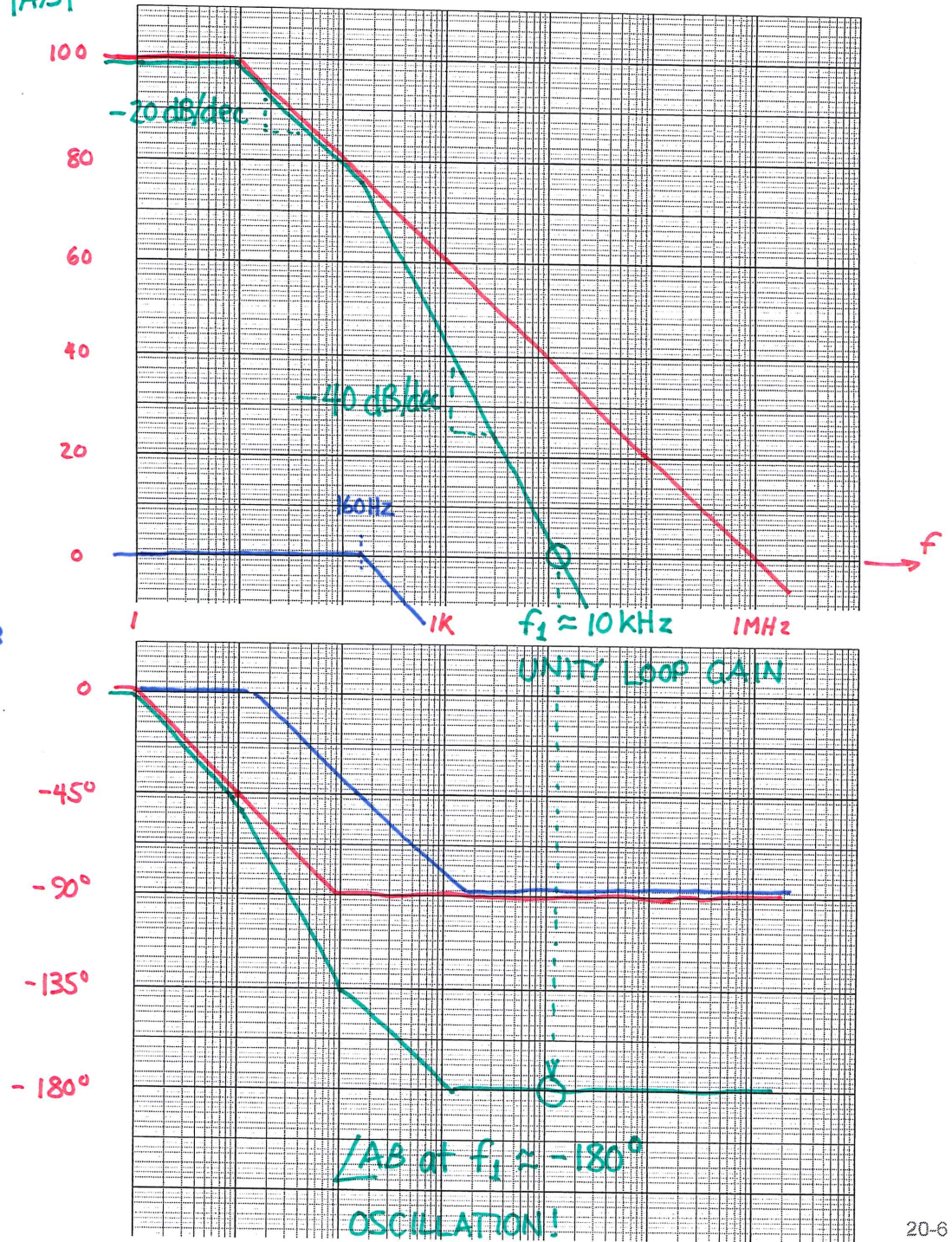

Intuitive view of stability

CONDITION: $|AB| = 1$


$\angle AB = -180$

PUTS POLES OF
CLOSED LOOP $\frac{V_{out}}{V_{in}}$

ON $j\omega$ AXIS


\Rightarrow CONTINUOUS SINUSOID

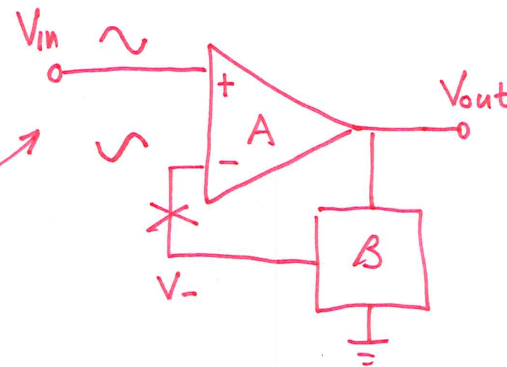180 PHASE INVERSION
AT THIS FREQUENCY
TURNS - FEEDBACK
INTO + FEEDBACK



A: $90^\circ \phi$ LAG

B: $90^\circ \phi$ LAG

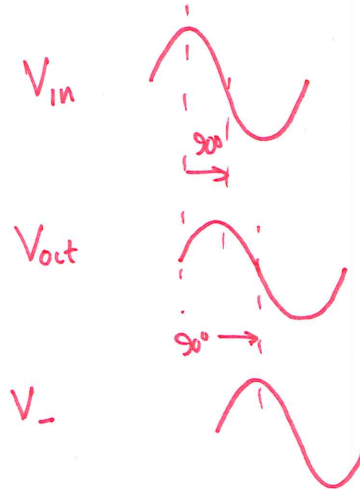

Practical Differentiator (Lab 6)

The circuit of Figure 6.1 can be made more stable by inserting a resistor in series with the capacitor, as shown in Figure 6.5.

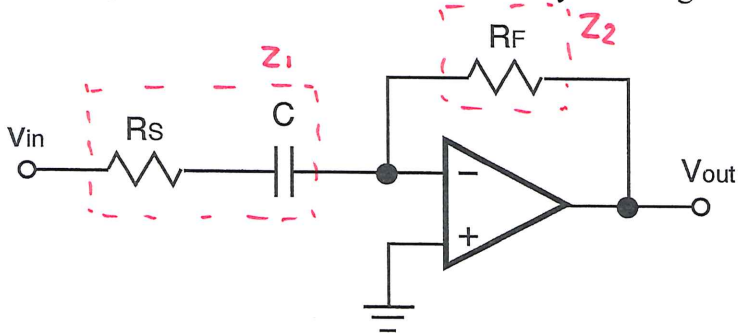



Figure 6.5

TRANSFER FUNCTION (ASSUME OP-AMP IDEAL)

$$\frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1} = \frac{-R_f}{R_s + \frac{1}{sC}} \cdot \frac{sC}{sC}$$

$$\frac{V_{out}}{V_{in}} = \frac{-sR_f C}{1 + sR_s C} \quad \left. \begin{array}{l} \} \text{ZERO (SAME AS)} \\ \} \text{POLE} \end{array} \right\}$$
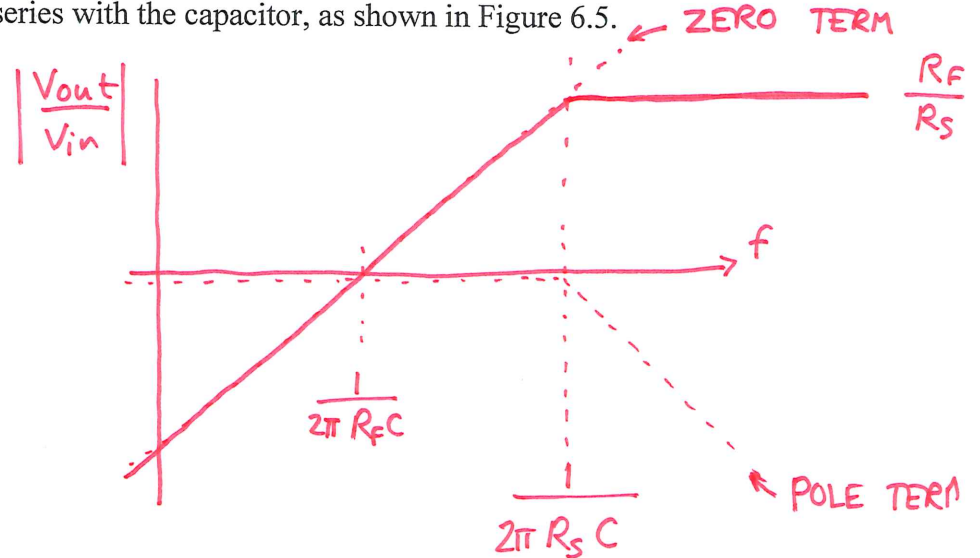
$$\text{POLE} = \frac{-1}{2\pi R_s C} \quad (\text{NEW})$$



SAME AS PURE DIFFERENTIATOR


BELOW POLE $\frac{1}{2\pi R_s C}$

FINITE GAIN AT HIGH FREQUENCIES

Practical Differentiator: Loop Gain

1

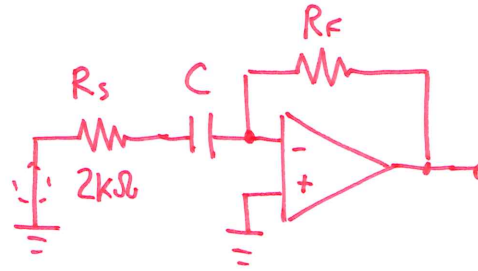Set all independent sources equal to zero




2

Break feedback loop (don't change loading)

2A

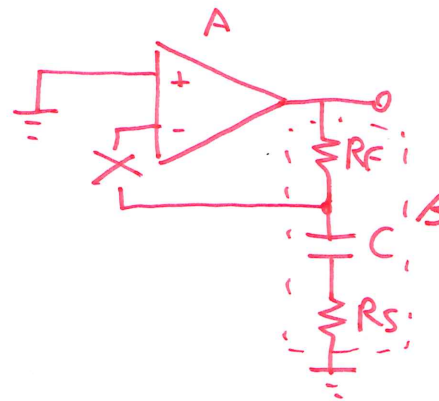Redraw in A, β format for clarity (optional)



$$B(s) = \frac{R_S + \frac{1}{sC}}{R_S + \frac{1}{sC} + R_F} \frac{sC}{sC}$$

$$B(s) = \frac{1 + sR_S C}{1 + s(R_S + R_F)C} \quad \begin{matrix} \text{ZERO} \\ \text{B: } \cancel{R_S} \end{matrix} \quad \text{POLE}$$

$$\text{ZERO: } f_Z = \frac{1}{2\pi R_S C} = \frac{1}{2\pi (2k)(0.01\mu F)} = 8 \text{ kHz} \quad \left. \vphantom{f_Z} \right\} \text{ NEW}$$

$$\text{POLE: } f_P = \frac{1}{2\pi (R_S + R_F)C} = \frac{1}{2\pi (102 \text{ k}\Omega)(0.01\mu F)} = 158 \text{ Hz} \quad \left. \vphantom{f_P} \right\} \approx \text{SAME}$$

3

Find $|A|, |\beta|$ $\angle A, \angle \beta$

Practical Differentiator: Stability Analysis

1

Plot Loop Gain

$$|A\beta| \angle A\beta$$

2

Find f_1

Frequency at
which $|A\beta|=1$

3

Check $\angle A\beta$ at f_1
compared to -180°

