

ECE3204 Lecture 22

Wien Bridge Oscillator Stability analysis (Ch. 10)

Handouts:
Wien Bridge with AGC
1-minute Quiz

$$\begin{aligned}
 B(s) &= \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + R + \frac{1}{sC}} \frac{sC(1+sRC)}{sC(1+sRC)} \\
 &= \frac{sRC}{sRC + sRC(1+sRC) + 1 + sRC} \\
 &= \frac{sRC}{sRC + sRC + s^2R^2C^2 + 1 + sRC}
 \end{aligned}$$

$$B(s) = \frac{sRC}{s^2R^2C^2 + 3sRC + 1}$$

Wien Bridge Oscillator

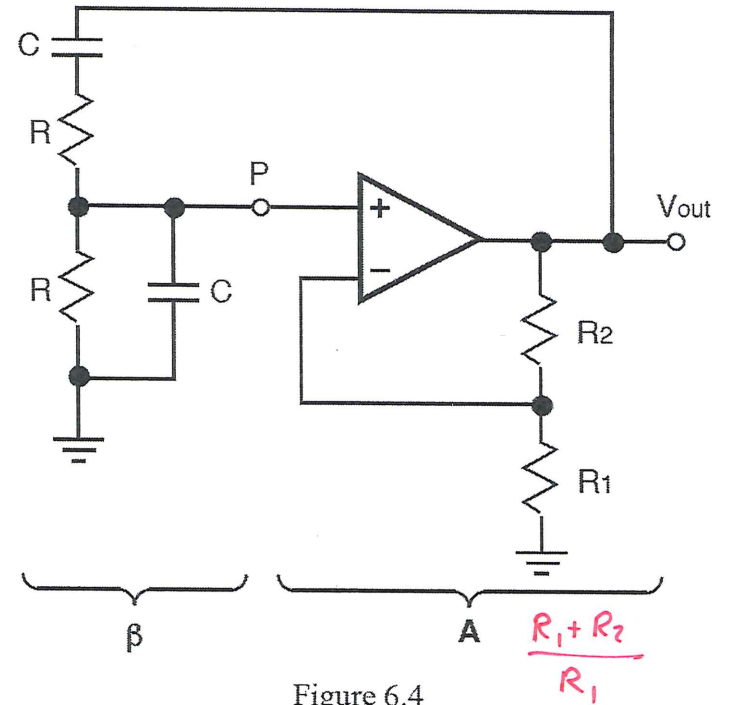


Figure 6.4

WHAT ω WILL HAVE
 0° PHASE SHIFT?
(PURELY REAL)
LET $s = j\omega$


$$\frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + 3j\omega RC}$$

PURELY REAL WHEN

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega = \frac{1}{RC} \quad \text{AT THIS } \omega$$

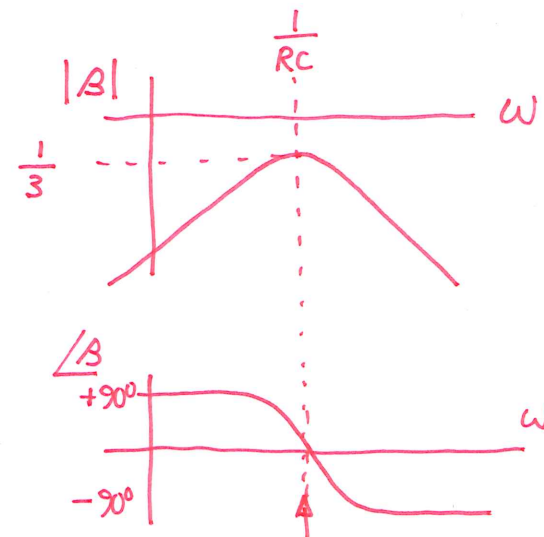
$$\begin{aligned}
 B &= \frac{j}{3j} \\
 &= \frac{1}{3}
 \end{aligned}$$



GAIN THROUGH β NETWORK
 $= \frac{1}{3}$ AT $\omega = \frac{1}{RC}$, $\angle = 0$

Intuitive View of Wien Bridge Oscillator

AB NETWORK

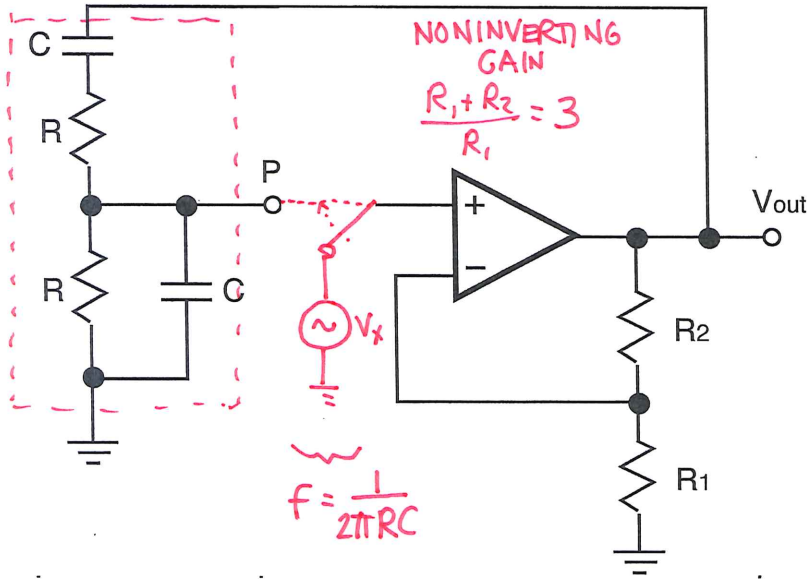


$$\frac{R_1 + R_2}{R_1}$$

1% LOW
2.97

3

1% HIGH
3.03

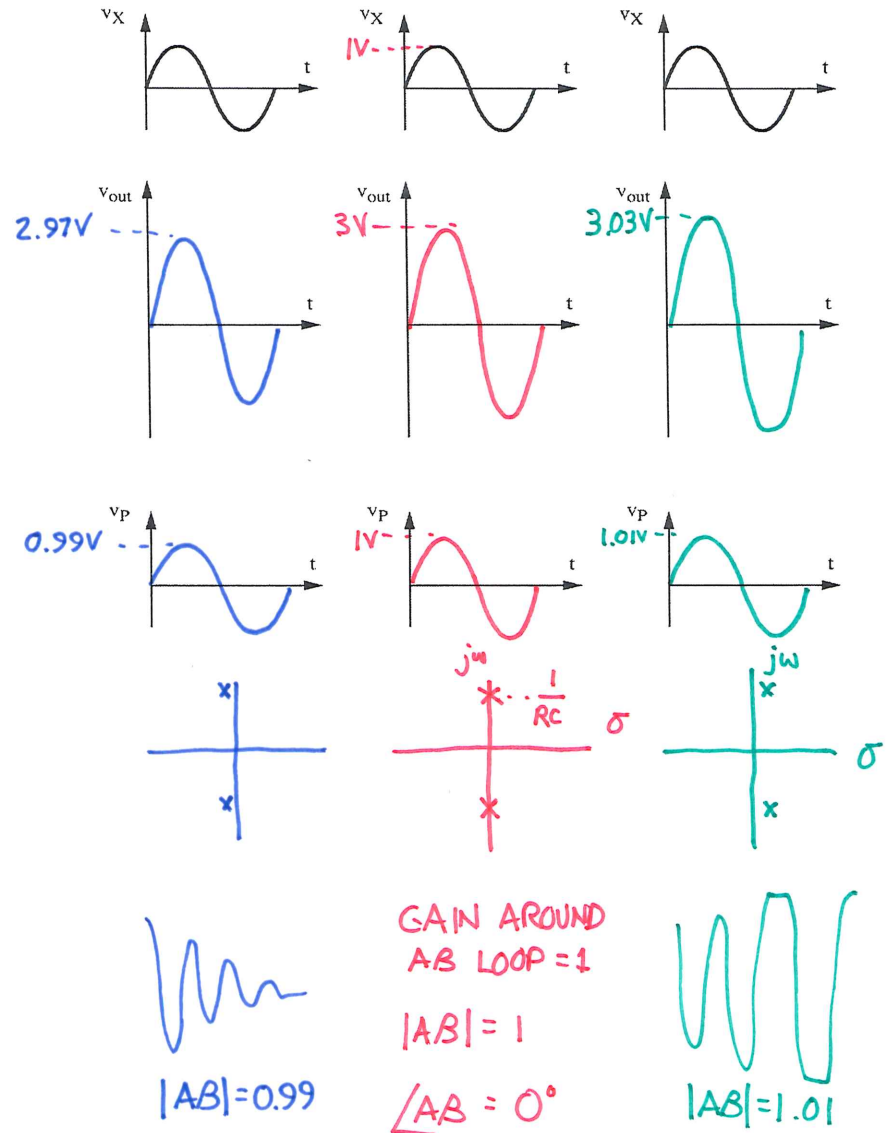


GAIN AROUND AB LOOP = 1

$$|AB| = 1$$

$$\angle AB = 0^\circ$$

"SELF CONSISTENT WAVEFORM"
SINUSOIDAL OSCILLATION

BNETWORK

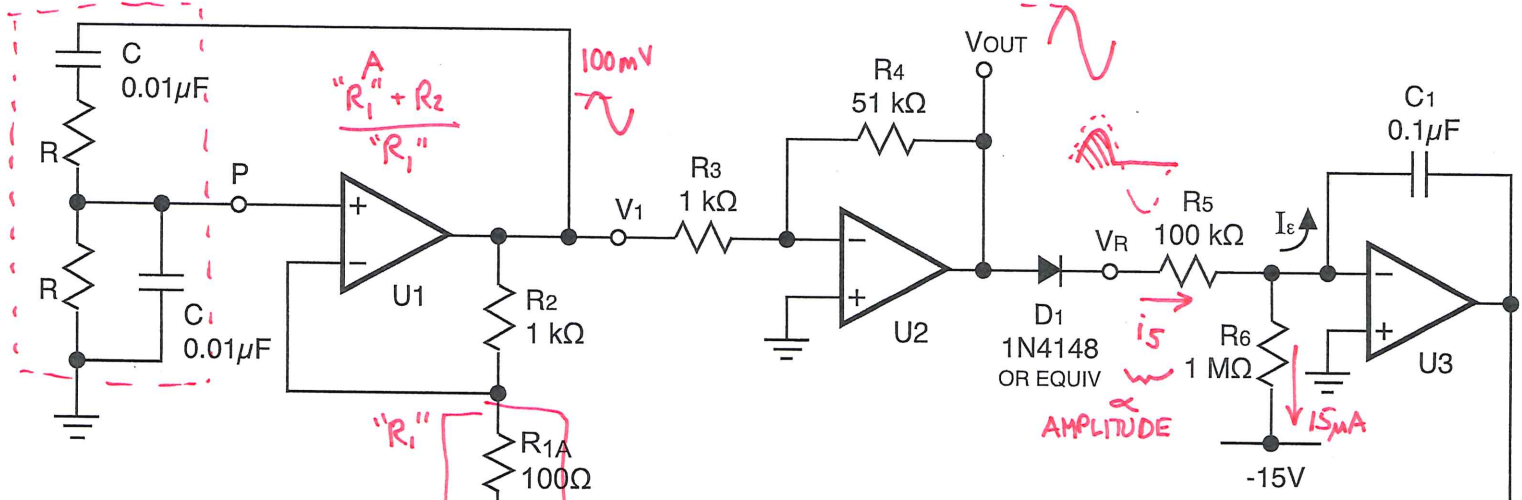

5V

100mV

AMPLITUDE $\propto i_s$

-15V

CONTROLS "A" GAIN



Figure 6.6