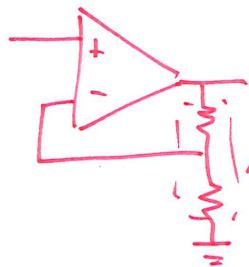


Dominant Pole Compensation

Revisit: Transimpedance amplifier (Lab 1)

Why does op-amp Open Loop Gain look like this?

UNCONDITIONALLY STABLE WITH RESISTIVE ( $\angle B = 0$ ) FEEDBACK





$B = 0.1$   
CLOSED LOOP GAIN = 10

RESISTIVE FEEDBACK  
(NO  $\phi$  SHIFT IN  $B$ )

CONDITION  $|AB| = 1$  FIND  $f_1$   
 $|A||B| = 1 \Rightarrow |A| = \left| \frac{1}{B} \right|$

PLOT  $\left| \frac{1}{B} \right|$   
ON SAME AXES AS  $|A|$

Open Loop Frequency Response

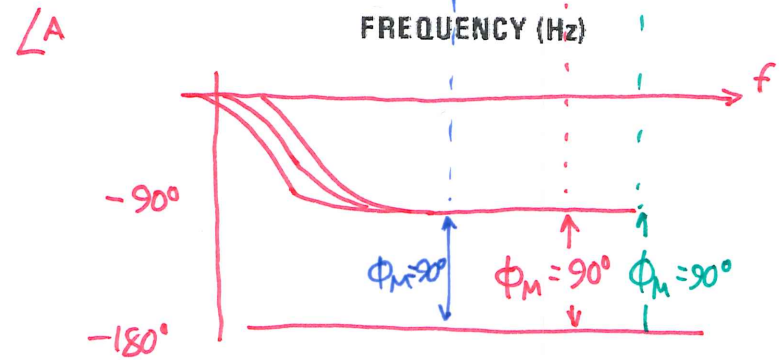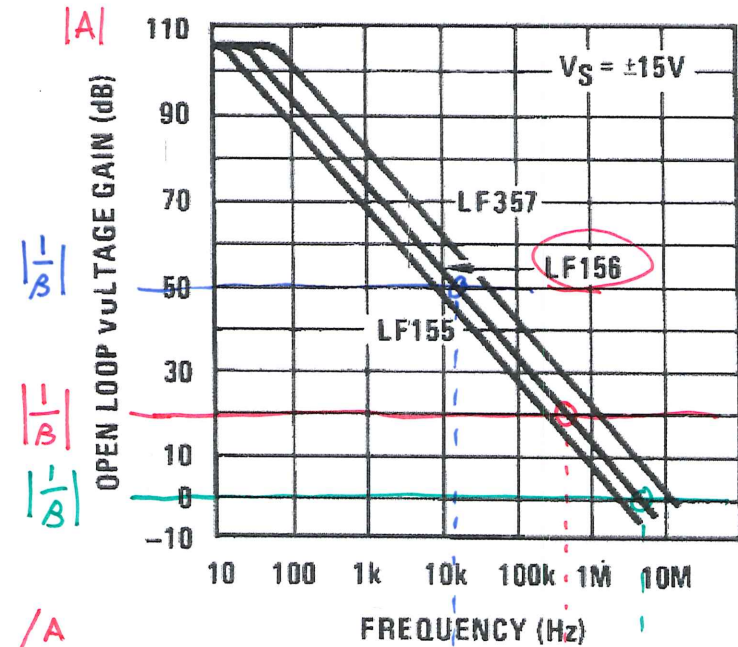

# One-Minute Quiz Op-Amp

$$A(s) = \frac{v_{out}}{v_{id}} = \frac{100,000}{\left(1 + \frac{s}{2\pi(10\text{kHz})}\right) \left(1 + \frac{s}{2\pi(3\text{MHz})}\right) \left(1 + \frac{s}{2\pi(100\text{MHz})}\right)}$$

"DOMINANT POLE" COMPENSATION

ANALYSIS: GIVEN A, B, FIND  $\phi_M$

OP-AMP DESIGN (ECE4902)

CHOOSE  $\phi_M$  WE WANT

DESIGN FOR A TRANSFER FUNCTION

WANT  $60^\circ$   $\phi_M$  (STABLE) WITH  
UNITY GAIN FEEDBACK


FIND  $-120^\circ$  LAG ( $\phi_M = 60^\circ$ ) ON  $\angle A$   
THIS WOULD BE  $f_1$  IF A WAS  
WHAT WE WANTED

THAT FREQUENCY SHOULD BE OUR  $f_1$   
WORK BACK TO DC GAIN




WITH 20 dB/DECADE SLOPE

NEED TO MOVE 100kHz POLE TO 10 Hz

HOW: SEE ECE4902

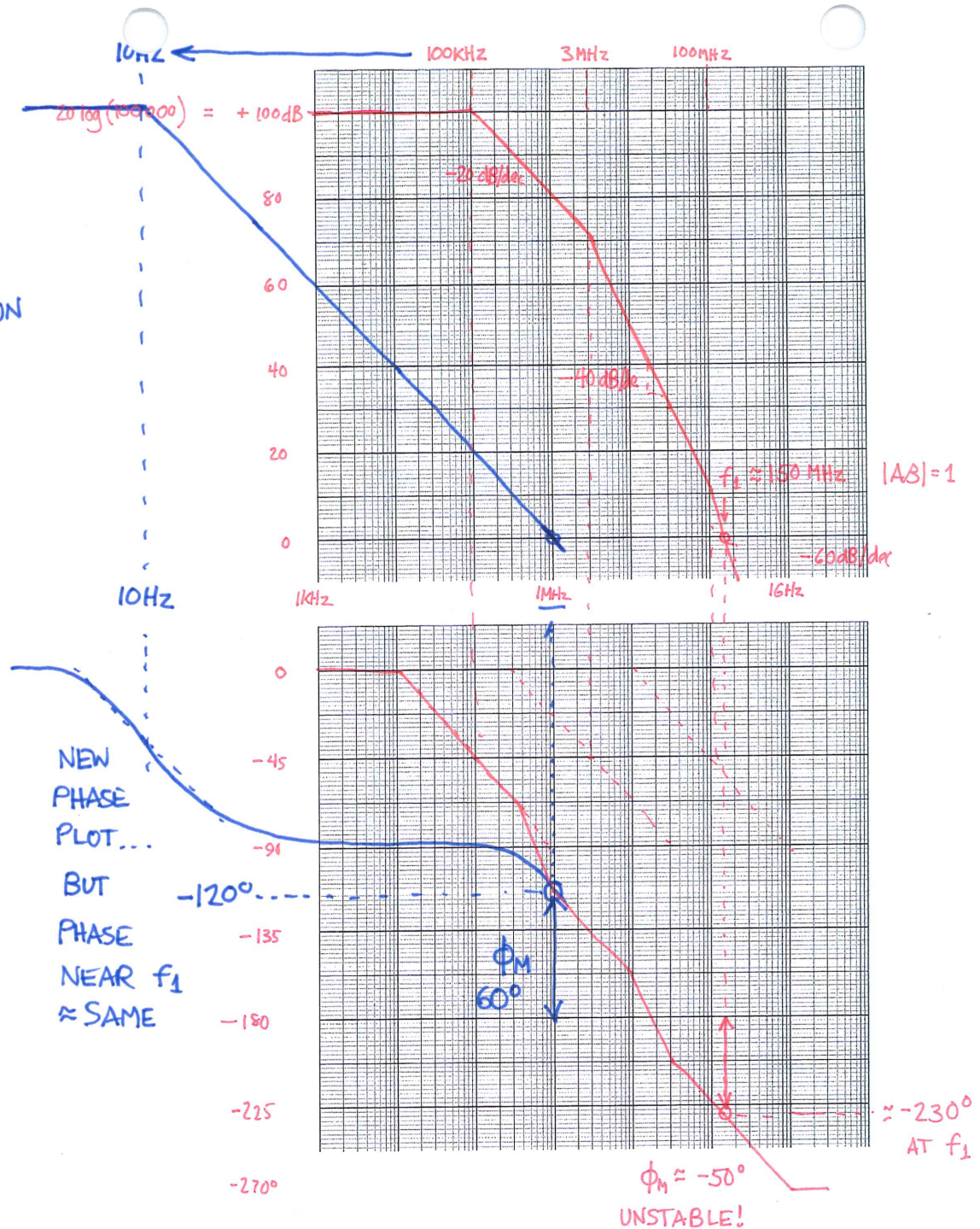

# Transimpedance Amplifier (Lab 1)

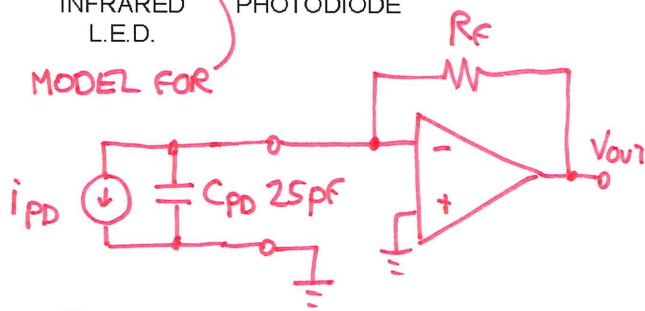
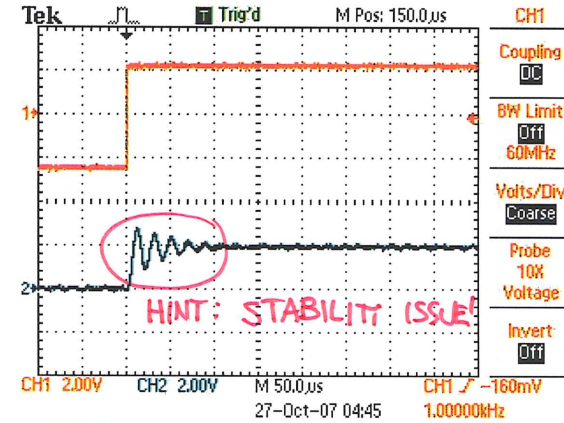
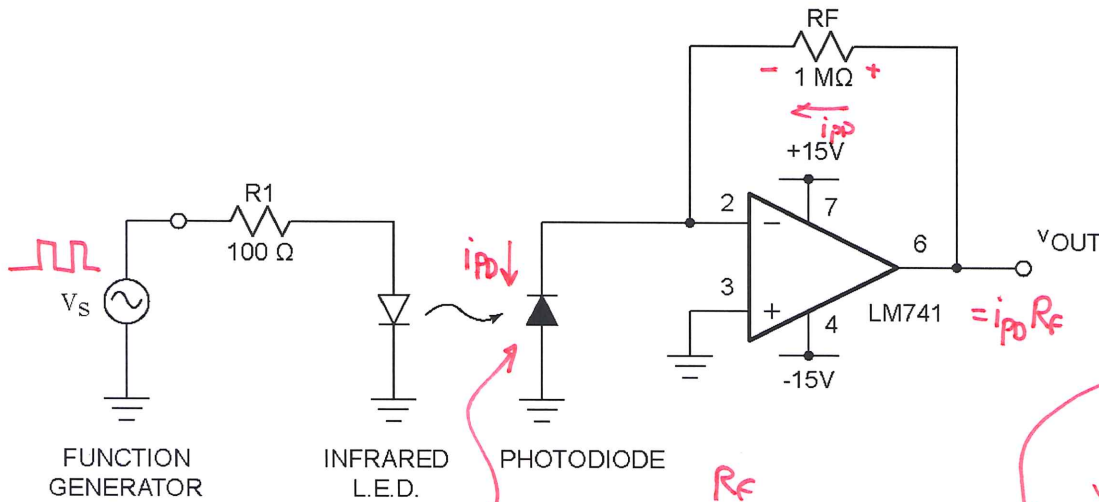


TURN OFF  $i_{pd} \Rightarrow$   
OPEN CIRCUIT


REDRAW TO SHOW  $\beta$

$$\beta = \frac{\frac{1}{sC_{PD}}}{R_F + \frac{1}{sC_{PD}}} = \frac{1}{sR_F C_{PD} + 1}$$

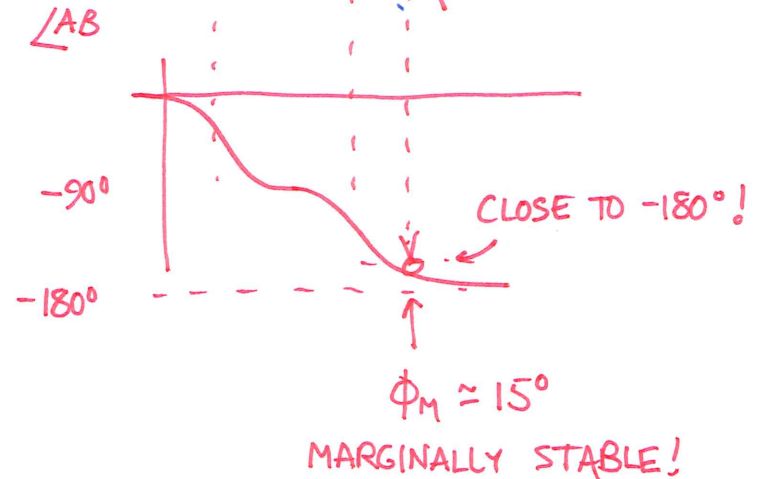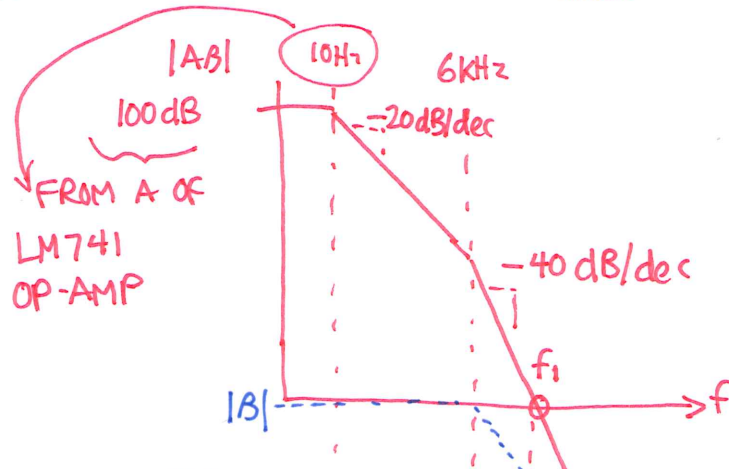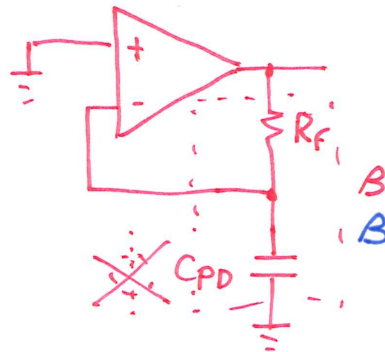
$$f_P = \frac{1}{2\pi(1M\Omega)(25pF)} = 6KHz$$


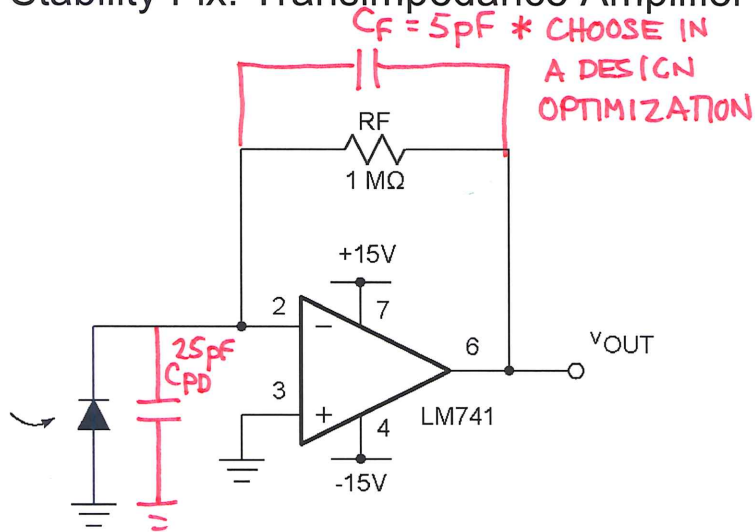
# Stability Fix: Transimpedance Amplifier



ANALYSIS FOR  $\beta$

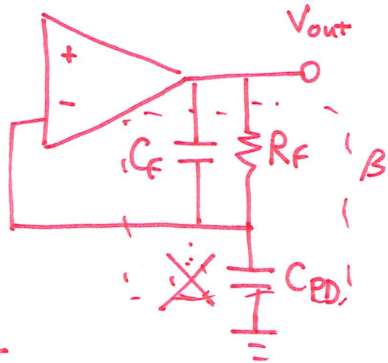

$$\beta = \frac{1}{sC_{PD}} \cdot \frac{1}{\frac{1}{1 + sR_f C_f} + R_f}$$

$$= \frac{1 + sR_f C_f}{1 + sR_f C_f + sR_f C_{PD}} = \frac{1 + sR_f C_f}{1 + sR_f (C_f + C_{PD})}$$

} ZERO 30KHZ  
 } POLE 5KHZ

