

A/D Converters

Exam 3 Preview

Tomorrow:

Exam 3

Hand in all late HW/Lab

TEST TOMORROW

EMPHASIS

FILTER CONCEPT

S-PLANE

SPECIFY  $T(s)$

MAP OF WAVEFORMS

STABILITY

S-PLANE

LOOP GAIN


PHASE MARGIN

INSTABILITY FROM  $\beta$

PLUS A LITTLE:


S/H

D/A

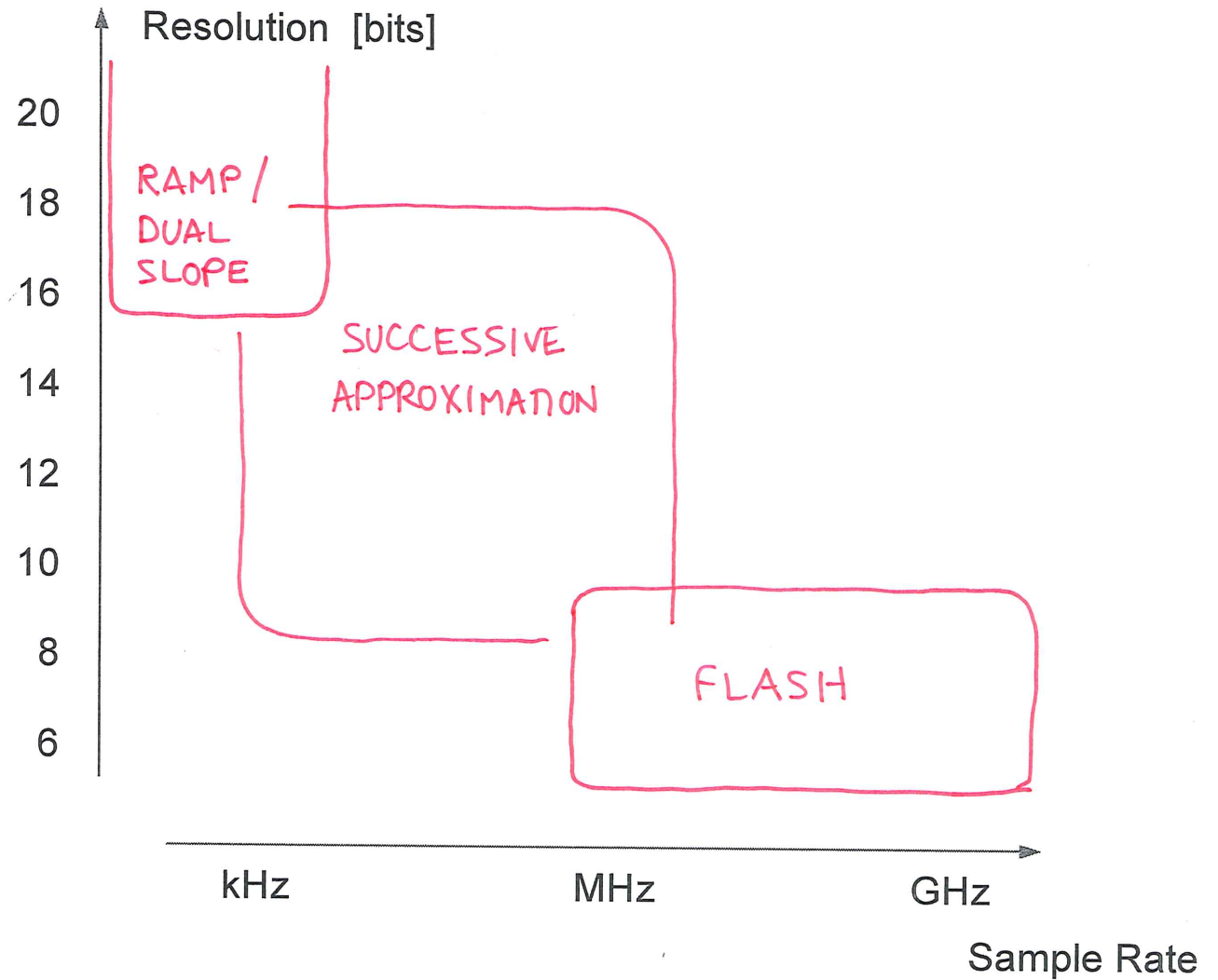
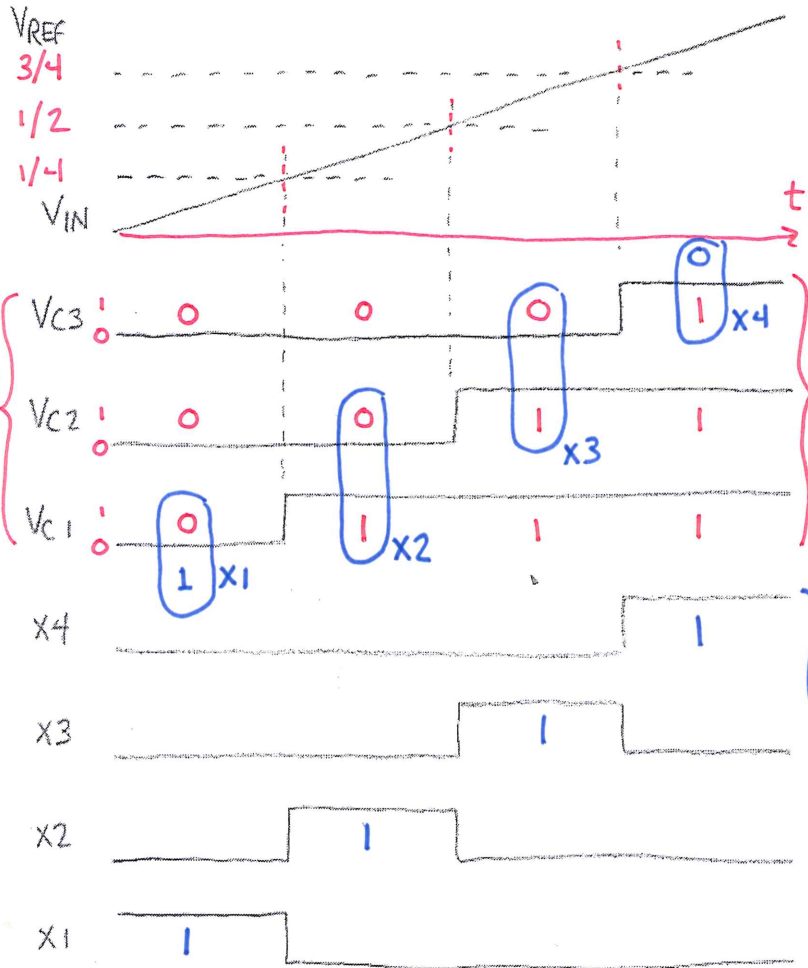
# Flash ADC


✓ FAST 100s MHz → GHz  
 X COMPLEXITY  $2^N - 1$  COMPS  
 4-8 BITS



"THERMOMETER CODE"

ONLY ONE ACTIVE ⇒

## "REFERENCE LADDER"

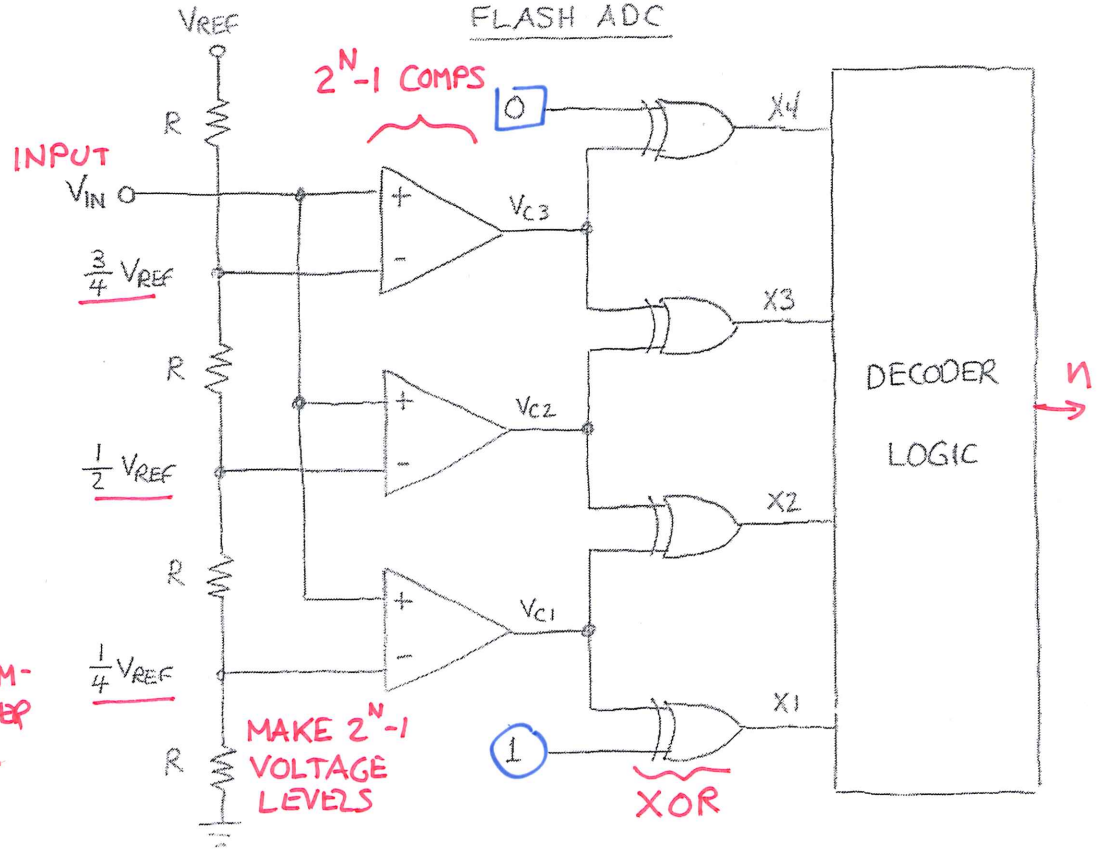

MAKE  $2^N - 1$  VOLTAGE LEVELS



XOR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

INPUTS DIFFERENT

11  
 10  
 01  
 00  
 N OUTPUT

# Ramp ADC

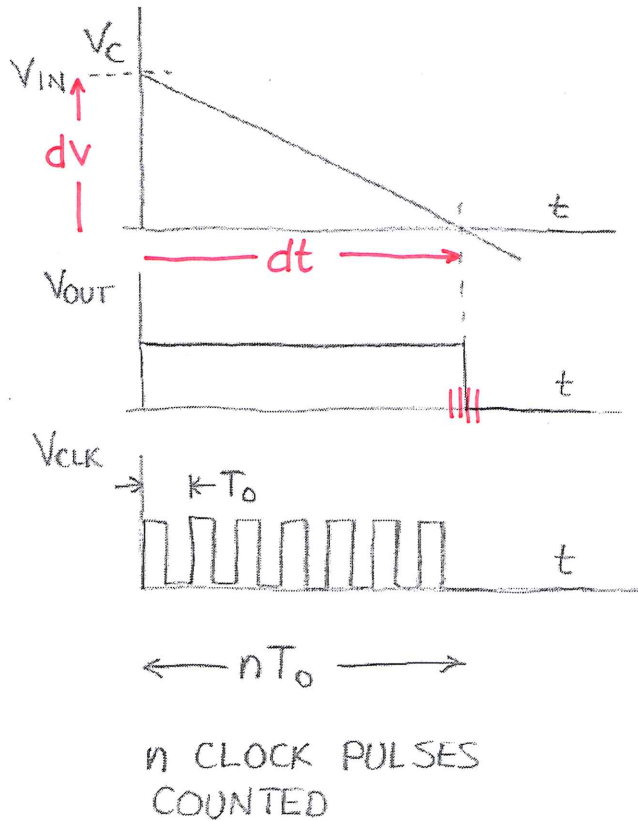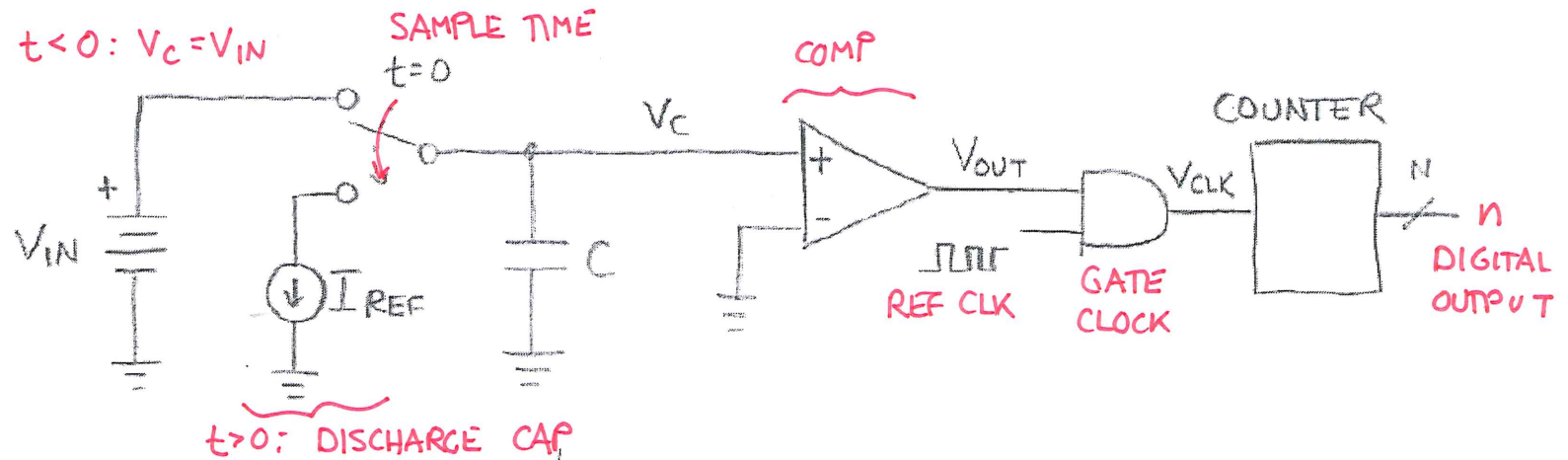

FOR CAPACITOR

$$\frac{I}{C} = \frac{dV}{dt}$$

$$\frac{I_{REF}}{C} = \frac{V_{IN}}{nT_0}$$

$$n = V_{IN} \left[ \frac{C}{I_{REF} T_0} \right]$$

STABLE
STABLE
KNOWN



✓ GOOD:  $n \propto V_{IN}$

BAD: PROPORTIONALITY FACTOR DEPENDS ON  $I_{REF}, T_0, C$
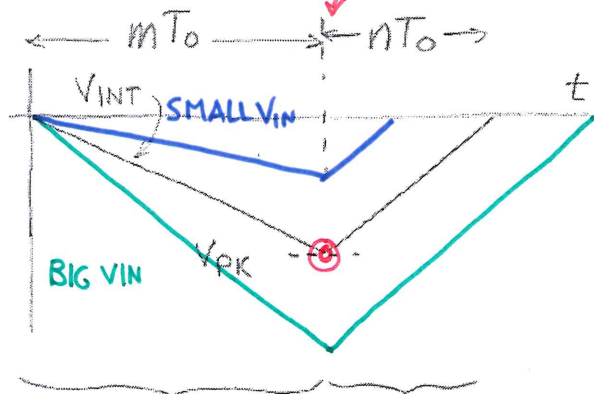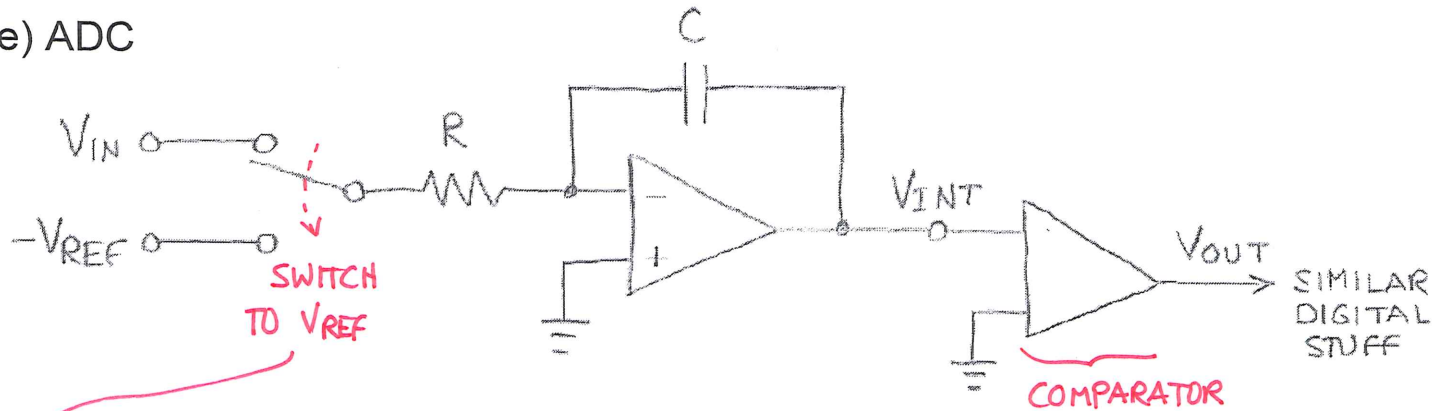
# Integrating (Dual-Slope) ADC

- ✓ SIMPLE
- ✓ SCALABLE
- ✗ SLOW

INTEGRATE  $V_{IN}$   
FOR FIXED TIME  $mT_0$



INTEGRATE  $V_{IN}$  FOR  $mT_0$   
 $m = 2^N$   
N-BIT ADC

INTEGRATE  $-V_{REF}$  UNTIL  $V_{INT} = 0$   
AFTER TIME  $nT_0$

$$V_{INT} = \frac{-1}{RC} \int_{t_0}^t V_{IN} dt + V_{INT}(t_0)$$

FOR INTEGRATOR

$$V_{PK} = -RC V_{IN} \underbrace{mT_0}_{\text{FIXED}}$$

⊙ INITIAL CONDITION FOR 2nd INTEGRATION

ALSO

$$-V_{PK} = -RC(-V_{REF}) \underbrace{nT_0}_{\text{FIXED}}$$

GET BACK TO ZERO: DEPENDS ON  $V_{PK}$

SOLVE FOR  $n$


$$\cancel{-RC V_{IN} mT_0} = \cancel{-RC V_{REF} nT_0}$$

$$n = V_{IN} \left[ \frac{m}{V_{REF}} \right] \text{ FIXED}$$


ONLY 1  
THING NEEDS  
TO BE STABLE!

NICE: NOW  
PROPORTIONALITY FACTOR  
DEPENDS ONLY ON  $V_{REF}$   
VALUES OF  $R, C, T_0$   
UNIMPORTANT (AS LONG AS  
THEY ARE STABLE DURING  
THE CONVERSION TIME)

# Counter (Feedback) ADC

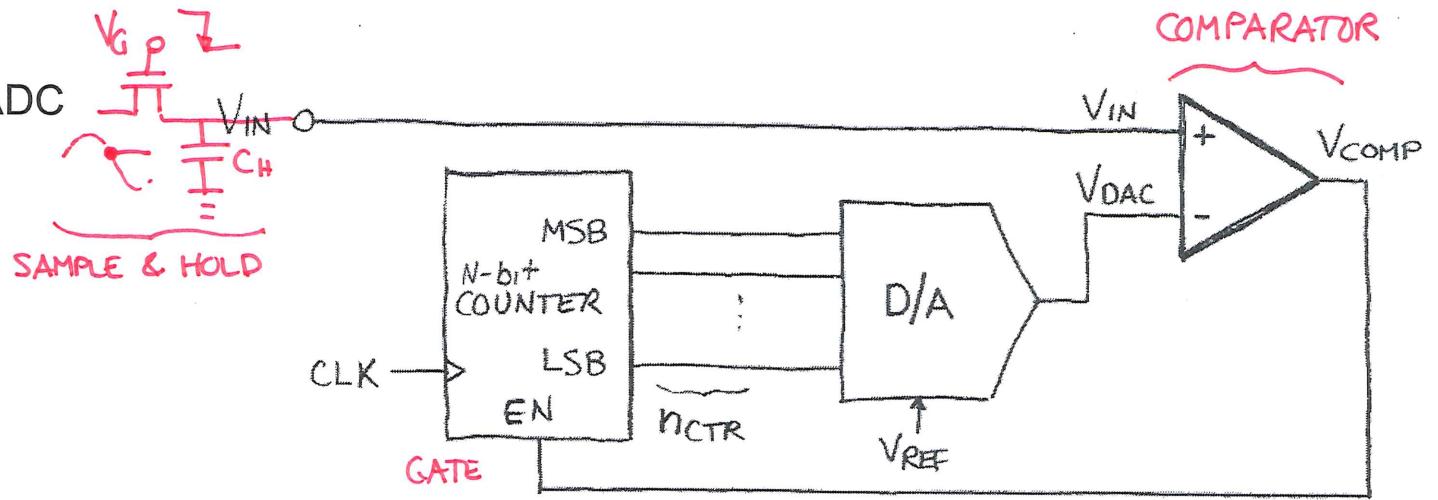


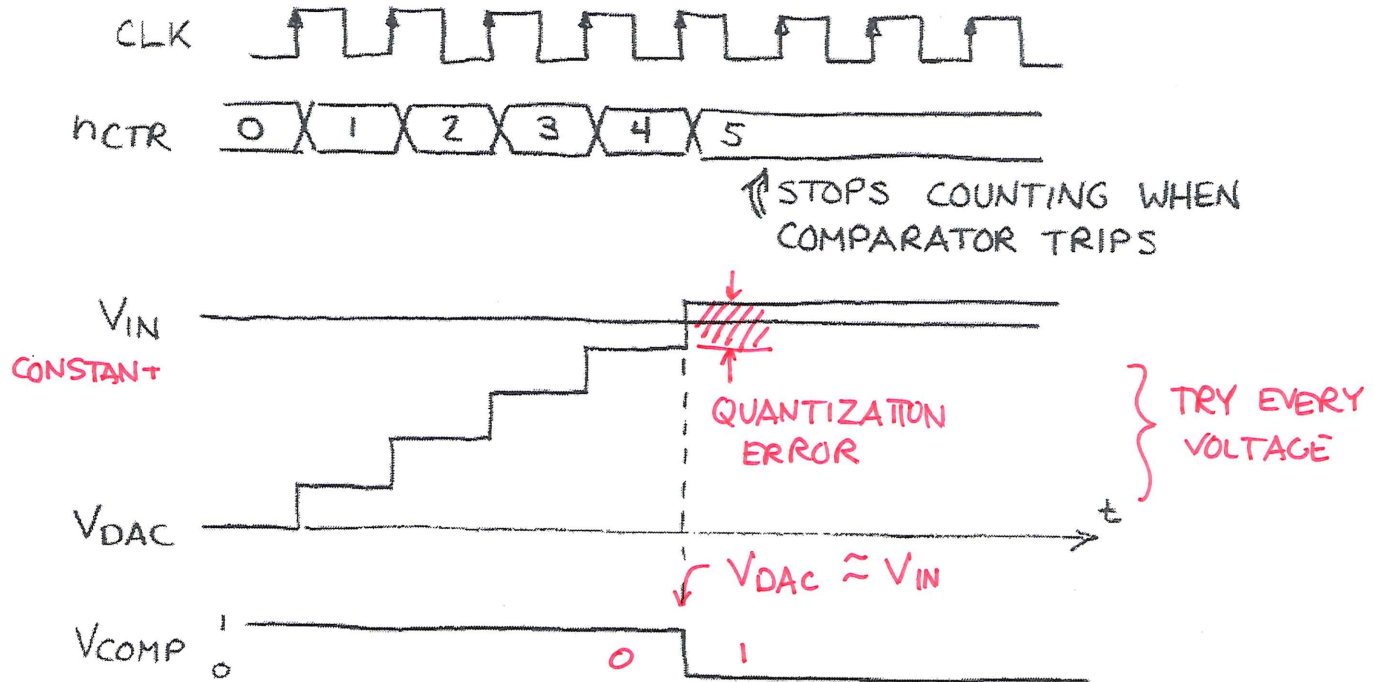X TAKES TOO LONG!  
 N-BIT ADC  
 $2^N$  COMPARISONS




# Successive Approximation ADC

✓ SPEED: N COMPARISONS  
NEED N BIT D/A

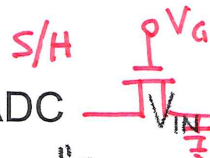

"SUCCESSIVE APPROXIMATION REGISTER"

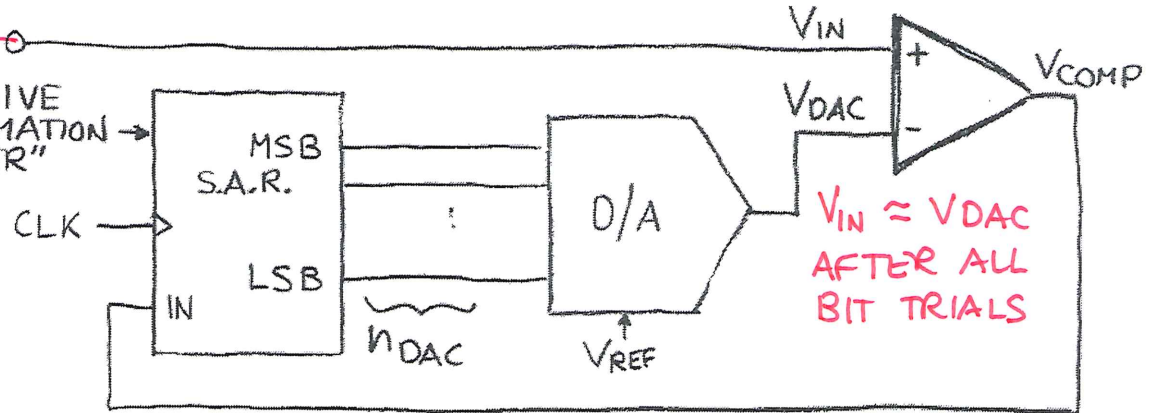

## BINARY SEARCH OF POSSIBLE D/A VALUES

TRY MIDSCALE

