


A/D Converters

Exam 3 Preview



**Tomorrow:**

Exam 3



Hand in all late HW/Lab

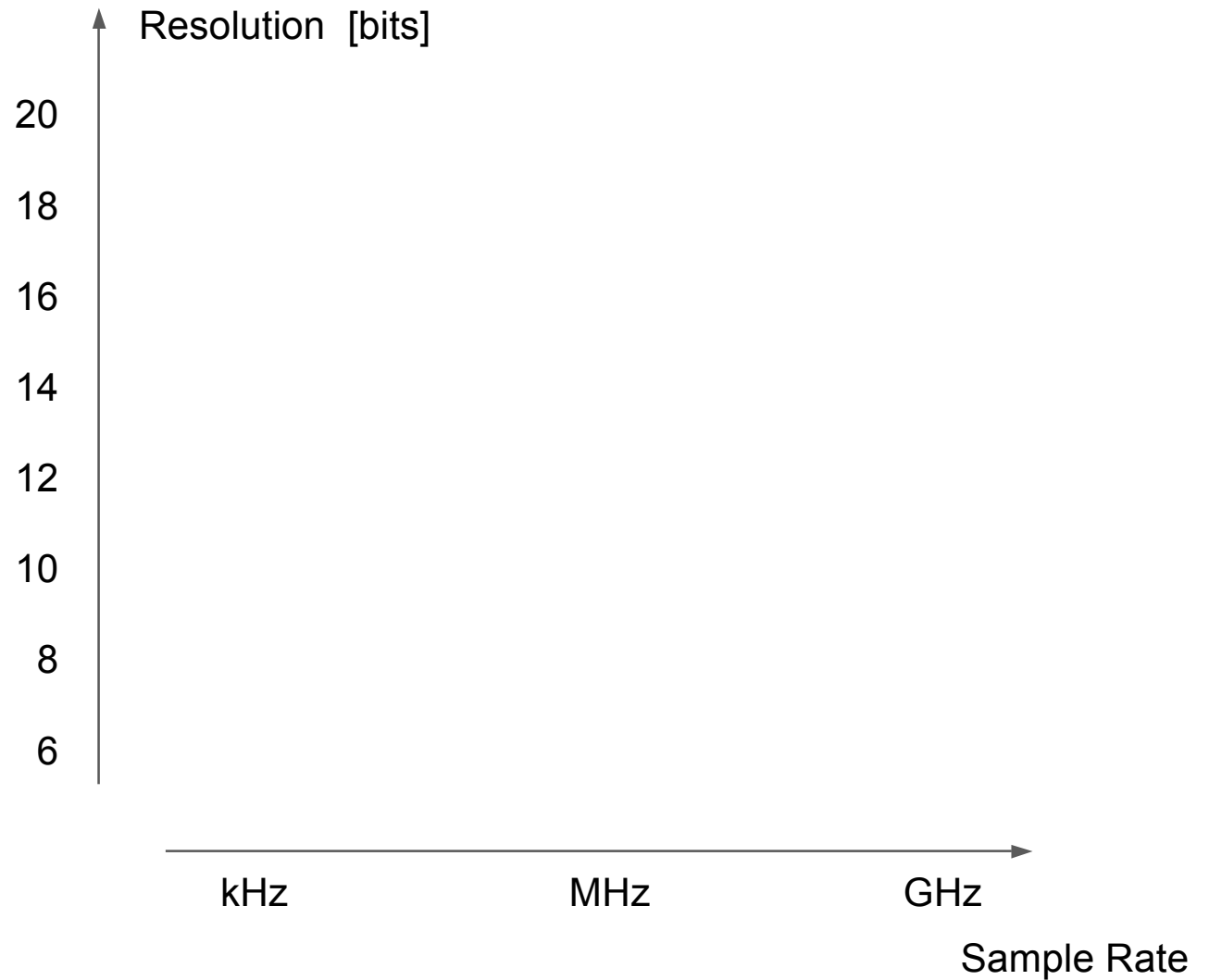

# Flash ADC

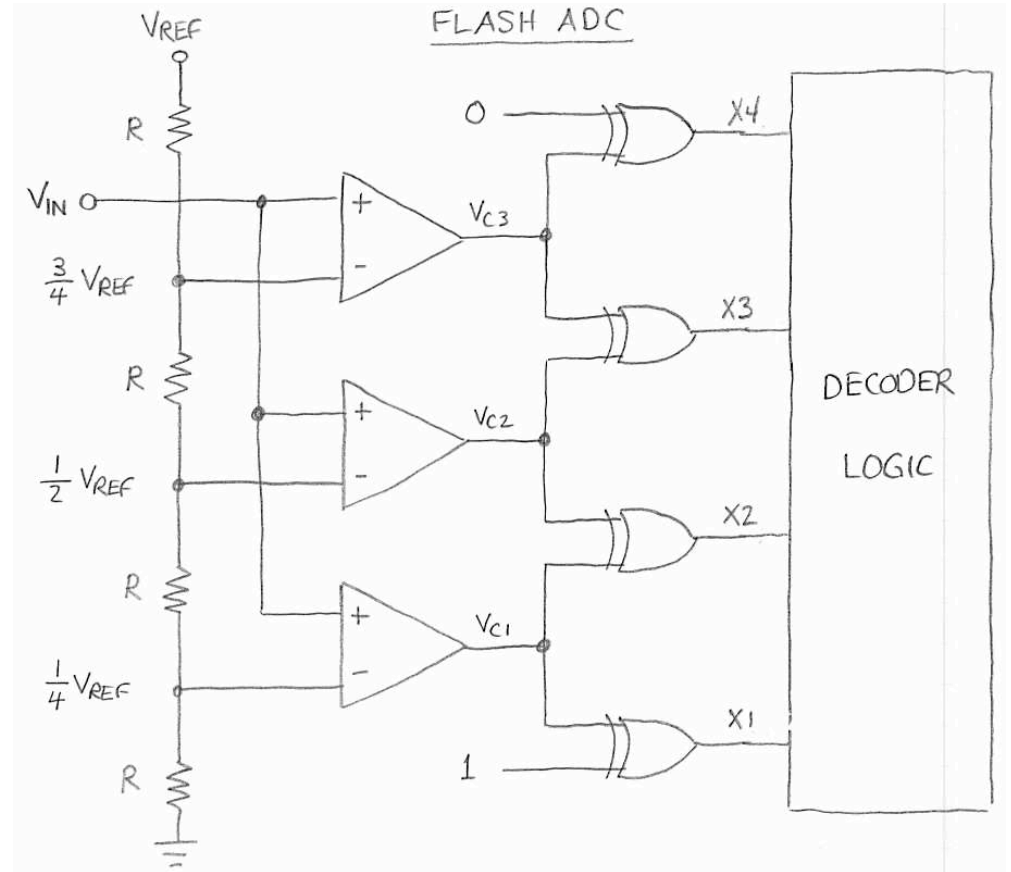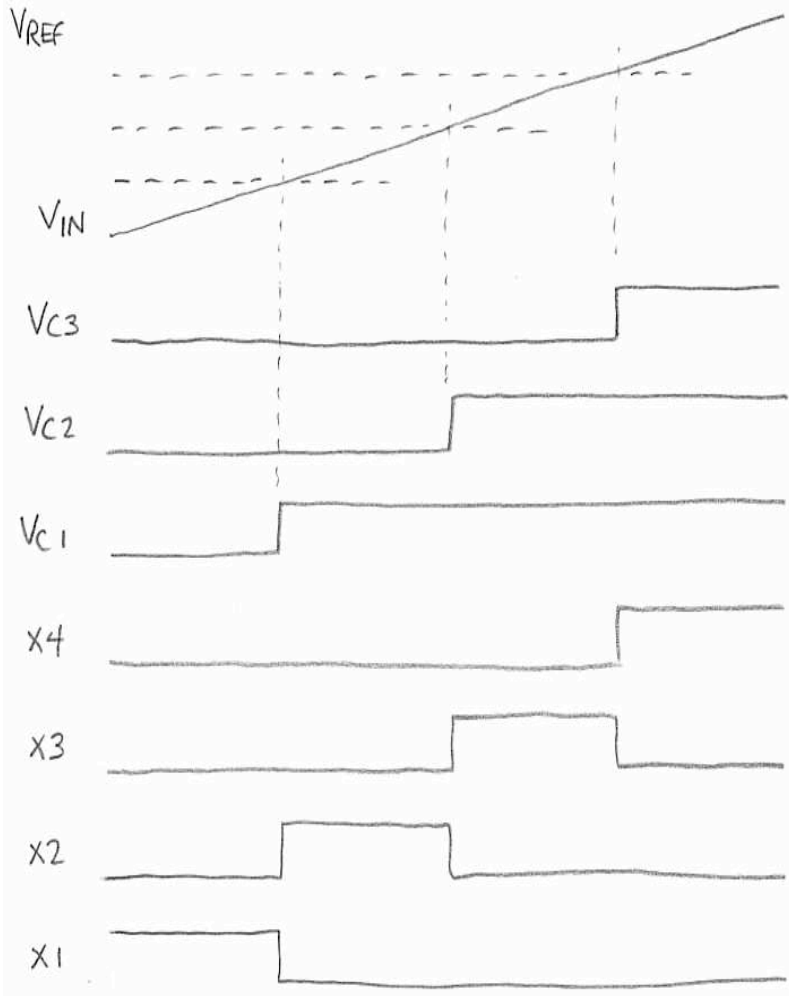

# Ramp ADC

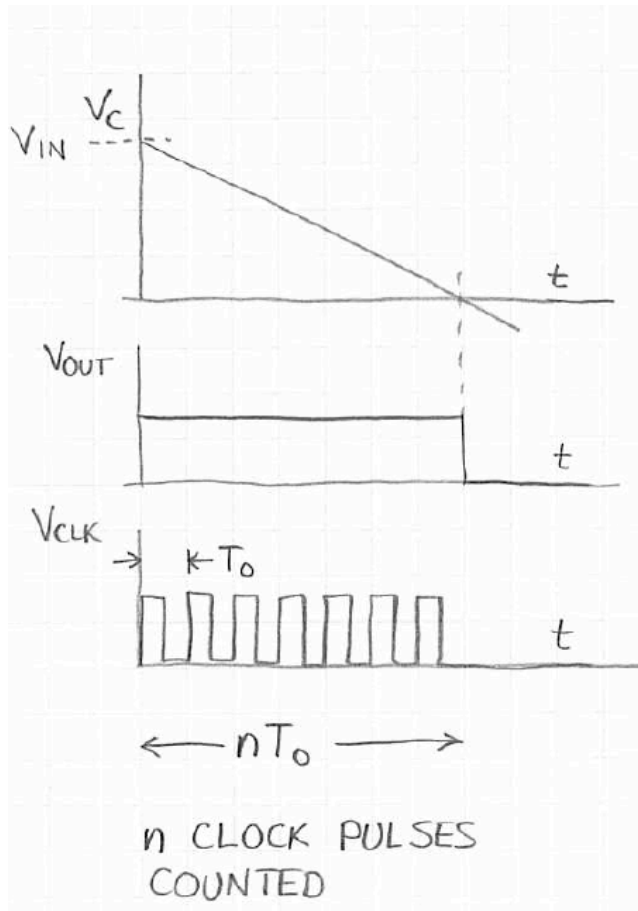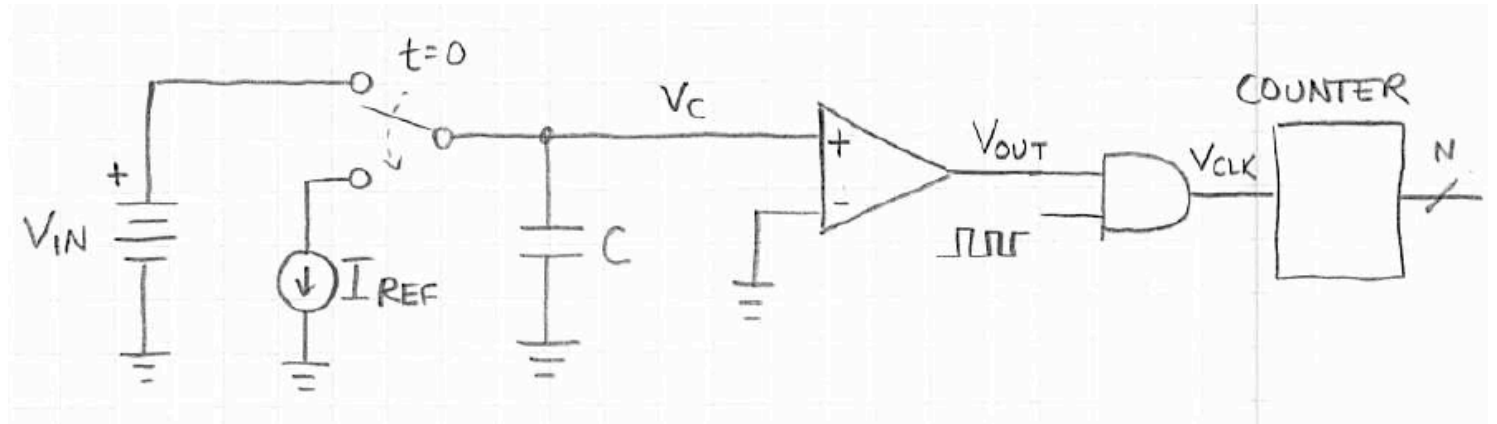

FOR CAPACITOR

$$\frac{I}{C} = \frac{dV}{dt}$$



$$\frac{I_{REF}}{C} = \frac{V_{IN}}{nT_0}$$

$$n = V_{IN} \left[ \frac{C}{I_{REF} T_0} \right]$$

GOOD:  $n \propto V_{IN}$

BAD: PROPORTIONALITY  
FACTOR DEPENDS  
ON  $I_{REF}$ ,  $T_0$ ,  $C$

# Integrating (Dual-Slope) ADC

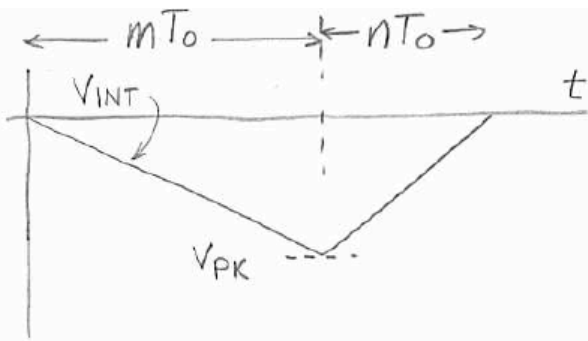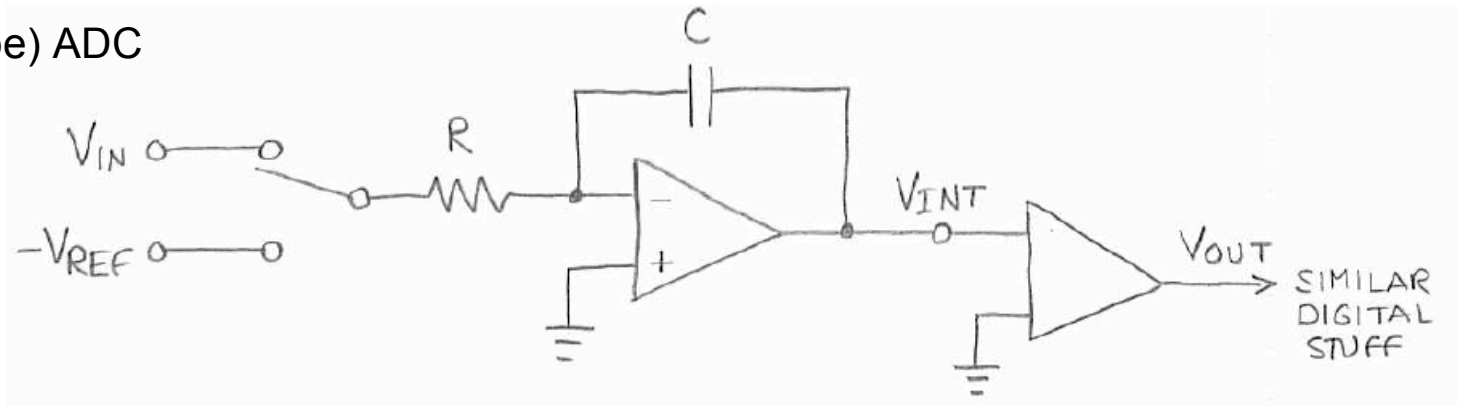

INTEGRATE  $V_{IN}$  FOR  $mT_0$   
 $m = 2^N$   
 N-BIT ADC

INTEGRATE  $-V_{REF}$  UNTIL  $V_{INT} = 0$  AFTER TIME  $nT_0$

FOR INTEGRATOR

$$V_{PK} = -RC V_{IN} m T_0$$

ALSO

$$-V_{PK} = -RC(-V_{REF})n T_0$$



SOLVE FOR  $n$

$$-RC V_{IN} m T_0 = -RC V_{REF} n T_0$$

$$n = V_{IN} \left[ \frac{m}{V_{REF}} \right]$$

NICE: NOW PROPORTIONALITY FACTOR DEPENDS ONLY ON  $V_{REF}$  VALUES OF  $R, C, T_0$  UNIMPORTANT (AS LONG AS THEY ARE STABLE DURING THE CONVERSION TIME)

# Counter (Feedback) ADC

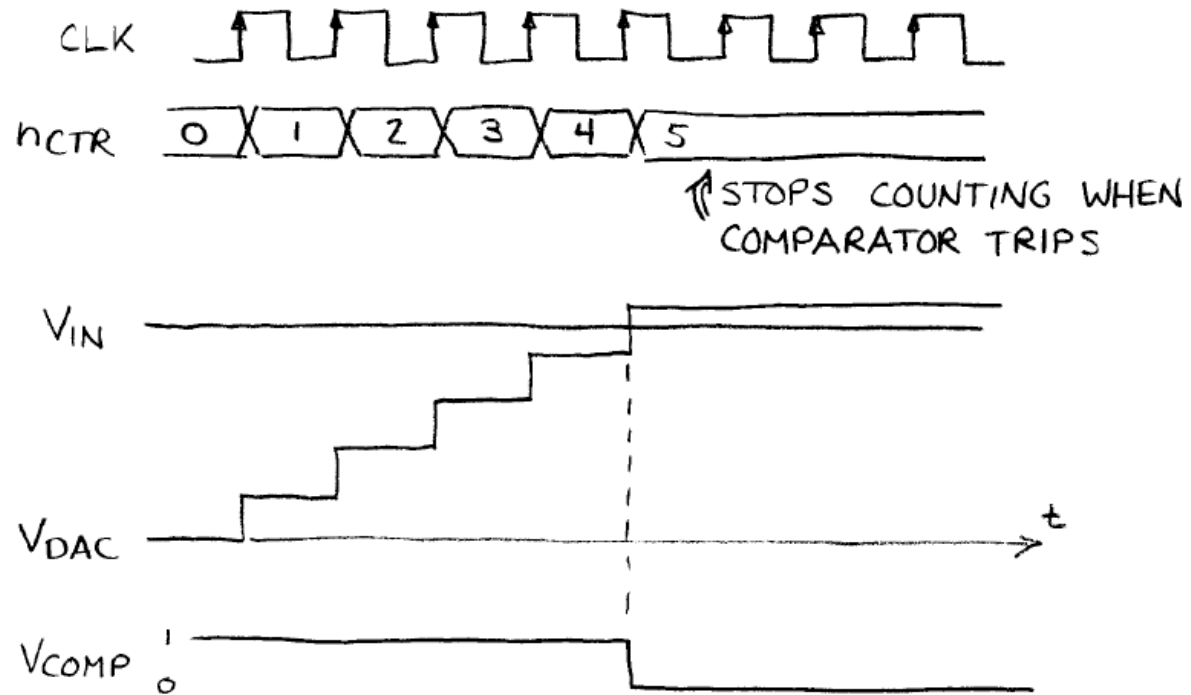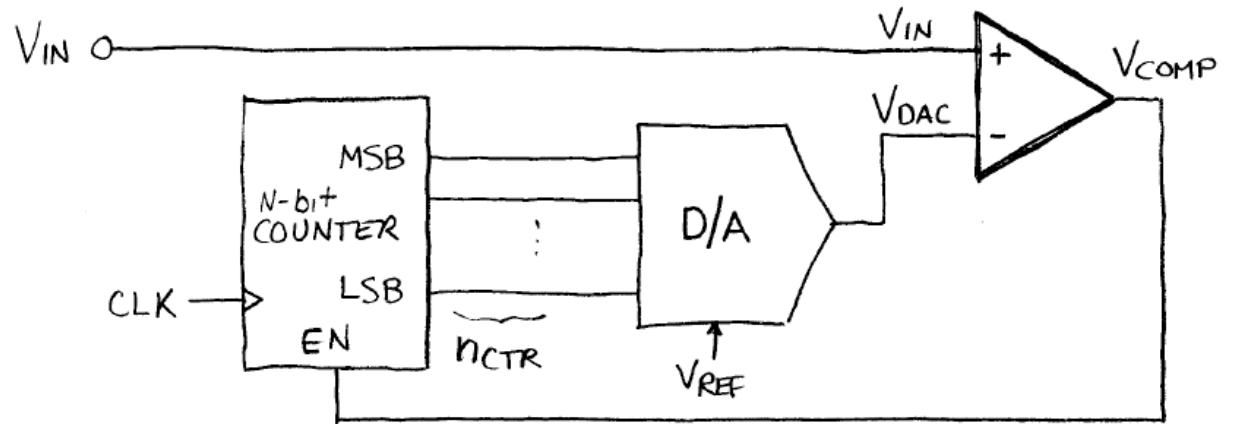

# Successive Approximation ADC

