
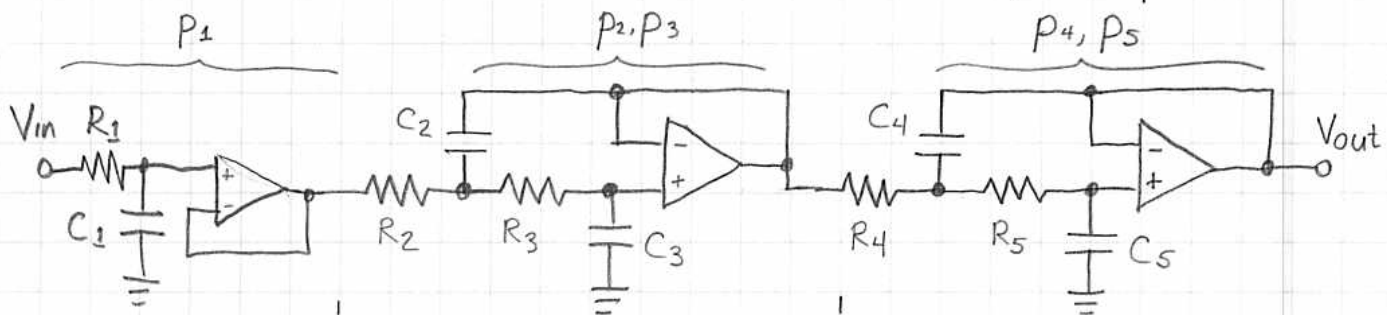


Example: DESIGN OF A 5th ORDER BUTTERWORTH LOWPASS FILTER USING SALLÉN AND KEY CIRCUITS

Nth order Butterworth has N poles in the left half plane, on a semicircle of radius ω_0 , equally spaced $180^\circ/N$ apart. For $N=5$:

Pole p_1 can be realized with a simple RC circuit. Pole pairs p_2/p_3 and p_4/p_5 can each be realized with Sallen and Key circuits

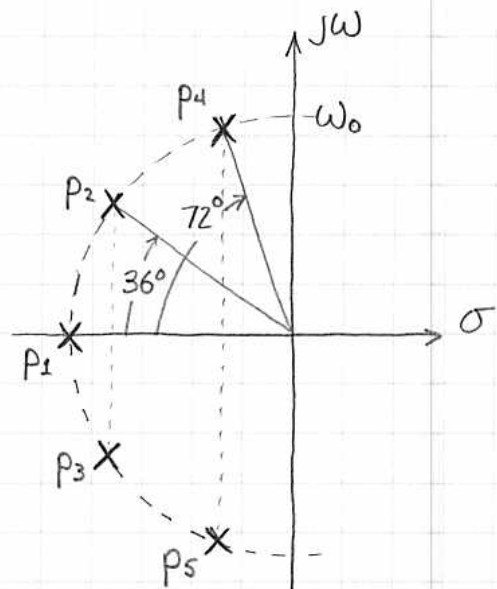Filter topology, for $f_{3dB} = 1\text{kHz}$
 $\omega_0 = 2\pi(1\text{kHz})$



$$\frac{1}{2\pi R_1 C_1} = 1\text{kHz}$$

$$R_1 = 16\text{ k}\Omega$$

$$C_1 = 0.01\mu\text{F}$$

$$\omega_0 = 995\text{ Hz}$$

$$\tan(36^\circ) = \sqrt{\frac{C_2}{C_3} - 1} = 0.7265$$

$$\frac{C_2}{C_3} = 1.528$$

$$\left. \begin{array}{l} C_2 = 0.015\mu\text{F} \\ C_3 = 0.01\mu\text{F} \end{array} \right\} \theta = 35.3^\circ$$

$$2\pi(1\text{kHz}) = \frac{1}{R\sqrt{(0.015\mu\text{F})(0.01\mu\text{F})}}$$

$$R = 12.99\text{ k}\Omega \approx 13\text{ k}\Omega$$

$$R_2 = R_3 = 13.0\text{ k}\Omega$$

$$\omega_0 = 999\text{ Hz}$$

$$\tan(72^\circ) = \sqrt{\frac{C_4}{C_5} - 1} = 3.078$$

$$\frac{C_4}{C_5} = 10.47$$

$$\left. \begin{array}{l} C_4 = 0.1\mu\text{F} \\ C_5 = 0.01\mu\text{F} \end{array} \right\} \theta = 71.6^\circ$$

$$2\pi(1\text{kHz}) = \frac{1}{R\sqrt{(0.1\mu\text{F})(0.01\mu\text{F})}}$$

$$R = 5.033\text{ k}\Omega \approx 5.1\text{ k}\Omega$$

$$R_4 = R_5 = 5.1\text{ k}\Omega$$

$$\omega_0 = 987\text{ Hz}$$