
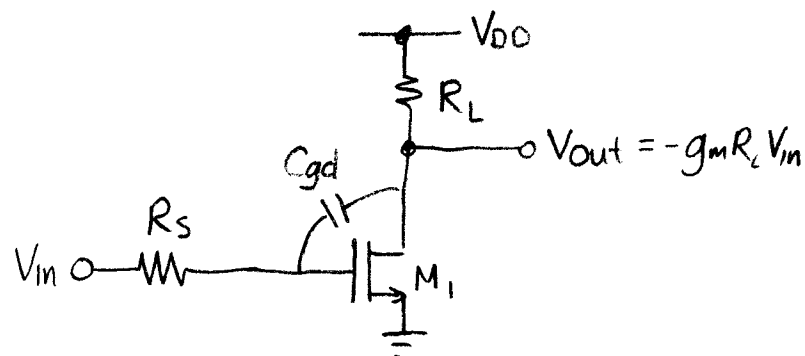



COMMON SOURCE AMPLIFIER

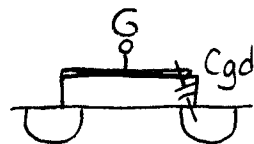

C_{gd} : GATE-DRAIN
PARASITIC CAP



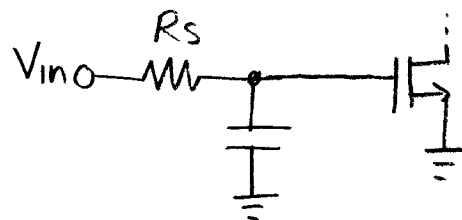ACROSS INVERTING GAIN:
MULTIPLIED BY MILLER EFFECT




$$C_M = (1 + g_m R_L) C_{gd}$$

$$f_{3dB} \leq \frac{1}{2\pi R_S C_M}$$

↓ ← ↑
LOWERS f_{3dB} !

WITH CASCODE

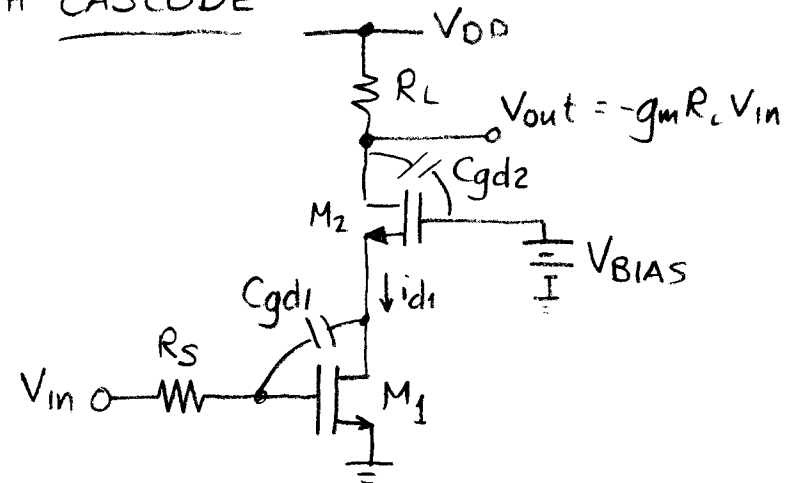

M2 (CASCODE MOSFET) "PASSES"
 i_{d1} TO V_{out} ; SAME GAIN

BUT: NEITHER C_{gd} SEES LARGE
INVERTING GAIN!
 C_{gd1} SEES GAIN OF -1; NO GAIN FOR C_{gd2}

NOW TWO POLES $\frac{1}{2\pi R_S (2C_{gd1})}$, $\frac{1}{2\pi R_L C_{gd2}}$

f_{3dB} MAY BE HIGHER, OR SIMILAR;

R_L MAY INCREASE FROM CASCODE

f_T WILL BE MUCH HIGHER