

Review: Analysis Techniques

- **Nodal Analysis**
- **KVL, KCL**
- **Thevenin's Theorem**

Keys:

- **FIRST** know what you're looking for
- **THEN** write simplest equations to get you there


Nodal Analysis

- **Voltage always relative (defined as a difference)**
- **Nomenclature / Conventions**
 - V_A **voltage at node A referenced to ground**
 - $V_{BC} = V_B - V_C$ **voltage drop from B to C**


KVL: Kirchhoff's Voltage Law

- **Sum of voltage drops around a loop = 0**
- **Voltage drop equations depend on element:**
 - **Ohm's law (R, L, C)**
 - **Value of voltage sources**
 - **Caution: ideal current source can have any voltage**
 - **Nonlinear model equations (diode, MOSFET, etc.)**

KVL Analogy: What goes up must come down

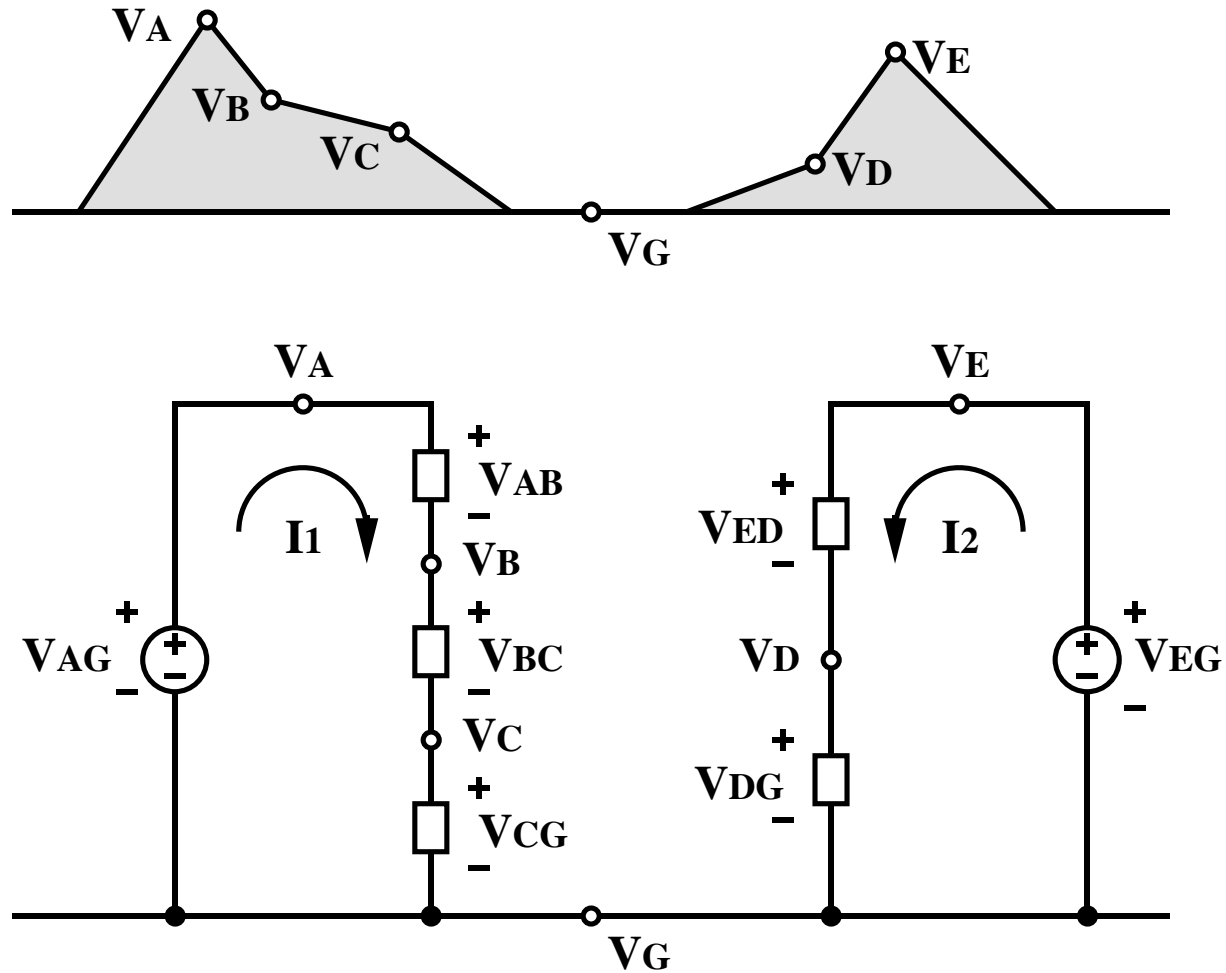


Formal KVL Loop

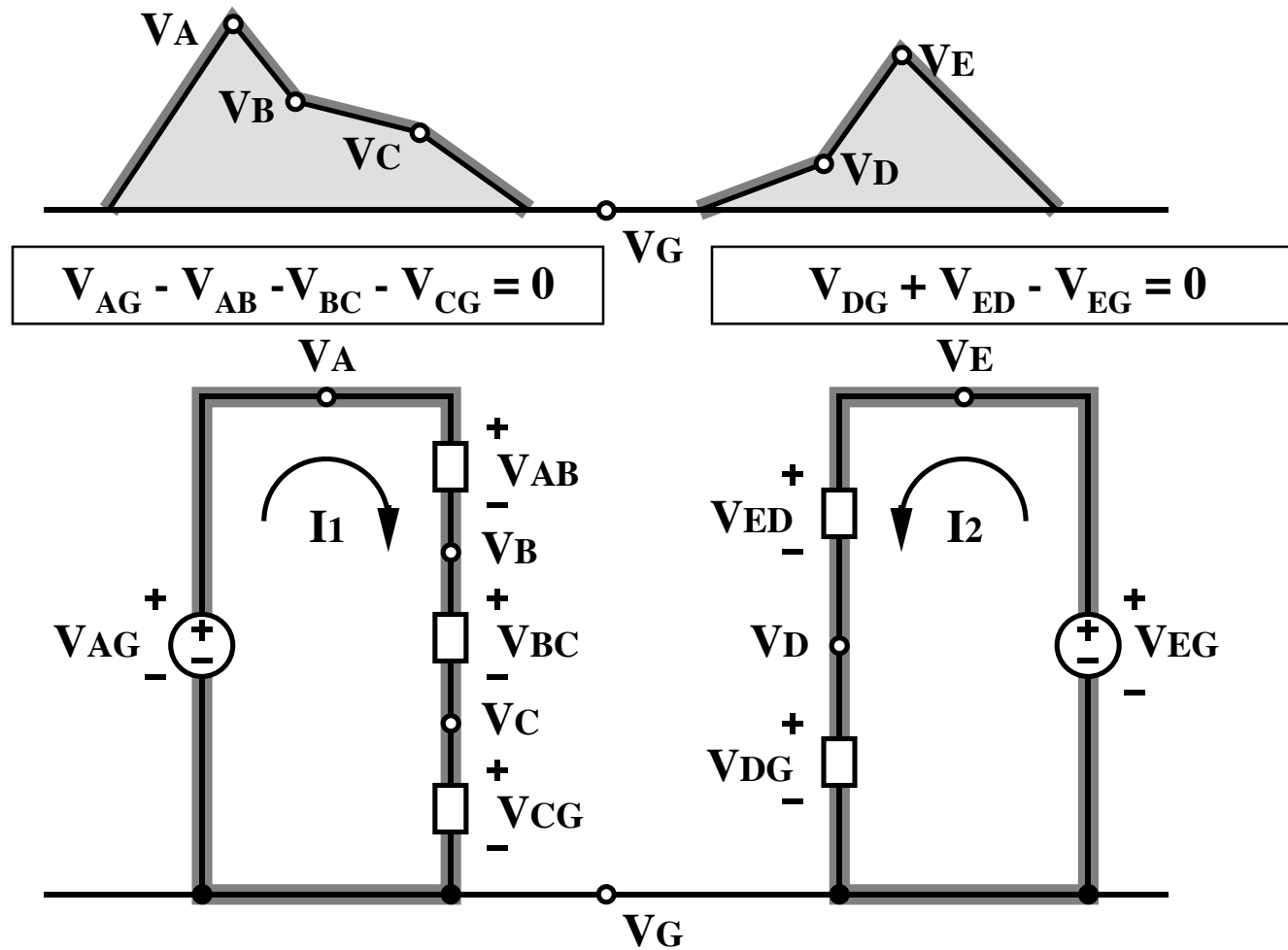


KVL Path

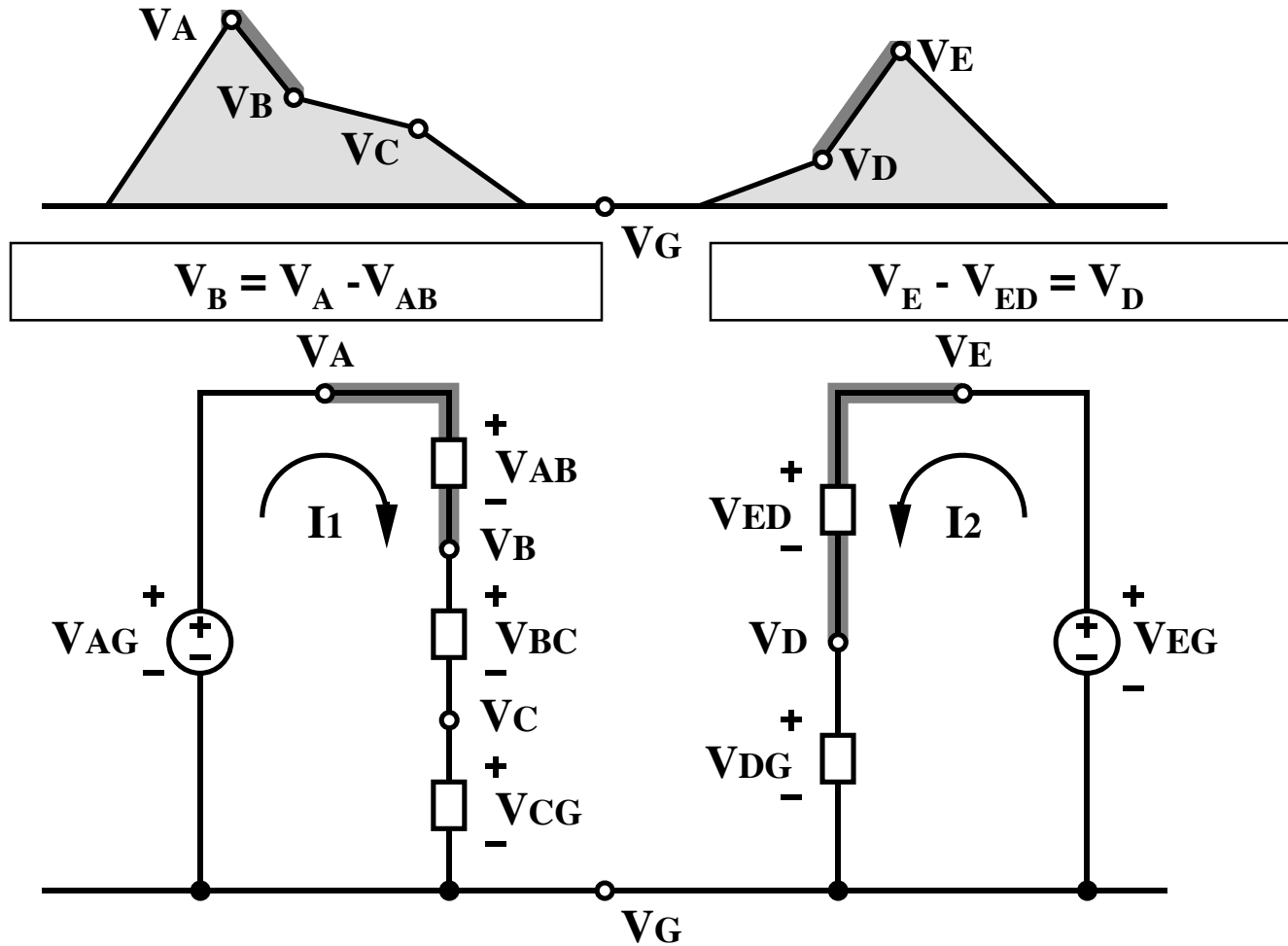- **Simpler equation: don't always need entire loop**



KVL Equations

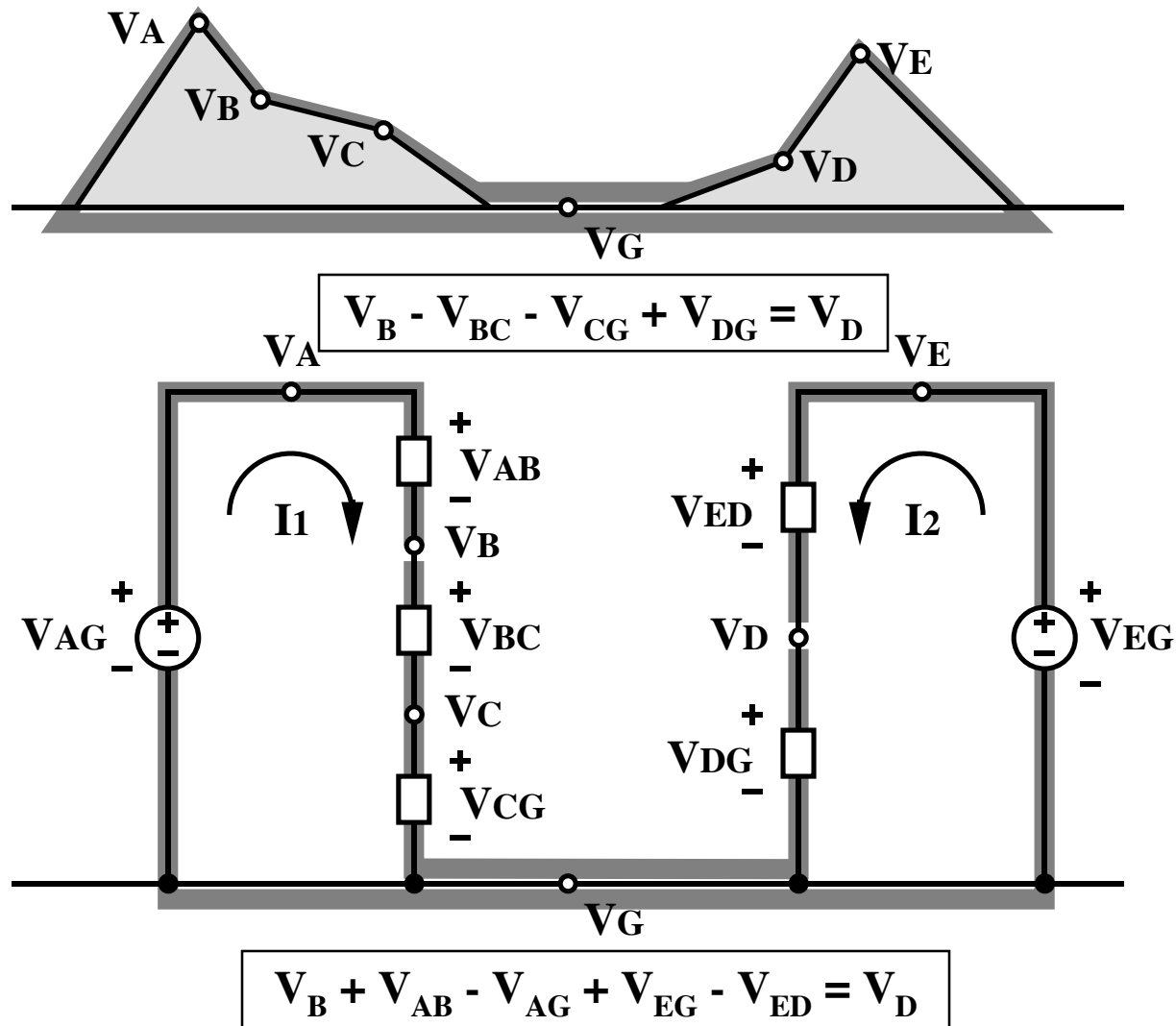
- Equations not unique: choose easier equation



More terms, but V_{AG} and V_{EG} are (known) sources

KVL “Jump”

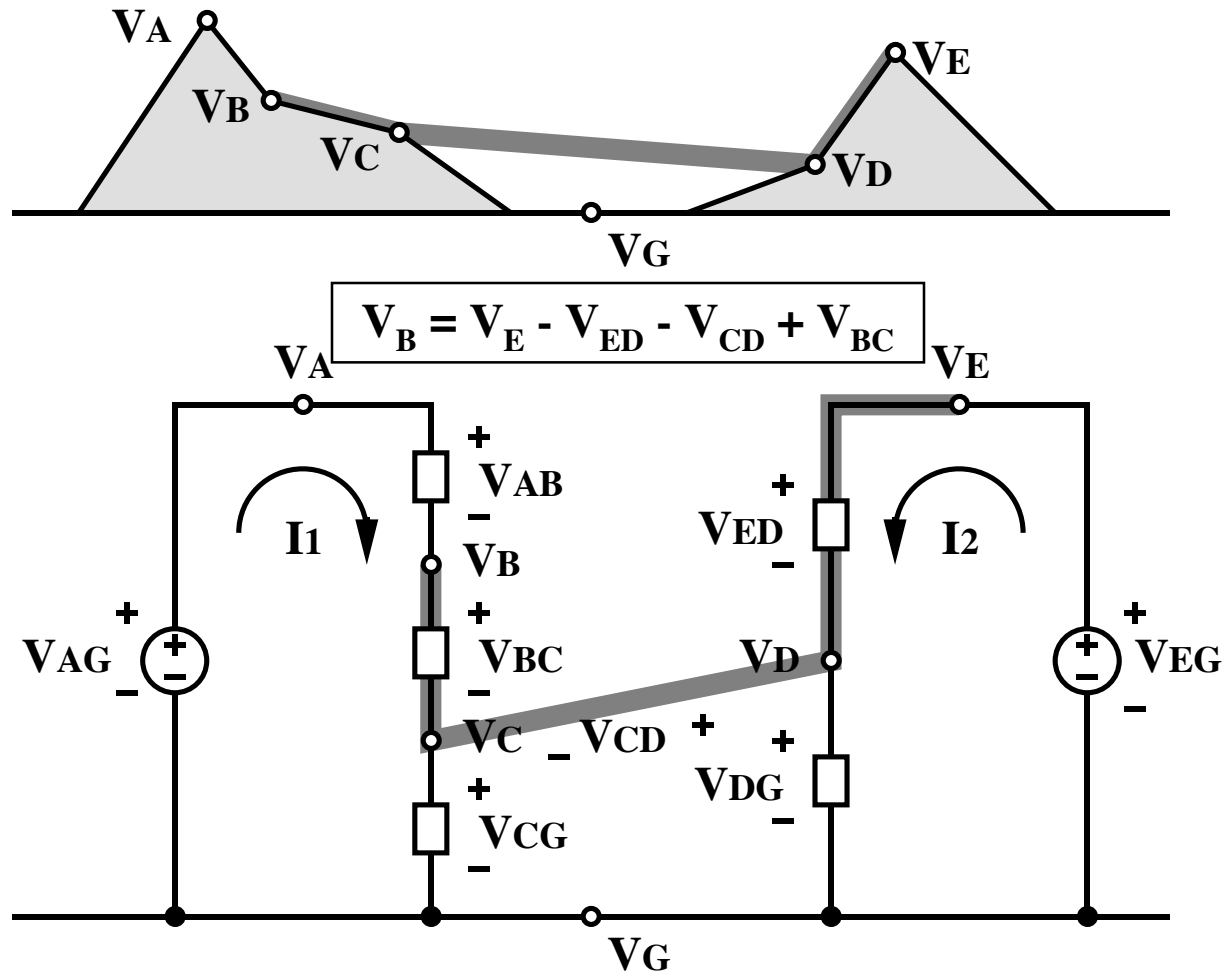- Define new voltage difference if appropriate



KCL: Kirchhoff's Current Law


- Sum of currents at a node = 0

$$I_1 - I_2 - I_3 + I_4 = 0$$

- KCL:


What goes in must come out

$$I_1 + I_4 = I_2 + I_3$$

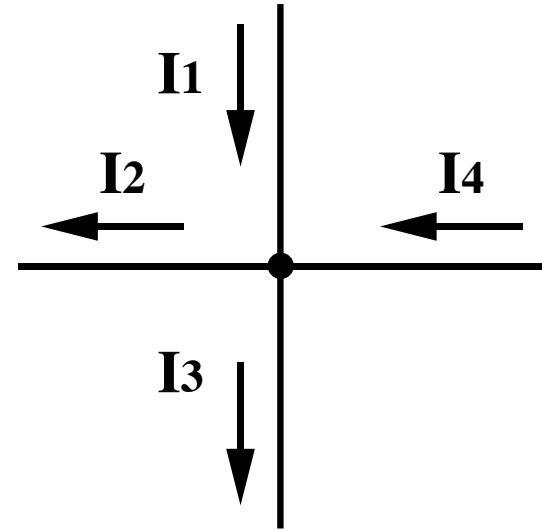


KCL Trouble

Example: Find I_{10}

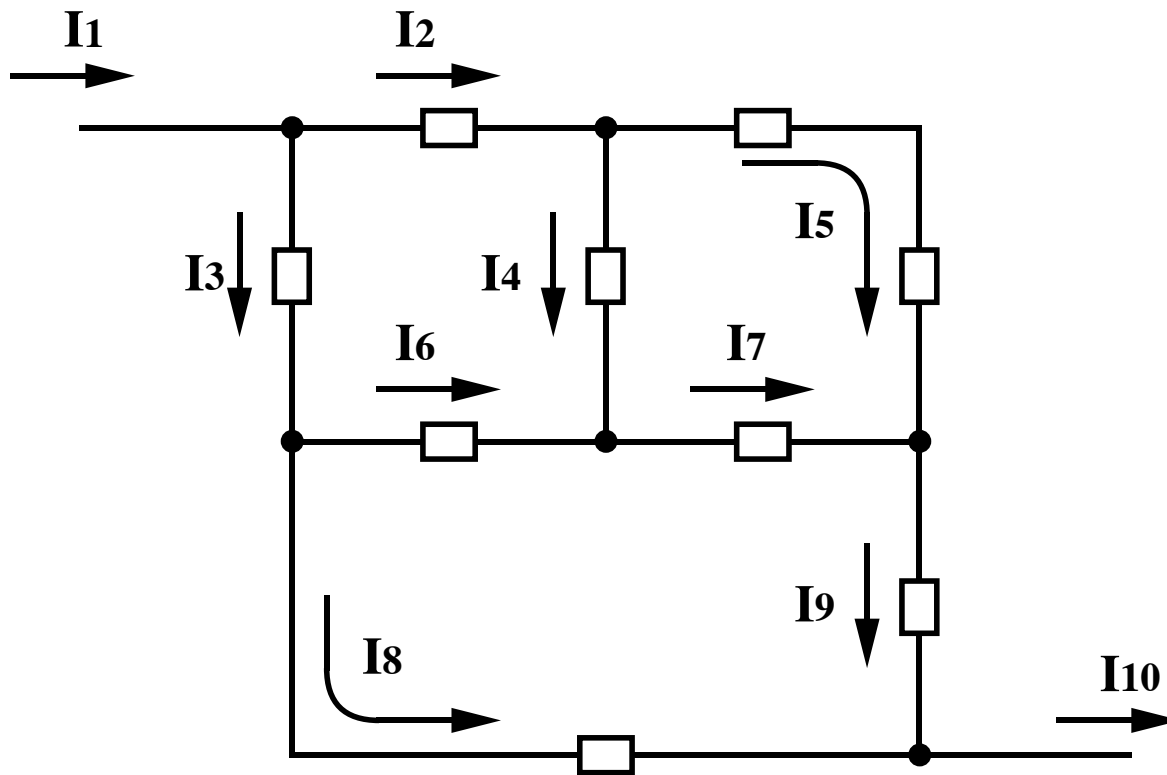

“Supernode”: What goes in must come out

$$I_{10} = I_1$$

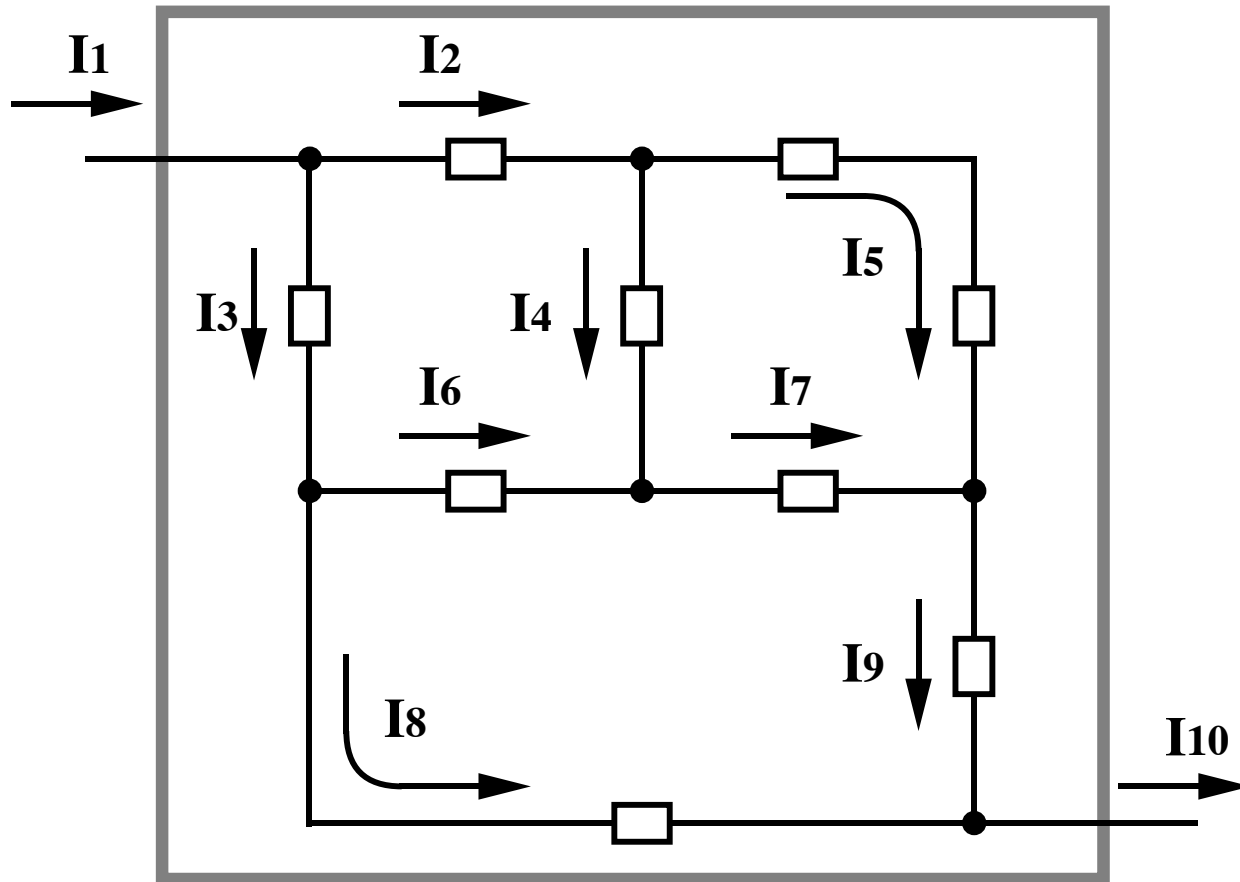

Thevenin's Theorem

- Simplify linear network with equivalent circuit

