

IMPEDANCE AT A NODE (GENERAL) (USE FOR R_{in} , R_{out} OF AMPLIFIER CIRCUITS)

PROCEDURE

① SUPPRESS (SET=0) ALL INDEPENDENT SOURCES


V SOURCE \rightarrow SHORT
I SOURCE \rightarrow OPEN

NEED TO KEEP
DEPENDENT SOURCES

② APPLY TEST SOURCE V_x } OR, IF EASIER,
③ CALCULATE ASSOCIATED i_x } APPLY i_x AND
CALCULATE V_x


④ IMPEDANCE AT NODE $\Rightarrow Z = \frac{V_x}{i_x}$

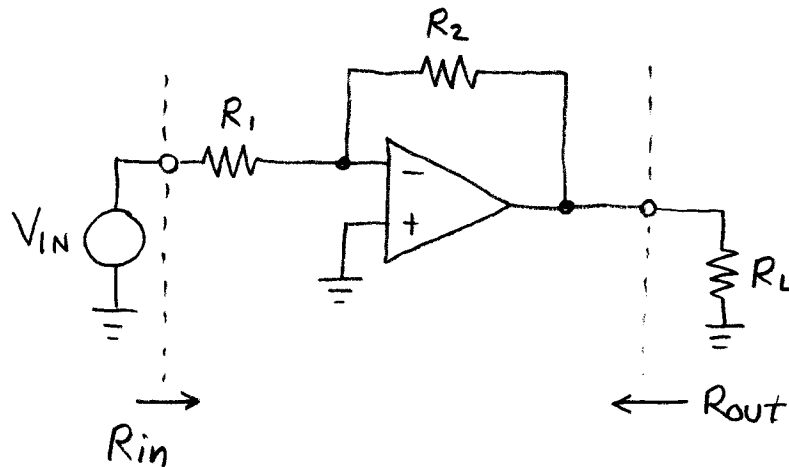EXAMPLE INVERTING OP-AMP CIRCUIT R_{in} , R_{out}



WHAT R_{in} DOES
 V_{IN} SEE?


WHAT R_{out} IS
DRIVING LOAD R_L ?

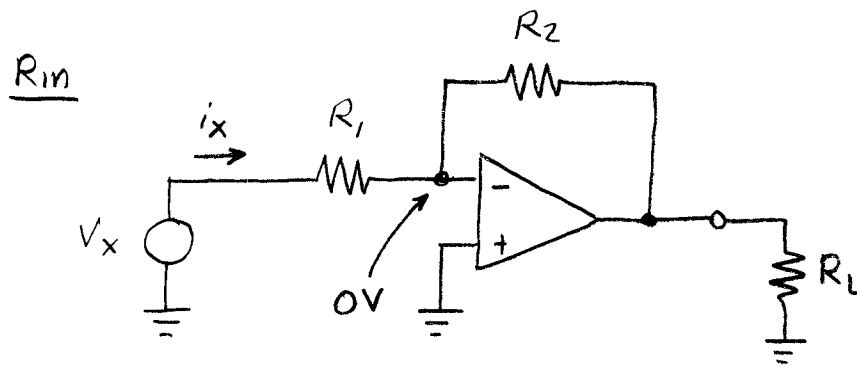

VIRTUAL GROUND: $V_- = 0$ (ASSUME IDEAL OP-AMP)

OHM'S LAW FOR R_1 : $i_x = \frac{V_x - 0}{R_1} = \frac{V_x}{R_1}$

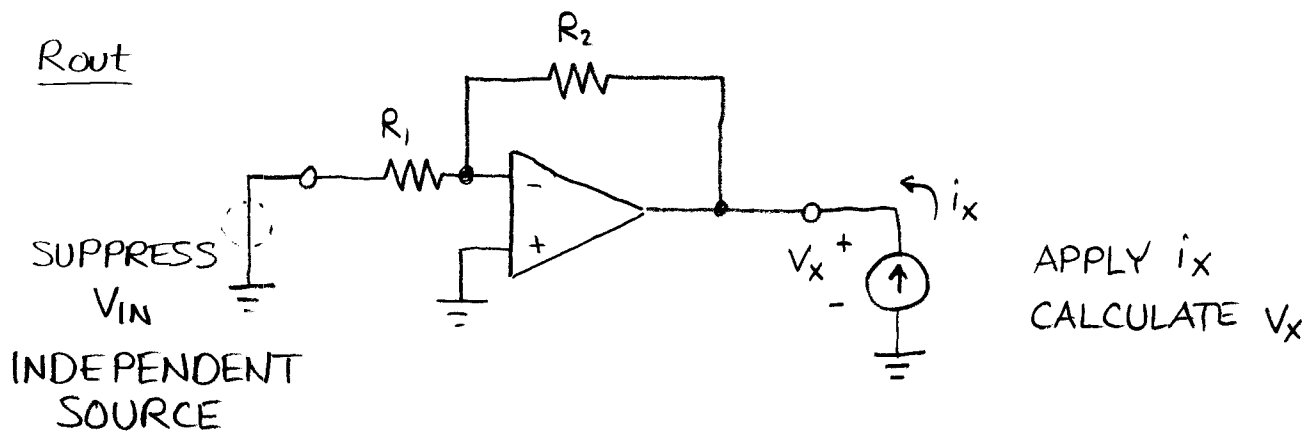SOLVE FOR $\frac{V_x}{i_x} = R_1 \Rightarrow \boxed{R_{in} = R_1}$



INVERTING AMPLIFIER WITH ZERO INPUT:

$V_x = 0$ REGARDLESS OF i_x

$\frac{V_x}{i_x} = 0 \Rightarrow \boxed{R_{out} = 0}$