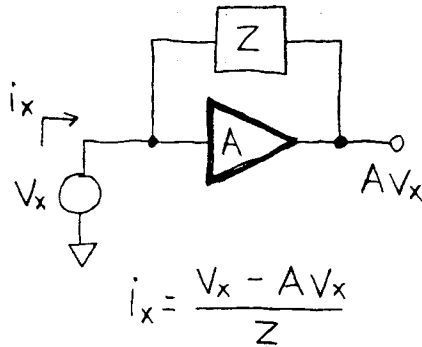


EES24 MILLER EFFECT


Consider any amplifier (not necessarily an op-amp) with gain A , and some impedance Z from input to output: what impedance does it "look like"?



$$\frac{V_x}{i_x} = \frac{Z}{(1-A)}$$




Impedance is reduced by factor $(1-A)$

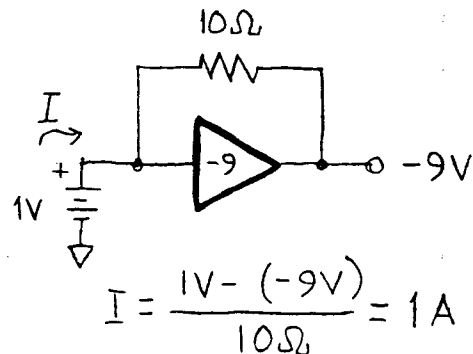EXAMPLE: $Z = 10\Omega$ resistor
 $A = -9$; $V_x = 1V$



Applying 1V causes 1A to flow:
source "sees" a 1Ω resistor!
 $1\Omega = 10\Omega / (1 - [-9])$

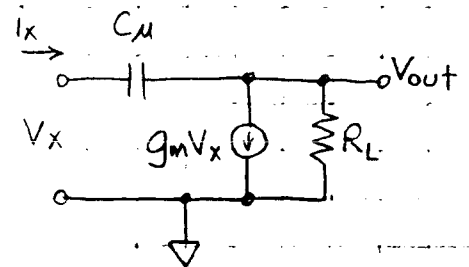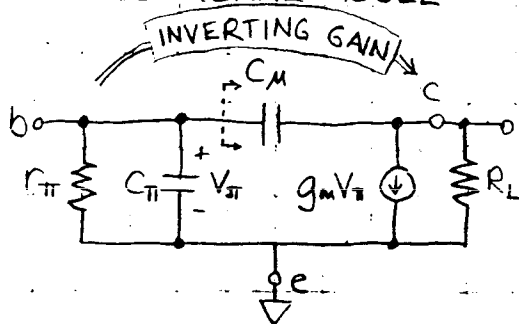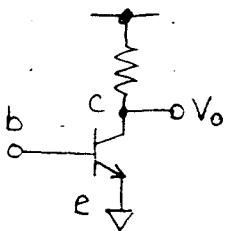UNILATERAL MODEL (or DOMINANT POLE MODEL) of bipolar transistor with resistive load at high frequencies:
COMMON EMITTER $\Rightarrow$ SMALL SIGNAL MODEL $\Rightarrow$ APPARENT IMPEDANCE OF C_M



Assuming current through C_M is much less than $g_m V_x$, then

$$-V_{out} = -g_m R_L V_x$$

$$i_x = (V_x - [-g_m R_L V_x]) s C_M$$

$$\frac{V_x}{i_x} = \frac{1}{s(1 + g_m R_L) C_M}$$

INVERTING GAIN:
 $A = -g_m R_L$

C_M IS "MILLER MULTIPLIED" BY $(1-A)$; APPEARS IN PARALLEL WITH C_π

Unilateral model (valid for input to output analysis only)

