
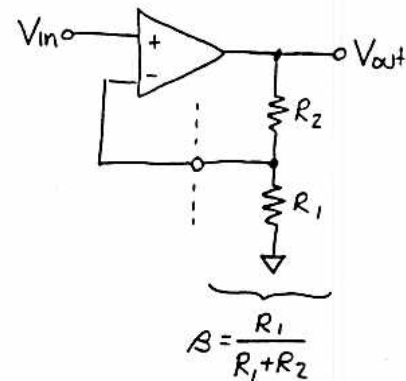


OP-AMP as a classical feedback system

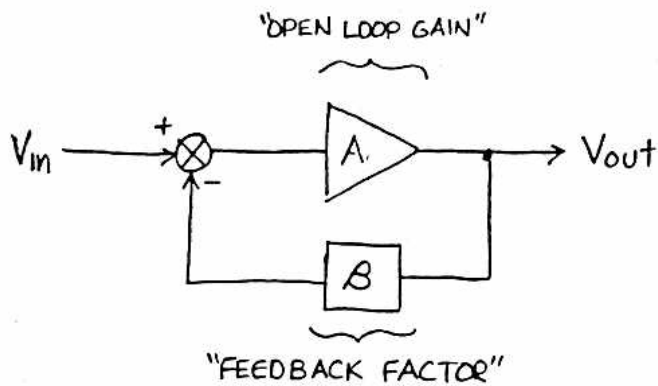


Equation around loop; A finite

$$V_{out} = A(V_{in} - \beta V_{out}) \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta}} \Rightarrow \frac{1}{\beta} \text{ as } A \rightarrow \infty$$

CLOSED-LOOP GAIN

Real op-amp has a single pole (STC) transfer function:
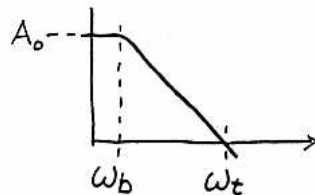
$$A = A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}}$$



Substitute

$$\frac{V_{out}}{V_{in}} = \frac{\frac{A_o}{1 + s/\omega_b}}{1 + \frac{A_o \beta}{1 + s/\omega_b}} \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{\left(\frac{A_o}{1 + A_o \beta}\right)}{1 + \frac{s}{[(1 + A_o \beta)\omega_b]}}$$

From general lowpass form:

LOW FREQUENCY CLOSED LOOP GAIN

$$A_{CL} = \frac{A_o}{1 + A_o \beta} \rightarrow \frac{1}{\beta} \text{ as } A_o \rightarrow \infty$$

CLOSED LOOP 3dB FREQUENCY

$$\omega_{3dB} = (1 + A_o \beta) \omega_b \quad \omega_b \text{ INCREASED BY FACTOR } (1 + A_o \beta)$$

"GAIN-BANDWIDTH PRODUCT"

$$A_{CL} \times \omega_{3dB} = \left(\frac{A_o}{1 + A_o \beta}\right) (1 + A_o \beta) \omega_b = A_o \omega_b = \omega_t$$

INDEPENDENT OF CLOSED LOOP GAIN!

CLOSED LOOP BANDWIDTH	×	CLOSED LOOP GAIN	=	GAIN-BANDWIDTH PRODUCT
(CONSTANT FOR A GIVEN OP-AMP)				

FOR LM741, $f_t = 1 \text{ MHz}$

FOR LM318, $f_t = 15 \text{ MHz}$