
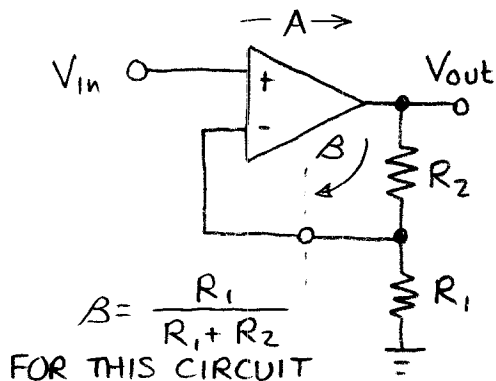


# OP-AMP AS A CLASSICAL FEEDBACK SYSTEM

OP-AMP CIRCUIT:

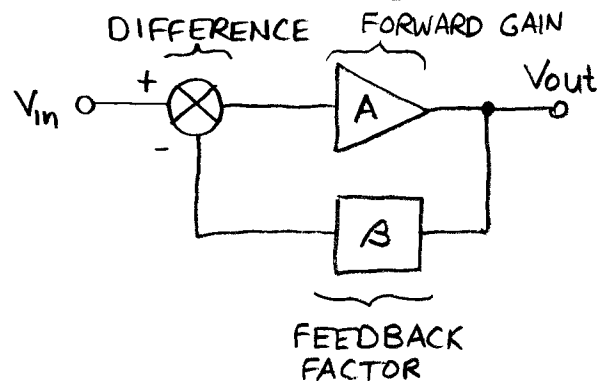

CLASSICAL FEEDBACK:




$\beta$ : "FEEDBACK FACTOR" FRACTION OF  $V_{out}$  FED BACK TO  $V_-$

FIND CLOSED LOOP GAIN  $G = \frac{V_{out}}{V_{in}}$

$$V_{out} = A(V_{in} - \beta V_{out}) \Rightarrow \boxed{\frac{V_{out}}{V_{in}} = \frac{A}{1 + A\beta} = G} \quad \begin{array}{l} \checkmark \text{ AS EXPECTED} \\ G \rightarrow \frac{1}{\beta} \\ \text{AS } A \rightarrow \infty \end{array}$$

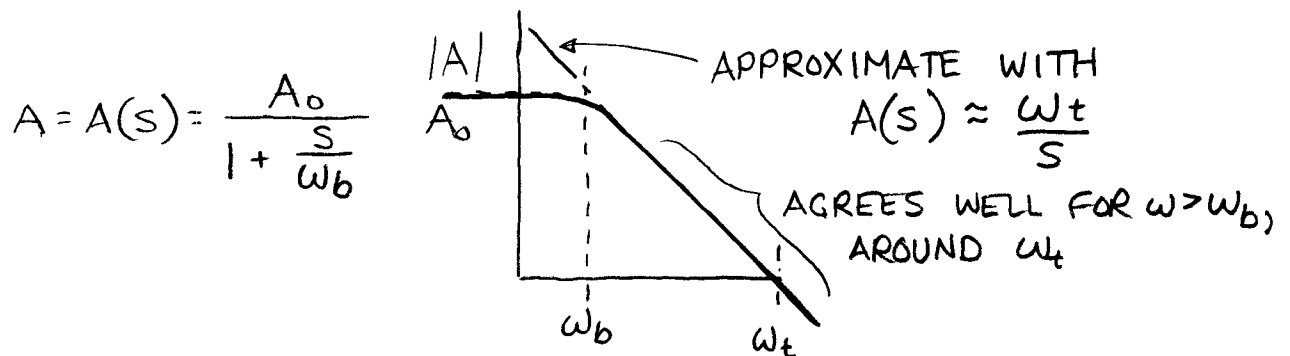WHAT IS CLOSED LOOP GAIN  $G$  WHEN  $A$  IS FINITE?  
REAL OP-AMP HAS SINGLE POLE TRANSFER FUNCTION



SUBSTITUTE IN  $G$  EXPRESSION

$$G = \frac{A}{1 + A\beta} = \frac{\frac{\omega_t}{s}}{1 + \beta \frac{\omega_t}{s}} \quad \left. \begin{array}{l} \text{MULTIPLY NUM, DEN} \\ \text{BY } \frac{s}{\beta \omega_t} \end{array} \right\}$$

MESSAGE INTO GENERAL FIRST ORDER FORM

$$G = \frac{[\text{DC GAIN}]}{1 + \frac{s}{[\omega_{3dB}]}}$$

$$G = \frac{\frac{\omega_t}{s} \frac{s}{B\omega_t}}{\left(1 + B \frac{\omega_t}{s}\right) \frac{s}{B\omega_t}} \Rightarrow \boxed{\frac{\frac{1}{B}}{1 + \frac{s}{B\omega_t}}}$$

} DC GAIN

} CLOSED LOOP BANDWIDTH  $\omega_{3dB}$

GAIN-BANDWIDTH TRADEOFF!:

WHEN WE CHOOSE A FEEDBACK FACTOR  $B$  (FRACTION  $< 1$ )

TO GET A CLOSED LOOP DC GAIN OF  $\frac{1}{B}$

CLOSED LOOP BANDWIDTH  $\omega_{3dB}$  IS  $B\omega_t$

UNITY GAIN FREQUENCY  $\omega_t$  REDUCED BY  $B$  FACTOR

INVERSE RELATIONSHIP: PRODUCT IS CONSTANT

$$\left[ \begin{array}{c} \text{CLOSED LOOP} \\ \text{GAIN} \end{array} \right] \times \left[ \begin{array}{c} \text{CLOSED LOOP} \\ \text{BANDWIDTH} \end{array} \right] = \left[ \begin{array}{c} \text{GAIN-BANDWIDTH} \\ \text{PRODUCT} \end{array} \right]$$

$\frac{1}{B}$

$\underbrace{B\omega_t}_{\omega_{3dB}}$

$\underbrace{\omega_t}_{\text{UNITY GAIN FREQUENCY}}$

FOR LM741,  $f_t = 1 \text{ MHz}$

FOR LF356,  $f_t = 4 \text{ MHz}$

GRAPHICALLY.

