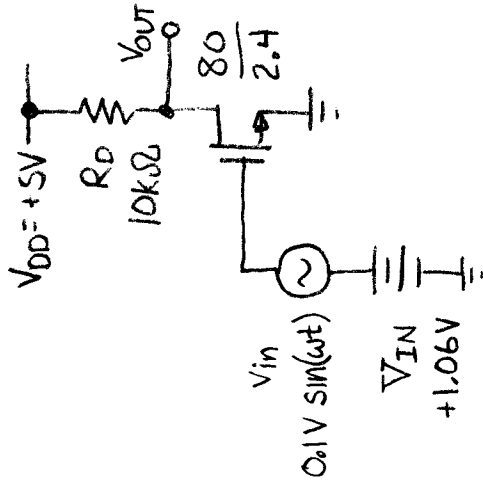


SMALL SIGNAL ANALYSIS SUMMARY

CIRCUIT




MOSFET

$$\mu C_{ox} = 7.42E-5 \frac{A}{V^2}$$

$$V_t = 0.61V$$

LARGE SIGNAL MODEL

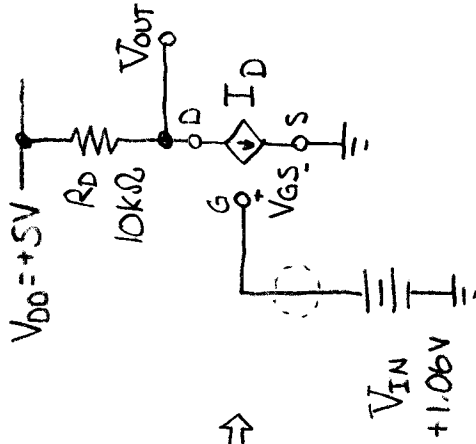

ACTIVE (SQ LAW) FOR I_D

$$I_D = \frac{7.42E-5}{2} \frac{80}{2.4} (1.06 - 0.61)^2$$

$$I_D = 251 \mu A$$

$$V_{eff} = 0.45V$$


$$V_{OUT} = 5V - (251 \mu A)(10k\Omega)$$

$$V_{OUT} = +2.49V$$

$$V_{DS} > V_{eff} \checkmark$$

$$2.49V > 0.45V$$

SMALL SIGNAL MODEL

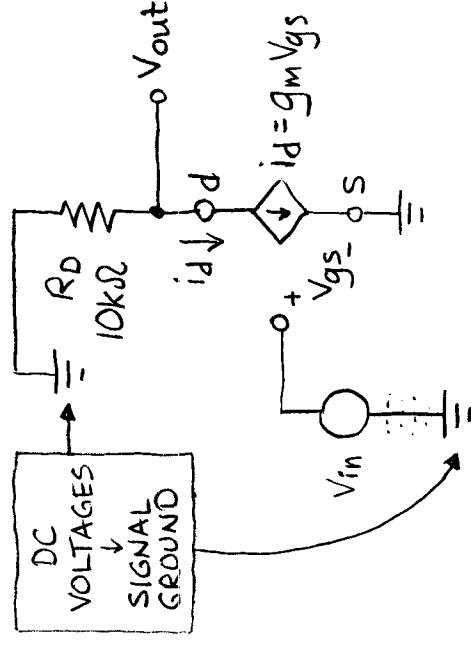

TRANSCONDUCTANCE g_m FROM DC BIAS

$$g_m = 7.42E-5 \frac{80}{2.4} (1.06 - 0.61)$$

$$g_m = 1.11 \text{ mA/V}$$

-SIGN: INVERTING AMPLIFIER

$$V_{out} = -i_d R_D = -g_m V_{gs} R_D = \underbrace{(-g_m R_D)}_{-11.1} V_{in}$$

small signal gain

$$\frac{V_{out}}{V_{in}} = -g_m R_D$$

"BUILD UP" OUTPUT FROM DC, SMALL SIGNAL "PIECES"

AT INPUT:

$$\underbrace{V_{IN}}_{\text{TOTAL}} = \underbrace{+1.06V}_{V_{IN}} + \underbrace{(0.1V) \sin \omega t}_{v_{in}}$$

OUTPUT $\Downarrow$ $\Downarrow$ CHANGE $\Downarrow$ PROPORTIONAL GAIN


$$\underbrace{V_{OUT}}_{\text{TOTAL}} = \underbrace{+2.49V}_{V_{OUT}} + \underbrace{(-1.11V) \sin \omega t}_{V_{out} = (-g_m R_o) v_{in}}$$

-11.1
FROM SMALL-SIGNAL ANALYSIS

IN GENERAL


$$\underbrace{V_{OUT}}_{\text{TOTAL OUTPUT}} = \underbrace{V_{OUT}}_{\text{OUTPUT DC OPERATING POINT}} + \underbrace{A_v}_{\text{SMALL SIGNAL GAIN}} \underbrace{v_{in}}_{\text{SMALL SIGNAL INPUT}}$$

SKETCH V_{OUT}

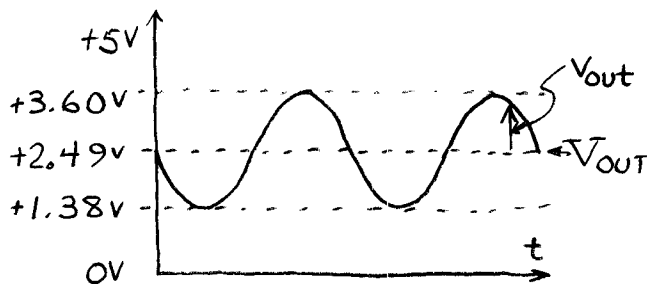

CHECK MAX, MIN PEAKS:
MEETS ACTIVE REGION
CONDITIONS FOR ALL V_{OUT}

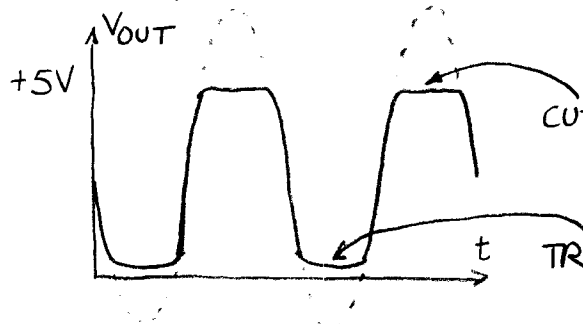WHAT IF $v_{in} = (1.0V) \sin \omega t$? SMALL SIGNAL MODEL PREDICTS



$$V_{OUT} = 2.49 + (-11.1) \sin \omega t$$

CUTOFF $\Leftarrow$ MAX PEAK = 13.6V?

CHECK PEAK VALUES

TRIODE $\Leftarrow$ MIN PEAK = -8.6V?