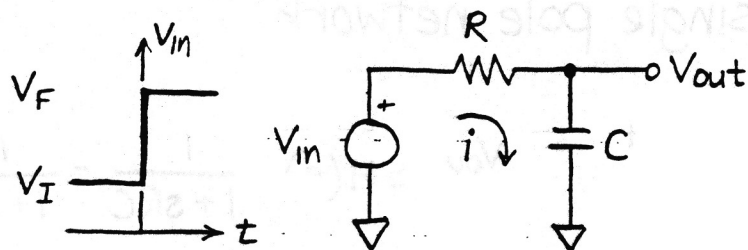


STEP RESPONSE OF FIRST ORDER SYSTEM



First order differential equation for V_{out}

$$\underbrace{V_{out} = V_{in} - iR}_{\text{KVL}} \Rightarrow \underbrace{i = C \frac{d}{dt} V_{out}}_{\text{CAPACITOR}} \Rightarrow \frac{d}{dt} V_{out} = \left(\frac{-1}{RC} \right) V_{out} + \left(\frac{1}{RC} \right) V_{in}$$

Solve differential equation; homogeneous solution: $V_{in}=0$
try solution of form $Ae^{-t/\tau}$; substitute

$$\frac{d}{dt} [Ae^{-t/\tau}] = \left(\frac{-1}{RC} \right) [Ae^{-t/\tau}]$$

$$\frac{-1}{\tau} Ae^{-t/\tau} = \frac{-1}{RC} Ae^{-t/\tau} \Rightarrow \tau = RC \quad \left. \vphantom{\frac{-1}{\tau}} \right\} \text{"TIME CONSTANT"}$$

Particular solution: when output is constant,
 $t \rightarrow \infty$, $dV_{out}/dt \rightarrow 0$; try constant solution $V_{out} = B$
As $t \rightarrow \infty$, $V_{in} = V_F$

$$\left(\frac{-1}{RC} \right) B + \left(\frac{1}{RC} \right) V_F = 0 \Rightarrow B = V_F$$

Boundary condition: at $t=0$, $V_{out} = V_I$ (voltage across C cannot change instantaneously)

$$Ae^{-0/\tau} + V_F = V_I \Rightarrow A = V_I - V_F$$

General solution:

$$V_{out}(t) = V_F - (V_F - V_I) e^{-t/\underbrace{RC}_{\tau}}$$

