

EN390W
Practical Aspects of Grounding, Power, and EMI
Module 1: Grounding and Power

Lecture Notes

ANNOTATED PDFS
WILL BE AVAILABLE

Prof. John McNeill
Worcester Polytechnic Institute
ECE Department

mcneill@ece.wpi.edu (508) 831-5567

Topic	Text Chapter
Module 1: Grounding and Power	
Introduction	1
Models for Ground and Power Distribution	
Grounding for Safety, Signal Integrity, Measurement	3
Analog Power Supply Decoupling	4
Parallel Plate Electromagnetics	
Practical Limitations of Passive Components	5
Analog and Digital Ground Issues	10
Digital Circuit Power Distribution	11
Module 2: EMI and Shielding	
Overview	1
Cabling Strategies	2
Interference Rejection through Balancing and Filtering	4
Low Frequency, High Frequency Shielding Techniques	6
A System Integration “War Story”	
RF and Transient Immunity	14
Digital Circuit Radiation	12
Conducted Emissions	13
Limits of Performance: Fundamental Noise Sources	8, 9

Introduction: Noise and Interference

Noise is any electrical signal present in a circuit other than the desired signal.

Types of noise sources:

- (1) intrinsic noise sources that arise from random fluctuations within physical systems, such as thermal and shot noise;
- (2) man-made noise sources, such as motors, switches, computers, digital electronics, and radio transmitters; and
- (3) noise caused by natural disturbances, such as lightning and sunspots.

Interference is the undesirable effect of noise.

If a noise voltage causes improper operation of a circuit, it is interference.

Noise cannot be eliminated, but can be reduced in magnitude, until it no longer causes interference.

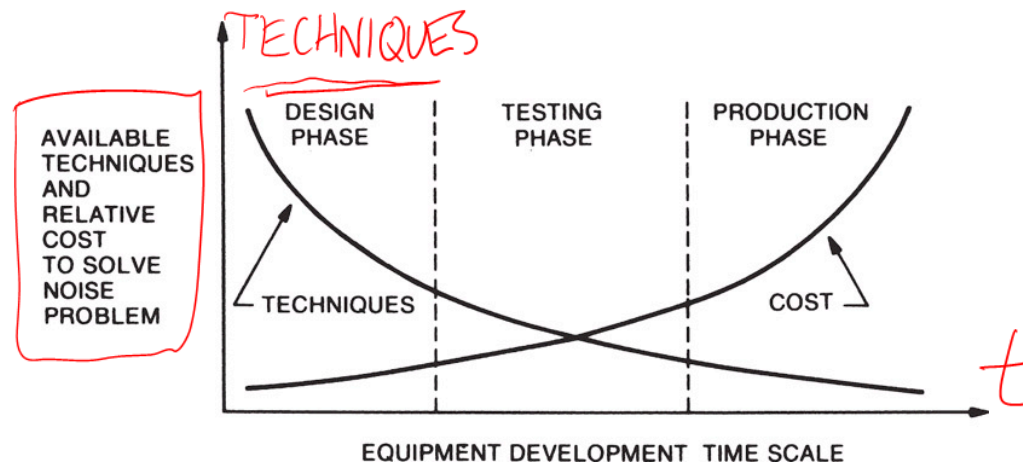


Figure 1-1: As equipment development proceeds, the number of available noise-reduction techniques goes down. At the same time, the cost of noise reduction goes up

Models for Noise Coupling

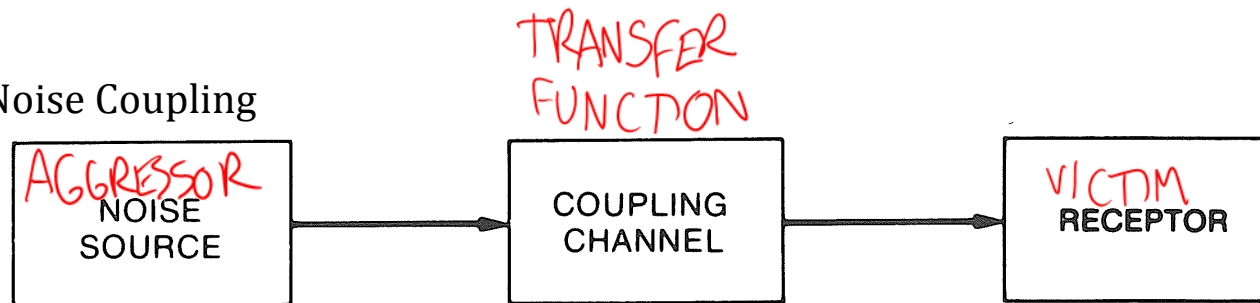


Figure 1-7: Before noise can be a problem, there must be a noise source, a receptor, and a coupling channel

 


Figure 1-8: In this example, the noise source is the motor, and the receptor is the low-level circuit. The coupling channel consists of conduction on the motor leads and radiation from the leads

Coupling through EM fields



 


Figure 1-12: When two circuits are coupled by an electric field, the coupling can be represented by a capacitor

MAGNETIC
FIELD

 

PHYSICAL
REPRESENTATION

 

EQUIVALENT
CIRCUIT

REPRESENTS
COUPLING
TRANSFORMER

INDUCTOR

$$V_L = L \frac{di_L}{dt}$$

i_L
+
 V_L
-

MUTUAL INDUCTANCE:

$$V_2 = M_{12} \frac{dI_s}{dt}$$

Figure 1-13: When two circuits are coupled by a magnetic field,
the coupling can be represented as a mutual inductance

Coupling through common impedance

KEY: DRAW
SYSTEM TO
EXPLICITLY
SHOW GND
CURRENTS

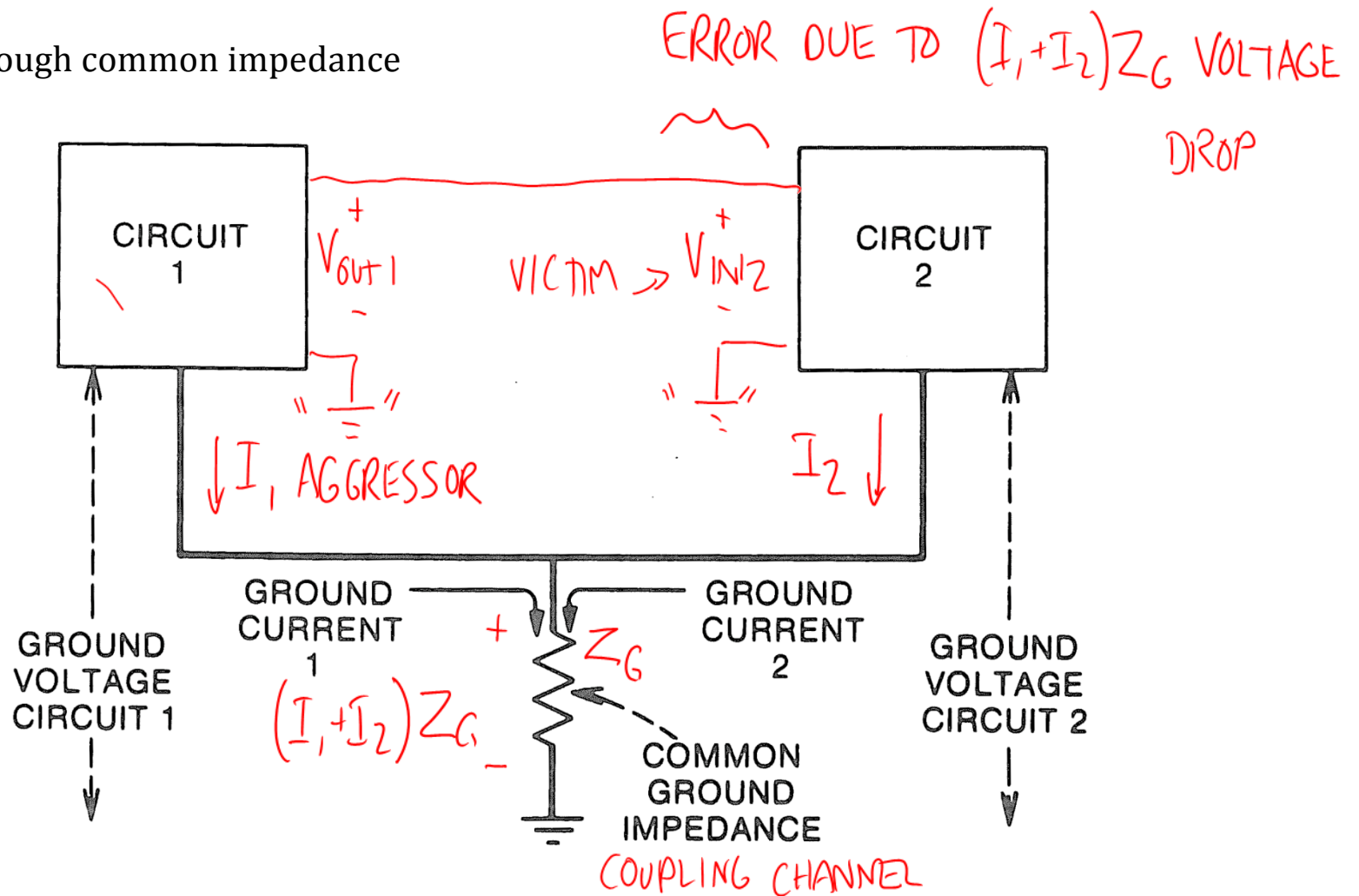


Figure 1-9: When two circuits share a common ground, the ground voltage of each one is affected by the ground current of the other circuit

2 FUNCTIONS OF "GROUND"
 ① VOLTAGE REFERENCE
 ② CURRENT RETURN PATH
 } $Z_G \neq 0$ CONFLICT!

 


Figure 1-10: When two circuits share a common power supply, current drawn by one circuit affects the voltage at the other circuit

KEY: SHOW CURRENT PATHS!

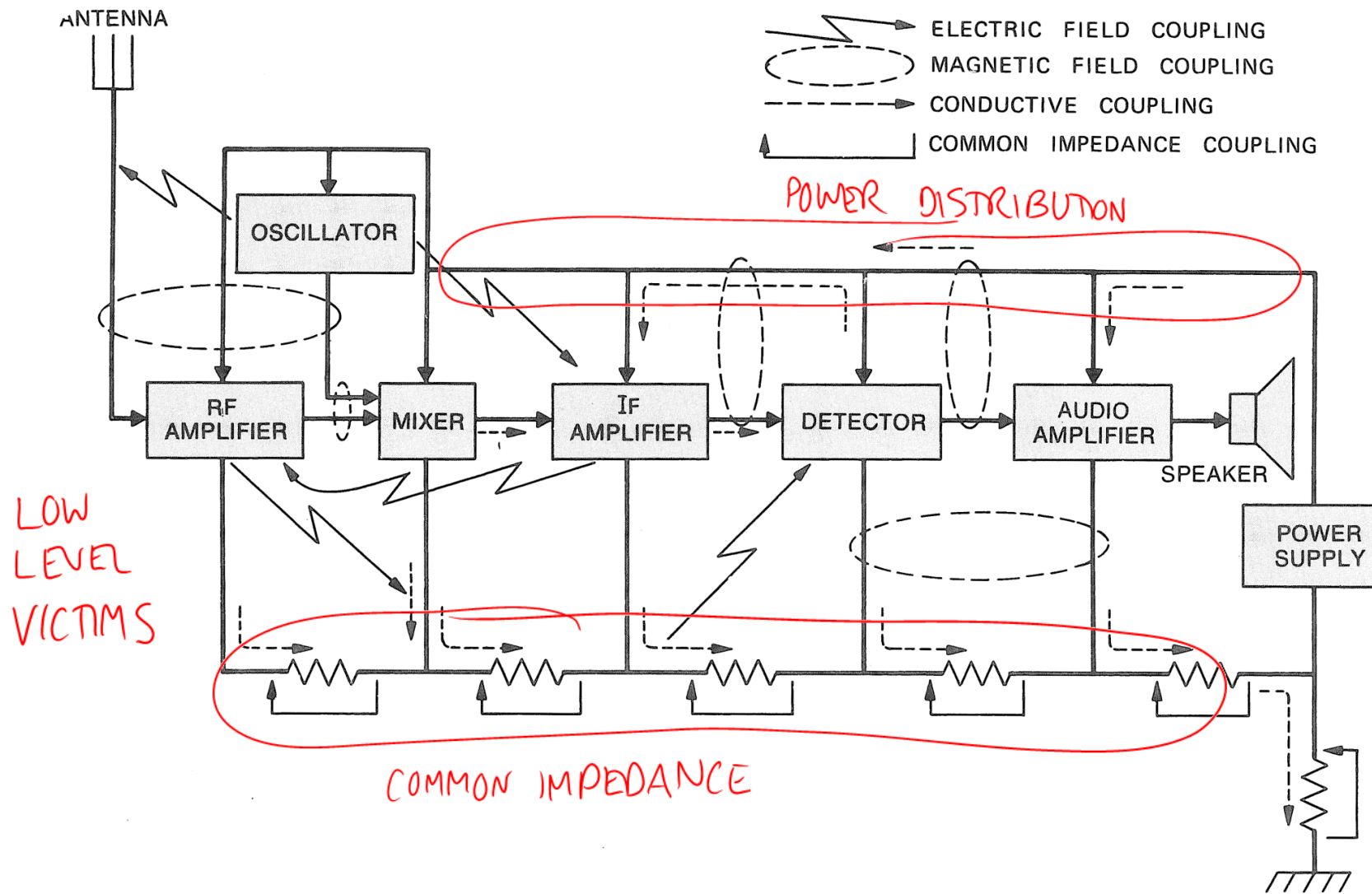


Figure 1-1. Within equipment, such as this radio receiver, individual circuit elements can interfere with one another in several ways.

Other Methods of noise coupling

 


Figure 1-11: Galvanic action can occur if two dissimilar metals are joined and moisture is present on the surface

CONNECTORS

SMALL ΔV CONTACT POTENTIAL

INCREASES IMPEDANCE

One Minute Quiz:

Think of a noise / interference problem you have encountered in your engineering experience.

If possible, describe it in terms of the source – channel – receptor model.

METHODS OF ELIMINATING INTERFERENCE

The following chapters present techniques by which interference between electronic circuits can be eliminated, or at least reduced. The primary methods available for combatting interference are listed as follows:

1. Shielding **BREAK FIELDS COUPLING: $M, C \rightarrow 0$**
2. Grounding **AVOID COMMON IMPEDANCE**
3. Balancing **VICTIM DIFFERENTIAL, GND NOT A REFERENCE**
4. Filtering **$\boxed{V} \boxed{A} \rightarrow f$ SHAPE TRANSFER FUNCTION OF COUPLING CHANNEL**
5. Isolation **SEPARATE VICTIM, AGGRESSOR CURRENTS**
6. Separation and orientation **BREAKING (OR REDUCING) FIELDS COUPLING**
7. Circuit impedance level control **$Z_G \rightarrow 0$ $Z_{ps} \rightarrow 0$**
8. Cable design **SHIELDING, GROUNDING, TWISTED PAIR**
9. Cancellation techniques (frequency or time domain).
DIFFERENTIAL VS COMMON MODE
INTERFERENCE \leftrightarrow TIME SLOTTING

*

Summary: Introduction

- Designing equipment that does not generate noise is as important as designing equipment that is not susceptible to noise.
- Noise sources can be grouped into the following three categories: (1) intrinsic noise sources, (2) man-made noise sources, and (3) noise caused by natural disturbances.
- To be cost effective, noise suppression must be considered early in the design.
- Electromagnetic compatibility is the ability of an electronic system to function properly in its intended electromagnetic environment.
- Electromagnetic compatibility should be a major design objective: designed into a product not added on at the end of the design.
- The following three items are necessary to produce an interference problem:
 - A noise source
 - A coupling channel
 - A susceptible receptor
- Three important aspects of noise / interference problems:
 - Frequency
 - Amplitude
 - Time (when does it occur)
- Metals in contact with each other must be galvanically compatible.
- Noise can be reduced in an electronic system using many techniques; a single unique solution to most noise reduction problems does not exist.

Grounding

Safety:

ISSUE: FAULT CAUSES UNSAFE VOLTAGE ON CHASSIS

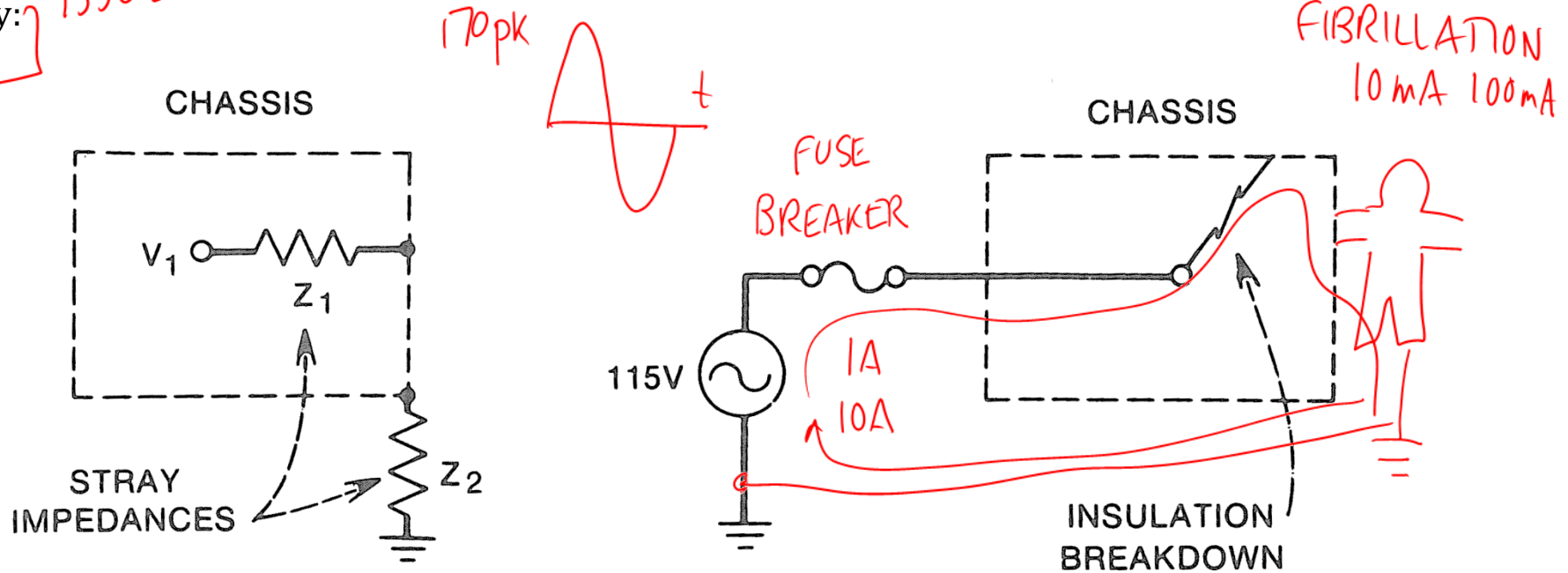


Figure 3-1. Chassis should be grounded for safety. Otherwise, it may reach a dangerous voltage level through stray impedances (left) or insulation breakdown (right).

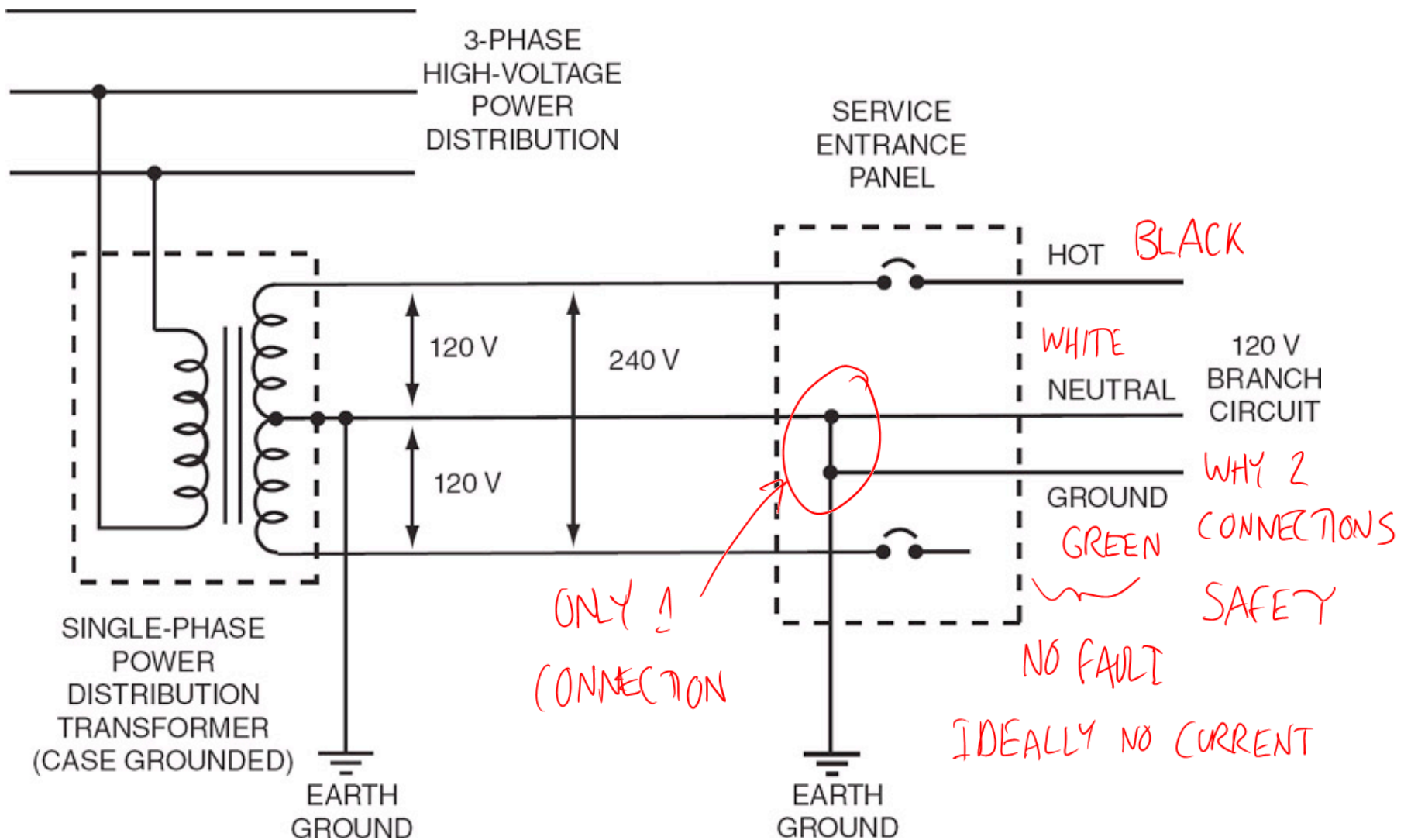


Figure 3-1: A single-phase residential service providing 120/240 V single-phase power

Safety: NEC specifies that the neutral and ground wires shall be connected together at *one and only one point*

 


Figure 3-2: Standard 120-V ac power distribution branch circuit has three conductors

Note: GFCI looks for $I_{HOT} \neq I_{NEUTRAL}$

PARTIAL FAULT: Z_{FAULT} NOT ENOUGH TO TRIP

 



Figure 3-3: A properly wired and grounded ac branch circuit

EARTH

PLUG " VIOLATES SAFETY PURPOSE



 


Figure 3-5: Fault current path in a standard 120-V ac power distribution branch circuit

NEC says very little about the issue of noise and interference control

Mostly concerned with electrical safety and fire protection.

System designer must find a way to satisfy the code and still produce a low-noise system.

NEC is only concerned with a frequency of 50/60 Hz and its harmonics.

An acceptable 60-Hz ground will not be an acceptable 1-MHz ground.

IEEE Std. 1100-2005, *IEEE Recommended Practice for Powering and Grounding Electronic Equipment*

Noise can be differential mode (hot to neutral) or common mode (neutral to ground)

Grounding, however, will only have an effect on the common-mode noise.

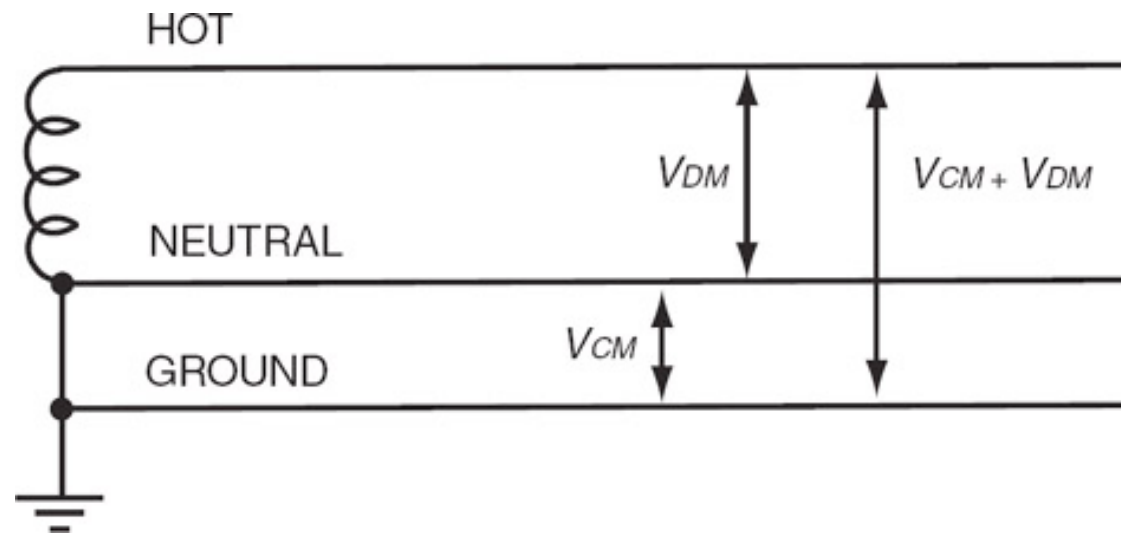


Figure 3-6: Differential-mode and common-mode noise

To control noise and interference, must create a low-impedance ground system that is effective not only at 50/60 Hz but also at much higher frequencies (10s – 100s MHz).

Supplemental ground conductors such as ground straps, ground planes, ground grids, and so on may be required.

NEC allows such supplemental ground conductors provided they meet the following two conditions:

1. They must be in addition to the ground conductors required by NEC, not in place of them.
2. They must be bonded to the NEC required ground conductors.

FREQUENCY RANGE

SIGNAL f RANGE

INTERFERING SIGNAL f

CAUTION: "Earth" ground INEFFECTIVE

 


Figure 3-7: Fault current path when the load is connected to an isolated or separate "quiet" ground. This configuration is dangerous and violates the NEC

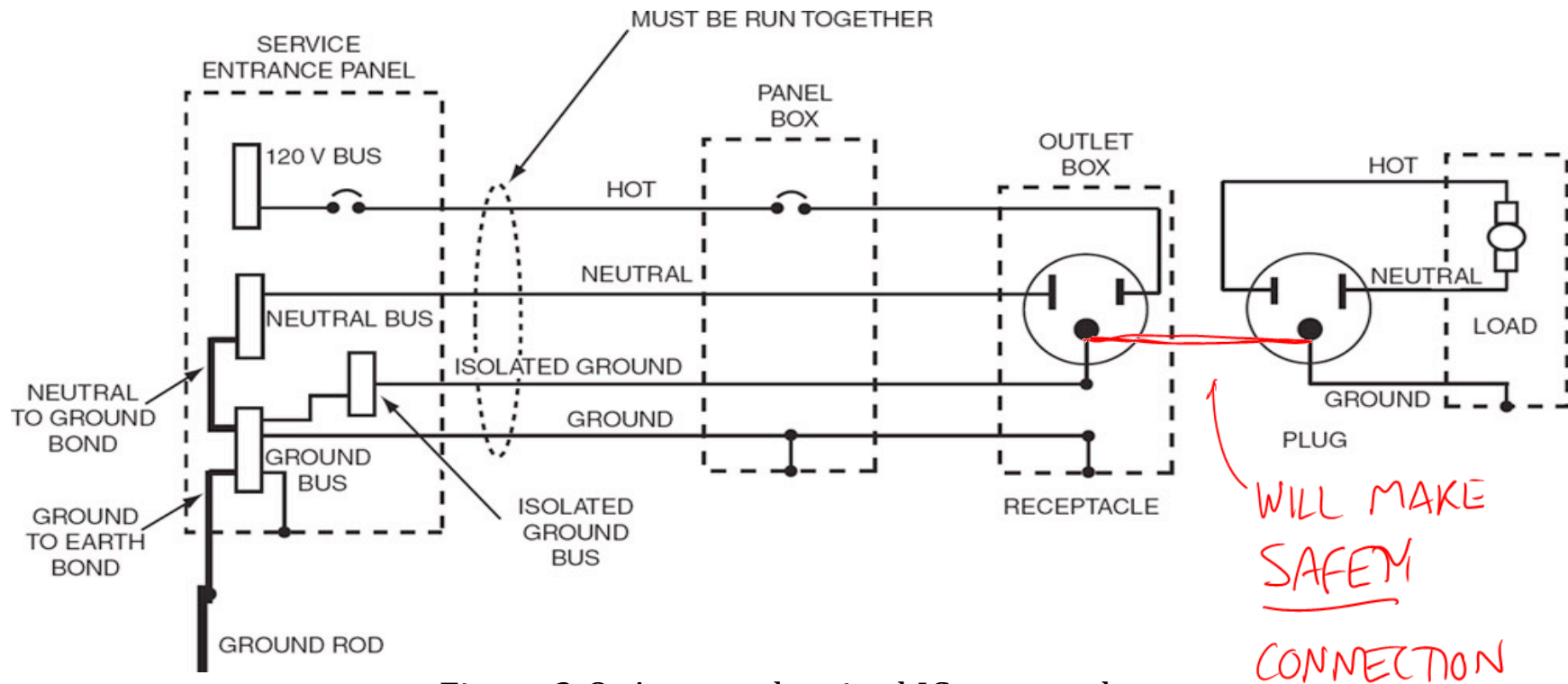


Figure 3-8: A properly wired IG receptacle

In practice, there will be small (safe) voltage difference between the grounds of outlets. Leakage currents, magnetic field induction, and currents that flow through EMI filter capacitors connected to the equipment ground cause these voltages.


Typically less than 100 mV, but in some cases, it is as high as a few volts.

These noise voltages, although safe, are excessive if coupled into most low-level signal circuits.

Therefore, *the ac power ground is of little practical value as a signal reference.*

Connection should be made to the ac power, or earth, ground only when required for safety.

Isolated Grounds

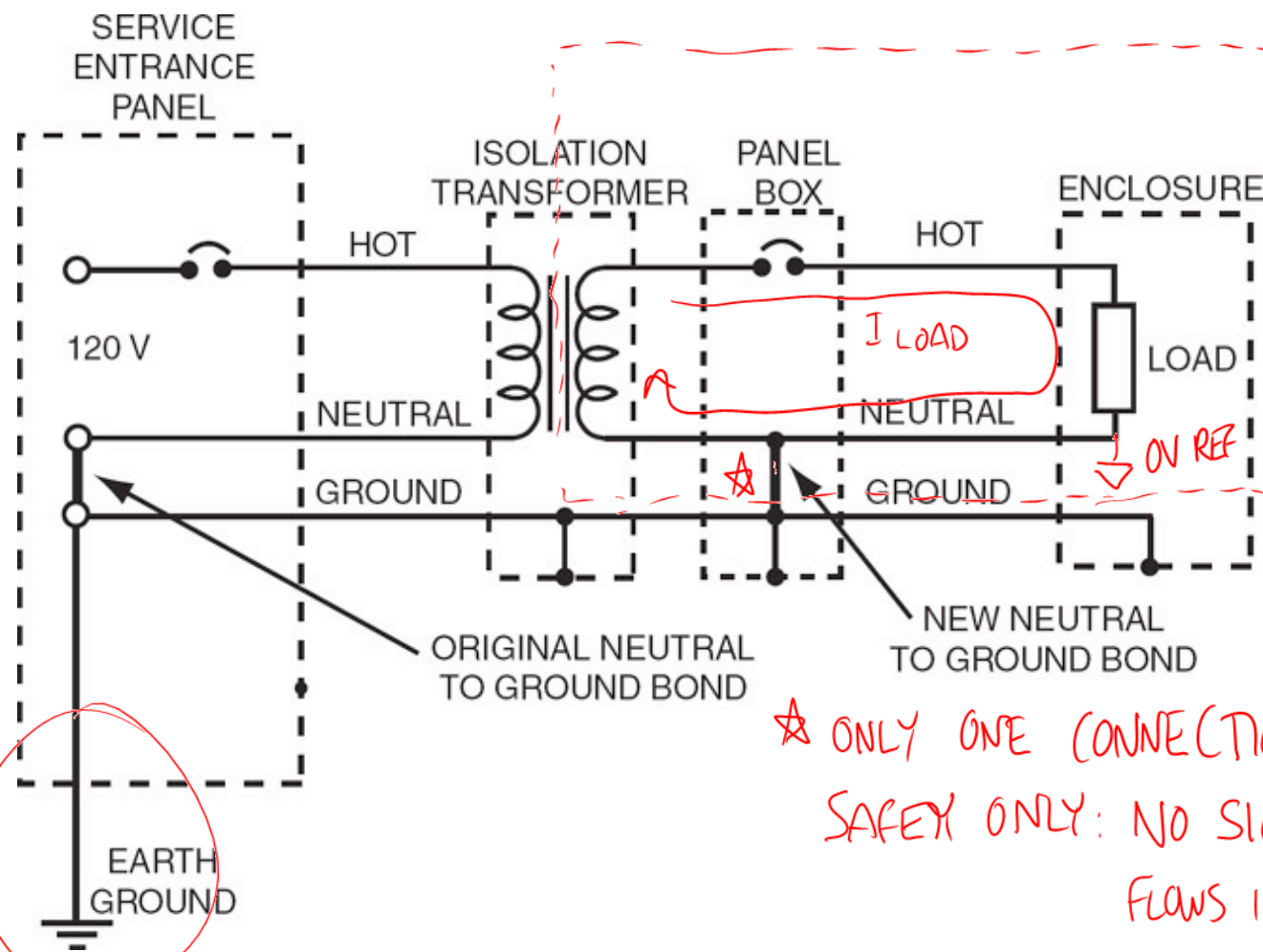


ONLY ONE
CONNECTION

ON REF FOR LOAD
RELATIVE TO
CAN BE DIFFERENT
OK: LOAD REF

★ ONLY ONE CONNECTION TO EARTH GROUND
SAFETY ONLY: NO SIGNAL CURRENT
FLOWS IN THAT PATH

Figure 3-9: An isolation transformer used to create a separately derived system. A new neutral-to-ground bond point is established at the transformer or first panel box after the transformer


Grounding Myths

1. The earth is a low-impedance path for ground current. ~~False~~, the impedance of the earth is orders of magnitude greater than the impedance of a copper conductor.
2. The earth is an equipotential. ~~False~~, this is clearly not true as a result of (1).
3. The impedance of a conductor is determined by its resistance. ~~False~~, what happened to the concept of inductive reactance? 
4. To operate with low noise, a circuit or system must be connected to an earth ground. ~~False~~, because airplanes, satellites, cars, and battery-powered laptop computers all operate fine without a ground connection. As a matter of fact, an earth ground is more likely to be the cause of a noise problem. More electronic system noise problems are resolved by removing (or isolating) a circuit from earth ground than by connecting it to earth ground.
5. To reduce noise, an electronic system should be connected to a separate "quiet ground" by use of a separate, isolated ground rod. ~~False~~, in addition to being untrue, this approach is dangerous and violates the requirements of the NEC.
6. An earth ground is unidirectional, with current only flowing into the ground. ~~False~~, because current must flow in loops, any current that flows into the ground must also flow out of the ground somewhere else.
7. An isolated receptacle is not grounded. ~~False~~, the term "isolated" refers only to the method by which a receptacle is grounded, not if it is grounded.
8. A system designer can name ground conductors by the type of the current that they should carry (i.e., signal, power, lightning, digital, analog, quiet, noisy, etc.), and the electrons will comply and only flow in the appropriately designated conductors. Obviously false.

CURRENT HAS TO FLOW IN A LOOP: FOLLOW COMPLETE PATH


Signal Grounds: Three basic objectives of signal grounding are as follows:

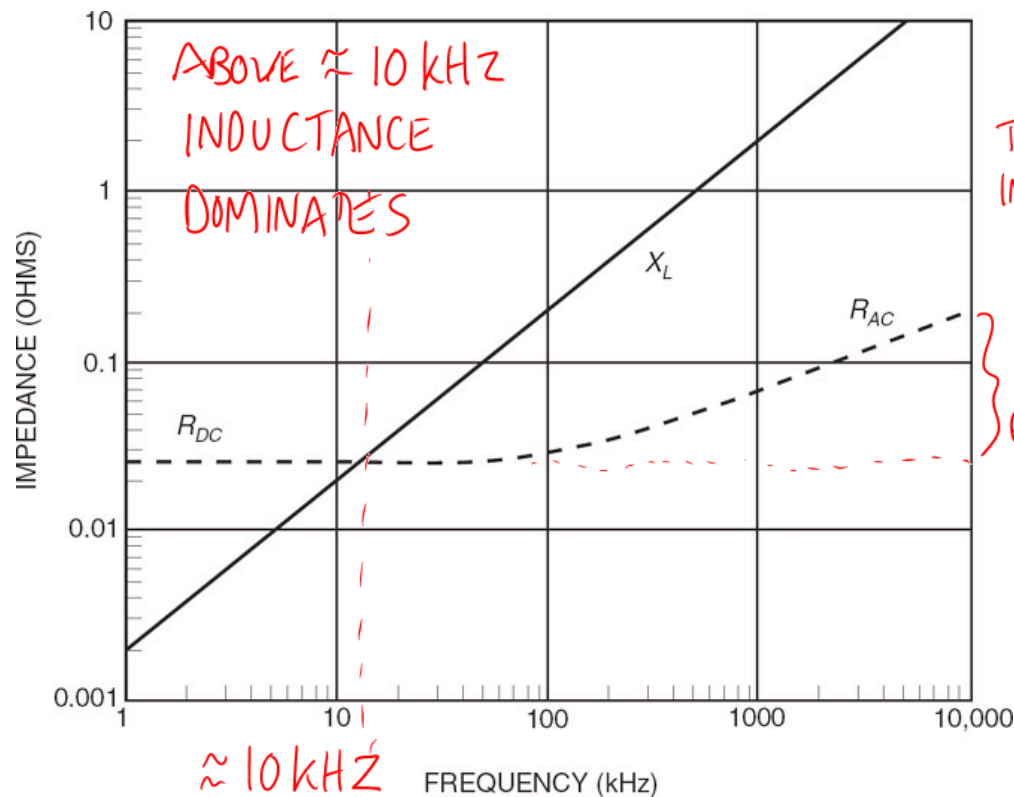1. Not to interrupt the ground return path $Z_g \rightarrow 0$
2. Return the current through the smallest loop possible AVOIDS RADIATION, LOWER IMPEDANCE
3. Be aware of possible common impedance coupling in the ground UNWANTED SHARED CURRENT PATHS



$$Z_g = R_g + j\omega L_g \quad (3-1)$$

SKIN EFFECT

 

AT HIGH FREQUENCIES RETURN CURRENT "PULLED" CLOSE

Figure 3-10: Resistance and inductive reactance versus frequency for a straight, 1-ft length of 24-gauge wire, located 1-in. above a ground plane

"HIGH FREQUENCIES"
 $|Z_L| > |Z_R|$

SURFACE RESISTANCE INCREASES

 


Figure 3-11: A double-sided PCB with a single trace on the topside and a full ground plane on the bottom side. How does the ground plane current flow between points A and B?

 


Figure 3-12: Ground plane current path, (A) at low frequency the return current takes the path of least resistance and (B), at high frequency the return current takes the path of least inductance

ALWAYS WANT TO MINIMIZE LOOP AREA LOWER L, LOWER Z_L LOWER EMISSION
 VISUALIZE WHERE CURRENT "WANTS" TO FLOW: CONTINUOUS PATH LOWER SUSCEPTIBILITY

Signal grounds can be divided into the following three categories:

1. Single-point grounds
2. Multipoint grounds
3. Hybrid grounds

In general, it is desirable that the topology of the power distribution system follows that of the ground.

Usually, the ground structure is designed first, and then the power is distributed in a similar manner.

Voltage drop along current path in “ground”

$$V_g = I_g Z_g \quad (3-2)$$

“GROUND”
IMPLIES
 $V_g = 0$

MINIMIZE IMPEDANCE
MINIMIZE
SHARED COMMON IMPEDANCE
(IF POSSIBLE, DON'T SHARE CURRENT PATHS)

Single Point Grounds

Single-point grounds are most effectively used at low frequency, from dc up to about 20 kHz. They should usually not be used above 100 kHz, although sometimes this limit can be pushed as high as 1 MHz. With single-point grounding, we control the ground topology to direct the ground current to flow where we want it to flow, which decreases I_g in the sensitive portions of the ground.

 


Figure 3-13: Two types of single-point grounding connections

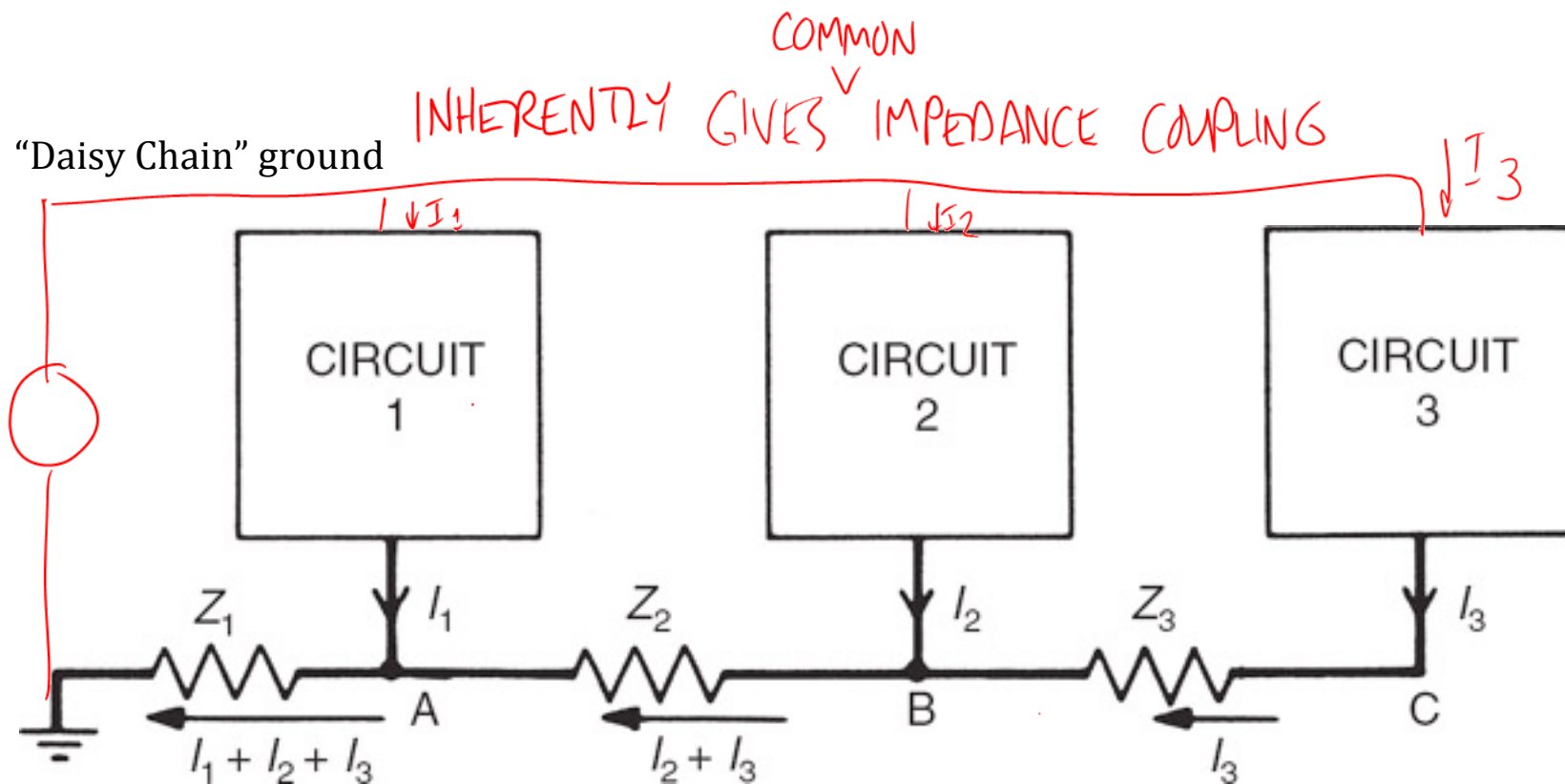


Figure 3-15: Common, or daisy chain, single-point ground system is a series ground connection and is undesirable from a noise standpoint, but it has the advantage of simple wiring

MAY BE OK IF I_1, I_2, I_3 SMALL } $I_g Z_g$ SMALL
 Z_1, Z_2, Z_3 REL TO SIGNAL

BLOCK TO BLOCK COMMUNICATION?


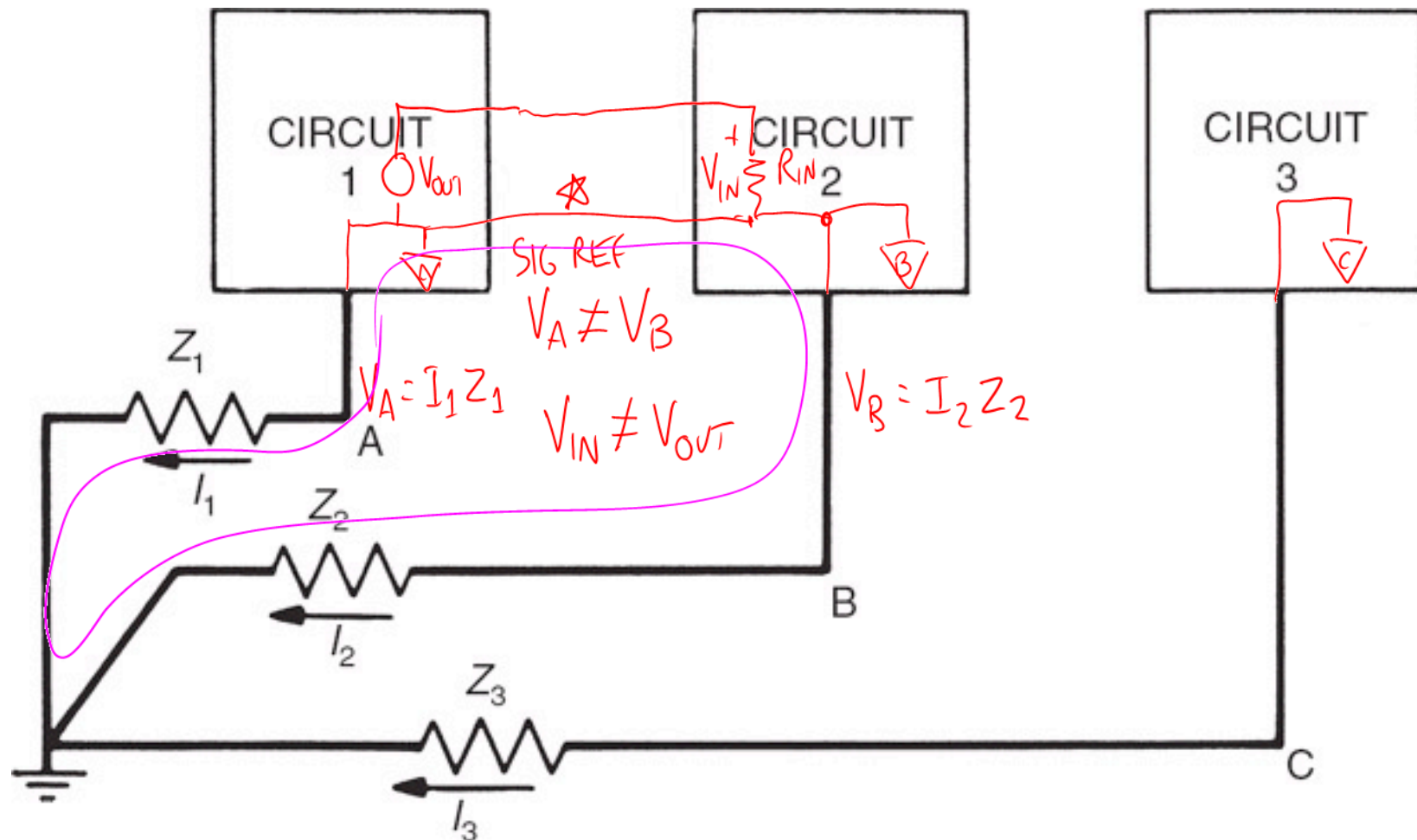


Figure 3-16: Separate, or parallel, single-point ground system is a parallel ground connection and provides good low-frequency grounding, but it may be mechanically cumbersome in large systems

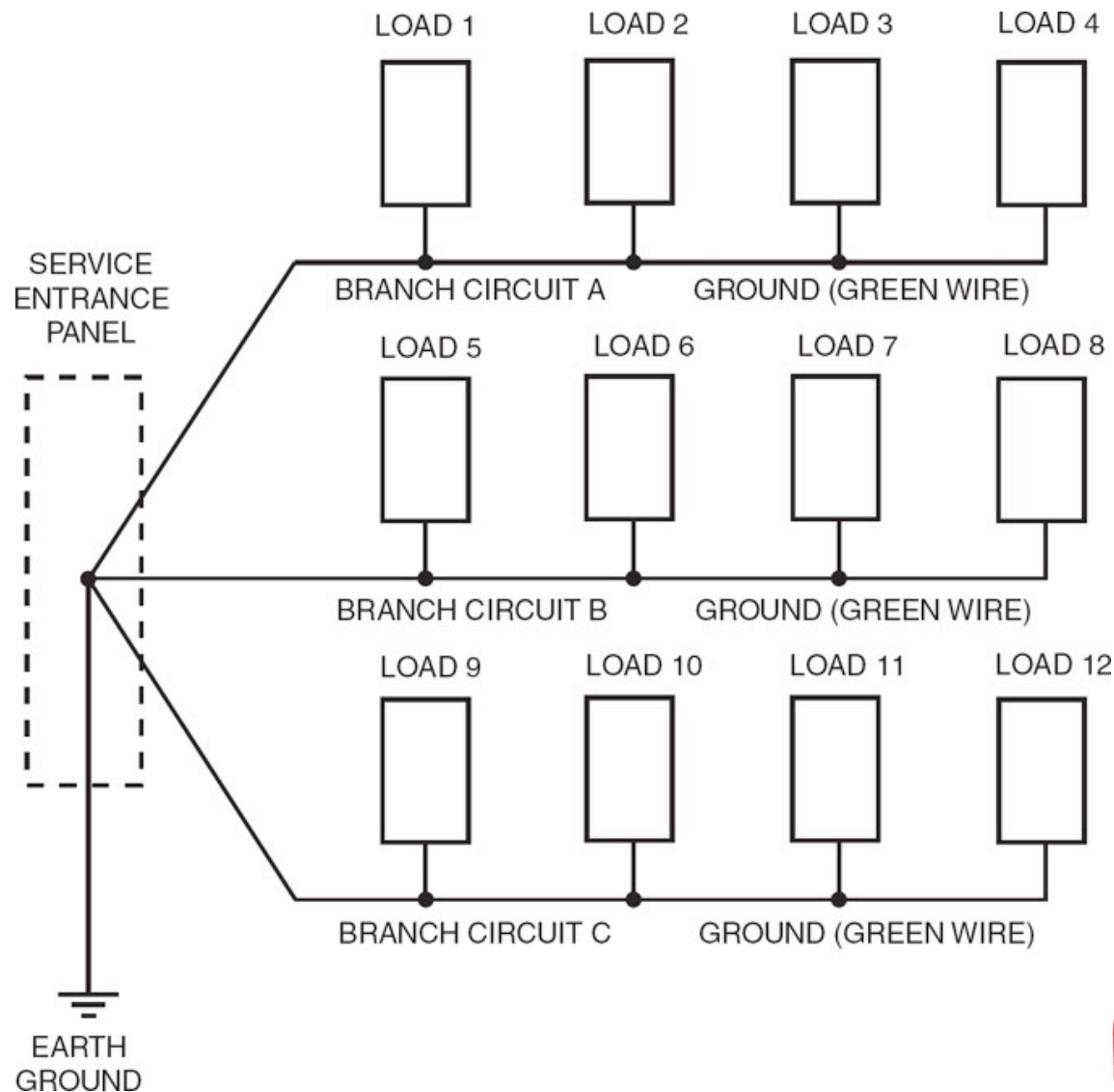TRY TO AVOID COMMON IMPEDANCE COUPLING BY FORCING I_1, I_2 DIFFERENT PATH
 ★ IF TIE ∇ TO ∇ VIOLATES "SEPARATE PATH" "GROUND LOOP"



STAR,
DAISY CHAIN
OK FOR
SAFETY

60 HZ
LIMIT V
DIFFERENCE!
 $|Z_L + Z_R| \ll 1\Omega$

FOR $f > 10\text{KHz}$
 $|Z_L|$ TOO BIG

Figure 3-17: A single-point ac power ground, as per the NEC

NO GOOD FOR SIGNAL GROUND!

Multipoint Grounds

 


Figure 3-14: Multipoint grounding connections

SMALL HAVE COMMUNICATION ISSUE (MAYBE)

 


Figure 3-19: Multipoint ground system is a good choice at frequencies above about 100 kHz. Impedances $R_1 - R_3$ and $L_1 - L_3$ must be minimized at the frequency of interest

$$V_{G1} \neq V_{G2} \neq V_{G3} \quad Z_{G1}, Z_{G2}, Z_{G3} \text{ SMALL ENOUGH}$$

OR: USE BLOCK-TO-BLOCK COMMUNICATION THAT CAN TOLERATE $V_{G1} \neq V_{G2}$

 



Figure 3-20: An example of common impedance coupling

Common impedance coupling becomes a problem when two or more circuits share a common ground and one or more of the following conditions exist:

1. A high-impedance ground (at high frequency, this is caused by too much inductance; at low-frequency this is caused by too much resistance).
2. A large ground current.
3. A very sensitive, low-noise margin circuit, connected to the ground.

One Minute Quiz:

COULD FIX WITH

 

V_{S1} is a 500mV signal source driving $R_{L1} = 10\text{ k}\Omega$ which is the input of an ADC with a 1mV LSB. For accurate measurement we would like to have $V_{L1} = V_{S1}$.

V_{S2} is a 5V power supply providing 0.5A of current to circuitry represented by R_{L2}

$Z_G = 0.1\text{ }\Omega$ is the (DC) resistance of 100 feet of 10 AWG copper wire.

What is the error in V_{L1} ? Express both in LSBs and as a fraction of the 500mV value of V_{S1} .

$$\text{KVL: } V_{S1} - V_{L1} - (I_1 + I_2)Z_G = 0 \Rightarrow \underbrace{V_{L1}}_{\text{OUT}} = \underbrace{V_{S1}}_{\text{SIGNAL (WANT)}} - \underbrace{(I_1 + I_2)Z_G}_{\text{ERROR}}$$

$$0.5\text{ A}(0.1\text{ }\Omega) = 50\text{ mV} \quad 50\text{ LSB}$$

500mV ← 10% error!

Single-point grounds overcome these problems by separating ground currents that are likely to interfere with each other and by forcing them to flow on different conductors.

However, the signal current paths and long lead lengths associated with single-point grounds increase the inductance, which is detrimental at high frequencies.

In addition, at high frequencies, single-point grounds are almost impossible to achieve because parasitic capacitance closes the ground loop.

Multipoint grounds overcome these problems by producing a very low ground impedance, effectively controlling the L_g term in Eq. 3-1.

Normally, at frequencies below 100 kHz, a single-point ground system may be preferable; above 100 kHz, a multipoint ground system is best.

 


Figure 3-18: At high frequency, single-point grounds become multipoint grounds because of stray capacitance

Chassis Grounds

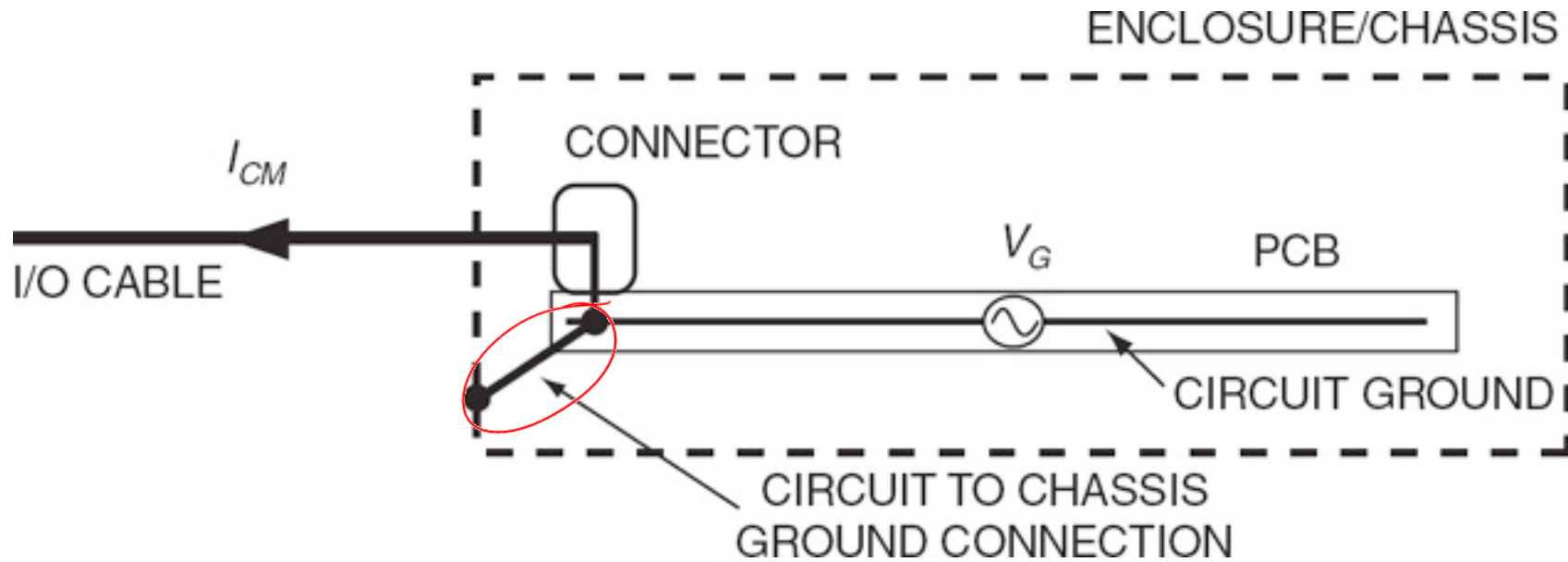


Figure 3-24:


Circuit ground should be connected to the enclosure (chassis) in the I/O area of the PCB

REASON: COMMON MODE EMI (MODULE 2)

SAFETY: COULD BE ANYWHERE

Equipment / System Grounding

Figure 3-31: A distributed system that consists of a multiplicity of widely separated elements

 

Considerations in distributed systems:

- What are the characteristics of the signal? *AMPLITUDE, f*
- What type of cabling and/or filtering will be used?
- Is the signal analog or digital?
- What is its frequency and amplitude?
- Is the signal balanced or unbalanced? (Balanced signals are more immune to noise than unbalanced signals.)
- Will the cabling be individual wires, twisted pairs (shielded or unshielded), ribbon cable, or coax?
- If shields are used, should they be grounded at one end, both ends, or hybrid grounded?
- Another important consideration is can or will some form of isolation or filtering be used?
- For example, can the signal be transformer or optically coupled to the cable?
- Filters and common-mode chokes can also be used to treat the I/O signals and to minimize the noise coupling.

Grounding Strategies

 


Figure 4-56—NEC-compliant equipment grounding for basic fault/personnel protection subsystem

Meets safety requirement but impedance may be too high for acceptable unit-to-unit "ground" potential variation

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

Grounding Strategies

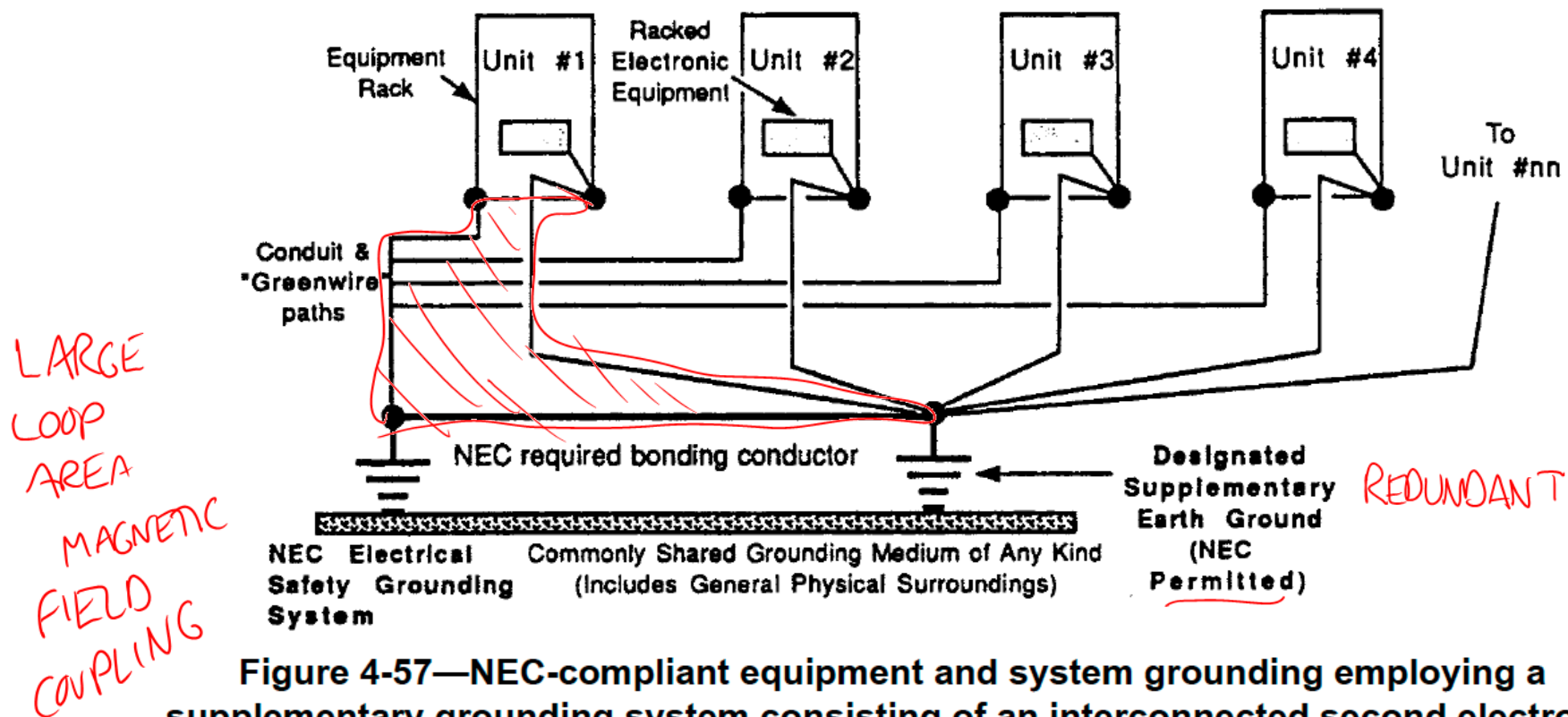


Figure 4-57—NEC-compliant equipment and system grounding employing a supplementary grounding system consisting of an interconnected second electrode at its associated grounding conductors

Figure 4-57 shows an electronic system to which a supplementary grounding system has been attached. Developed from Figure 4-56 by adding supplementary grounding conductors and related earth ground. NEC-compliant, but is likely to also be electrically “noisy.”

Also poor EMC practice because of the cabinet penetration by the supplementary grounding conductors.

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

Grounding Strategies

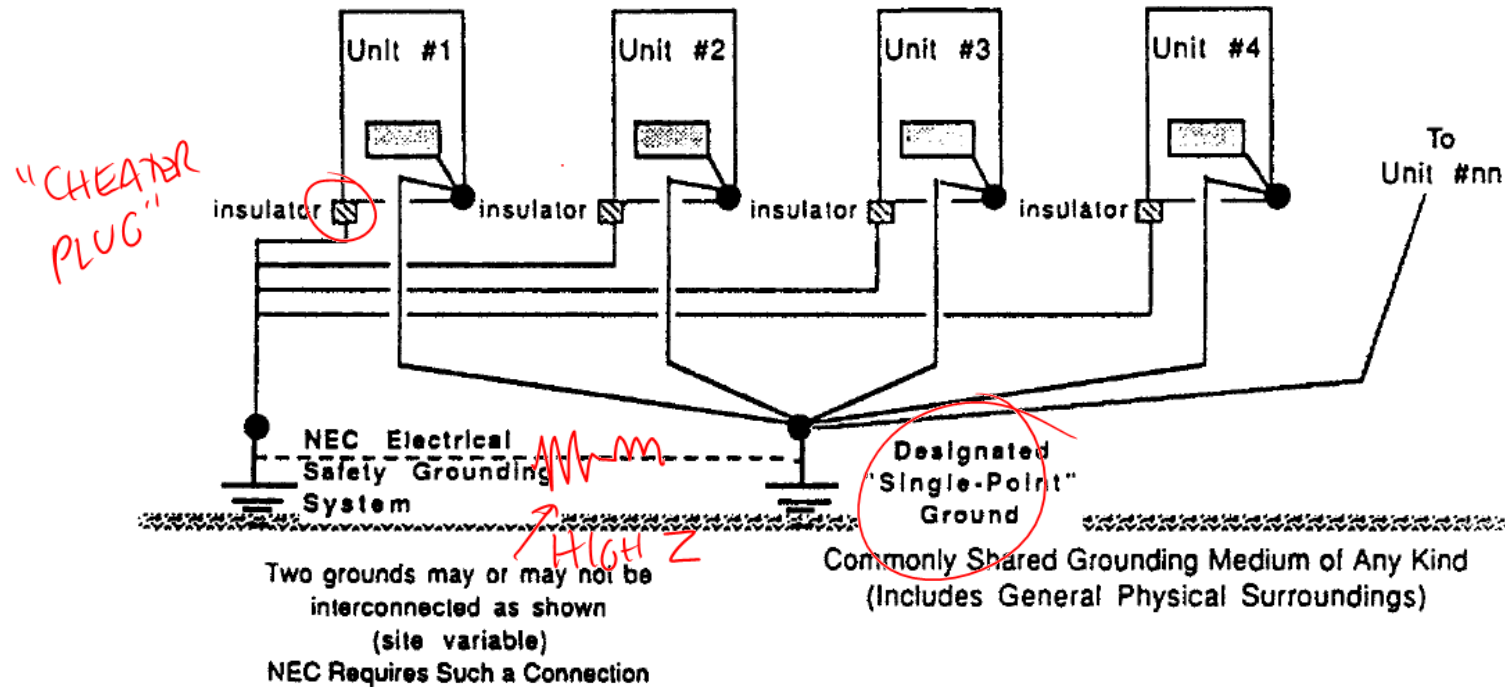


Figure 4-58—Non-NEC-compliant general configuration of an SPG design used with equipment being powered from building ac supply

X DON'T DO THIS

Figure 4-58 shows unsafe modification using “cheater plugs” to obtain a single point ground configuration. Does not meet NEC requirements due to broken equipment grounding paths in branch circuits at the point of connection to the load equipment.

Vulnerable to lightning and ground-fault current damage and is generally “noisy” as well.

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

"Zero Signal Reference Plane" (ZSRP)

 


Figure 3-26: A ZSRP is the optimum way to provide a low-impedance ground connection between individual equipment enclosures that is effective over the widest frequency range

Much more in text section 3.3

Grounding Strategies

DON'T ALWAYS NEED EXPENSE OF SRS/ZSRP
SOLVE WITH BLOCK-BLOCK SIGNALING TECHNIQUES

The need for a signal reference structure (SRS) is minimal when **all of the inter-unit signal-level and telecommunication circuits are interfaced to the associated electronic equipment via optically or isolation transformer coupled means**, and where these interfaces have good common-mode voltage breakdown characteristics.

However, the need for an SRS may easily rise to that of a requirement in the event any of the following three conditions are established:

- 1) When the logic ac-dc power supplies used in the associated electronic equipment are installed with one of the terminals (e.g., the “common”) connected to the equipment’s metal frame/enclosure. This is typical and recommended practice in the commercial ITE and electrical business equipment industries, and others as well.
- 2) When the signal-level circuits and logic ac-dc power supply common terminals are OEM dielectrically insulated or galvanically isolated from equipment ground against recommended practice, and are instead connected to an insulated “ground” terminal that is intended for connection to an externally installed signal ground reference circuit.
- 3) There are actual performance problems occurring with the equipment, which can be assigned to common-mode electrical noise or similar common-mode interference related to the equipment’s existing grounding system, whatever its design, or to the signal-level inter-unit cabling system.

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

"Single Point Ground" Impedance Issue

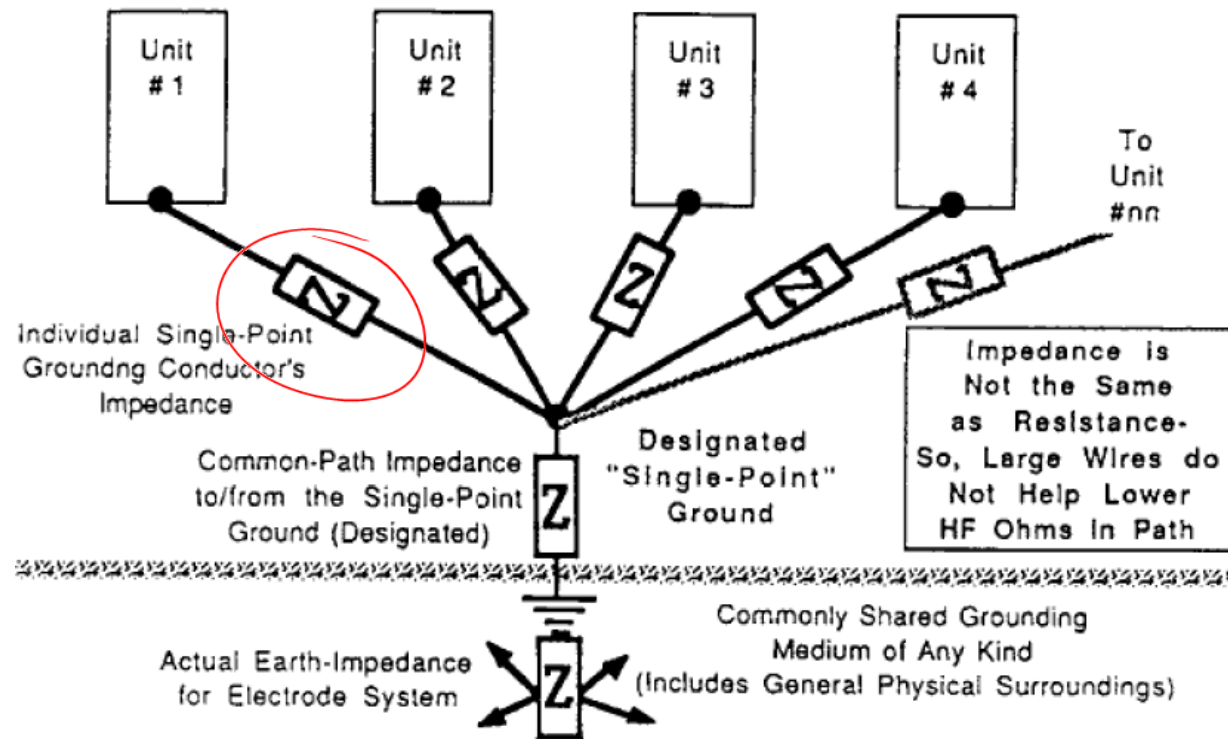


Figure 4-63—Typical $Z = R \pm jX$ impedance values

Meets safety requirement but impedance may be too high for acceptable unit-to-unit "ground" potential variation

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

Grounding Strategies

Items to be collectively referenced to a designated ground reference point via the broadband multi-point method

 


Figure 4-64—Recommended practice (simplified diagram) for dc—high-frequency grounding of electronic systems powered from building ac power system

Low impedance paths for current at both low and high frequencies

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

Much better impedance over frequency performance:

 


Figure 4-66—Impedance of grounding conductors for a computer system

Decision: Isolate critical signal & return paths to avoid need for ZSRP?

Source: IEEE Std. 1100-2005, available at ieeexplore.ieee.org

Ground Loops

Figure 3-33 shows a system grounded at two different points. Two different ground symbols are shown in the figure to emphasize the fact that the two physically separated ground points are likely to be at different potentials. This configuration has three potential problems, as follows:

1. A difference in ground potential V_G between the two grounds may couple a noise voltage V_N into the circuit as shown in Fig. 3-33. The ground potential is usually the result of other currents flowing through the ground impedance.
2. Any strong magnetic fields can induce a noise voltage into the loop formed by the signal conductors and the ground, which is designated as "ground loop" in Fig. 3-33.
3. The signal current has multiple return paths and may, especially at low-frequency, flow through the ground connection and not return on the signal return conductor.

 


Figure 3-33: A ground loop between two circuits

- All ground loops are not bad, and some ground loops are benign.
- Most actual ground-loop problems occur at low frequency, under 100 kHz, and they are usually associated with sensitive analog circuits, such as audio or instrumentation systems. Classic example: 50/60-Hz hum coupling into an audio system.
- Ground loops are seldom a problem at high frequency, above 100 kHz, or in digital systems.
- Some ground loops are actually helpful, for example, in the case of a cable shield being grounded at both ends in order to provide magnetic field shielding (see text section 2.5)

If ground loops are a problem, then they can be dealt with in one of three ways as follows:

1. Avoid them by using single-point or hybrid grounds. This technique is usually only effective at low frequencies, and often it makes the situation worse when attempted at high frequency.
2. Tolerate them by minimizing ground impedance (e.g., by using a ZSRP) and/or by increasing the circuit noise margin (e.g., by increasing the signal voltage level or by using a balanced circuit).
3. Break them by using one of the techniques discussed below.

The ground loop shown in Fig. 3-33 can be broken by one of the following:

1. Transformers
2. Common-mode chokes
3. Optical couplers

 


Figure 3-34: A transformer used to break a ground loop ground between two circuits

INHERENTLY DIFFERENTIAL

IF DC CONTINUITY NOT NEEDED

 


Figure 3-36: A common-mode choke used to break the ground loop between two circuits

PRESENTS HIGH IMPEDANCE TO COMMON MODE V_G

DIFFERENTIAL V_1, V_2 SAME

 


Figure 3-37: An optical coupler used to break the ground loop between two circuits

NO PATH FOR V_G TO CAUSE CURRENT
 GREAT FOR DIGITAL
 HARDER FOR ACCURATE ANALOG

 


Figure 3-38: A balanced circuit can be used to cancel out the effect of a ground loop

CANCELLATION NEVER PERFECT

MATCHING CAN USUALLY BE MADE GOOD ENOUGH

SUBTRACTED OUT

Common-Mode Choke (Low Frequency)

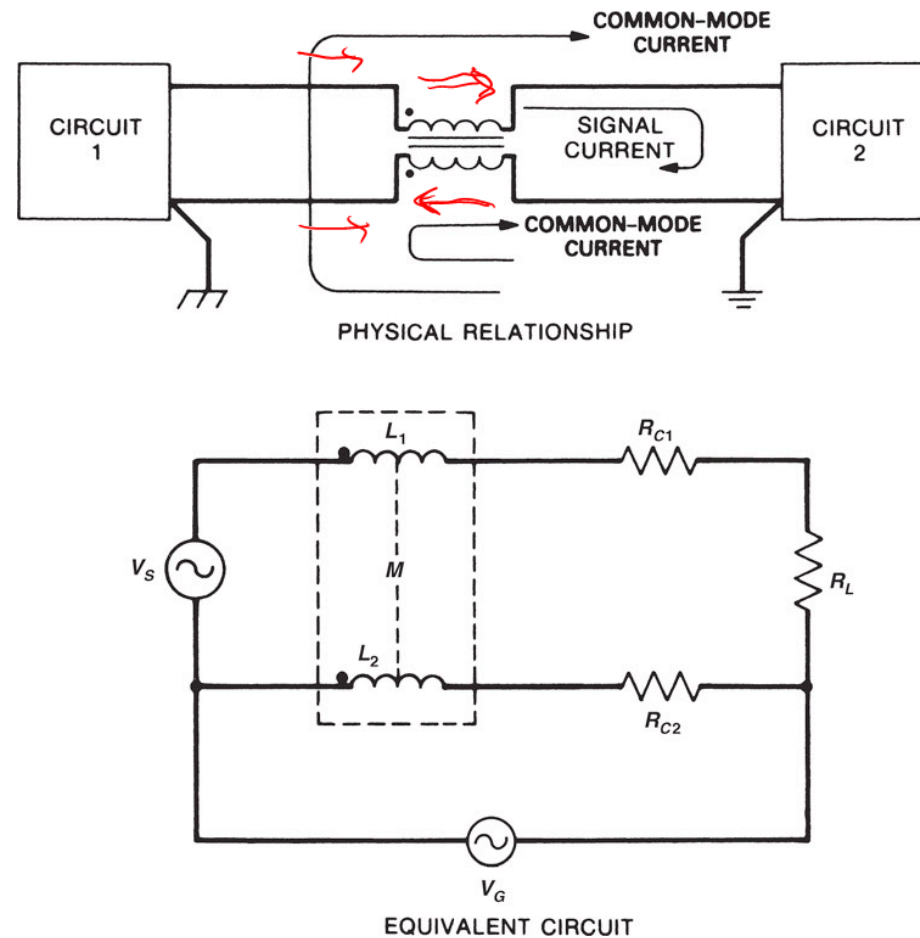


Figure 3-39: When dc or low-frequency continuity is required, a common-mode choke can be used to break a ground loop

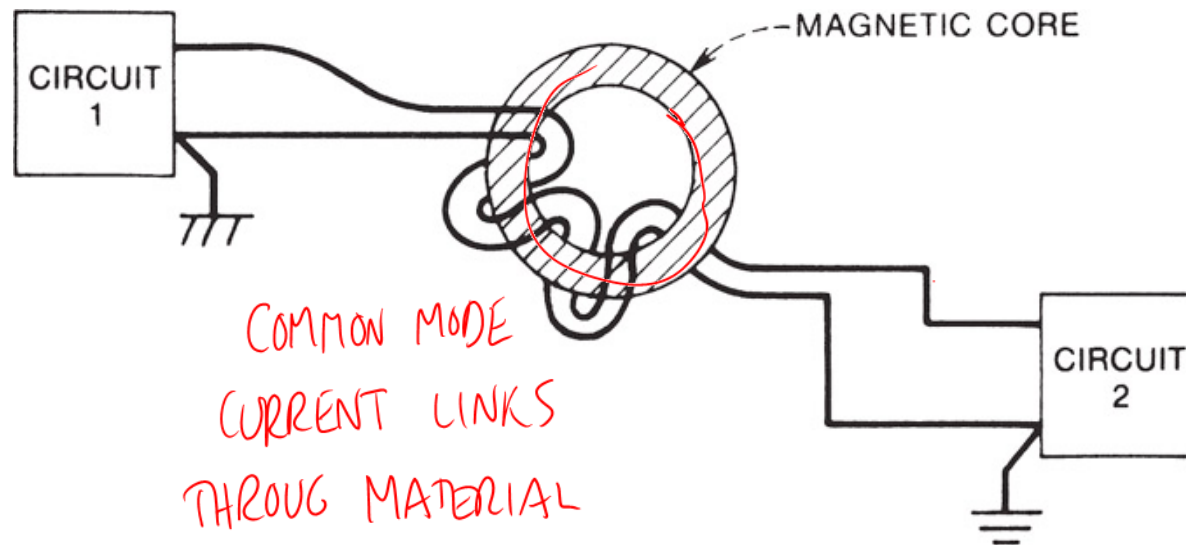


Figure 3-43: An easy way to place a common-mode choke in the circuit is to wind both conductors around a torodial magnetic core. A coaxial cable may also be used in place of the conductors shown



Common-Mode Choke (High Frequency)

PARASITIC CAPACITIVE COUPLING
LOW Z PATH FROM V_{cm} TO LOAD


 


Figure 3-44: Equivalent circuit of a common-mode choke with parasitic shunt capacitance C_s

 The presence of the parasitic capacitance severely limits the maximum insertion loss possible at high frequencies.



Summary: Grounding

- All conductors have finite impedance, which consists of both resistance and inductance.
- A ground conductor longer than $1/20$ wavelength is not a low impedance.
- Grounds fall into two categories, safety grounds and signal grounds.
- The ac power ground is of little practical value as a signal ground.
- The earth is not a low impedance and is polluted with noisy power currents; not equipotential.
- Make connections to earth ground only when required for safety.
- Do not look to an earth ground as a solution to your EMC problems.
- Single-point grounds should only be used at low frequencies, typically below 100 kHz.
- Use multipoint grounds at high frequencies, typically above 100 kHz, and with digital circuits.
- One purpose of a good ground system is to minimize the noise voltage produced when two or more ground currents flow through a common ground impedance.
- The best way to make a low-impedance ground connection over the widest range of frequencies, between separate pieces of equipment, is by connecting them with a plane or grid.
- To minimize ground noise voltage,
 - At low-frequency, control the ground topology (direct the current).
 - At high-frequency, control the ground impedance.
- Ground loops can be controlled by:
 - Avoiding them
 - Tolerating them
 - Breaking them
- Three common ways to break a ground loop are:
 - Isolation transformers
 - Common-mode chokes
 - Optical couplers

Analog Power Supply Decoupling and Routing

 


Figure 4-14: A dc power distribution system as it might appear on schematic

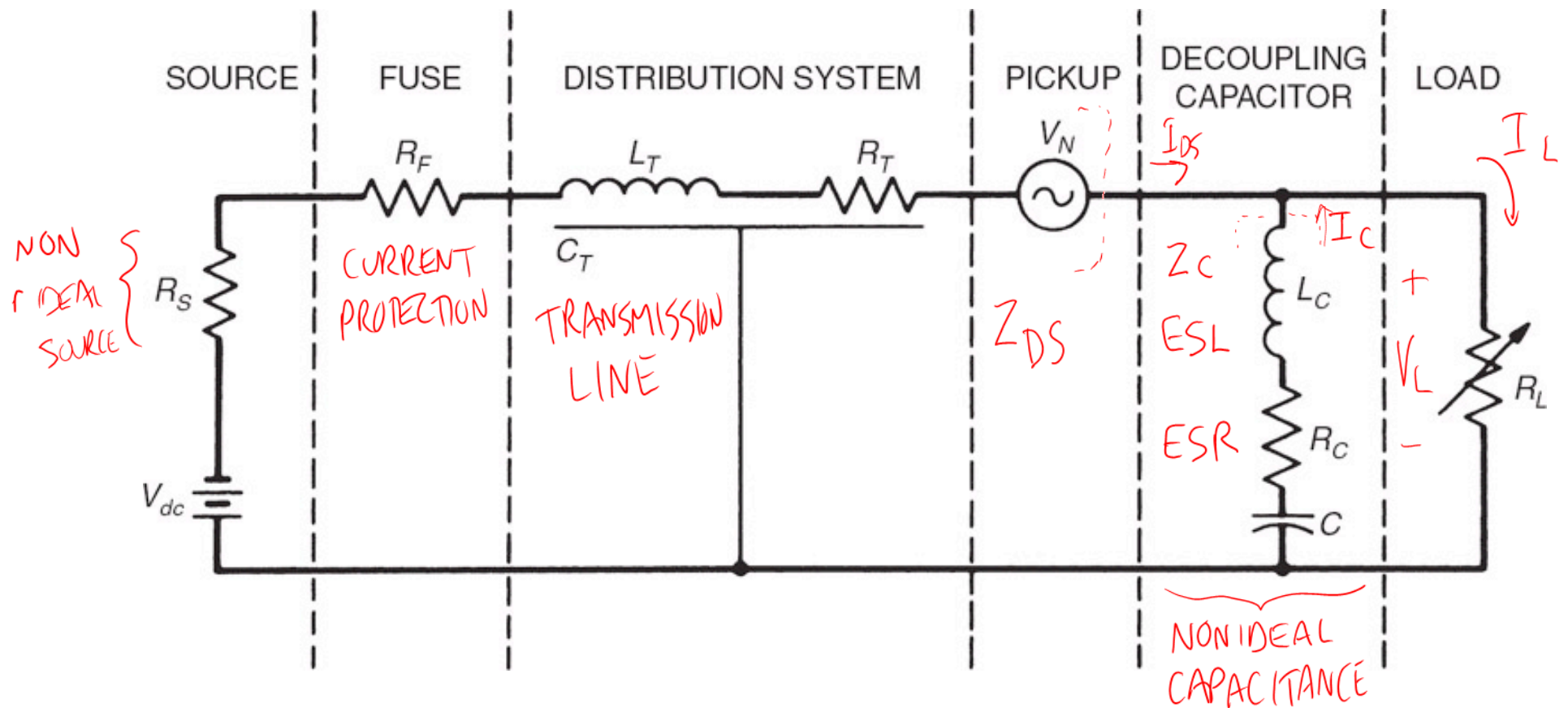


Figure 4-15: The actual circuit for a dc power distribution system, including parasitics

WHAT HAPPENS TO (IDEALLY CONSTANT) V_L AS A FUNCTION OF I_L
 TRANSIENTS: WANT: $|Z_C| \ll |Z_{DS}|$


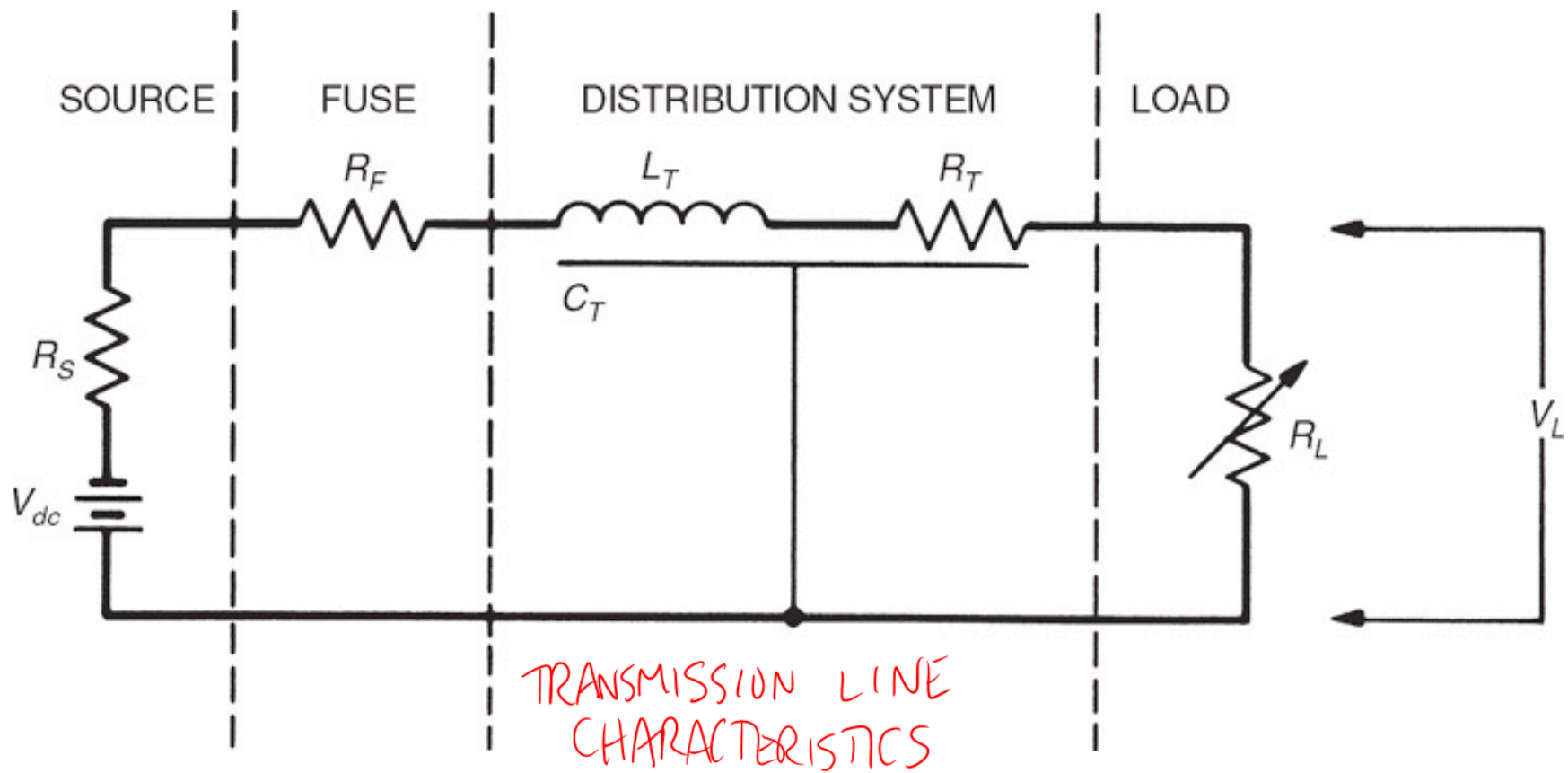


Figure 4-16: Circuit of Fig. 4-15, less the decoupling capacitor and noise pickup voltage

SYST
CABLING


PARALLEL WIRES

 

$$Z_0 = \frac{120}{\sqrt{\epsilon_r}} \cosh^{-1} \left(\frac{D}{d} \right)$$

$$\text{FOR } D/d \geq 3, Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln \left(\frac{2D}{d} \right)$$


WIRE OVER GROUND

 

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \cosh^{-1} \left(\frac{2h}{d} \right)$$

$$\text{FOR } 2h/d \geq 3, Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \left(\frac{4h}{d} \right)$$


PARALLEL FLAT CONDUCTORS

 

$$\text{FOR } w \gg h \text{ and } h \gg t, Z_0 = \frac{377}{\sqrt{\epsilon_r}} \left(\frac{h}{w} \right)$$


PCB

FLAT CONDUCTOR OVER GROUND PLANE

 

$$\text{FOR } w \gg h, Z_0 = \frac{377}{\sqrt{\epsilon_r}} \left(\frac{h}{w} \right)$$

FLAT CONDUCTORS SIDE BY SIDE

 

$$\text{FOR } w \gg t, Z_0 = \frac{120}{\sqrt{\epsilon_r}} \ln \left(\frac{\pi(h+w)}{w+t} \right)$$

Table 4-3: Relative Dielectric Constants of Various Materials

Material	ϵ_r
Air	1
Styrofoam	1.03
Polyethylene foam	1.6
Cellular polyethylene	1.8
Teflon _[a]	2.1
Polyethylene	2.3
Polystyrene	2.5
Nylon	3
Silicone rubber	3.1
Polyester	3.2
Polyvinylchloride	3.5
Epoxy resin	3.6
Delrin TM	3.7
Getek _[a]	3.9
Epoxy glass	4.5
Mylar _[b]	5
Polyurethane	7
Glass	7.5
Ceramic	9

Figure 4-17: Characteristic impedance for various conductor configurations

One Minute Quiz:

DC power is distributed on a 0.1" trace of 1oz. copper on an epoxy resin PCB, 0.032" above a solid ground plane.

What is the characteristic impedance?


How wide should the trace be for an impedance of 5Ω ?

$$Z = \frac{377\Omega}{\sqrt{3.6}} \frac{0.032}{0.1} = 63\Omega$$

FOR 5Ω : DESIGN



$$5\Omega = \frac{377\Omega}{\sqrt{3.6}} \frac{0.032}{W} \Rightarrow W = 1.2"$$

 LOW Z WIDE TRACE $W \uparrow$
CLOSE TO
GND RETURN $h \downarrow$



POWER SUPPLY REJECTION RATIO PSRR

OP-AMP (EXAMPLE)

  


BAND AT HIGH FREQ

$$PSRR = \frac{A_{PS}}{A_{OL}} \rightarrow 0$$

Coupling through power supply distribution networks

Between subcircuits

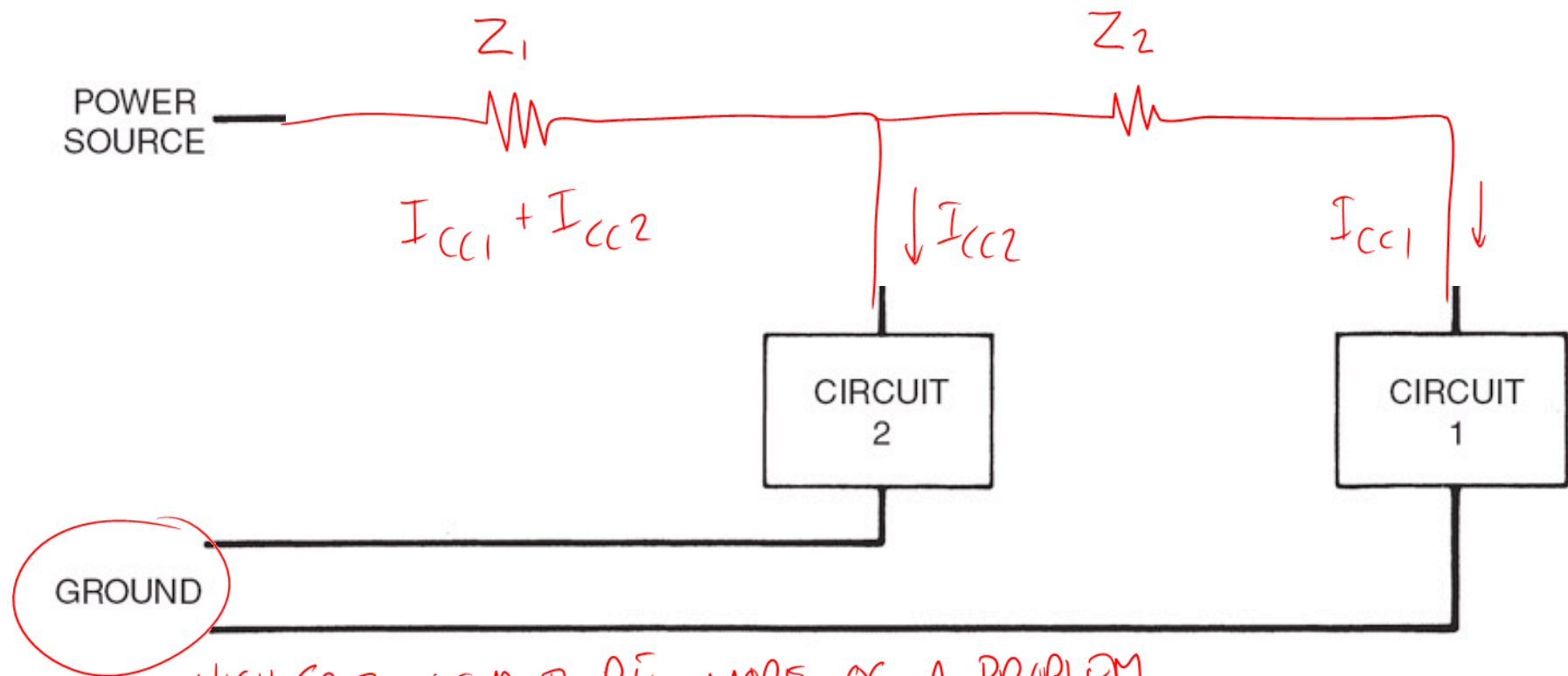
COMMON IMPEDANCE COUPLING: CHANGES SUPPLY V



HIGH FREQ TEND TO BE MORE OF A PROBLEM

① $|Z_1|$ INCREASES (INDUCTIVE)

② PSRR WORSE AT HIGH FREQ

 

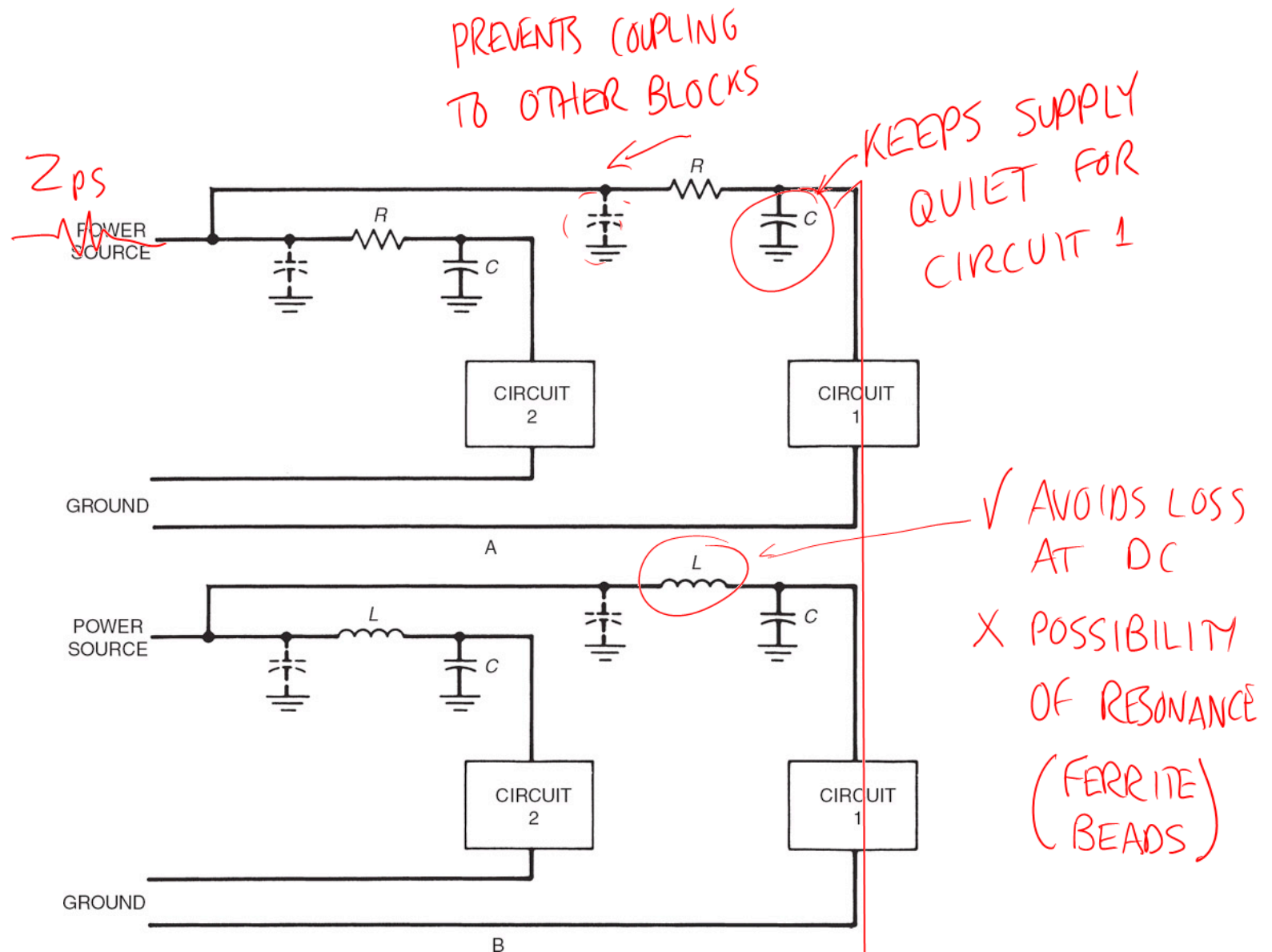


Figure 4-18: Circuit decoupling with (A) resistance-capacitance and (B) inductance-capacitance networks

Coupling through power supply distribution networks: Within subcircuits

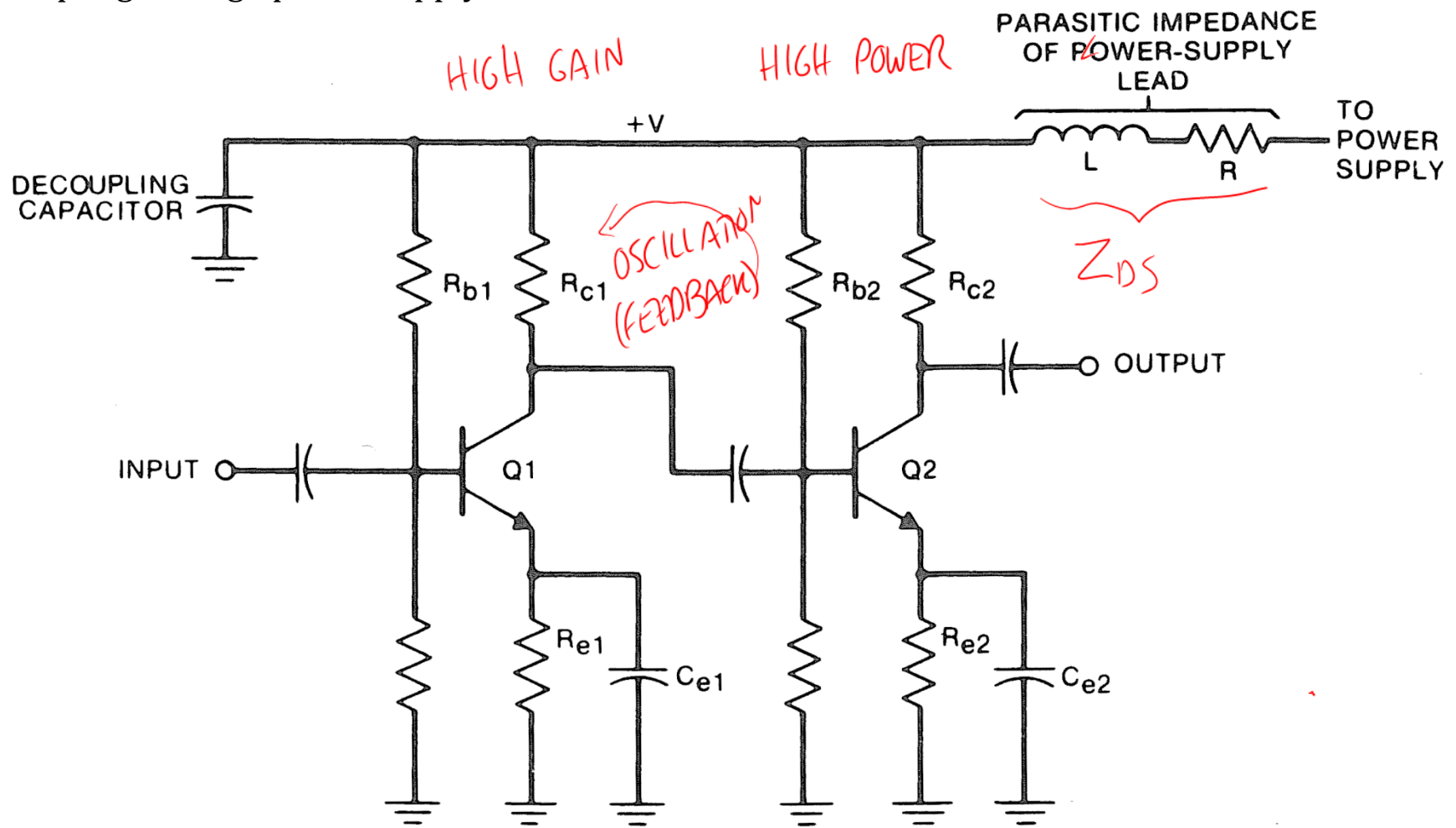


Figure 4-20: Power supply decoupling for a two-stage amplifier

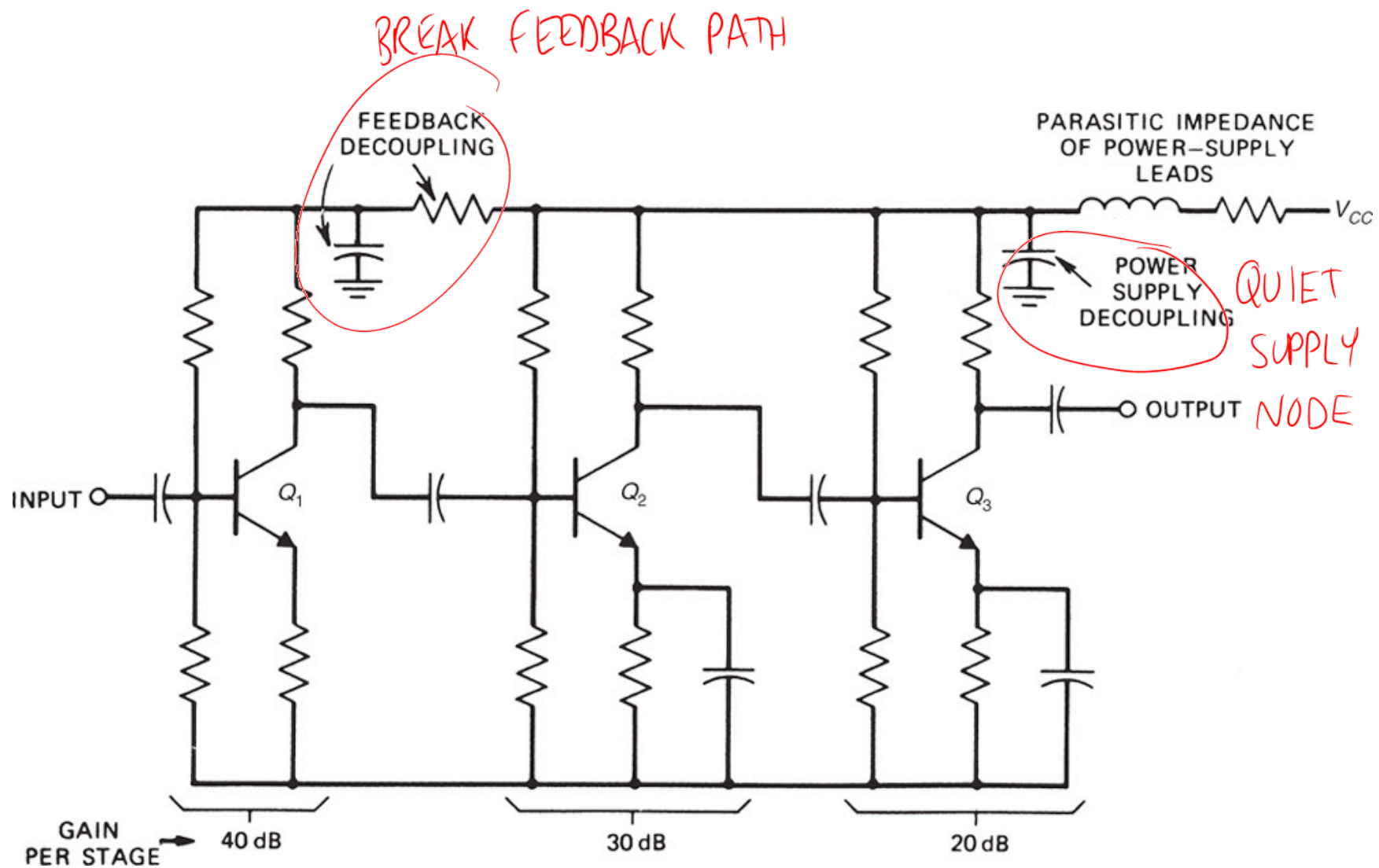


Figure 4-23: Power supply feedback decoupling between stages of an amplifier

Caution: Energy storage in inductance vs. loss in resistance

 


Figure 4-19: Effect of damping factor on filter response

FEEDTHROUGH
CAPACITORS

INCREASED
FILTERING
EFFECTIVENESS

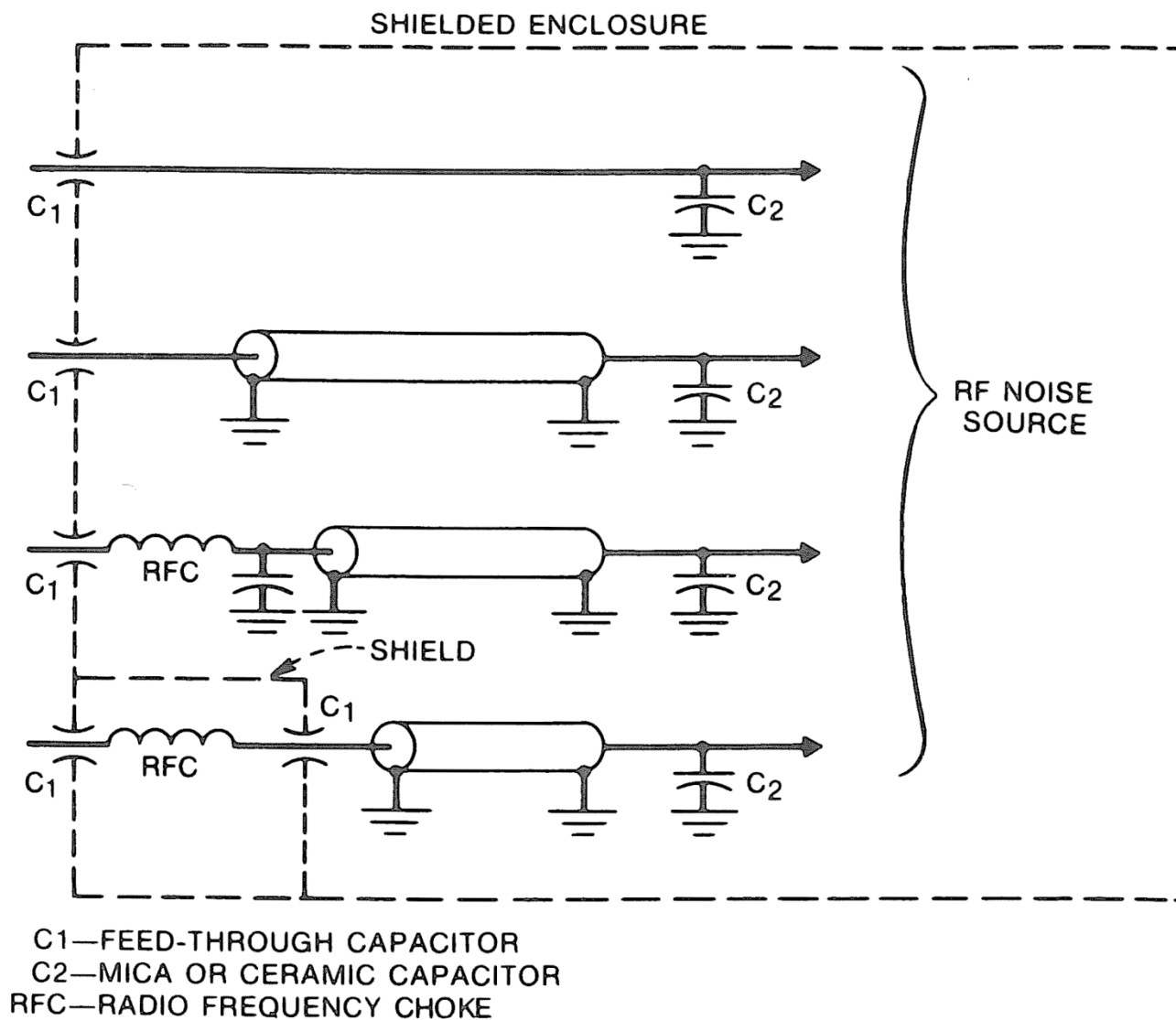


Figure 4-18. Various high-frequency lead-filtering methods. Effectiveness increases from top toward bottom.

Summary: Analog Power Supply Decoupling and Routing


- The lower the characteristic impedance of a dc power distribution circuit, the less the noise coupling over it.
- Because many dc power distribution systems do not provide a low impedance, decoupling capacitors should be used at each load.
- From a noise point of view, a dissipative filter is preferred to a reactive filter.
- Some amplifier circuits will oscillate when driving a capacitive load, unless properly compensated and/or decoupled.
- To minimize noise, the bandwidth of a system should be no more than that necessary to transmit the desired signal.

Parallel Plate EM Fields

- Electric field demonstration relatively easy
 - Rub a balloon on your sweater, stick it to a wall
 - See lightning, spark after shuffling across carpet
 - Opposite charges attract
 - E field tells you which way charges move (force acting on charge)
- Magnetic field
 - ???
 - Try a different way to look at things...

(Acknowledgment: Paul Brokaw, Analog Devices)


Cause and Effect: Ohm's Law

 


$$V = I R$$

- Which is cause, which is effect?
- V cause, I effect?
- I cause, V effect?

Chemistry vs. Electrical Engineering

 

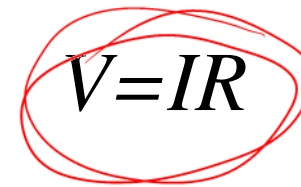 
 

$$V=IR$$

Cause

Effect

- No arrow!
- V, I just "go together"
- View either as cause, effect
- Whatever is best for your purpose

You're the cause



V , I go together - Resistor doesn't care

What causes magnetic field?



- Usual answer: current
 - Usually introduced in terms of current in a wire creating an associated magnetic field
 - Physics (force-based) approach
- Think about it another way ...
 - Better way for circuit designers
 - What effect is field describing?
- Look at capacitance, inductance

Capacitance

- Represents energy stored in electric field
- Capacitor voltage can't change instantaneously
- Time delay required to “build up” energy in field
- C tells you how much V results from applied A-sec

$$I_C = C \frac{dV_C}{dt}$$
  
$$\Rightarrow V_C = \frac{1}{C} \underbrace{\int I_C dt}_{\substack{\text{A} \cdot \text{sec} \\ Q}}$$





Inductance

- Represents energy stored in magnetic field
- Inductor current can't change instantaneously
- Time delay required to “build up” energy in field
- L tells you how much I results from applied V-sec

$$V_L = L \frac{dI_L}{dt}$$
  
$$\Rightarrow I_L = \frac{1}{L} \underbrace{\int V_L dt}_{V \cdot \text{sec}}$$



Different Approach to Magnetic Field

- Electric Field
 - Represented by capacitance
 - Voltage is result; cause is applied A-sec (charge)
- Magnetic Field
 - Represented by inductance
 - **Current is result; cause is applied V-sec**



Units of magnetic flux density

- Magnetic flux density B

$$[tesla] = \left[\frac{V \cdot \text{sec}}{m^2} \right]$$

Meaning

  - Apply 1V for 1sec to loop with area of 1m² (cause)
- Result is B field of 1 tesla (effect)
- What about current???



What about current?

- Observed that resulting current for a given V-sec/m² depends on material in which field lines exist
- Described with permeability μ , magnetic field H:

$$\vec{H} = \left(\frac{1}{\mu} \right) \vec{B}$$

- H gives current through Ampere's law

$$I_{encl} = \oint \vec{H} \cdot d\vec{\ell}$$

- Units: H must have units [A/m]
⇒ Permeability μ will have units [Hy/m]
- Hint: μ will be involved in value of inductance!



Units of electric flux density

- Electric flux density D

$$\left[\frac{\text{coul}}{\text{m}^2} \right] = \left[\frac{\text{A} \cdot \text{sec}}{\text{m}^2} \right]$$

Meaning

  - Apply 1A for 1sec to capacitor plates with area of 1m^2 (cause)
- Result is D flux of $1 \text{ A} \cdot \text{sec}/\text{m}^2$ (effect)
- What about voltage?



What about voltage?

- Observed that resulting voltage for a given A-sec/m² depends on material in which field lines exist
- Described with permittivity ϵ , electric field E :

$$\vec{E} = \left(\frac{1}{\epsilon}\right) \vec{D}$$


- E gives voltage through path integral

$$V_{ab} = \int_a^b \vec{E} \cdot d\vec{\ell}$$

- Units: E must have units [V/m]
 \Rightarrow Permittivity ϵ will have units [F/m]
- Hint: ϵ will be involved in value of capacitance!

Parallel Plate Electromagnetics


 
- Area = 1m^2 a little large for our purposes ...
- Use geometry suited to PCB design: parallel plates
- Determine inductance, capacitance
- Assumption: Field density negligible outside volume enclosed by plates



Magnetic Field / Inductance

Procedure:

  - B from V-sec, area perpendicular to field lines
- H from μ , B
- Current I from H , path integral
- Inductance from definition of L



Magnetic Field / Inductance

B from V-sec, geometry

$$B = \frac{V_L \cdot t}{\ell \cdot h}$$

H from μ , B



$$H = \left(\frac{1}{\mu} \right) B = \frac{V_L \cdot t}{\mu \cdot \ell \cdot h}$$

Path integral

$$I = \oint \vec{H} \cdot d\vec{\ell} = \frac{w \cdot V_L \cdot t}{\mu \cdot \ell \cdot h} \quad \text{SHORT}$$

Inductance

 
 
$$I = \left(\frac{1}{L}\right) \int V_L dt \Rightarrow L = \underbrace{\mu}_{\text{MATERIAL}} \underbrace{\frac{\ell \cdot h}{w}}_{\text{GEOMETRY}} \quad \mathbf{V}$$



Electric Field / Capacitance

Procedure:

  - D from A-sec, area perpendicular to field lines
- E from ϵ , D
- Voltage V from E , path integral
- Capacitance from definition of C



Electric Field / Capacitance

D from A-sec, geometry

$$D = \frac{I_C \cdot t}{\ell \cdot w}$$

E from ϵ , D

$$H = \left(\frac{1}{\epsilon}\right) D = \frac{I_C \cdot t}{\epsilon \cdot \ell \cdot w}$$




Path integral

$$V = \int \vec{E} \cdot d\vec{\ell} = \frac{h \cdot I_C \cdot t}{\epsilon \cdot \ell \cdot w}$$

Capacitance

$$V = \left(\frac{1}{C}\right) \int I_C dt \Rightarrow C = \epsilon \frac{\ell \cdot w}{h}$$

A
SEPARATION

   

MINIMIZE CAP
(REDUCE COUPLING)

$\ell, w \downarrow$ $h \uparrow$
SMALL FAR AWAY

MAXIMIZE CAP
(LOWER Z_{SD})


$\ell, w \uparrow$ $h \downarrow$
BIG CLOSE

Parallel Plate Summary

- PCB trace: Energy in both electric, magnetic fields

$$C = \epsilon \frac{\ell \cdot w}{h}$$


$$L = \mu \frac{\ell \cdot h}{w}$$

 


Transmission Line Impedance

- Lumped L, C model (limit as segment length $\rightarrow 0$)

$$Z = j\omega L + \left(\frac{1}{j\omega C} \right) \Big| Z \Rightarrow Z = \sqrt{\frac{L}{C}} = \sqrt{\left(\mu \frac{\ell h}{w} \right) \left(\frac{1}{\epsilon} \frac{h}{\ell w} \right)} = \frac{h}{w} \sqrt{\frac{\mu}{\epsilon}}$$

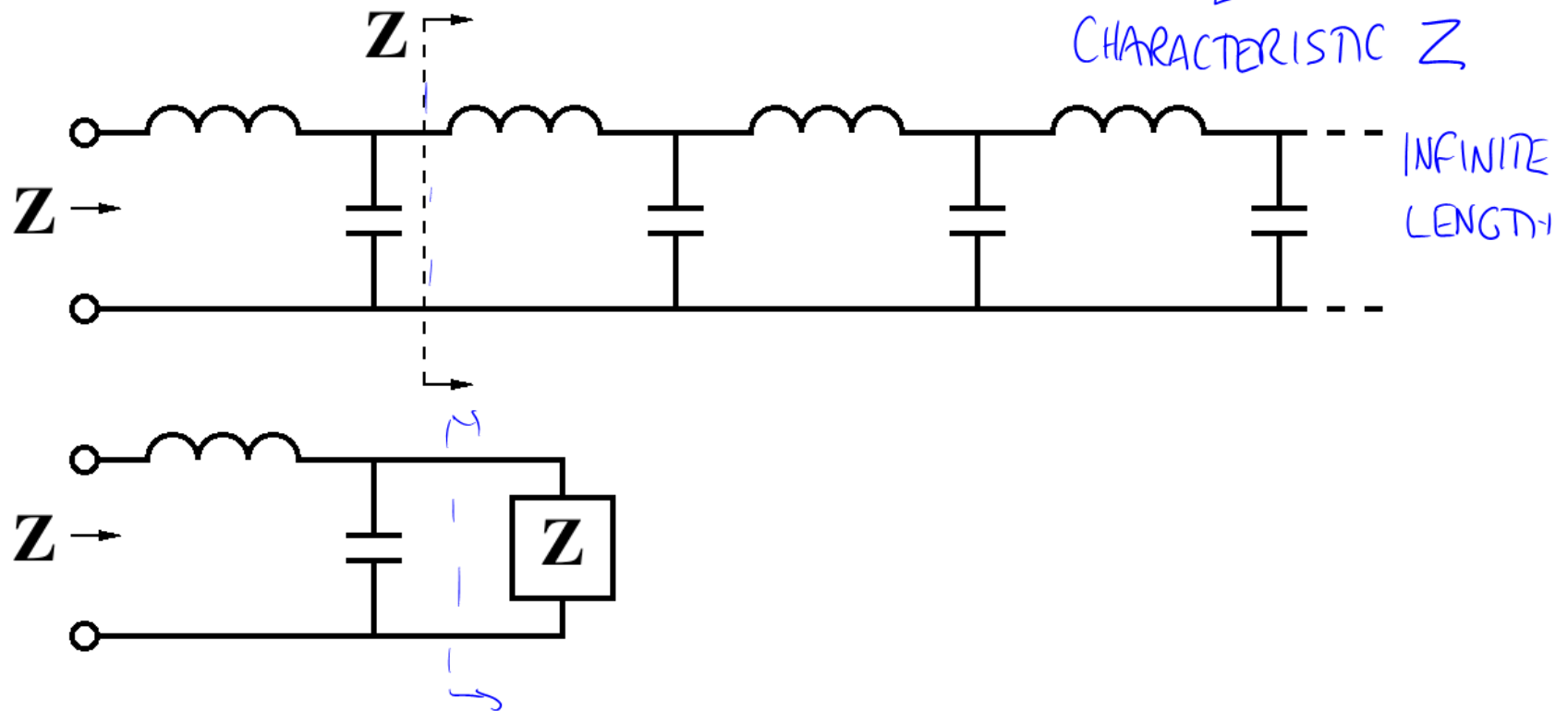

Qualitative interpretation

 

$$Z = \underbrace{\frac{h}{w}}_{\text{GEOMETRY}} \underbrace{\sqrt{\frac{\mu}{\epsilon}}}_{\text{MATERIAL}}$$

Low impedance

- Wide, close to return path (supply distribution)
- High current (energy in magnetic field)

High impedance

- Narrow, far from return (low power signal)
- Low current (energy in electric field)

Summary: Parallel Plate Electromagnetics

- Electric Field
Represented by capacitance
Voltage is result; cause is applied A-sec (charge)
- Magnetic Field
Represented by inductance
Current is result; cause is applied V-sec
- To minimize energy stored (and potentially coupled into and/or radiated from) magnetic field:
Always think of current return path; provide easy (low energy, low inductance) return
Minimize area of loop for current return
Maximize width of current path for low impedance

Ideal vs. Real Components:

Capacitor

Inductor

Transformer

Resistor

Conductor

Transmission Lines

Ferrite Beads

Capacitors


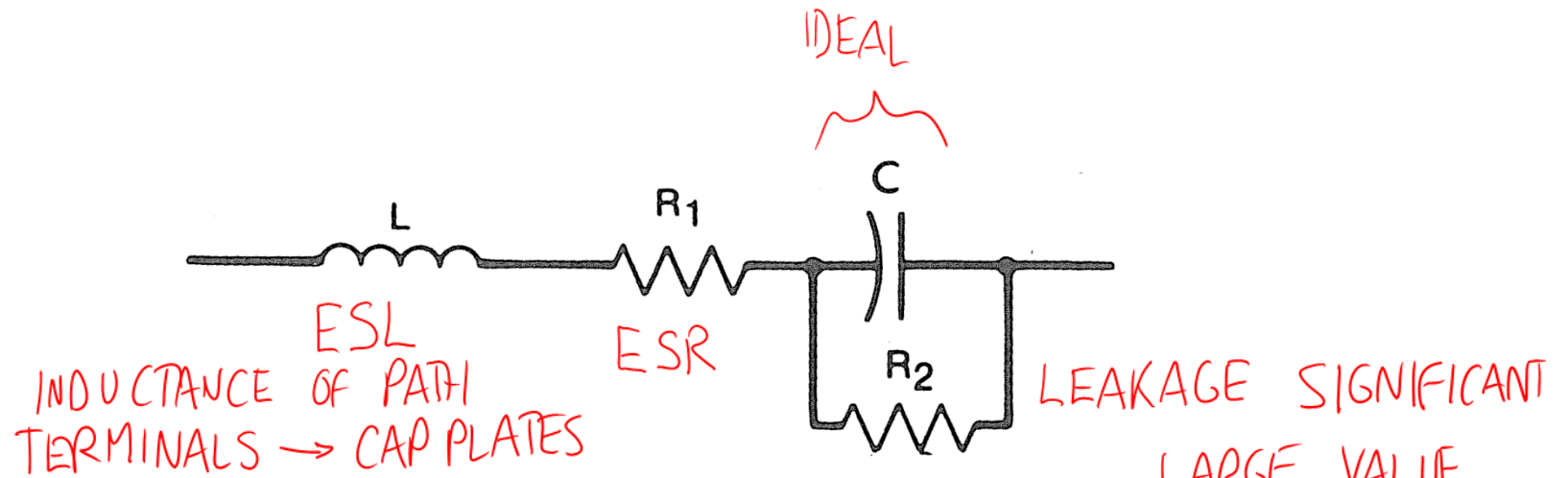


Figure 5-1. Equivalent circuit for a capacitor.

IDEAL $|Z|$
 $|Z_c| = \frac{1}{\omega C}$

 

$|Z|$ INDUCTIVE!?

Figure 5-2. Effect of frequency on the impedance of a $0.1 \mu F$ paper capacitor.

 


Figure 5-3: Approximate usable frequency ranges for various types of capacitors

Multilayer Ceramic Capacitor (MLCC)

 


Figure 5-5: Multilayer ceramic capacitor construction

Advantage: Increase C , decrease L

Values up to $10\mu\text{F}$ – $100\mu\text{F}$, depending on rated voltage

**LOWER $V \Rightarrow$ THINNER DIELECTRIC
 \Rightarrow MORE C / VOLUME**

Film Capacitor


 


Figure 5-4. *Band on tubular capacitor indicates the end that is connected to the outside foil. This end should be connected to ground.*

 

Feedthrough Capacitor

 


Figure 5-6: Typical feed-through capacitor

 


Figure 5-7: Lead inductance in standard and feed-through capacitors

 



Figure 5-8: Impedance of 0.05- μ F capacitors, showing improved performance of feed-through capacitor

Table 5-2: Self-Resonant Frequencies of Ceramic Capacitors

Capacitance Value (pf)	Self-Resonant Frequency	
	1/4-in Leads	1/2-in Leads
10,000	12	" - "
1000	35	32
500	70	65
100	150	120
50	220	200
10	500	350

Inductors

SHUNT CAPACITANCE

 

LOSS MECHANISMS

- COPPER RES
- LOSSES IN CORE MATERIAL

Figure 5-9: Equivalent circuit for an inductor

IDEAL (DOMINATES AT LOW f)

WORSE FOR
RADIATING
MAG FIELD
(ALSO PICKUP)

 
 


Figure 5-10: Magnetic fields from (A) air core and (B) closed magnetic core inductors

Transformers

 


Figure 5-11: An actual transformer has capacitive as well as magnetic coupling between primary and secondary windings

 


Figure 5-12: Grounded electrostatic shield between transformer windings breaks capacitive coupling

 


Figure 5-13: Two unshielded transformers can provide electrostatic shielding

 


Figure 5-14: Equivalent circuit for a resistor

Table 5-3 Impedance of a 1-M Ω , $\frac{1}{2}$ -W Carbon Resistor Measured at Various Frequencies

Frequency (kHz)	Impedance	
	Magnitude (k Ω)	Phase Angle (degrees)
1	1000	0
9	1000	-3
10	990	-3
50	920	-11
100	860	-16
200	750	-23
300	670	-28
400	610	-32
500	560	-34

Another good reason to prefer SM metal film to carbon composition resistors:

 


Figure 5-15: Effect of frequency and current on noise voltage for a 10-kΩ. carbon composition resistor

Conductors

LOWER Z? FATTER WIRE DOESN'T HELP MUCH FOR INDUCTANCE

Table 5-4 Inductance and Resistance of Round Conductors

Wire Size (AWG)	Diameter (in.)	Resistance (mΩ/in.)	Inductance (μH per in.)		
			0.25 in. Above Ground Plane	0.5 in. Above Ground Plane	1 in. Above Ground Plane
26	0.016	3.39	0.021	0.025	0.028
24	0.020	2.13	0.020	0.023	0.027
22	0.025	1.34	0.019	0.022	0.026
20	0.032	0.85	0.017	0.021	0.024
18	0.040	0.53	0.016	0.020	0.023
14	0.064	0.21	0.014	0.017	0.021
10	0.102	0.08	0.012	0.015	0.019

One Minute Quiz

For a 22 AWG wire 0.25" above ground plane, at what frequency does the reactive impedance of the wire inductance $|Z_L|$ equal the DC resistance?

$|Z_L| = R$ BOUNDARY BETWEEN LOW f, HIGH f

DC

RES 1.34 mΩ

$$L = 19 \text{ nH} \quad |Z_L| = \omega L = 2\pi f (19 \text{ nH}) \Rightarrow f = \frac{1.34 \text{ m}\Omega}{2\pi (19 \text{ E-}9 \text{ H})} = 11 \text{ kHz}$$

"HIGH FREQ"


Transmission Lines

- When conductors become long (a significant fraction of the wavelength of the signals on them) they can no longer be represented as a simple *lumped-parameter* series R-L network
- The voltage and current will be different at different points along the conductor.
- Under these circumstances, the signal conductor and its return path must be considered together as a transmission line, and a *distributed-parameter* model of the line must be used.
- A common rule, when working in the frequency domain, is that the conductor should be treated as a transmission line if its length is greater than 1/10 of a wavelength
- In the case of a digital signal, in the time domain, when the signal rise time is less than twice the propagation delay (the reciprocal of the velocity of propagation) of the line.

 Example: Slow, fast logic families


Faster Edge Rates

- Transmission Line Effects
- Rise time \times Propagation velocity $<$ Trace length




Reflection Example

- Clock Distribution Network

 

Reflection Example: $t_r \approx 10\text{ns}$
 
$$\underbrace{(1.0E-8[\text{sec}])}_{\text{RISE TIME}} \cdot \underbrace{(0.7 \cdot (3.0E+10[\text{cm/sec}]))}_{\text{VELOCITY}} = 210\text{cm} > \underbrace{30\text{cm}}_{\text{MAX LENGTH OF TRANSMISSION LINE}}$$




MAX LENGTH
OF TRANSMISSION
LINE

Transmission line effects negligible

Reflection Example: $t_r \approx 200\text{ps}$

$$\underbrace{(2.0E-10[\text{sec}])}_{\text{RISE TIME}} \cdot \underbrace{(0.7 \cdot (3.0E+10[\text{cm/sec}]))}_{\text{VELOCITY}} = 4.2\text{cm} < 30\text{cm}$$

 - Transmission line reflection problems:
 - Multiple clocking
 - Confusion for multilevel signaling (e.g. Rambus®)



Types of transmission lines

CABLE



COAX

PCB



MICROSTRIP



STRIPLINE

CABLE



BALANCED
LINE



WAVEGUIDE

Note that the conductors of a transmission line are just the guides for the electromagnetic energy. The electromagnetic energy is propagated in the dielectric material. In a transmission line, the velocity of propagation v of the electromagnetic energy is equal to

$$v = \frac{c}{\sqrt{\epsilon_r}}, \quad (5-14)$$

} DIELECTRIC CONST

The three most important properties of a transmission line are its characteristic impedance, its propagation constant, and its high-frequency loss.

Lossy transmission line

 


Figure 5-18: Distributed parameter model of a two-conductor transmission line

R, L, G, C PER UNIT LENGTH

Characteristic Impedance:

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$



IN GENERAL, SOME VARIATION
VS. ω DUE TO
 R, G LOSSES (5-15)

IF ~~LOSS~~
(NEGLIGIBLE) $R \rightarrow 0$
 $G \rightarrow 0$

$$Z_0 = \sqrt{\frac{L}{C}}$$

ω INDEPENDENT

Lossless transmission line

  

Propagation along lossy line

 


Figure 5-21: Time domain response of a square wave on a lossy transmission line, showing both amplitude and rise time degradation

CAN COUNTERACT WITH GAIN, EQUALIZATION IN RECEIVER

Ferrites

TYPICAL DIMENSIONS
DIAMETER—.05" TO 0.3"
LENGTH—0.1" TO 0.5"


 


Figure 5-23: (A) Ferrite bead on conductor, (B) high-frequency equivalent circuit, and (C) typical schematic symbol

Ferrites specified by impedance vs. frequency

GREAT FOR
DC SUPPLY
FILTERING

 

$$Z=0$$

AT
DC

HF MODE

 


Figure 5-24: Impedance, resistance, and inductance of a Type 43 ferrite core. (© 2005 Fair-Rite Corp., reproduced with permission)

 


Figure 5-25: Recommended frequency range of various ferrite materials when used in noise suppression applications. (© 2005 Fair-Rite Corp., reproduced with permission)

SPECIFIED BY $|Z|$ AT FREQ / OVER f RANGE
 REACTIVE OR DISSIPATIVE
 NON-LOSSY LOSSY

 


Figure 5-26: Ferrite bead used to form a L-filter to keep high-frequency oscillator noise from the load

 


Figure 5-27: Resistive ferrite bead used to damp out ringing on long interconnection between fast logic gates

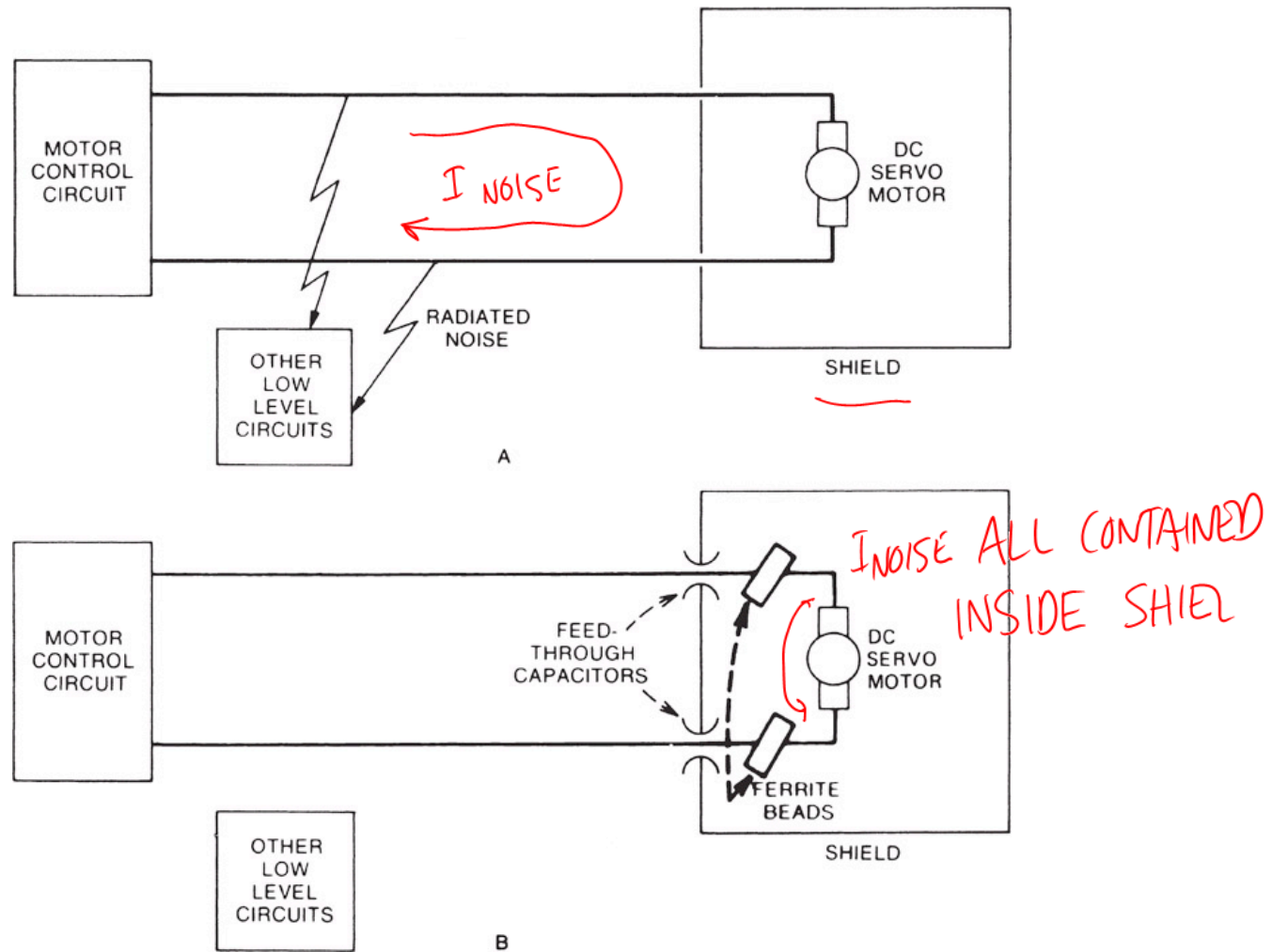


Figure 5-29: (A) High-frequency commutation noise of motor is interfering with low-level circuits, (B) ferrite bead used in conjunction with feed-through capacitors to eliminate interference

 


Figure 5-30: Ferrite beads and feed-through capacitors used to filter commutation noise on dc motor's power leads

Caution: Saturation of ferrite in presence of DC bias

 


Figure 5-31: Impedance versus frequency plot of a ferrite bead as a function of the dc bias current.
(© 2005, Fair-Rite Products Corp., reproduced with permission)

- Ferrite cores are commonly used as CM chokes (sec. 3.5) on multiconductor cables.
- The ferrite core acts as a one-turn transformer or common-mode choke, and can be effective in reducing the conducted and/or radiated emission from the cable, as well as suppressing high-frequency pickup in the cable.
- Figure 5-32 shows a ferrite core on a universal serial bus (USB) cable used to reduce the radiated emission from the cable.
- Snap-on cores (shown in Fig 5-22) can also be applied easily as an after-the-fact fix to cables, even if they have large connectors at the ends.



ONE CORE
WORKS FOR
MULTIPLE
CONDUCTORS
DOES NOT AFFECT
DIFFERENTIAL

Figure 5-32: Ferrite core used on a USB cable to suppress radiated emissions

Summary: Ideal vs. Real Components:

- Capacitors

All capacitors have a self resonant frequency (SRF) and look inductive for frequencies $>$ SRF
Multilayer ceramic capacitors (MLCC) have highest SRF and are least nonideal
- Inductor

Closed core inductors (e.g. toroids) create less external magnetic field
Parasitic capacitance limits frequency range over which inductors behave inductively
- Transformer

Parasitic capacitance also limits effectiveness of transformer isolation
- Resistor

In terms of noise, metal film resistors are more nearly ideal than carbon composition
- Conductor

Above audio frequencies, a conductor has more inductive reactance than resistance.
Flat rectangular conductor will have less ac resistance and inductance than a round shape.
- Transmission Lines

Important when conductor length is longer than $1/10$ wavelength
- Ferrite Beads

When used for noise suppression, ferrites are used in the frequency range where their impedance is resistive.
Ferrites couple ac resistance (loss) into a circuit with little or no low-frequency impedance.
Ferrites are normally characterized by specifying their impedance versus frequency.

Analog and Digital Circuit Grounding Issues

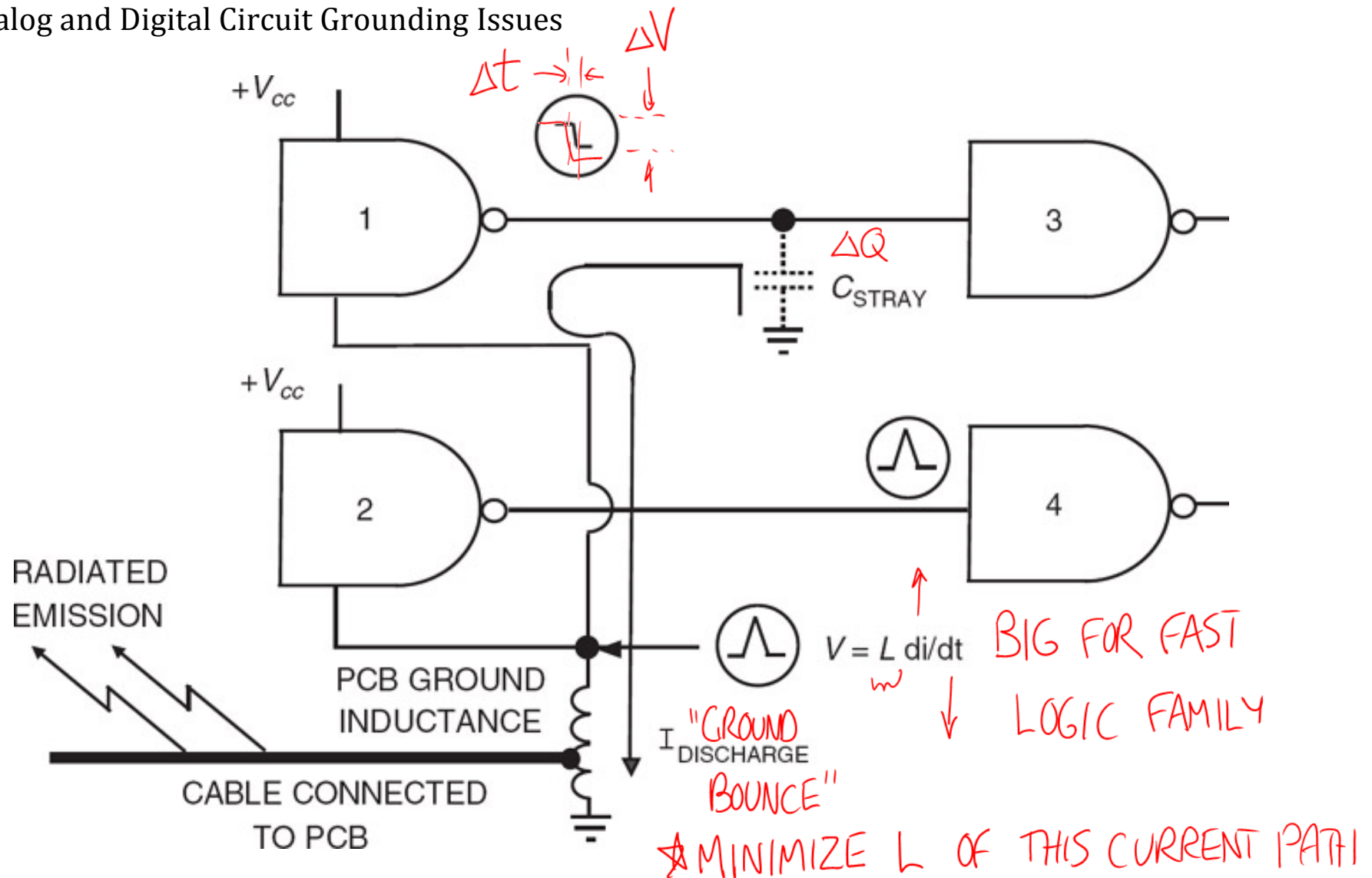


Figure 10-1: Ground noise is created when output of gate 1 switches from high to low


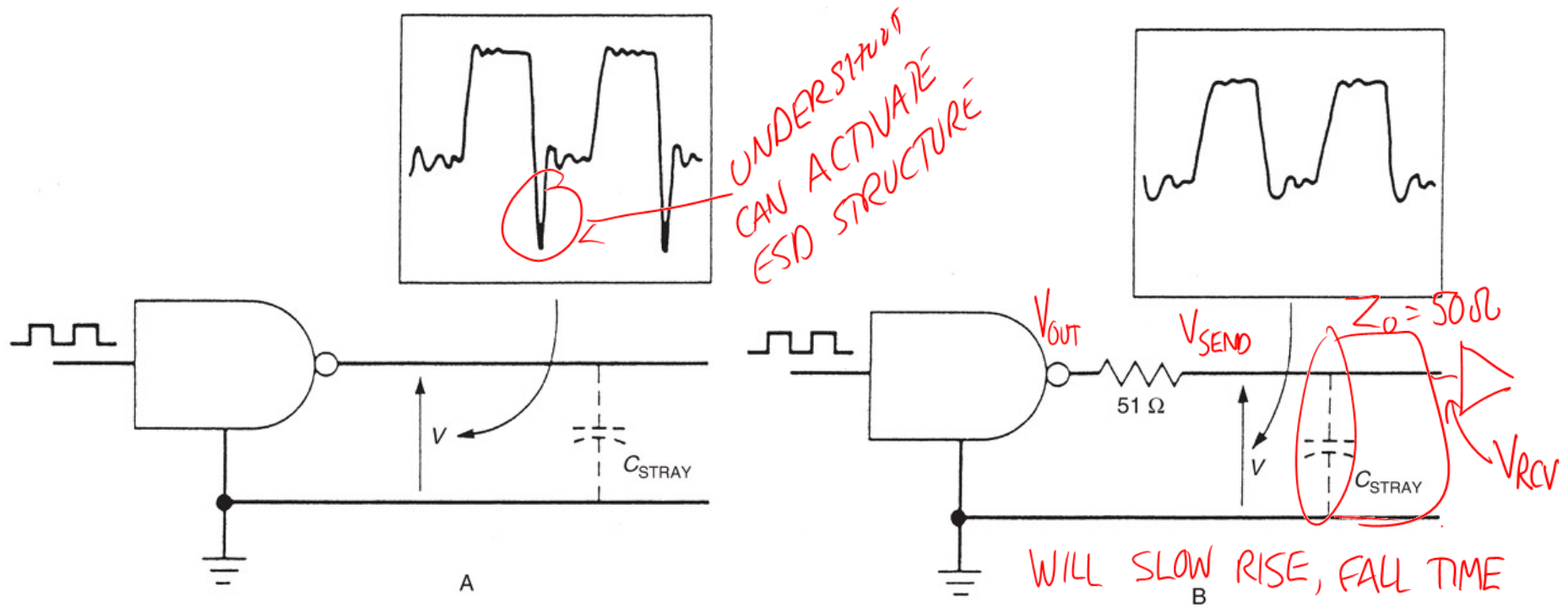


Figure 10-2
TTL output voltage waveshape with (A) ringing caused by stray capacitance and ground inductance, and
(B) ringing damped by the addition of an output resistor

TERMINATION OPTIONS WHEN TRANSMISSION LINE EFFECTS ARE
RECEIVE END

 

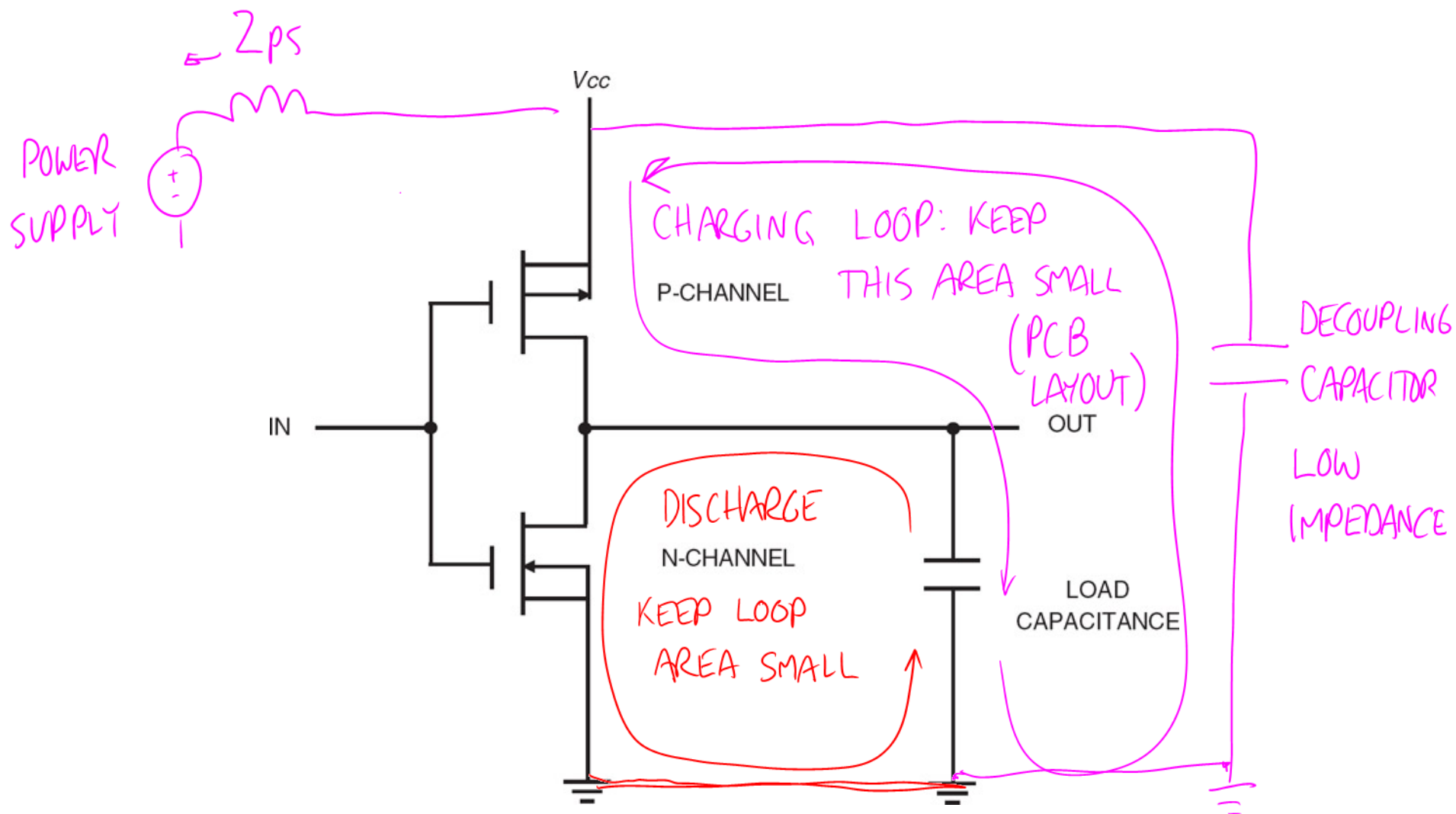


Figure 10-3: Basic schematic for a CMOS logic gate that has a totem pole output circuit

Table 10-1: Impedance of a 1-in Long Printed Circuit Board Trace (15 nH of inductance)

Frequency (MHz)	Rise Time (ns)	Impedance (Ω)
1	318	0.1
10	32	1
30	11	2.8
50	6.4	4.7
100	3.2	9.4
300	1.1	28
500	0.64	47
1000	0.32	94

1 GHz

IMPORTANCE
OF MINIMIZING
TRACE LENGTH
FOR CHARGE
DISCHARGE
CURRENTS

A typical printed circuit board (PCB) trace (a 1-oz copper conductor 0.006 in. wide, and 0.02 in. from a return conductor) has a resistance of 82 m Ω /in ([Eq. 5-10](#)) and a loop inductance of 15 nH/in (Eq. 10-5). The impedance of the 15-nH inductance versus frequency, which is related to the logic rise/fall time by [Eq. 10-2](#), is given in Table 10-1.


 


Figure 10-5: A grid-type ground on a printed circuit board

 

BAD: SLOT



LARGE
LOOP
AREA
HIGHER L ,
 $|Z|$

Figure 10-6: Typical printed circuit board ground plane

OK TO HAVE SMALL HOLES AS LONG AS
A SMALL LOOP CURRENT PATH IS AVAILABLE


 


Figure 10-7: Electric and magnetic fields surrounding a microstrip line

SIGNAL

POWER

GND

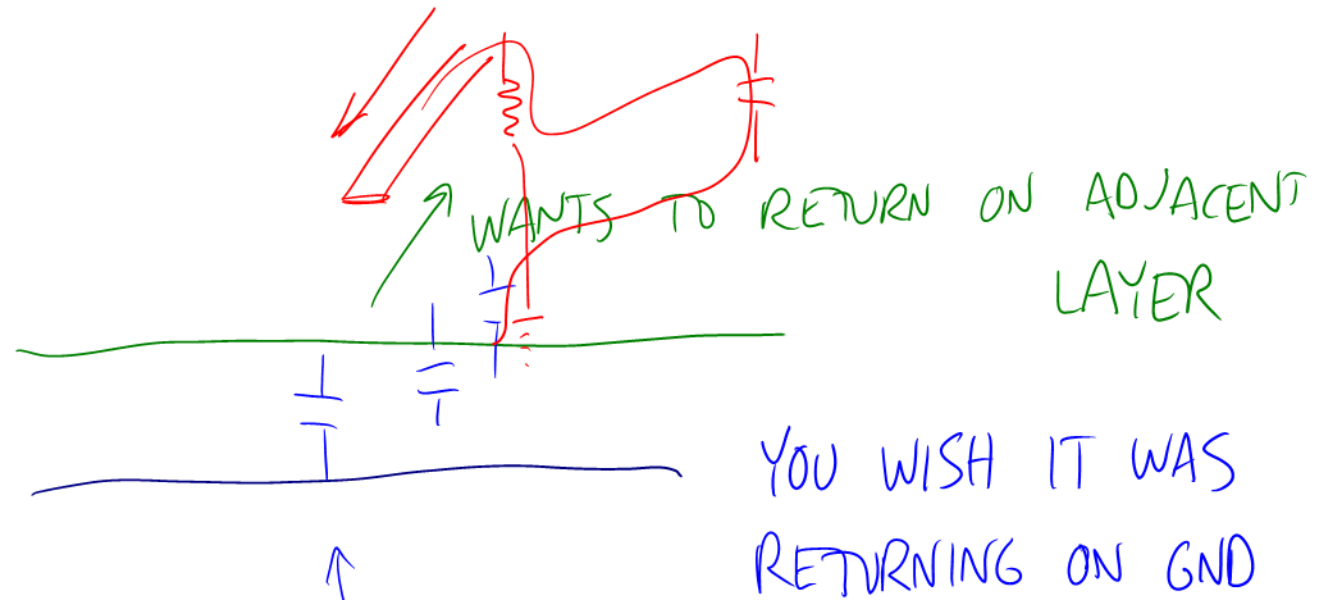

NEED LOW IMPEDANCE
DECOUPLING (BYPASS) CAPS
BETWEEN POWER GND
FOR TRANSIENT CURRENT THAT
NEEDS TO FLOW

Figure 10-9: Normalized reference plane current density for a microstrip line

 


Figure 10-8: Configuration of a microstrip line

Figure 10-12: Normalized reference plane current densities for a stripline (solid) and microstrip (dotted)

 


Figure 10-11: Configuration of a stripline

 
 


Figure 10-17: Test board for ground plane inductance measurements

 


Figure 10-19: Measured ground plane inductance (nH/in) versus trace height in mils (1-mil = 0.001 in). Data point for 7-mil trace height omitted from plot because it is believed to be in error, see Section 10.6.2.3

 




Figure 10-23: Ground plane inductive reactance X_{Lg} and resistance R_g for a 0.010-in-wide trace, as a function of trace height in mils at a frequency of 200 MHz

h SMALL

 SMALL CROSS SECTION

h LARGE

 LARGE Cu CROSS SECTION

 


Figure 10-26: Calculated ground plane voltage (mV/in) at 50 MHz, for a 0.050-in-wide trace. Measured values are indicated by the dots

FIG 10.8


 



Figure 10-27: Representation of the ground plane current under a microstrip trace

USE MULTIPLE VIAS
IF POSSIBLE
LOWER TOTAL Z

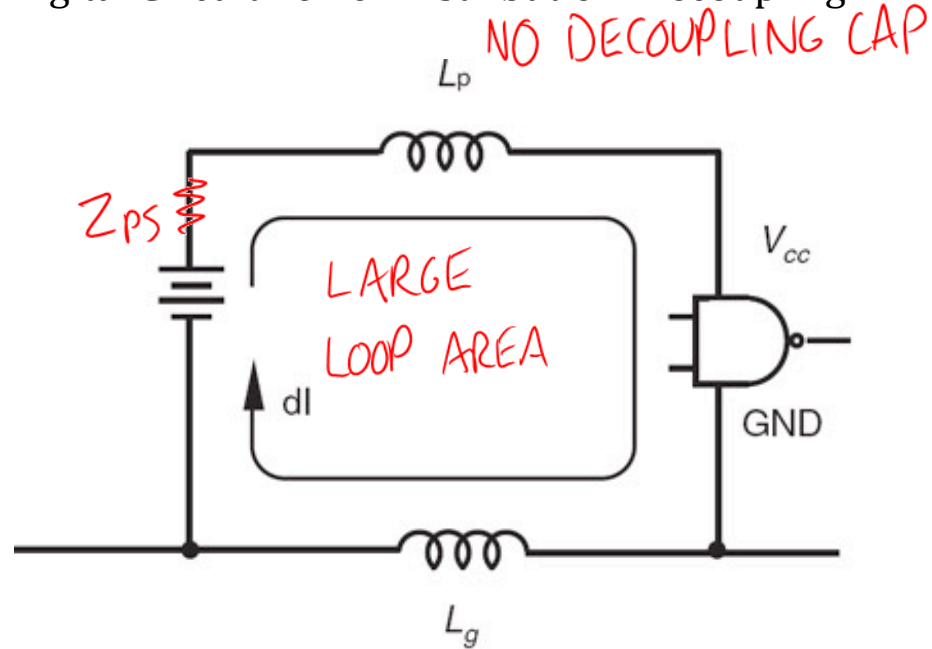Digital Circuit Power Distribution: Decoupling



A

 

B

1. Reduce the effect of one integrated circuit (IC) upon another (inter-IC coupling).
2. Provide a low impedance between power and ground, so that the IC operates as intended by its designers (intra-IC coupling).^[*]

 


Figure 11-2: Transient currents produced when a CMOS logic gate switches




 
 
 
 


Figure 11-4: Envelope of Fourier spectrum of an isosceles triangular wave

FREQ RANGE FOR WHICH $|Z_{\text{DECOUPLING}}|$ NEEDS TO BE LOW

Figure 11-6: (A) Ideal decoupling network and (B) actual decoupling network

 

 


Figure 11-7: Equivalent circuit for decoupling capacitor connected to an integrated circuit, for a DIP package with power and ground on diagonally opposite pins of the IC

30 nH IN LOOP!



 


Figure 11-8: Impedance of different value decoupling capacitors in series with 30 nH of inductance

 

WITHOUT DECOUPLING CAPACITORS

A

 

WITH DECOUPLING CAPACITORS

B

Figure 11-9: Measured V_{cc} -to-ground noise voltage versus frequency for a printed circuit board with and without decoupling capacitors

DECOUPLING HELPS FOR $f < 70\text{MHz}$


 


Figure 11-9: Measured V_{cc} -to-ground noise voltage versus frequency for a printed circuit board with and without decoupling capacitors. Note little improvement above 70MHz; see sec 11.3

DECOUPLING
CAPS
 C_1, C_2, C_3

 

The requirements for effectively paralleling multiple L - C networks are as follows:

1. Make all the capacitors the same value; this way they share the current equally.
2. Each capacitor must feed the IC through a different inductance than the others. Therefore, they cannot be located together, because of the mutual inductance that would occur. Spread them out.


 


Figure 11-11: The IC as a noise current generator

MODEL FOR

I_{cc}

 ANALYSIS MODEL: IMPEDANCE OF
DECOUPLING NETWORK






MORE
SMALLER
VALUE
CAPACITORS
⇒ PARASITIC
L IN PARALLEL
SMALLER!
(ALSO HELPS
WITH ESR)

Figure 11-12 is a plot of the impedance versus frequency for various numbers (1, 8, 64, 512) of identical L - C networks in parallel. In all cases, the *total* capacitance equals $0.1 \mu\text{F}$ and the inductance in series with each capacitor is 15 nH .

Decoupling capacitor strategy

What is ΔQ required by load?

  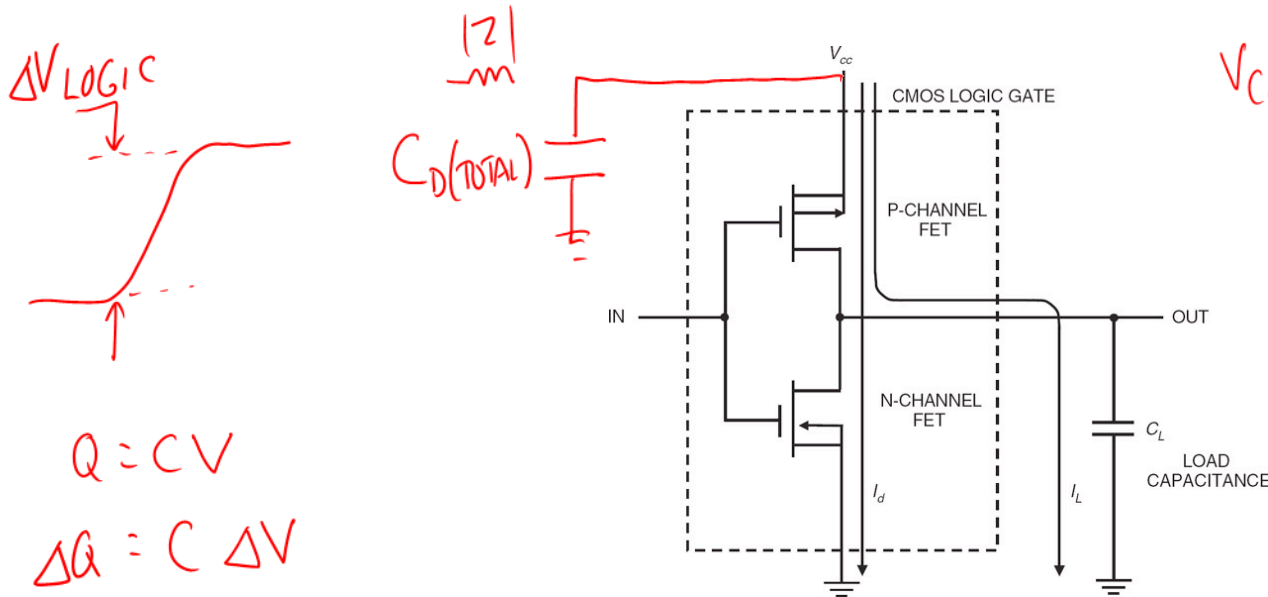How much supply voltage ΔV_{CC} can circuit tolerate?




$$\Delta Q = C_{D(TOTAL)} \Delta V_{CC}$$

$$Q = CV$$

$$\Delta Q = C \Delta V$$
 
$$\Delta Q = C_{L(TOTAL)} \Delta V_{LOGIC}$$



EQUATE BY CHARGE CONSERVATION

$$C_{L(TOTAL)} \Delta V_{LOGIC} = C_{D(TOTAL)} \Delta V_{CC}$$

TO MINIMIZE L
 AS MANY SMALL, LOW
 ESL CAPS AS POSSIBLE
 DISTRIBUTED OVER PCB
 (ALSO HELP FROM DISTRIBUTED PCB LAYER CAP)

$$C_{D(TOTAL)} = C_{L(TOTAL)} \frac{\Delta V_{LOGIC}}{\Delta V_{CC}}$$

SWING
 CHANGE IN SUPPLY
 TOTAL LOAD CAP

 


Figure 11-14: Impedance versus frequency for a decoupling network consisting of a 0.1 and a 0.01- μ F capacitor, both in series with 15 nH of inductance



 


Figure 11-15: (A) Decoupling network with two different value capacitors, and (B) the equivalent circuit of A for a frequency f where $f_{r1} < f < f_{r2}$

Figure 11-19: Stackup of a typical embedded capacitance printed circuit board

 

 ANOTHER NICE FEATURE: EVERY
SIGNAL PLANE HAS A REFERENCE PLANE (GND OR PWR)
ADJACENT



The velocity of propagation of electromagnetic energy in a dielectric was given in [Eq. 5-14](#) and is repeated here:

$$v = \frac{c}{\sqrt{\epsilon_r}}, \quad (11-9)$$

where c is the speed of light (12 in/ns) and ϵ_r is the relative dielectric constant of the material.

The radius of the effective capacitance area is equal to

$$r = vt = \frac{12t}{\sqrt{\epsilon_r}}, \quad (11-10)$$

where r is the radius in inches, t is the time required to move the charge in nanoseconds, and ϵ_r is the relative dielectric constant of the material. If we want to move charge on an FR-4 epoxy-glass PCB ($\epsilon_r = 4.5$) in 0.5 ns, then r would be equal to approximately 3 in.

*PI FILTER
AT HIGH FREQ*


 


Figure 11-21: Filter used to feed power to an isolated power plane

** CAUTION*

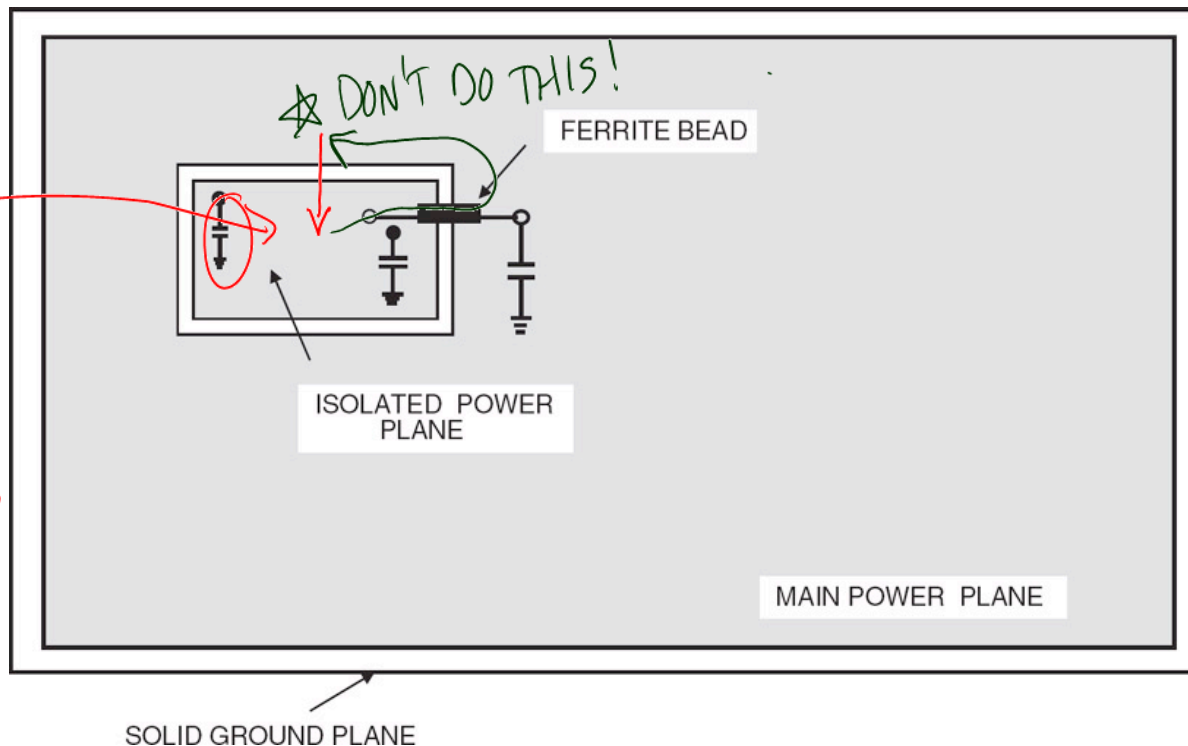** BE SURE ALL
CURRENT LOOPS
IN THIS REGION
STAY "LOCAL"
TO ANY DECOUPLING
CAPACITORS*



*ANY SIGNALS
MOVING IN/OUT
OF THIS REGION
MUST NOT USE
THIS PLANE
AS A REFERENCE
PLANE*

Figure 11-22: Example of an isolated power plane

Effect of decoupling on Radiated Emissions

 


Figure 11-24: Current in the IC to decoupling capacitor loop, for the case of (A) one decoupling capacitor, and (B) two identical decoupling capacitors


Decoupling Capacitor Value

For effective decoupling at low frequencies (below the decoupling network resonance), the total decoupling capacitance must satisfy the following two requirements:

 - (1) the total capacitance must be large enough to have an impedance below the target impedance at the lowest frequency of interest (see [Section 11.4.5](#)) and
- (2) the total capacitance must be large enough to supply the transient current required by the IC when it switches, while keeping the supply voltage within the required tolerance. (SLIDE 1-148)


One Minute Quiz:

An IC requires a transient current of 500 mA for 2 ns. For proper operation it is necessary to limit the power supply voltage transient to less than 0.1 V. What is the total value of decoupling capacitance required to meet criterion (2)?



$$\Delta Q = C \Delta V$$
 
$$C = \frac{\Delta Q}{\Delta V} = \frac{1 \text{ E-9 coul}}{0.1 \text{ V}} = 0.01 \mu\text{F}$$



Decoupling Capacitor Type

Low-frequency effectiveness: value of capacitance C

High-frequency performance: determined solely by how low the inductance can be driven. L


Inductance is determined by how many capacitors are used and the inductance in series with each.

The internal inductance of a multilayer SMT capacitor is primarily determined by its package size.


A 1206 capacitor will have an inductance of about 1.2 nH, whereas an 0603 capacitor will have an inductance of about 0.6 nH.

Use the smallest package size practical for the application, and then use the largest value capacitor readily available in that package size. Choosing a smaller value capacitor provides no improvement in the high-frequency performance, but it will degrade the low-frequency effectiveness.


Decoupling Capacitor Placement

 


INDUCTANCE: 2.8 nH

 

INDUCTANCE: 2.1 nH

 


INDUCTANCE: 1.1 nH

 


INDUCTANCE: 0.7 nH

MULTIPLE VIAS (2)

 

Inductance: 0.5 nH

MULTIPLE VIAS (3)

 

INDUCTANCE: 0.4 nH

VIAS IN PAD
BEST

Figure 11-25: Inductance of various 0805 SMT decoupling capacitor mounting configurations

Bulk Decoupling Capacitors

The value of the bulk capacitor is not critical, but it should be greater than the sum of all the values of the IC decoupling capacitors that it serves.

One bulk decoupling capacitor should be located where power comes onto the board. Other bulk capacitors should be located strategically around the board.

It is better to err on the side of too much bulk decoupling capacitance than on the side of too little.

The bulk decoupling capacitors will typically have values in the 5- to 100- μ F range (10 μ F being a typical value) and should have a small equivalent series inductance.

Multilayer ceramic capacitors are becoming more common in this application.

In the past, tantalum electrolytic capacitors were common.

Aluminum electrolytic capacitors have inductances an order of magnitude or more higher than tantalum and should not be used.

Power Entry Filters

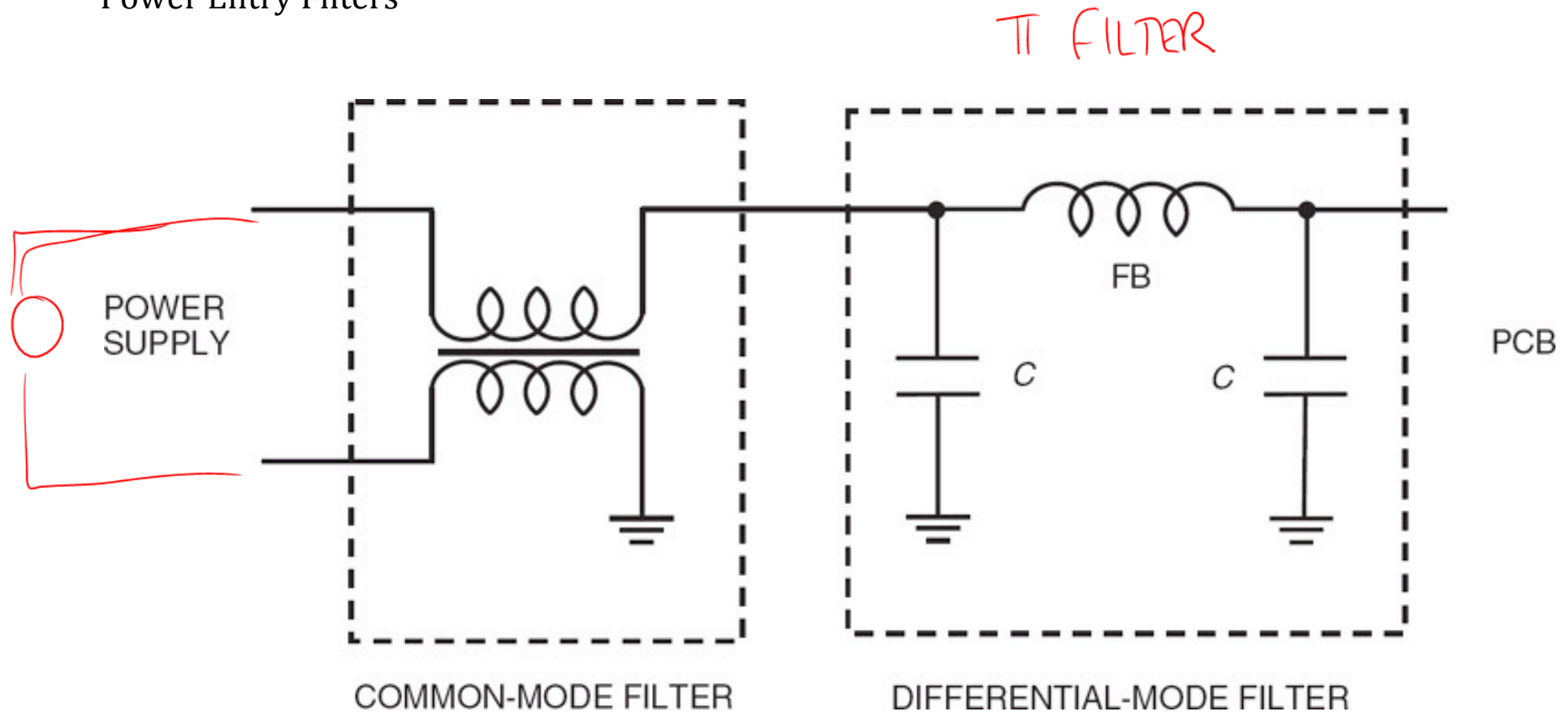


Figure 11-26: A typical power entry filter

Typical values for the filter elements are 0.1 to 0.01 μF for the capacitors and a ferrite bead whose impedance is between 50 and 100 Ω across the frequency range of interest. In this application, it is important to avoid saturation of the ferrite bead by the dc current. If an inductor is used, then typical values would be from 0.5 to 5 μH .

Summary: Digital Power Distribution

- Decoupling capacitors are needed to supply, through a low-inductance path, some or all of the transient power supply current required when an IC logic gate switches.
- Decoupling capacitors are needed to short out, or at least reduce, the noise injected back into the power ground system.
- Decoupling is not the process of placing a capacitor adjacent to an IC to supply the transient switching current; rather it is the process of placing an L – C network adjacent to the IC to supply the transient switching current.
- The value of the decoupling capacitor(s) is important for the low-frequency decoupling effectiveness.
- The value of the decoupling capacitor(s) is not important at high frequencies. At high frequencies, the most important criteria is to reduce the inductance in series with the decoupling capacitors.
- Effective high-frequency decoupling requires the use of a large number of capacitors.
- In most cases, the use of single value decoupling capacitors perform better than when multiple value capacitors are used.
- For *optimum* high-frequency decoupling, discrete capacitors should not be used at all; rather, a distributed capacitor PCB structure should be used.
- The number one rule of decoupling is to have the current flow through the smallest loop possible.

Summary: Day 1 Grounding and Power

- Ground and power are the among first things you should think about when designing a high speed or high current or high accuracy system
- There are many techniques available to reduce interference to an acceptable level, and the earlier you think about them in the design process the more options are available and the lower will be the cost of implementation
- Noise and interference can be understood in terms of basic system concepts such as the source – channel transfer function – receptor model and use of circuit elements (capacitance and inductance) to represent electric field and magnetic field coupling
- “Ground” means different things to different people. Be clear on the use of ground for safety, voltage reference, current return, shielding, etc. in different applications
- Current has to flow in a loop and wants to return by the lowest impedance path. Always give the current the smallest loop area return path possible and watch out for common impedance coupling so that high current return paths do not affect low level signal voltage reference ground paths $V_g = I_g Z_g$
- Power supply distribution and decoupling needs to be intentionally designed
- Passive elements used in distribution and decoupling are nonideal, and often it is the parasitic nonidealities that end up setting critical performance limitations
- Even digital is analog and often digital traces on a PCB need to be designed as analog transmission lines to maintain acceptable digital signal integrity

