

**ECE 2201
Term A-2023**

Problem Set 4

Due: Monday, September 25, 2023

NOTES:

(1) You must show all work to receive credit. Answers alone are not sufficient.

(2) The book problems may have been used before and I am sure solutions are floating about. Be sure you know how to do these problems **ON YOUR OWN**, since you will be tested in each area.

Section 5.3: MOSFET Circuits at DC (pg. 298)

1. D5.43
2. D5.45 (Note: This problem refers to Fig. E5.10 which is on page 277.)
3. 5.47
4. D5.48 (PMOS)
5. D5.49
6. 5.53
7. 5.54 (a) (V1 through V7)

* Problems 8-10 have been graciously provided by Prof. McNeill (see attached)

8. CMOS Inverter and Propagation Delays
9. MOSFET Logic Gate
10. How small is "small v_{DS} ", anyway?

8. CMOS Inverter and Propagation Delays

Figure 4-1 shows a CMOS logic inverter driving a capacitive load of 100pF, and being controlled by a digital input signal V_{in} switching between 0 and 5V. Several parameters are also given for each MOSFET, and the supply voltage is 5V. **NOTE: The process parameters for the devices are NOT equal!**

 



Figure 4-1

M1 :	<u>P-Channel</u>
	$W_p = 50\mu\text{m}$
	$L_p = 10\mu\text{m}$
	$k'_p = 70\mu\text{A} / \text{V}^2$
	$ V_{tp} = 1.1\text{V}$
M2:	<u>N-Channel</u>
	$W_n = 50\mu\text{m}$
	$L_n = 10\mu\text{m}$
	$k'_n = 150\mu\text{A} / \text{V}^2$
	$V_{tn} = 1.1\text{V}$

- a) Determine the *propagation delays* t_{PLH} (low-to-high output transition) and t_{PHL} (high-to-low output transition) for this CMOS inverter.

NOTE: Use the simple resistor/switch MOSFET models presented in class.

- b) If V_{in} is a 2MHz, 0 to 5V square wave with a 50% duty cycle, sketch two cycles of the input and output voltage waveforms to scale, relative to one another.
- c) One desirable feature of a CMOS inverter is to have equal propagation delays. Assuming that the channel length, L of each device is fixed, what new width should the PMOS device have, in order to achieve this result?
- (d) Repeat part (a), but use the constant saturation current model for each MOSFET when it turns on, instead of the resistor model.
- (e) How do the propagation delays compare to the resistive model?

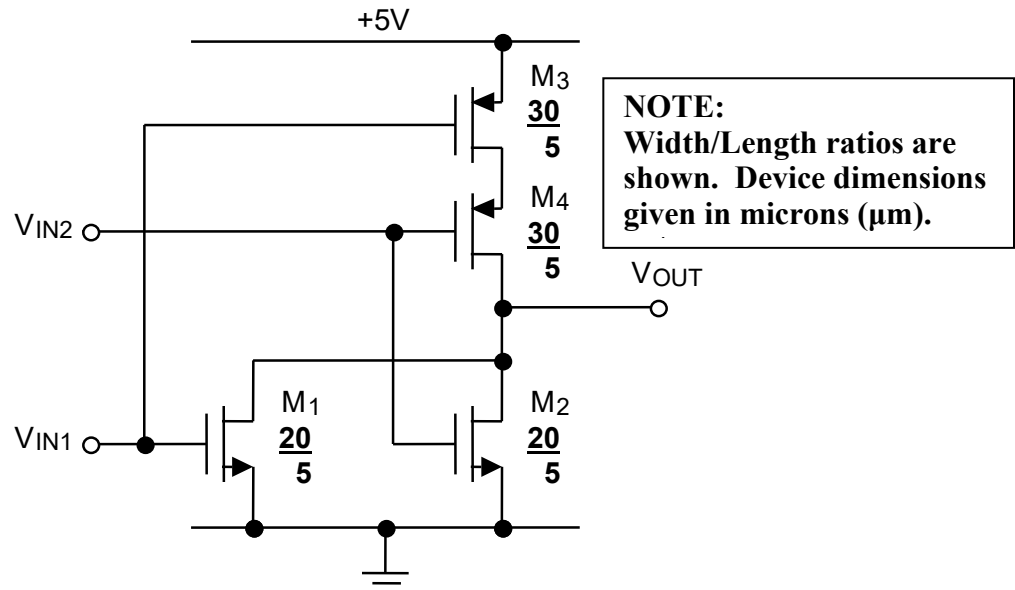9. MOSFET Logic Gate Analysis

- Fill in the table below showing the state of each MOSFET (ON or OFF) and the output voltage for each combination of input logic states.
- If 0V represents a logic low, and +5V represents a logic high, what is the logic gate function of this circuit?

V _{IN1}	V _{IN2}	M1	M2	M3	M4	V _{OUT}
0V	0V					
0V	+5V					
+5V	0V					
+5V	+5V					

- If $k_n' = 50\mu\text{A}/\text{V}^2$, $k_p' = 25\mu\text{A}/\text{V}^2$ AND $V_{tn} = |V_{tp}| = 1.2\text{V}$, determine the output resistance R_{out} , of this logic gate for each input combination. **NOTE: Don't forget to include the device dimensions!**

IN1	IN2	R _{out}
0	0	
0	1	
1	0	
1	1	

10. How small is "small v_{DS} ", anyway?

The full triode region equation:

$$i_D = k_n' \left(\frac{W}{L} \right) \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (\text{Eq.1})$$

gives a nonlinear relationship between v_{DS} and i_D , due to the v_{DS}^2 term. Assuming the v_{DS}^2 term to be negligible allowed us to approximate the relationship between v_{DS} and i_D as linear, which gives a resistive behavior:

$$\frac{v_{DS}}{i_D} = r_{DS} = \frac{1}{k_n' \left(\frac{W}{L} \right) (v_{GS} - V_t)} \quad (\text{Eq.2})$$

Several people have asked, what is a "small enough" v_{DS} ? The answer depends on how accurate you need to be. As v_{DS} gets larger, the difference between Eq.1 and Eq.2 gets larger (see Figure 2.0 below).

- a) Find a **value for the fraction $v_{DS} / (v_{GS} - V_t)$** , for which the current i_D predicted by the resistive approximation of Eq.2 is within **10%** of the actual current value given by the full triode model of Eq.1?
- b) For what fraction is the error less than **1%**?

 


Figure 2.0