

LAB 3, P1:

- THE DATA POINTS CAN BE USED TO FIND V_t AND $K_n'(W/L)$ FOR THE MOSFET AS FOLLOWS:
- MOSFET SWITCH RESISTANCE, r_{DS} CAN BE FOUND USING THE FOLLOWING FORMULA (AS LONG AS V_{DS} IS SMALL)

$$r_{DS} = \frac{1}{K_n'(W/L)(V_{GS} - V_t)}$$

- USING TWO DATA POINTS, (r_{DS1}, V_{GS1}) AND (r_{DS2}, V_{GS2}) , TWO EQ'S CAN BE USED TO ISOLATE V_t :

$$r_{DS1} = \frac{1}{K_n'(W/L)(V_{GS1} - V_t)} \quad [\text{EQ. 1}]$$

$$r_{DS2} = \frac{1}{K_n'(W/L)(V_{GS2} - V_t)} \quad [\text{EQ. 2}]$$

- TAKE THE RATIO OF THESE TWO EQ'S, AND SOLVE FOR V_t . (THE $K_n'(W/L)$ TERM CANCELS OUT)

$$\frac{r_{DS1}}{r_{DS2}} = \frac{V_{GS2} - V_t}{V_{GS1} - V_t}$$

- SOLVING FOR V_t :

$$V_t = \frac{r_{DS1} V_{GS1} - r_{DS2} V_{GS2}}{r_{DS1} - r_{DS2}} \quad [\text{EQ. 3}]$$

- CHOOSE TWO DATA POINTS AND SOLVE FOR V_t . FOR GREATER ACCURACY, CHOOSE POINTS AT EXTREME ENDS OF THE CURVE.

V_{GS}	r_{DS}
1.5V	3190 Ω
\vdots	\vdots
4V	180 Ω


USING THESE POINTS YIELDS:

$$\underline{V_t = 1.35 \text{ VOLTS}}$$

- NOW PLUG THIS VALUE FOR V_t INTO EQ. 1 (OR EQ. 2) ALONG W/ THE APPROPRIATE DATA PT. AND SOLVE FOR $K_n'(W/L)$

$$\underline{K_n'(W/L) = 2096 \text{ mA/V}^2}$$

LAB 3, P2 :

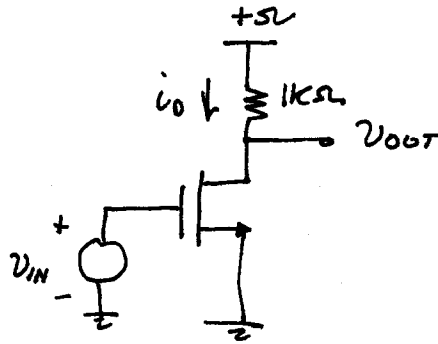


- FOR $V_{IN} = 0$, MOSFET IS OFF, $i_D = 0$ AND $V_{OUT} = \underline{+5V}$
- FOR $V_{IN} = +5V$, MOSFET IS ON
- ASSUMING TRIODE (RESISTIVE) REGION, FIND r_{DS} :

$$r_{DS} = \frac{1}{K_n (W/L) (V_{DS} - V_G)} = \frac{1}{(2.096 \text{ mA/V}^2) (5V - 1.35V)}$$

$$= \underline{130.7 \Omega}$$

- CIRCUIT MODEL BECOMES :

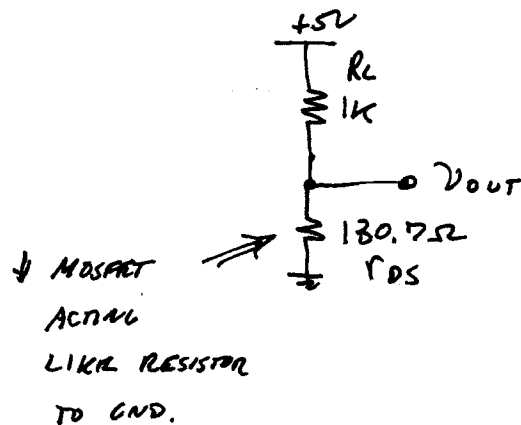

- APPLYING VOLTAGE DIVIDER,

$$V_{OUT} = \left(\frac{r_{DS}}{R_L + r_{DS}} \right) V_{DD} = \left(\frac{130.7 \Omega}{1000 \Omega + 130.7 \Omega} \right) 5V$$

$$\therefore \underline{V_{OUT} = 0.578 \text{ VOLTS}}$$

- CIRCUIT IS A LOGIC INVERTER

V_{IN}	V_{OUT}
0V	5V
5V	0.578V