

**ECE 2201 – LAB 4B****MOSFET SWITCHING APPLICATIONS****Introduction to Pulse Width Modulation (PWM)  
A Motor Speed Controller****PURPOSE:**



The purpose of this laboratory assignment is to investigate the basic operation of a Pulse-Width-Modulated (PWM) Motor Speed Controller using an N-channel power MOSFET.

Upon completion of this lab you should be able to:

- Understand the basic operation of a PWM motor speed controller.
- Adjust the duty cycle of a PWM control signal from 5-95%.
- Display appropriate waveforms on an oscilloscope.

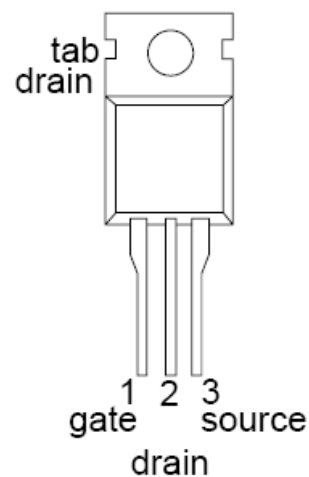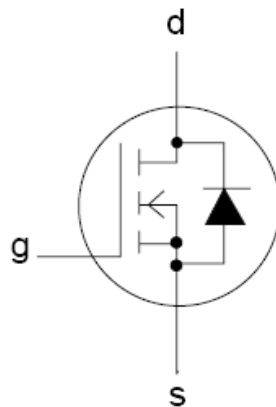**MATERIALS:**

- ECE Lab Kit
- DC Power Supply
- DMM
- Function Generator
- Oscilloscope
- IRF520 or IRF530 power N-Channel MOSFET
- DC MOTOR



PRELAB

P1. Read over the lab. SIMULATE the circuit of Fig. 4-1B using Multisim and vary the duty cycle of the control signal from 5 to 95%. Record the waveforms at the gate of the MOSFET (node 1), as well as the voltage at the drain terminal (node 2). Provide simulations for 25%, 50% and 75% duty cycle.

BACKGROUND

The circuit of Fig. 4-1B shows an IRF520 N-channel power MOSFET used to control the speed of a DC motor. The gate of the MOSFET is being driven by a pulse-width-modulated (PWM) signal to minimize power losses in the circuit.

The duty cycle (% ON-time) of the control signal determines the average DC voltage applied to the motor, thus controlling its speed. Since the MOSFET switch has a low resistance when on (ideally  $0\Omega$ ) and a high resistance when off (ideally infinite), very little power is dissipated in the MOSFET during normal operation.

The diode in the circuit is used as a “free-wheeling diode” to provide a path for the induced motor current to flow, when the MOSFET turns off. Without this diode, a high voltage spike would occur across the MOSFET during turn-off and would damage or destroy the MOSFET.

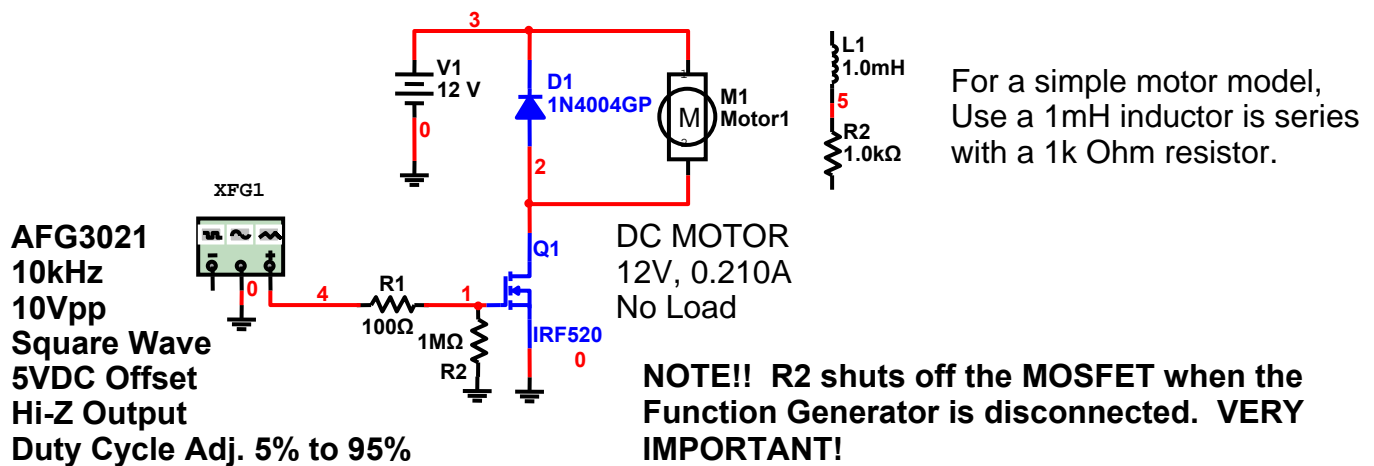


Figure 4-1B.

## LAB PROCEDURE

### Function Generator Set-Up

- L2. Set up the function generator to provide a 10Vpp square-wave with a DC offset of 5V and a frequency of 10kHz. Set the output of the generator to HI-Z so that its output voltage levels match the settings on the screen.

NOTE: If you are getting twice the amplitude than you expect, it is because you are not operating in HI-Z mode.

IMPORTANT: Check the control signal for proper voltage levels using an oscilloscope BEFORE connecting it to the MOSFET! It should be a 0 to 10 Volt square-wave signal.

### PWM Signal

- L3. Verify that you can adjust the duty-cycle of the control signal from 5 to 95%. The duty cycle refers to the percentage of time that a square-wave signal is high. Set the duty cycle to 50% before proceeding to the next step in the lab.
- L4. Build the circuit of Fig. 4-1B. Connect the function generator to the MOSFET and verify that the motor is spinning. Vary the duty cycle from 5 to 90 percent and confirm that the motor speed varies in proportion to it.

**ALSO, be sure to connect resistor R2 which discharges the MOSFET gate-source capacitance if the function generator is disconnected. Otherwise, the motor might not turn off and the MOSFET will overheat.**

- L5. Connect two channels of the oscilloscope to monitor the voltages on the Gate and Drain of the MOSFET. Record waveforms for 25%, 50% and 75% duty cycle.

## WRITE-UP

- W1. Provide a comparison of simulated and measured waveforms for the PWM motor speed controller.