
 


CMOS LOGIC GATES

BASIC LOGIC FUNCTIONS:

 


- IF A "AND" B ARE ON, LIGHT IS ON.
- "AND" IMPLIES WIRING SWITCHES IN SERIES!



- IF A "OR" B IS ON, LIGHT IS ON.
- "OR" IMPLIES WIRING SWITCHES IN PARALLEL!

UTILIZING MOSFETS (NMOS)


 


A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

} THIS IS NAND!

* COULD ADD AN INVERTER TO REALIZE AND FUNCTION.

  
Q: CAN WE ELIMINATE THE PULL-UP RESISTOR?




A	B	PMOS		NMOS		OUT	R _{OUT}
		M ₁	M ₂	M ₃	M ₄		
0	0	ON	ON	OFF	OFF	1	$r_{Dsp} \parallel r_{Dsn}$
0	1	ON	OFF	OFF	ON	1	r_{Dsp}
1	0	OFF	ON	ON	OFF	1	r_{Dsp}
1	1	OFF	OFF	ON	ON	0	$r_{Dsn} + r_{Dsn}$

NOTE

OUTPUT RESISTANCE

 

Q: FIND R_{TH} ?

 

LOOSE ENDS :

- 1) EXPANDABLE (3 INPUT, 4?, 5? ... n?)
- 2) PROPAGATION DELAYS
- 3) WHAT IF WE WIRED PMOS IN SERIES & NMOS IN PARALLEL?

NOR

- 4) 3-INPUT GATES? M-INPUT GATES?