

## Lecture 17 – Introduction to BJT's

## Bipolar Junction Transistors

## BJT Structure (NPN)

- Collector
- Base
- Emitter

## BJT Operation

- B-E Junction (Forward Bias)
- C-B Junction (Reverse Bias)
- Drift vs. Diffusion

BJT Symbol and Currents ( $i_B$ ,  $i_C$ ,  $i_E$ )BJT Current Gain ( $\beta$ ,  $h_{FE}$ )

## Useful BJT Relationships

- Gain Equations
- Current Ratios
- Typical  $\beta$  (Beta) Values
- Typical  $\alpha$  (Alpha) Values


## BJT DEMO

## Lab5 Prep – Beta Meter

## INTRO TO BJT'S

## (BIPOLAR JUNCTION TRANSISTORS)
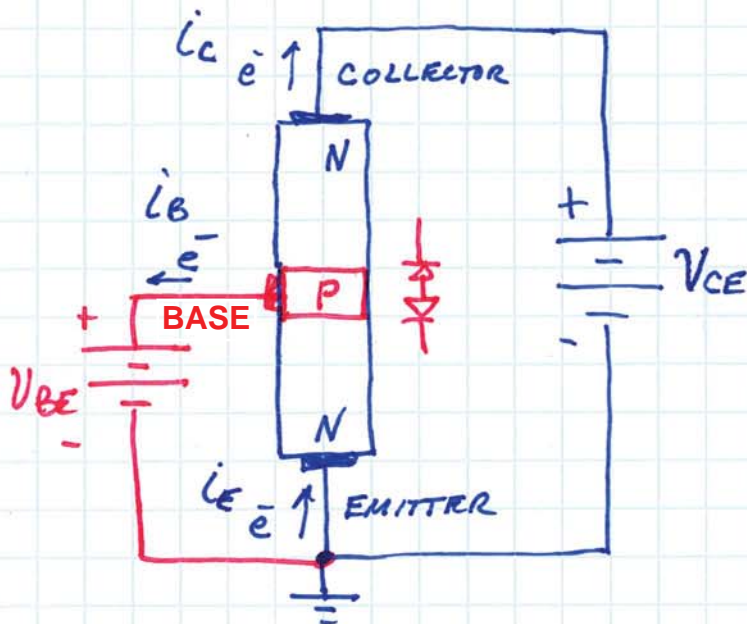
## • STRUCTURE: WILLIAM SHOCKLEY'S REVENGE



• NPN STRUCTURE

• THIN BASE, LIGHTLY DOPED


• HEAVILY DOPED EMITTER

\* DEVICE IS OFF w/ ONE PN JUNCTION REVERSE BIASED (C-B)

## • OPERATION:

1. FORWARD BIAS B-E JUNCTION (DIODE)
2. ELECTRONS FLOW FROM E to B BUT!
3. MOST ELECTRONS AT CONDUCTION BAND ENERGY LEVEL TAKE TIME TO FALL TO VALENCE BAND ENERGY LEVEL IN BASE.
4. MOST WILL DIFFUSE INTO COLLECTOR!!!
5. BE FORWARD BIASED, CB REVERSE BIASED.

## • SYMBOL AND CURRENTS:

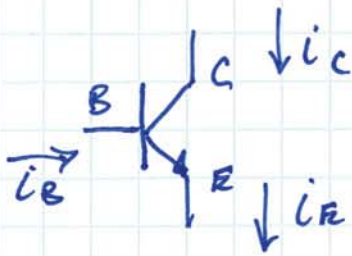

CONVENTIONAL  
CURRENT  
DIRECTION SHOWN

$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

(BETA)

KCL! SUPERNOOK!  
ALWAYS TRUE!!

CURRENT GAIN! BETA

\* BJT IS FUNDAMENTALLY A  
CURRENT GAIN AMPLIFIER !!

BJT  
• IMPORTANT RELATIONSHIPS

• GAIN EQS.

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

• RATIOS:

$$\beta = \frac{I_C}{I_B}$$

(BETA)

$$(\beta + 1) = \frac{I_E}{I_B}$$

$$\left(\frac{\beta}{\beta + 1}\right) = \frac{I_C}{I_E}$$

$$\left(\frac{\beta}{\beta + 1}\right) \equiv \alpha \text{ ALPHA}$$

• TYPICAL  $\beta$  VALUES

$$\beta = 100 \text{ (BOOK)}$$

$$\beta = 25$$

POWER TRANSISTOR

$$\beta = 200$$

SMALL SIGNAL TRANSISTOR

• TYPICAL  $\alpha$  VALUES:


$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

$$\alpha < 1 \quad \alpha \approx 1$$


ALWAYS



## BJT - DEMO

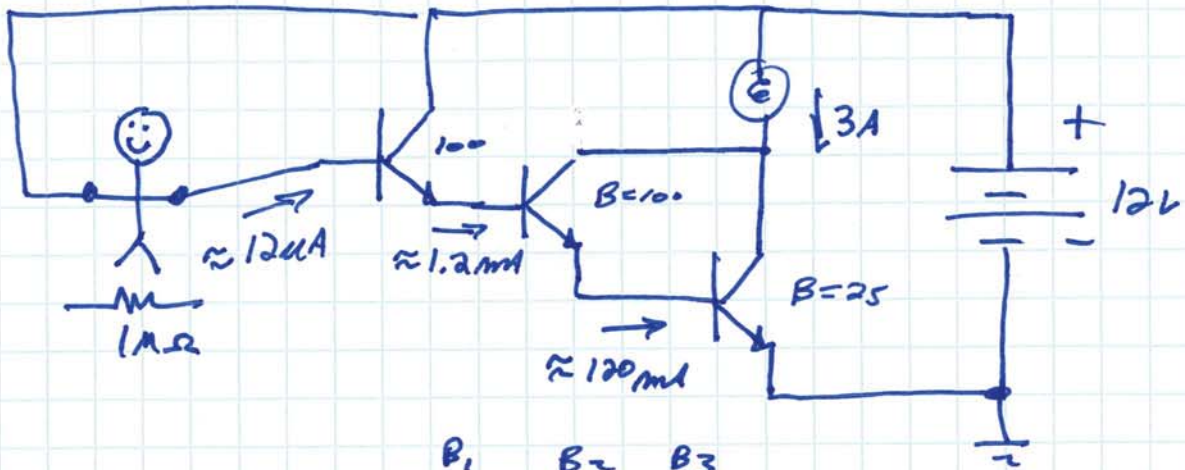
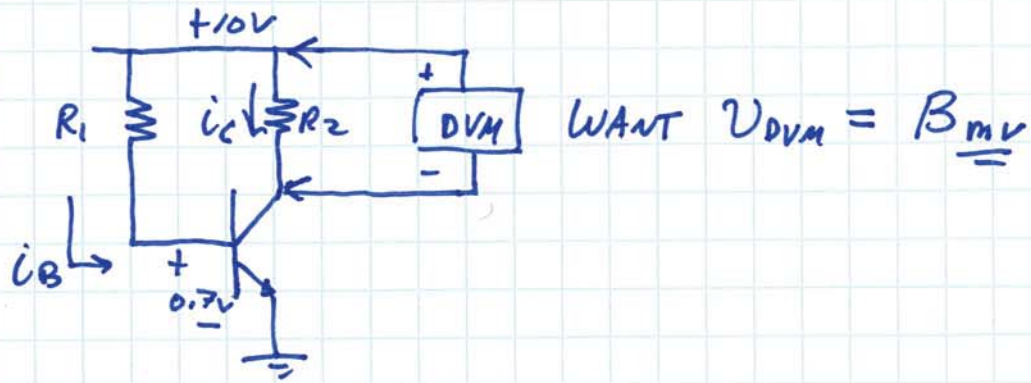
$$I_1 \quad I_2 \quad I_3 \\ (12\mu A) (\beta_1) (\beta_2) (\beta_3) = 3A$$



KVL:  $10V = R_1 \cdot I_B + 0.7V$  For  $I_B = 10\mu A$ ,

$$10V = R_1 (10\mu A) + 0.7V$$

$$\therefore R_1 = 930K\Omega \approx \boxed{1M\Omega} = R_1$$

$$I_C = \beta (10\mu A)$$

WANT  $V_{DVM} = B_{mV} = R_2 I_C$

$$1 B_{mV} = R_2 (\beta) (10\mu A)$$

$$1mV = R_2 (10\mu A)$$

$$\therefore R_2 = \frac{1mV}{10\mu A} = \boxed{100\Omega} = R_2$$

\* MORE PRECISELY,  $R_1 = 930K\Omega$  ,  $R_2 = 100\Omega$

OR ,  $R_1 = 1M\Omega$  ,  $R_2 = 107.5\Omega$