

Lecture 19

BJT Common Emitter (CE) Amplifier


BJT Common Emitter (CE) Amplifier (w/ R_B)

- DC Bias Analysis
- Small-Signal (ac) Analysis
- Beta Dependency


BJT Common Emitter (CE) Amplifier (w/ R_E)

- DC Bias Analysis
- Small-Signal (ac) Analysis
- Beta Independence !

COMMON EMITTER BJT AMPLIFIER

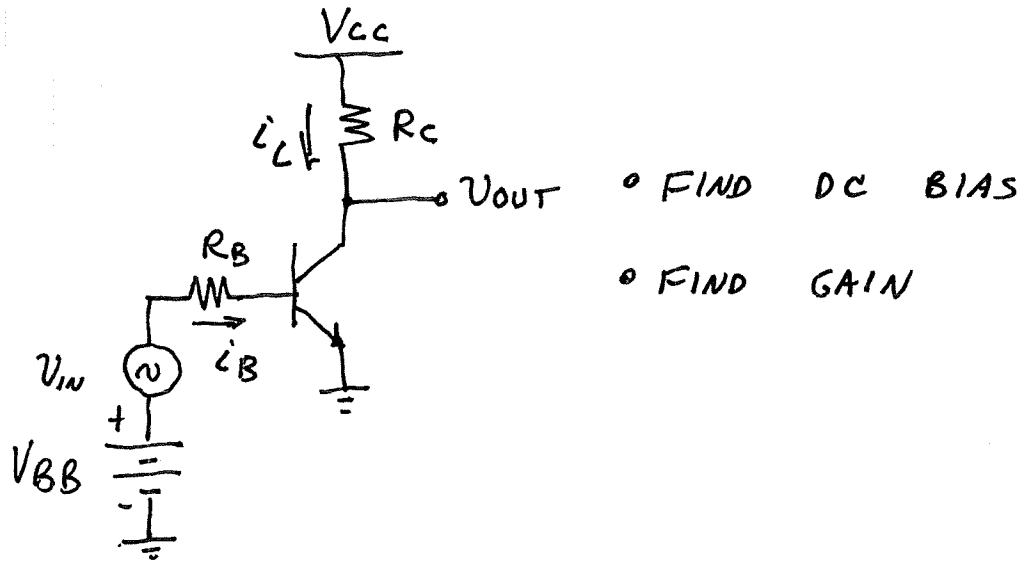

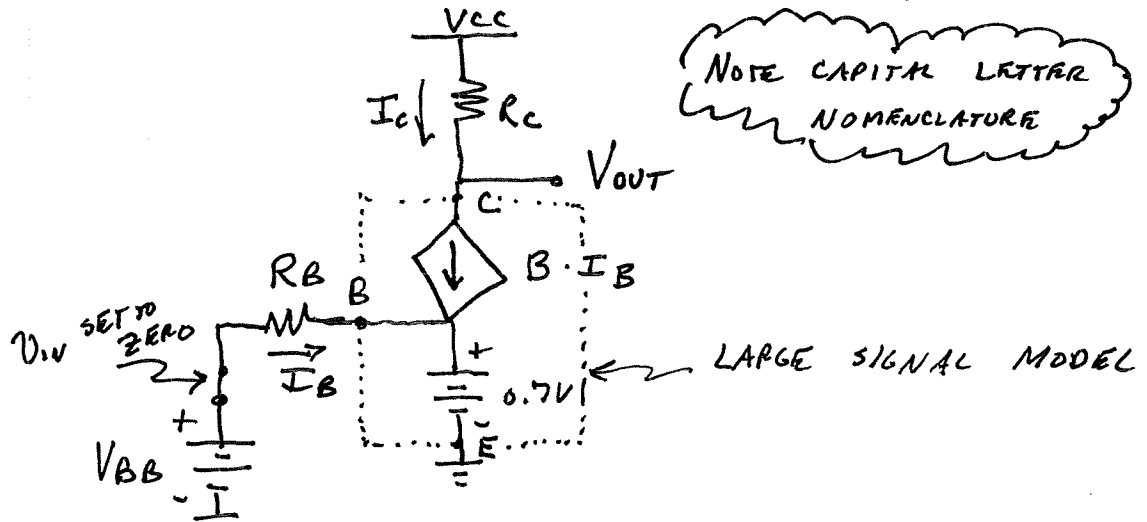DC BIAS (USE CONSTANT VOLTAGE DROP MODEL w/ CURRENT SOURCE)



KVL AT INPUT:

$$V_{BB} = R_B I_B + 0.7V$$

$$I_B = (V_{BB} - 0.7V) / R_B$$

NOW AT OUTPUT:


$$I_C = \beta \cdot I_B = \beta \left(\frac{1}{R_B} \right) (V_{BB} - 0.7V)$$

$$V_{OUT} = V_{CC} - I_C \cdot R_C = V_{CC} - \beta \left(\frac{R_C}{R_B} \right) (V_{BB} - 0.7V)$$

NOTE BETA DEPENDENCE (BAD)

NOW SMALL-SIGNAL AC ANALYSIS (SET DC SOURCES TO ZERO)

SMALL-SIGNAL (ac)

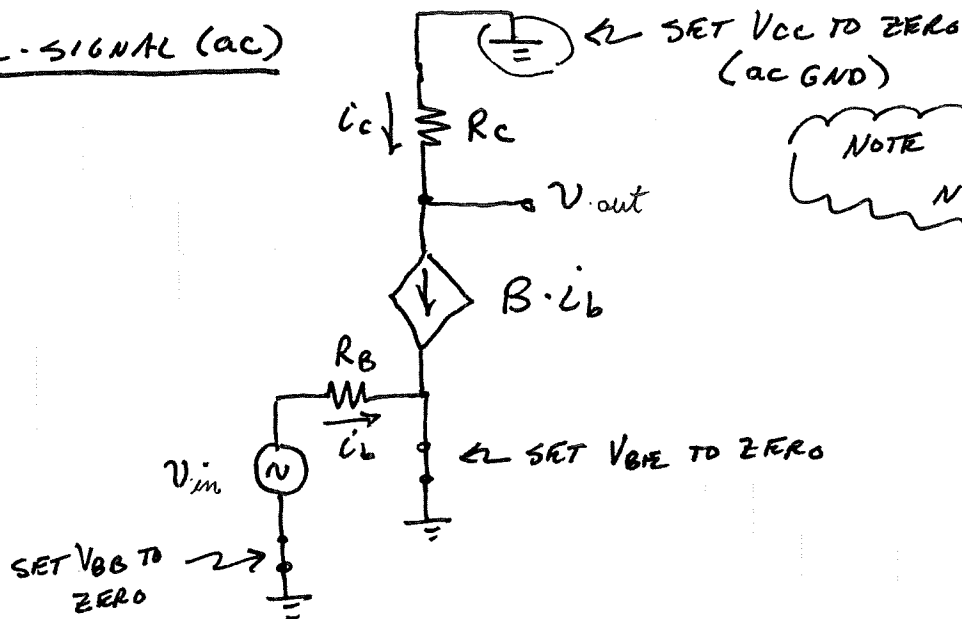

KVL AT INPUT:

$$V_{in} = R_B \cdot i_b$$

$$i_b = \frac{V_{in}}{R_B}$$

AT OUTPUT:

$$i_c = \beta \cdot i_b = \beta \left(\frac{1}{R_B} \right) V_{in}$$

$$V_{out} = 0 - i_c \cdot R_C = -\beta \left(\frac{R_C}{R_B} \right) V_{in}$$

$$V_{out} = -\beta \left(\frac{R_C}{R_B} \right) V_{in}$$

A_v (VOLTAGE GAIN)


$$A_v = \frac{V_{out}}{V_{in}} = -\beta \left(\frac{R_C}{R_B} \right)$$

↑

NOTE BETA DEPENDENCE (BAD)

ELIMINATING BETA DEPENDENCE


(MOVE $R_B \rightarrow R_E$)

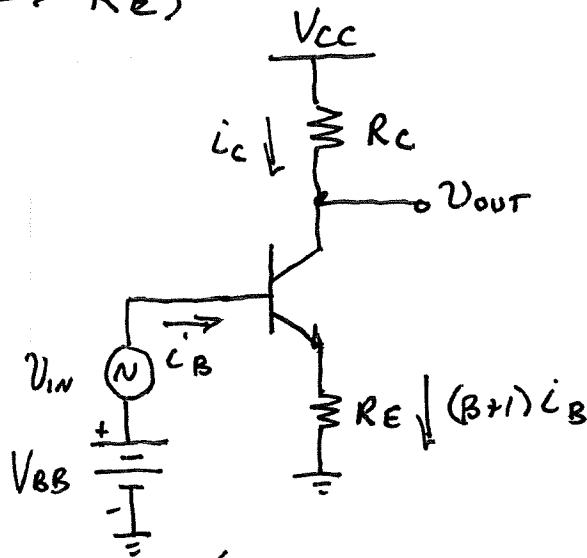

- FIND DC BIAS
- FIND GAIN

DC BIAS

(USE LARGE SIGNAL MODEL)

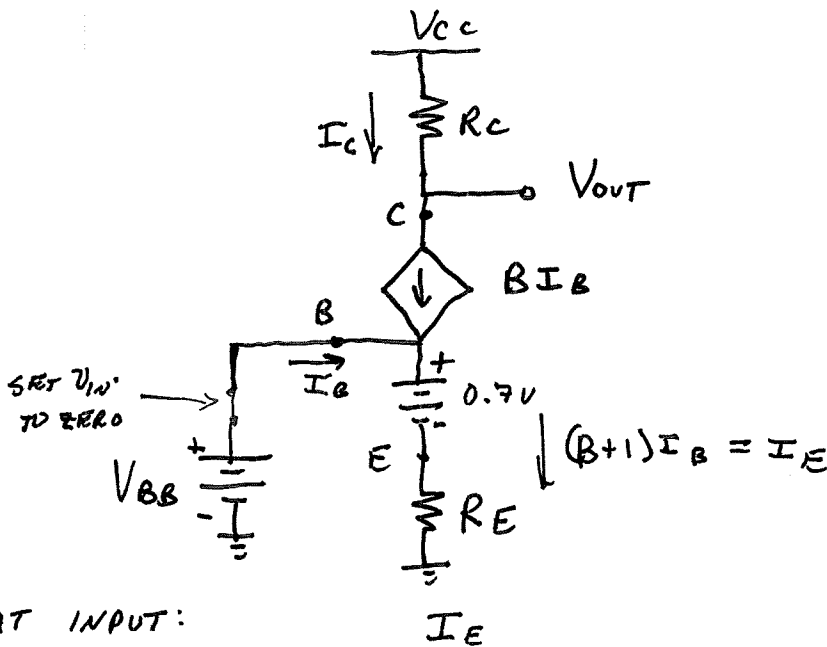

KVL AT INPUT:

$$V_{BB} = R_E (B+1)I_B + 0.7V$$

$$I_B = (V_{BB} - 0.7V) / (B+1)R_E$$

AT OUTPUT:


$$I_C = B \cdot I_B = \left(\frac{B}{B+1}\right) \left(\frac{1}{R_E}\right) (V_{BB} - 0.7V)$$

$$V_{OUT} = V_{CC} - I_C \cdot R_C = \boxed{V_{CC} - \left(\frac{B}{B+1}\right) \left(\frac{R_C}{R_E}\right) (V_{BB} - 0.7V)}$$

↑ BETA INDEPENDENCE
? (GOOD!)

NOW SMALL SIGNAL AC (SET DC SOURCES TO ZERO)

BITAR

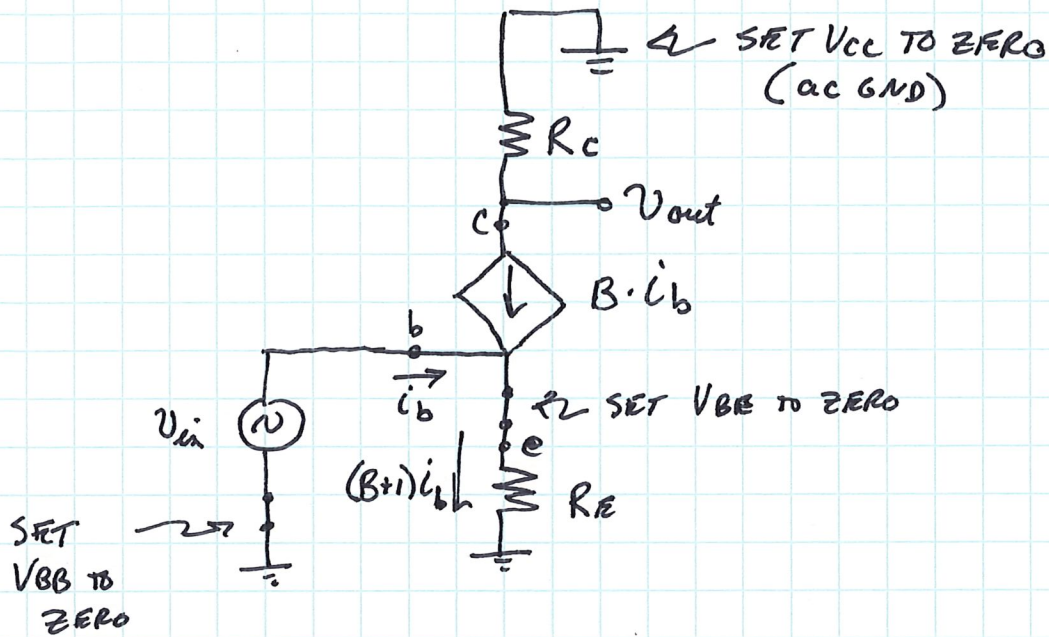

KVL AT INPUT:

$$V_{in} = R_E \overbrace{(B+1) I_b}^{I_c}$$

$$I_b = \frac{V_{in}}{(B+1) R_E}$$

AT OUTPUT:

$$I_c = B I_b = \left(\frac{B}{B+1} \right) \left(\frac{1}{R_E} \right) V_{in}$$

$$V_{out} = 0 - R_C \cdot I_c = - \left(\frac{B}{B+1} \right) \left(\frac{R_C}{R_E} \right) V_{in}$$

$$V_{out} = - \underbrace{\left(\frac{B}{B+1} \right) \left(\frac{R_C}{R_E} \right)}_{A_v \text{ (VOLTAGE GAIN)}} V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = - \left(\frac{B}{B+1} \right) \left(\frac{R_C}{R_E} \right) \approx - \frac{R_C}{R_E}$$

↑ NOTE BETA INDEPENDENCE (GOOD!)