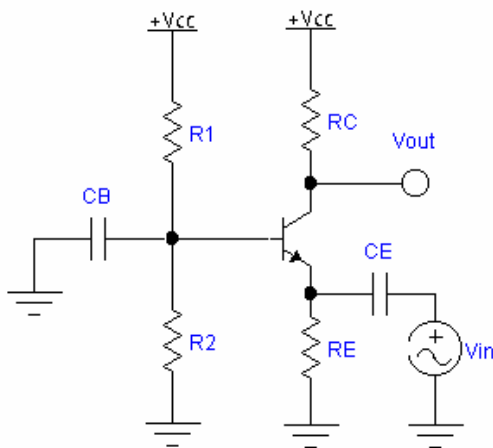


Transistor Amplifiers

Small Signal Modeling Examples

5. Common Base (C-B) Amplifier



DC Bias

$$V_B = V_{CC} [R_2 / (R_1 + R_2)]$$

if $(\beta + 1) R_E \gg R_1 \parallel R_2$

$$V_E = V_B - 0.7$$

$$I_E = V_E / R_E$$


$$I_C \approx I_E$$

$$V_{RC} = I_C (R_C)$$

Check for saturation, ($V_{RC} > V_{CC}$)

$$V_{OUT(BIAS)} = V_{CC} - V_{RC}$$

Small Signal Model

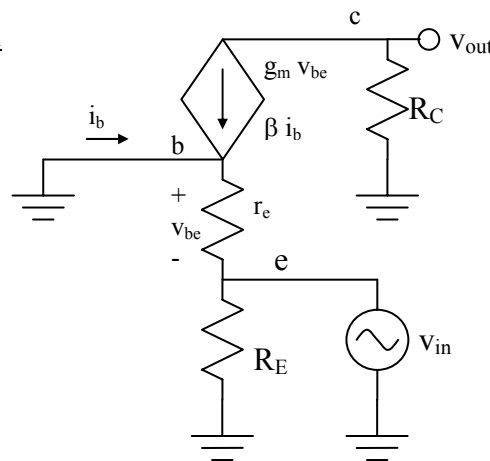

Small Signal (ac) Parameters

$$g_m = I_C(BIAS) / V_T$$

$$r_e = \beta / (\beta + 1) (1/g_m)$$

$$\approx 1 / g_m$$

Voltage Gain (A_V)

$$v_{out} = -g_m v_{be} R_C$$

$$v_{in} = -v_{be}$$

$$A_V = v_{out} / v_{in}$$

$$= -g_m v_{be} R_C / (-v_{be})$$

$$= +g_m R_C \approx +R_C / r_e$$

Input & Output Impedance (R_{in} , R_{out})

$$R_{in} = R_E \parallel r_e$$

$$R_{out} = R_C$$

Notes:

- (1) R_{in} can be made low.
- (2) Same voltage gain as C-E amp.
- (3) The common base amplifier can operate at higher frequencies.