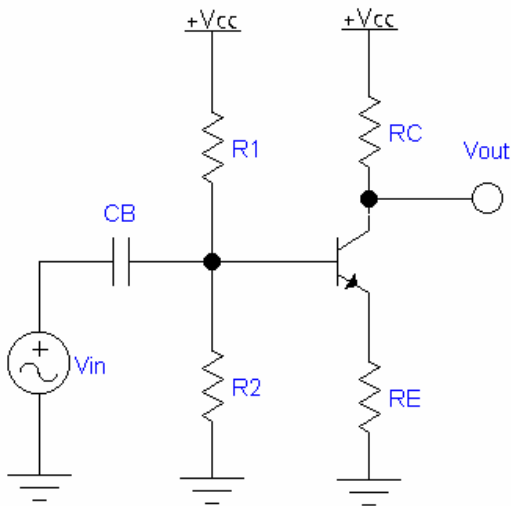


Transistor Amplifiers

Small Signal Modeling Examples

2. Common Emitter Amplifier (Voltage Divider Bias w/ R_E)



DC Bias

$$V_B \approx V_{CC} [R_2 / (R_1 + R_2)]$$

if $(\beta + 1)R_E \gg R_1 \parallel R_2$

$$V_E = V_B - 0.7$$

$$I_E = V_E / R_E$$



$$I_C \approx I_E$$

$$V_{RC} = I_C (R_C)$$

Check for saturation, ($V_{RC} > V_{CC}$)

$$V_{OUT (BIAS)} = V_{CC} - V_{RC}$$

Small Signal Models

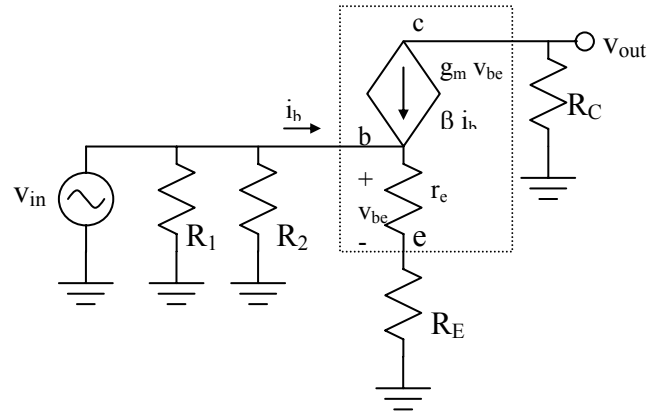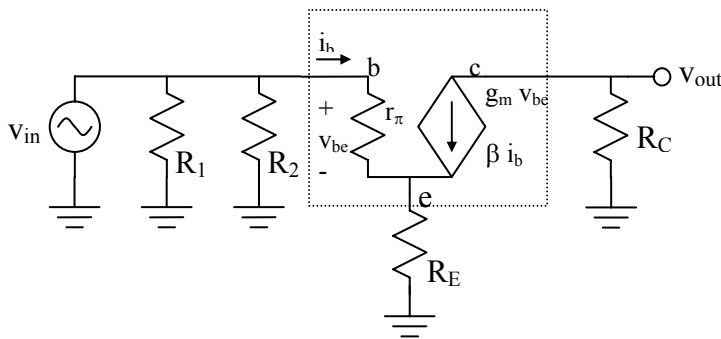

Small Signal (ac) Parameters

$$g_m = I_{C (BIAS)} / V_T$$

$$r_\pi = \beta / g_m$$

$$r_e = \beta / (\beta + 1) (1/g_m) \approx 1/g_m$$

Voltage Gain (A_v)

$$v_{out} = -\beta i_b R_C$$

$$v_{in} = i_b r_\pi + (\beta + 1) i_b R_E$$

$$= i_b (\beta + 1) (R_E + r_e)$$

$$A_v = v_{out} / v_{in} = -\beta R_C / [(\beta + 1)(R_E + r_e)]$$

$$A_v \approx -R_C / (R_E + r_e) \approx -R_C / R_E, \text{ if } R_E \gg r_e$$

Input & Output Impedance (R_{in}, R_{out})

$$R_{in} = R_1 \parallel R_2 \parallel (r_\pi + (\beta + 1) R_E)$$

$$= R_1 \parallel R_2 \parallel [(\beta + 1) (R_E + r_e)]$$

$$R_{out} = R_C$$

Notes:

- (1) Voltage gain is controlled by R_C / R_E .
- (2) R_{in} can be made quite large.