
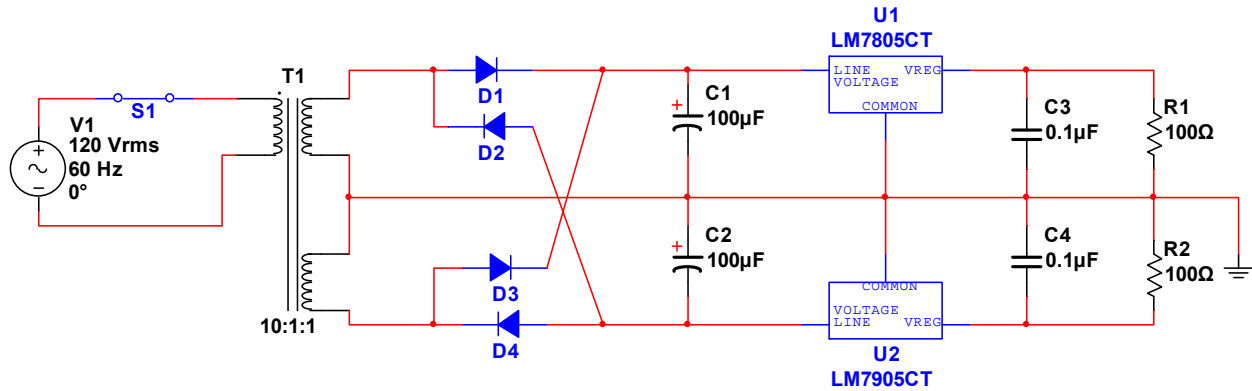


Dual Power Supply (+/- 5V)

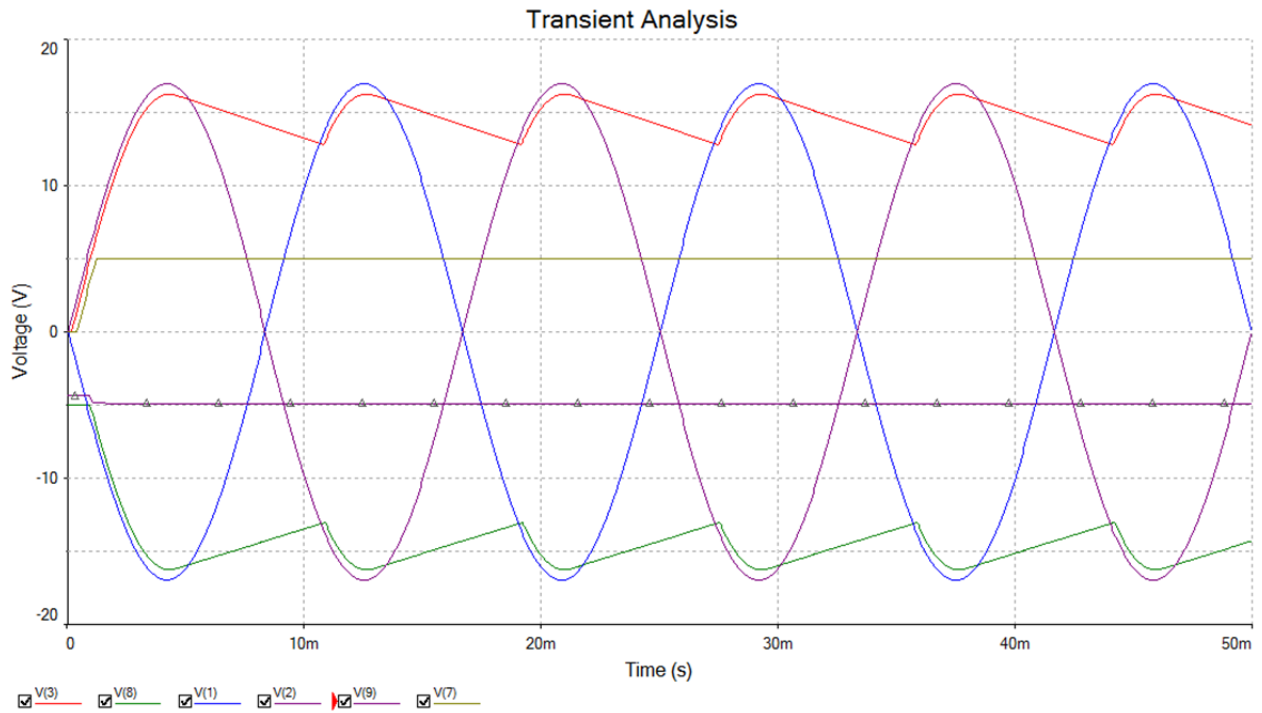

Waveforms:



Interview Question:

Can you identify the nodes in the circuit where each of these waveforms can be measured?