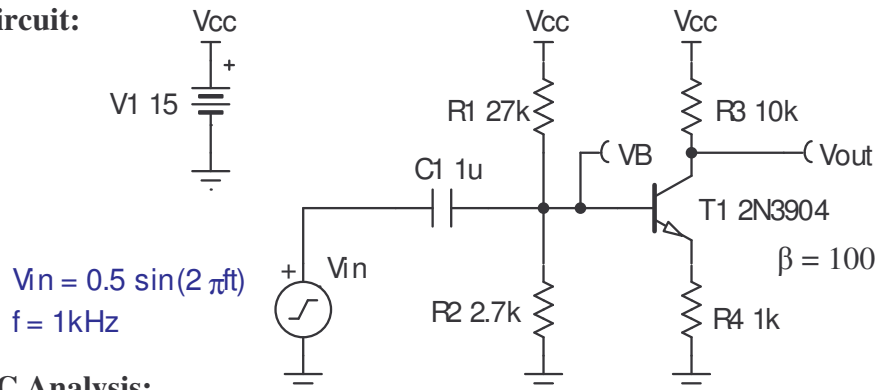


## Common Emitter (CE) Amplifier w/ Voltage Divider Bias & Emitter Resistance

### 1. Circuit:



### 2. DC Analysis:

(1) Treat the capacitor as an open-circuit since its reactance  $(1/j\omega C) = \infty$  for DC ( $\omega = 0$ ).

(2) Determine the Open-Circuit (Thevenin) Voltage of the divider:

$$V_{th} = \left( \frac{R2}{R1 + R2} \right) \cdot V_{CC} = \left( \frac{2.7k}{27k + 2.7k} \right) \cdot 15V = 1.36V$$

(3) Determine the Thevenin Resistance of the divider:

$$R_{th} = R1 \parallel R2 = 27k\Omega \parallel 2.7k\Omega = 2.45k\Omega$$

(4) Check to see if  $(\beta + 1)R_E \gg R_{th}$ . If so,  $V_B \approx V_{th}$ :

$$101k \gg 2.45k? \quad \text{YES, by a factor of 40+.} \quad \therefore V_B \approx 1.36V$$

(5) Determine  $V_E$ :  $V_E = V_B - V_{BE} = 1.36V - 0.7V = 0.66V$

(6) Determine  $I_E$ :  $I_E = V_E / R_E = 0.66V / 1k\Omega = 0.66mA$

(7) Determine  $I_C$ :  $I_C = \left( \frac{\beta}{\beta + 1} \right) \cdot I_E = \left( \frac{100}{101} \right) \cdot 0.66mA = 0.65mA$

\* Notice that  $I_C \approx I_E$ !

(8) Find voltage across  $R_C$ :  $V_{RC} = I_C \cdot R_C = 0.65mA \cdot 10k = 6.5V$

(9) Find  $V_{OUT(DC)}$ :  $V_{OUT(DC)} = (V_{CC} - V_{RC}) = (15V - 6.5V) = 8.5V$

(10) Verify *ACTIVE Region*, is  $V_{SAT} < V_{OUT(DC)} < V_{CC}$ ?

$$0.2V < 8.5V < 15V? \quad \text{YES!} \quad \therefore V_{OUT(DC)} = 8.5V$$

## Common Emitter (CE) Amplifier w/ Voltage Divider Bias & Emitter Resistance


### 3. Small-Signal (ac) Analysis ( using T-model of BJT ):

- (1) Determine Small-Signal Parameters  $g_m$  and  $r_e$  for T-model using DC bias:

$$g_m = \frac{I_{C(Bias)}}{nV_T} = \frac{0.65mA}{1 \cdot (26mV)} = 25mA/V$$

$$r_e = \left( \frac{\beta}{\beta + 1} \right) \frac{1}{g_m} \approx \frac{1}{g_m} = \frac{1}{25mA/V} = 40\Omega$$

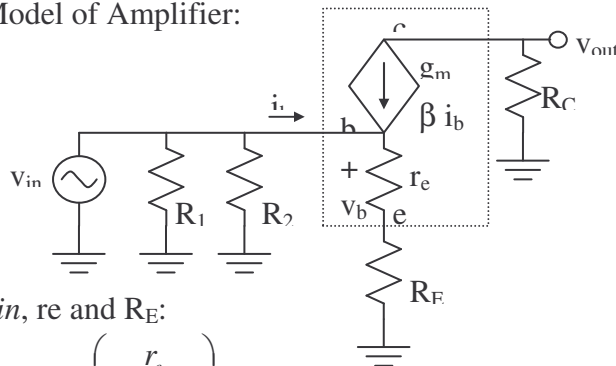- (2) Draw Small-Signal Model of Amplifier:



- (3) Find  $v_{be}$  in terms of  $v_{in}$ ,  $r_e$  and  $R_E$ :

$$v_{be} = v_{in} \left( \frac{r_e}{r_e + R_E} \right)$$

- (4) Solve for  $i_c$ :
- $$i_c = g_m \cdot v_{be} = v_{in} \left( \frac{g_m \cdot r_e}{r_e + R_E} \right) \approx v_{in} \left( \frac{1}{r_e + R_E} \right)$$

- (5) Solve for  $v_{out}$ :
- $$v_{out} = -R_C \cdot i_c = -v_{in} \left( \frac{R_C}{r_e + R_E} \right)$$

- (6) Solve for  $A_v$  (Voltage Gain):

$$A_v \equiv \frac{v_{out}}{v_{in}} = - \left( \frac{R_C}{r_e + R_E} \right) = - \frac{10k\Omega}{40\Omega + 1k\Omega} = -9.62$$

- (7) Compare to Approximation:

$$A_v \cong - \frac{R_C}{R_E} = - \frac{10k\Omega}{1k\Omega} = -10 \text{ (within 5\%)}$$

- (8) Solve for  $v_{out}$ :
- $$v_{out} = A_v \cdot v_{in} = -9.62(0.5Vpk) = -4.81Vpk$$


### 4. Determine Net Output Response:

- (1)  $v_{OUT(NET)} = V_{OUT(DC)} + v_{out(ac)}$


- (2)  $v_{OUT} = 8.5 - 4.81 \sin(2\pi ft)$  Volts , where  $f = 1kHz$

## Common Emitter (CE) Amplifier w/ Voltage Divider Bias & Emitter Resistance

### 5. Simulation:

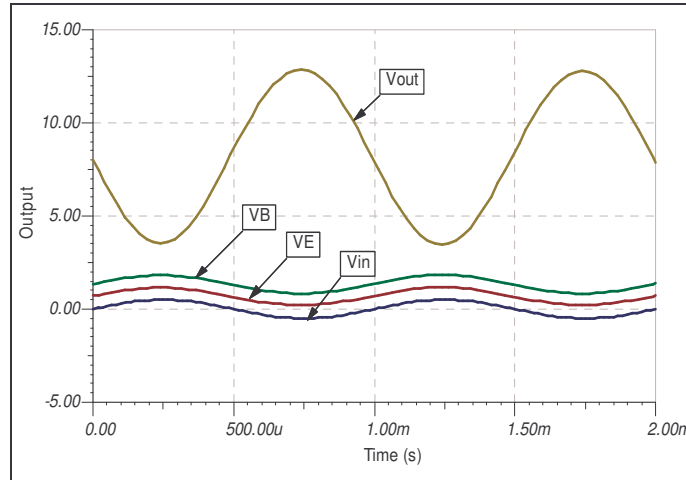

### 6. Lab Circuit:

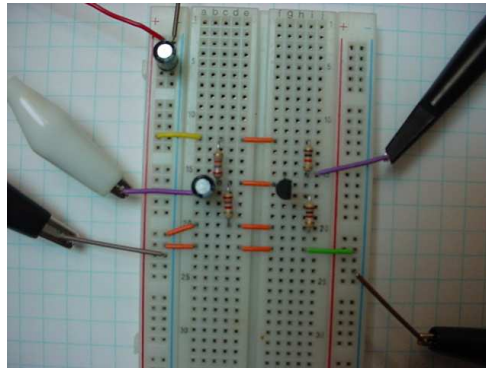

### 7. Lab Measurement:

